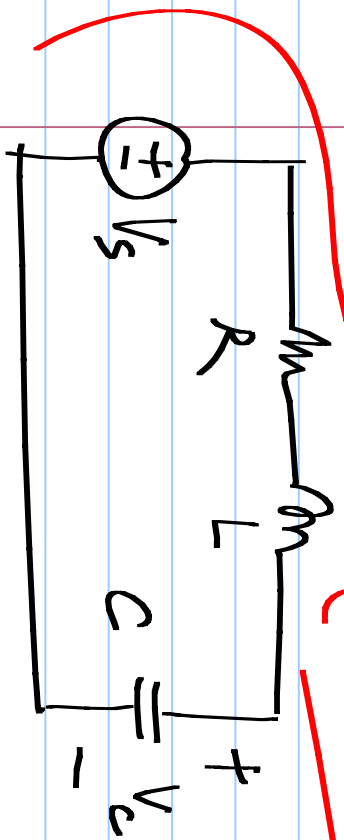


Lecture 27

single loop of
series R, L, C
(null ed ckt)

$$LC \frac{d^2 V_c}{dt^2} + RC \cdot \frac{dV_c}{dt} + V_c = V_s$$



Zero input response ($V_s = 0$)

$$a_2 \frac{d^2 V_c}{dt^2} + a_1 \frac{dV_c}{dt} + V_c = 0$$

Series R, L, C circuit -

$$a_2 p^2 + a_1 p + 1 = 0$$

real & distinct: $k_1 \exp(p_1 t) + k_2 \exp(p_2 t)$

real, repeated: $(k_1 + k_2 t) \exp(p_1 t)$

complex conj. : $k_1 \exp(p_1 t) + k_1^* \exp(p_1^* t) + k_2 \exp(p_2 t) + k_2^* \exp(p_2^* t)$

real & distinct: $k_1 \exp(p_1 t) + k_2 \exp(p_2 t)$

real, repeated: $(k_1 + k_2 t) \exp(p_1 t)$ $k_0 = |k_1|$

complex conj.: $2 \cdot k_0 \exp(p_r t) \cdot \cos(p_i t + \phi_k)$ $\phi_k = \angle k_1$

$$\begin{aligned} Q &= \frac{1}{R} \sqrt{\frac{L}{C}} \\ \} &= \frac{R}{2} \sqrt{\frac{L}{C}} \end{aligned}$$


$$\begin{aligned} & a_2 p^2 + a_1 p + 1 \\ & \approx p^2 + 2\zeta \omega_n p + \omega_n^2 \end{aligned}$$

natural frequency

damping factor

Quality factor


$$Q = \frac{1}{2\zeta}$$

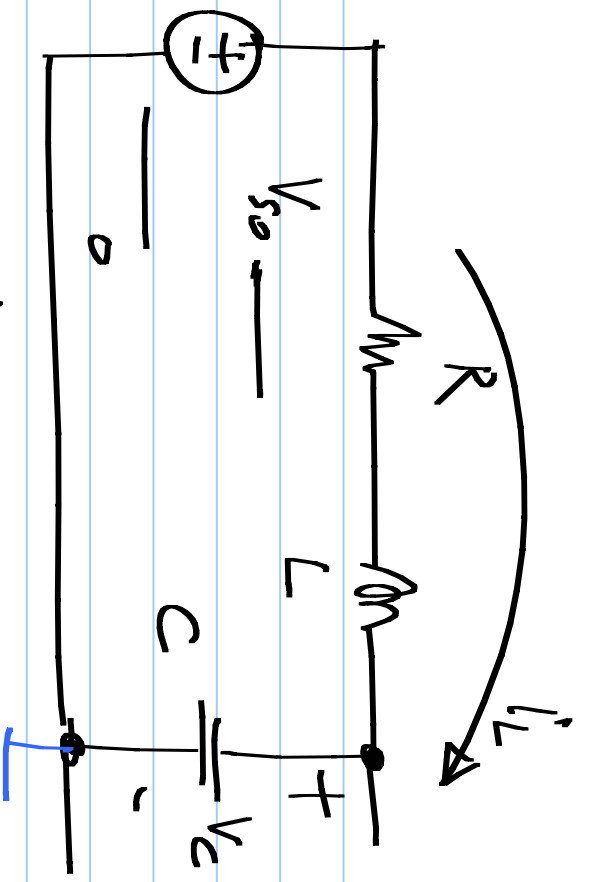

Critically damped:



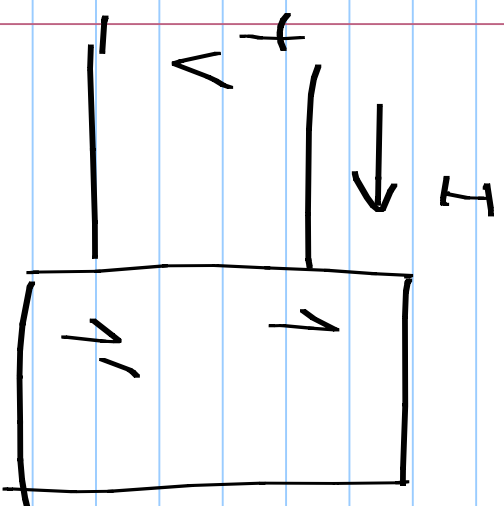Sinusoidal steady state response: G : conductance



$I_{p \text{ exp}}(j\omega t + \phi)$

B : susceptance

(steady state)

$$\underline{V} = \underline{Z} \underline{I} = R + jX$$

(Impedance)

Resistance

Reactance

$V_{p \text{ exp}}(j\omega t)$

$$\underline{I} = \underline{Y} \underline{V} = G + jB$$

(Admittance)

\bar{Z}

\bar{Y}

Resistor
 R

$$R + j0$$

$$\frac{1}{R + j0}$$

Inductance

$$0 + j\omega L$$

$$0 - \frac{j}{\omega L}$$

L


Capacitance

$$0 - \frac{j}{\omega C}$$

$$0 + j\omega C$$

C

First order (RC)

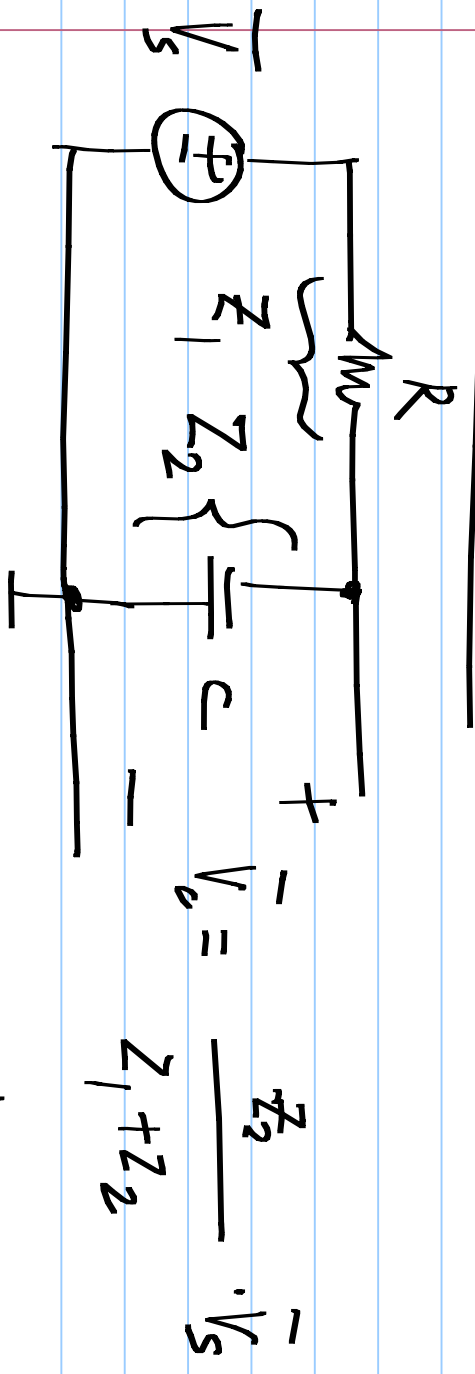

$$V_o = \frac{Z_2}{Z_1 + Z_2} \cdot V_s$$


$$= \frac{-j/\omega C}{R - j/\omega C}$$


$$V_s = V_p \cos \omega t \quad = \quad \frac{1}{1 + j\omega RC}$$

$$\frac{V_o}{V_s} = \frac{1}{1 + j\omega CR}$$

$$\left| \frac{V_o}{V_s} \right| = \frac{1}{\sqrt{1 + (\omega CR)^2}}$$
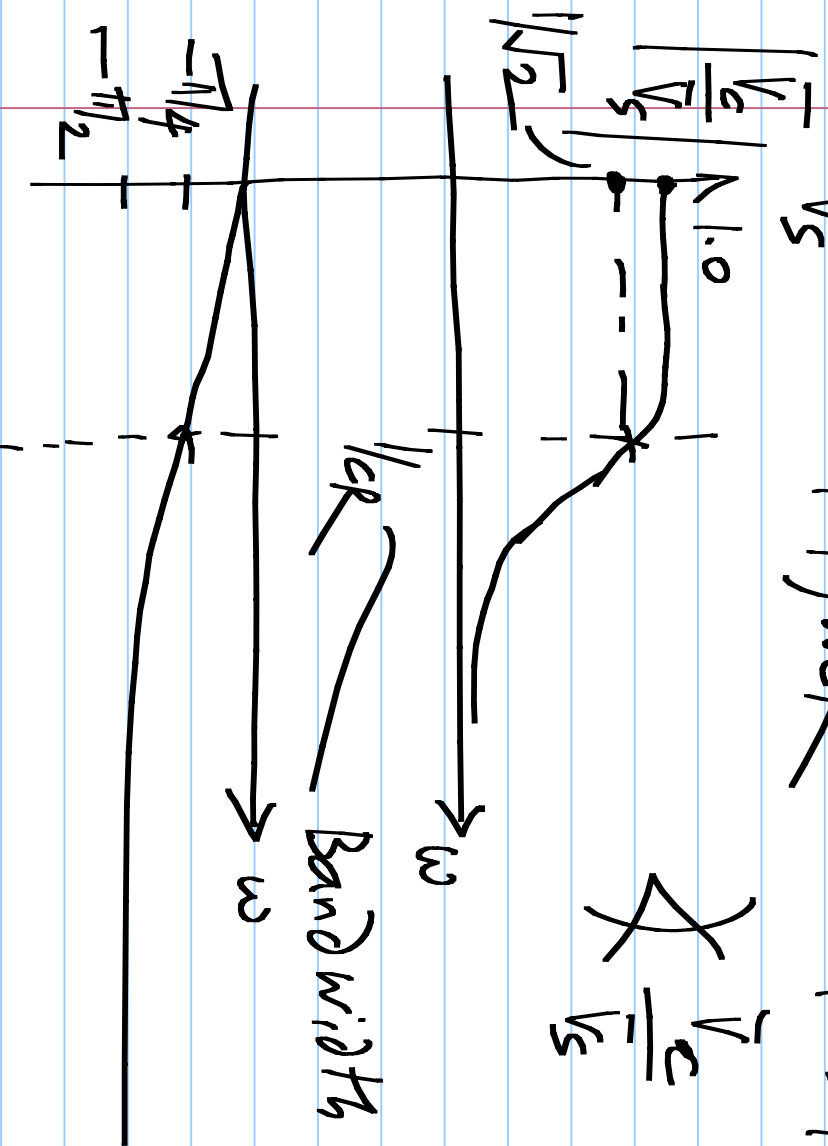
$$\angle \frac{V_o}{V_s} = -\tan^{-1}(\omega CR)$$



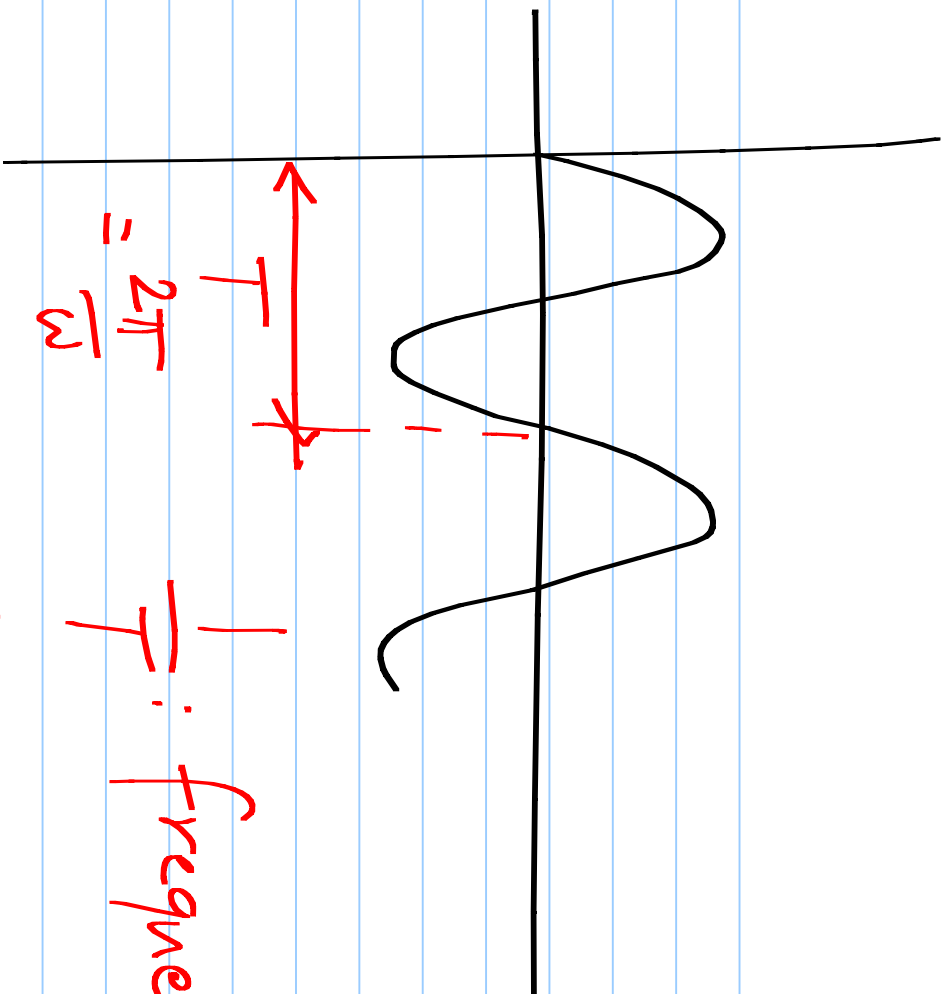

$\frac{1}{T}$: frequency (Hz) = f

$\frac{2\pi}{T}$: freq. (rad/s) ω