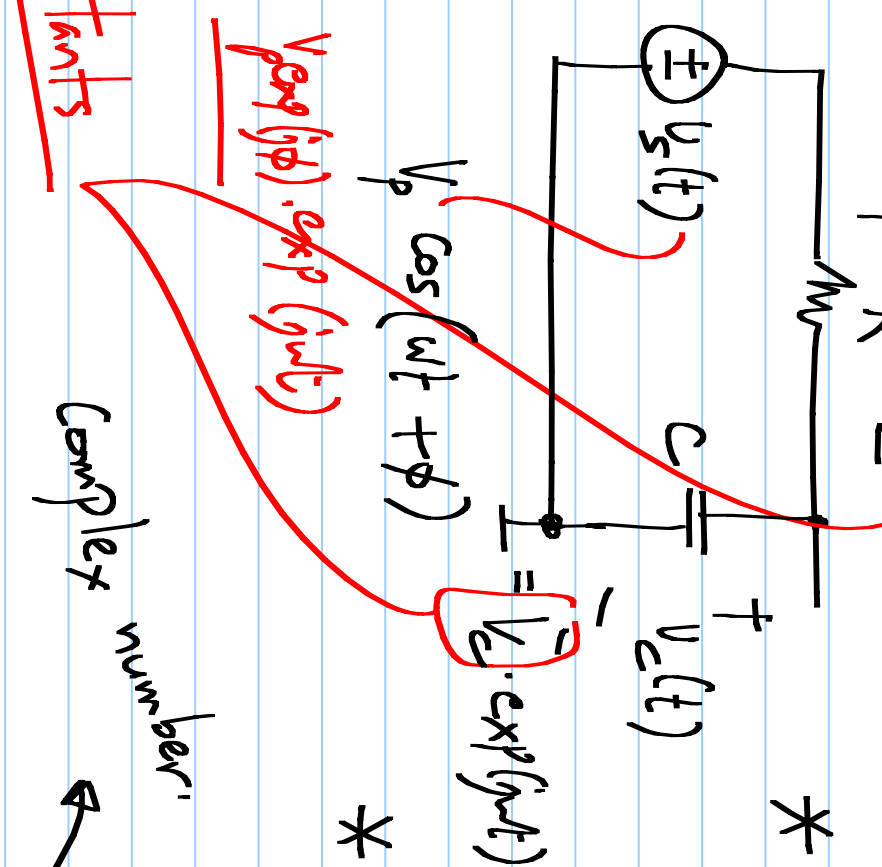


Lecture 28

$$v_R(t) = \bar{V}_R \exp(j\omega t) \quad * \text{ KVL, KCL equations}$$

Can be written in terms of phasors







* Response to $v_s \cos(\omega t + \phi)$
 = Real { Response to $V_p \exp(j\phi) \exp(j\omega t)$ }

* Steady-state response of a linear circuit to $\exp(j\omega t)$

Complex number \rightarrow $() \exp(j\omega t)$

Constants

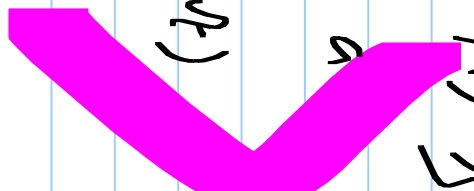

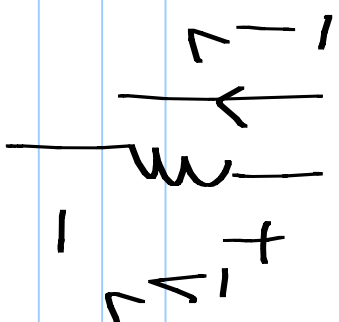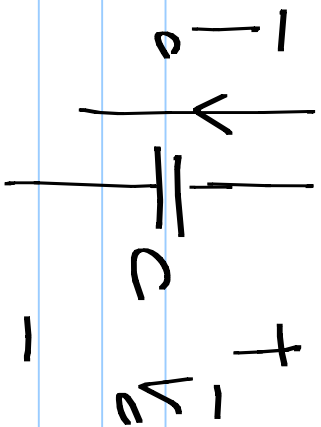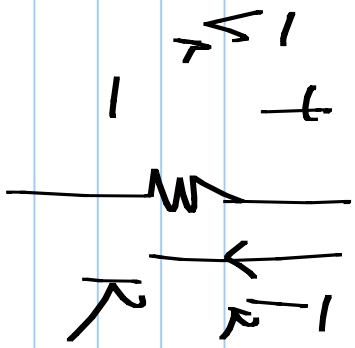



$$\vec{V}_R = R \cdot \vec{I}_R$$

$$\vec{V}_C = \frac{1}{g_{wC}} \cdot \vec{I}_C$$

$$\vec{V}_L = g_{wL} \cdot \vec{I}_L$$

Element relationships ~ Ohm's law

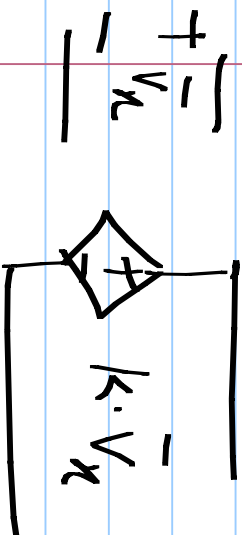


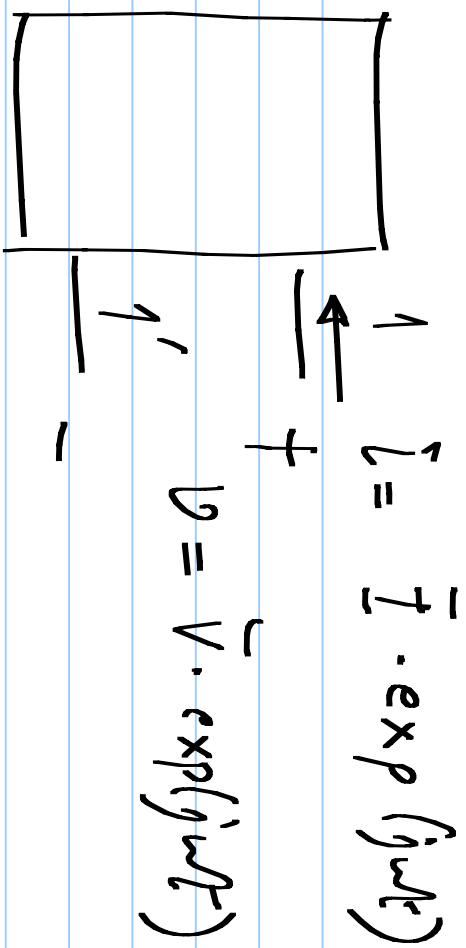



$$\frac{\bar{V}}{\bar{I}} = \bar{Z} = R + jX$$

impedance

$$\frac{\bar{I}}{\bar{V}} = \bar{Y} = G + jB$$

admittance

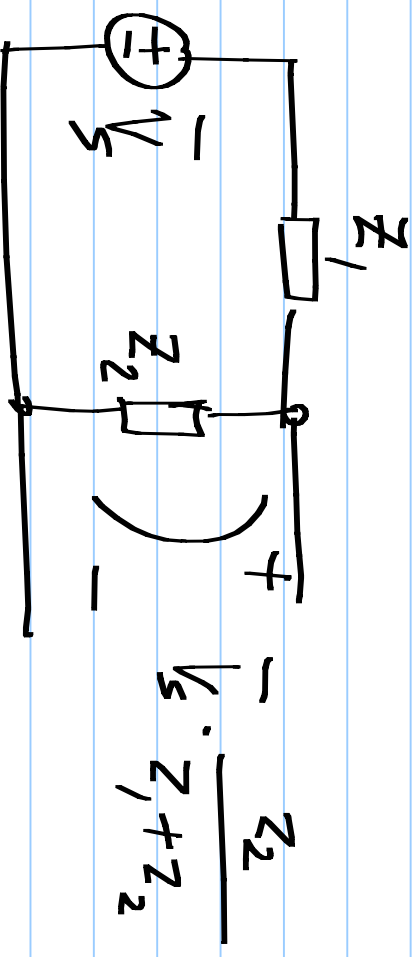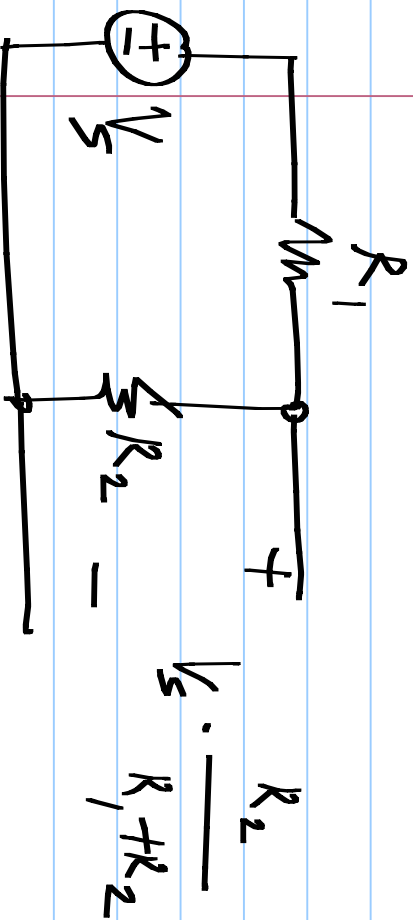

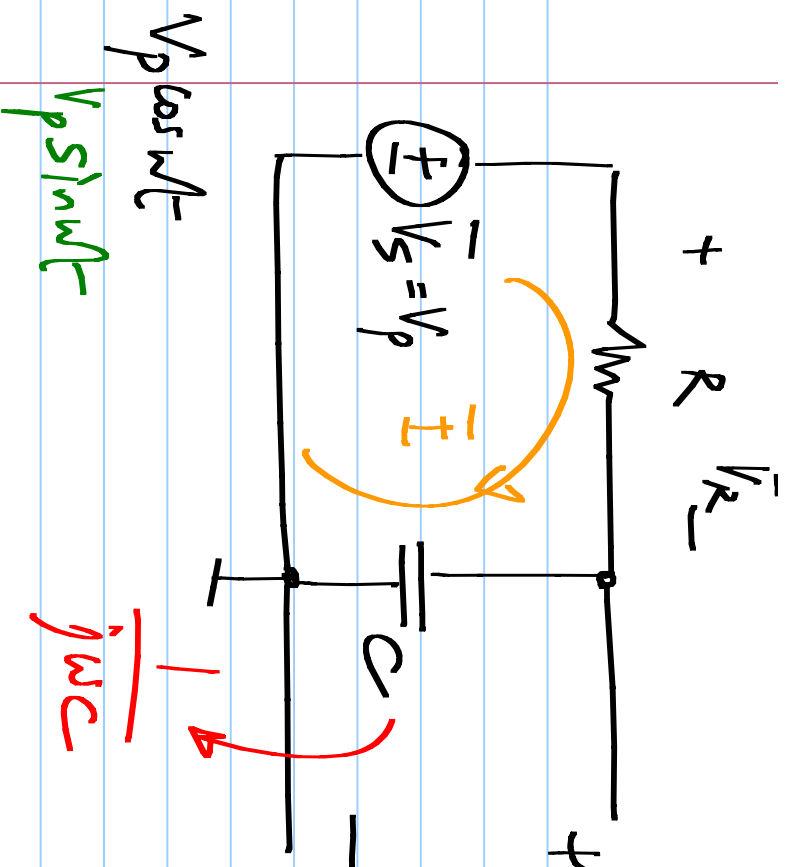

$$V_p \cos \omega t - V_p \sin \omega t$$


$$\bar{V}_R = \bar{V}_s \cdot \frac{j\omega C R}{1 + j\omega C R}$$

$$= \bar{V}_s \cdot \left(\frac{1}{1 + j\omega C R} \right)$$

Phase of the output

Phasor diagram: phasors on the complex plane

Single frequency

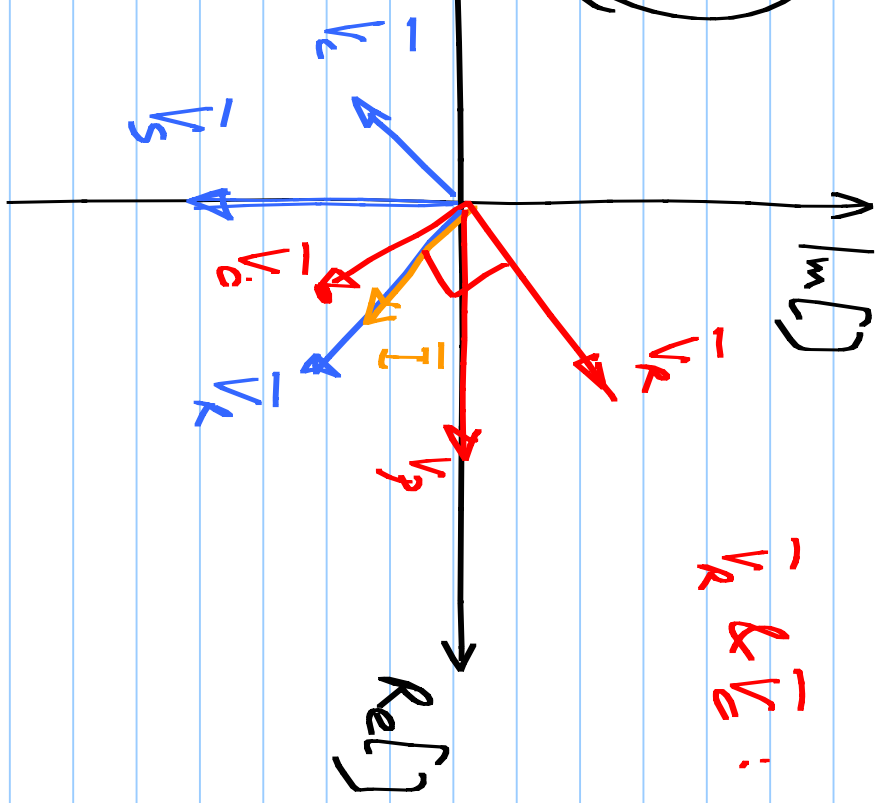

\bar{V}_R & \bar{I} : 90° w.r.t each other

R: \bar{V}_R, \bar{I} coincident

L: \bar{I}_L lags \bar{V}_L by 90°


C: \bar{I}_C leads \bar{V}_C by 90°

$$\frac{V_o}{V_s} = \frac{1}{1 + j\omega CR}$$

Transfer function

$$\text{Magnitude} = \sqrt{1 + (\omega CR)^2}$$

Low pass filter

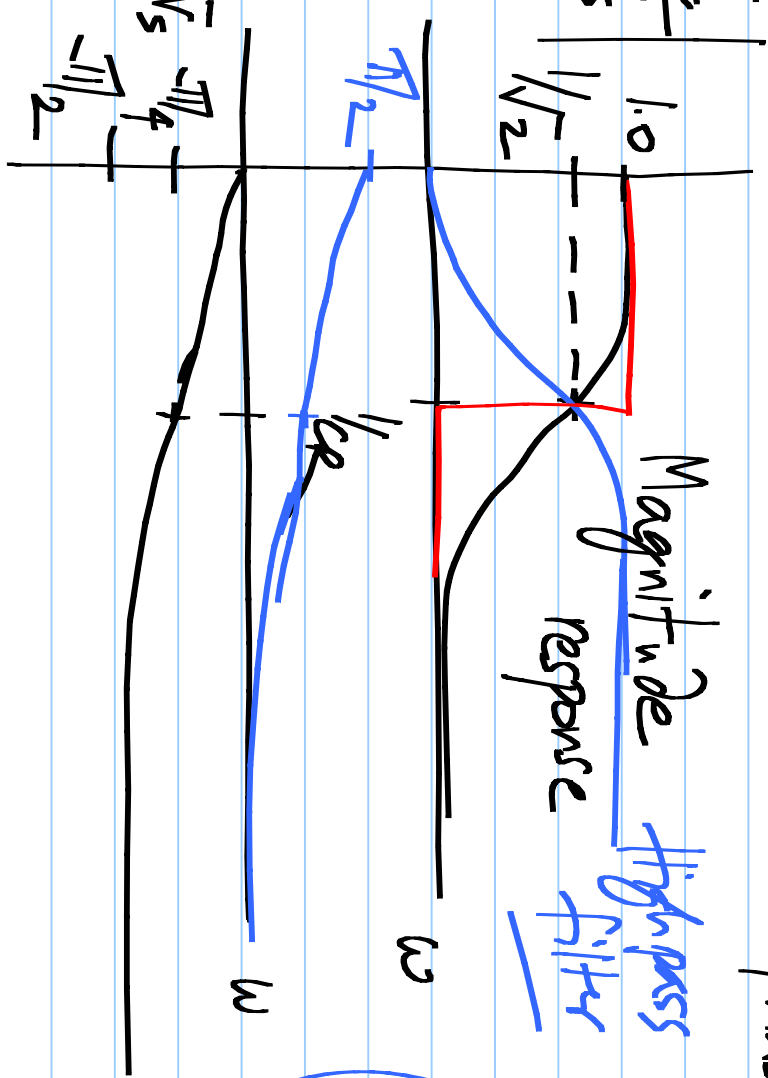

Magnitude response
high pass filter

$$= -\tan^{-1}(\omega CR)$$


$$\frac{\pi}{2} - \tan^{-1}(\omega CR)$$

$\omega \gg 1/CR$, $\omega \ll 1/CR$


$\omega \gg 1/CR$, $\omega \rightarrow 1/CR$


$$\frac{V_o}{V_s} = \frac{1}{1 + j\omega CR}$$

$$\omega = \omega_1$$

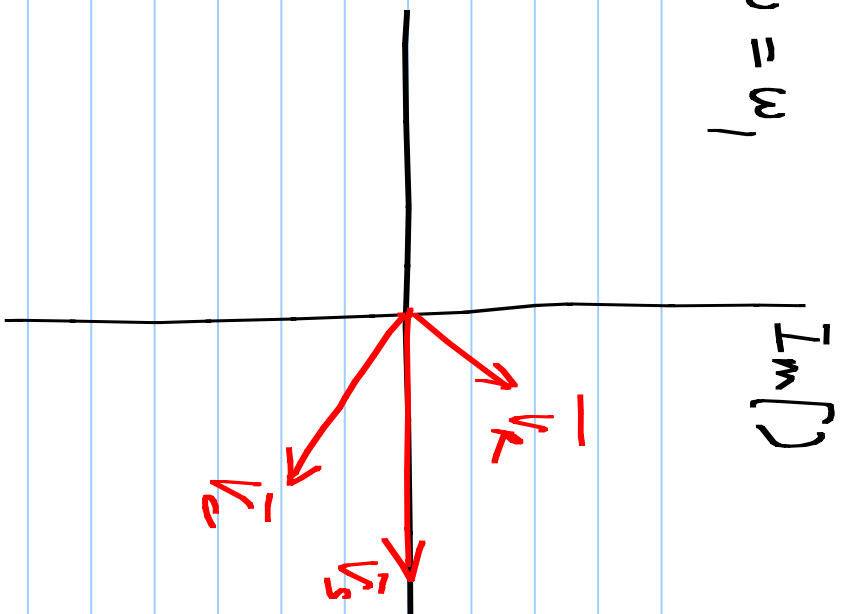

$$\omega_2 > \omega_1$$

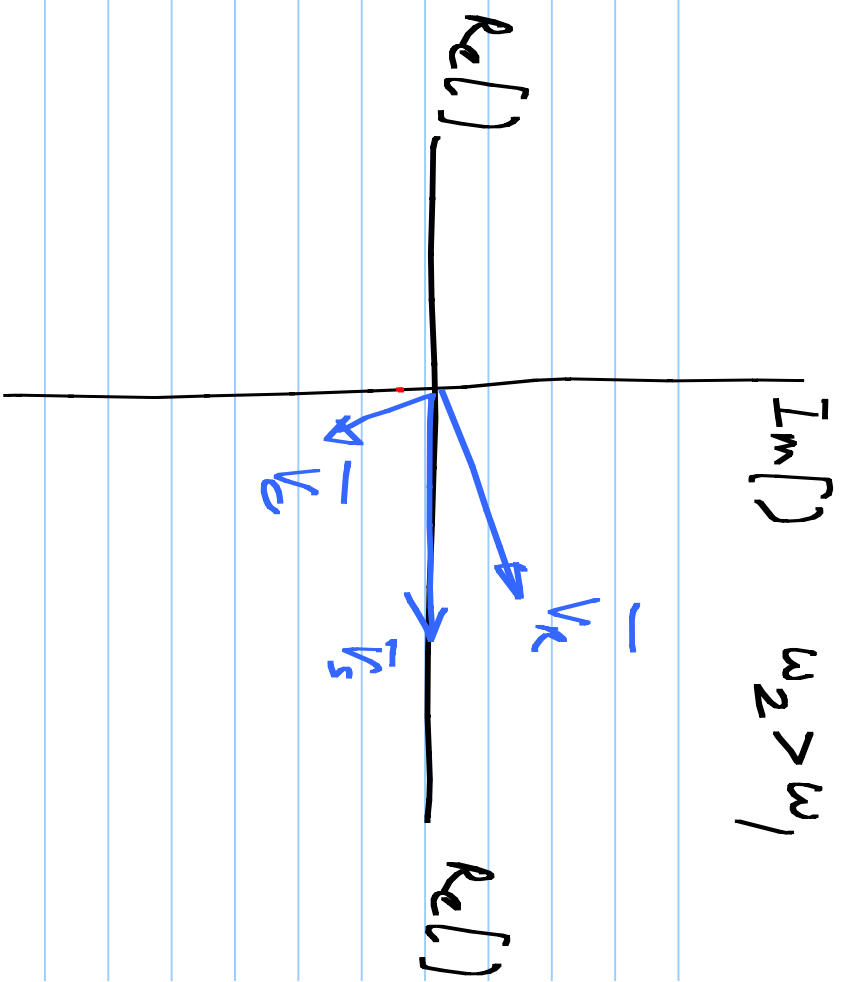

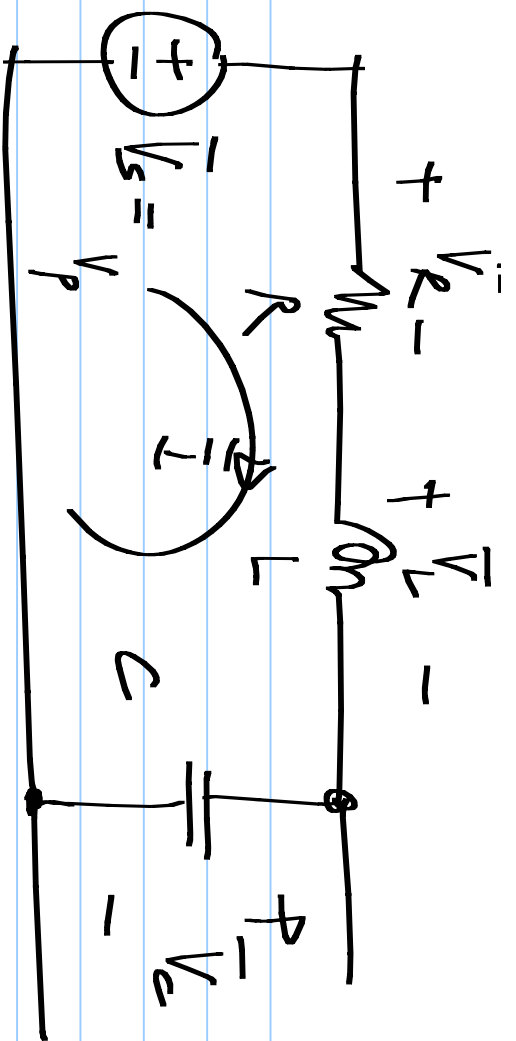

$$\bar{V}_s = \bar{V}_p + j0$$

$$= \bar{V}_p / 0$$

* Draw phasor diagram with $\bar{V}_s, \bar{V}_R, \bar{V}_L, \bar{V}_C, \bar{I}$

* Draw $\left| \frac{\bar{V}_C}{\bar{V}_s} \right|$ & $\angle \frac{\bar{V}_C}{\bar{V}_s}$ versus ω