

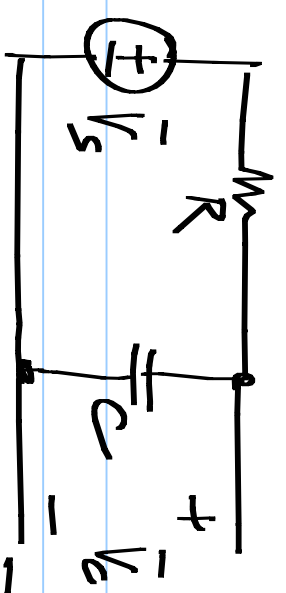


Lecture 29

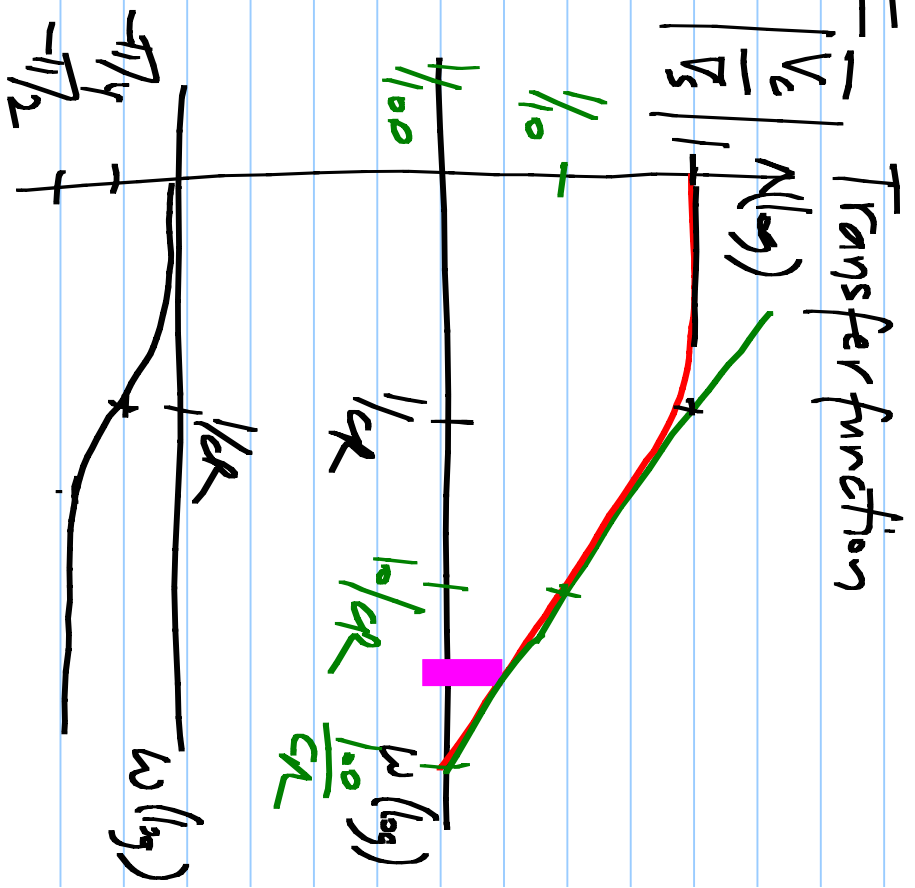

$$\frac{V_c}{V_s} = \frac{1}{1 + j\omega RC}$$

Transfer function

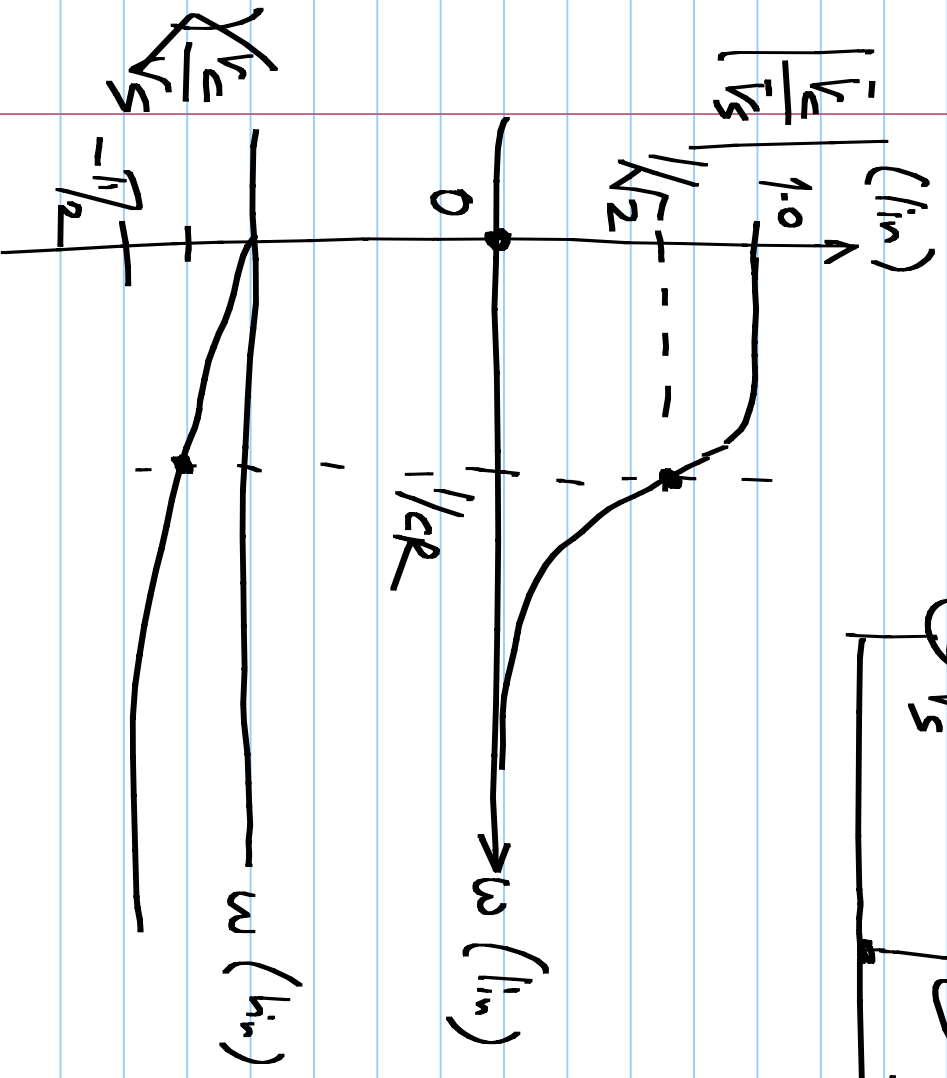

$$\left| \frac{v_e}{v_s} \right| \approx \frac{1}{w_{CR}} \quad \text{if } w \gg \frac{1}{CR}$$

$$\log \left| \frac{v_e}{v_s} \right| = -\log(CR) - \log(w)$$

$$\cancel{X} \frac{1}{v_s} = -\tan^{-1}(w_{CR}) = -\tan^{-1}\left(\frac{w}{1/CR}\right)$$

$$+\tan^{-1}(w_{CR}) = +\pi \quad w_{CR} = \tan(\pi)$$

$$+\tan^{-1}(w_{2CR}) = +\left(\frac{\pi}{2} - \pi\right) \quad w_{2CR} = \tan\left(\frac{\pi}{2} - \pi\right) \stackrel{!}{=} \frac{1}{\tan \pi}$$



decibel unit : $20 \log_{10} \left| \frac{V_0}{V_S} \right|$ dB

$20 \log_{10}$ (voltage ratio, current ratio)



Bode Plots

3 dB bandwidth

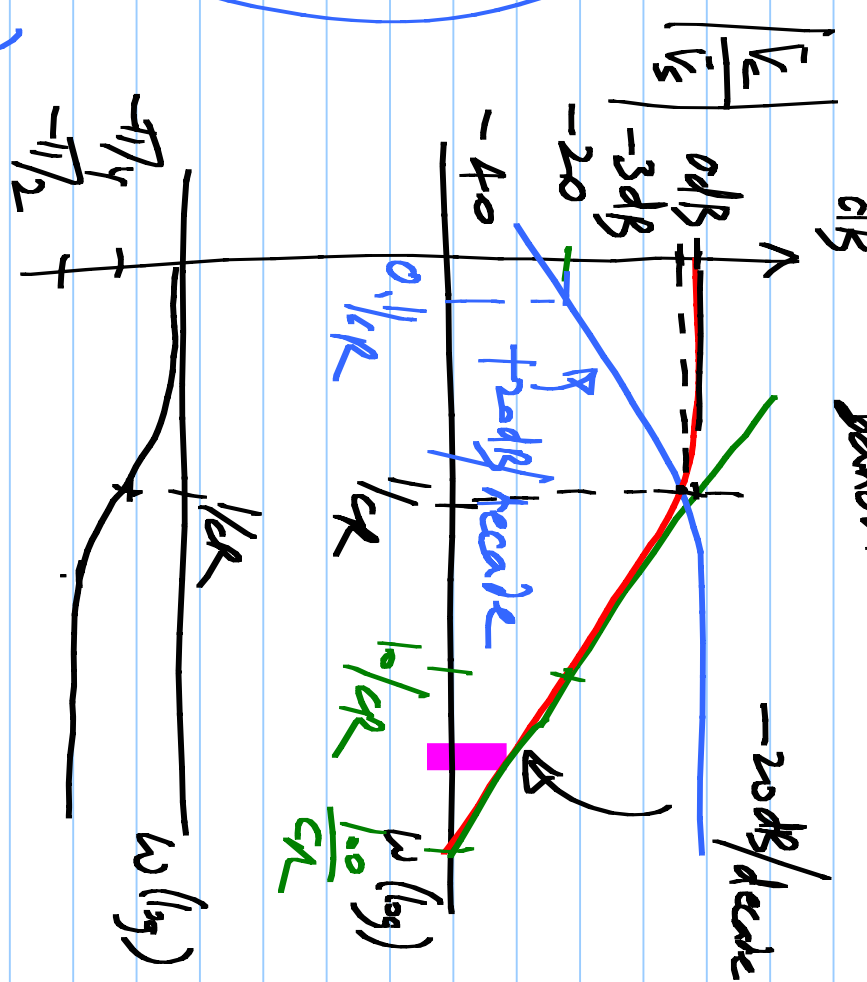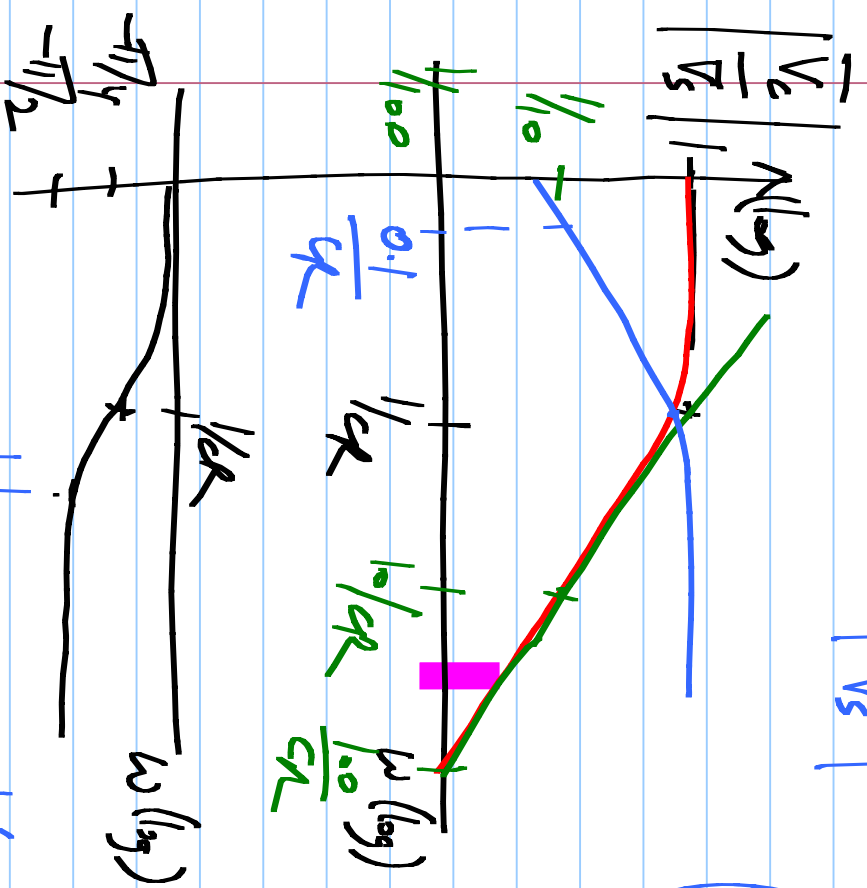


Hendrik W Bode

$$\left| \frac{V_R}{V_S} \right| = \left| \frac{j\omega CR}{1 + j\omega CR} \right| \approx \omega CR \quad \omega \ll 1/CR$$


$$\omega \gg 1/CR$$

$$\log \left| \frac{V_R}{V_S} \right| = \log(\omega CR) + \log(\omega)$$

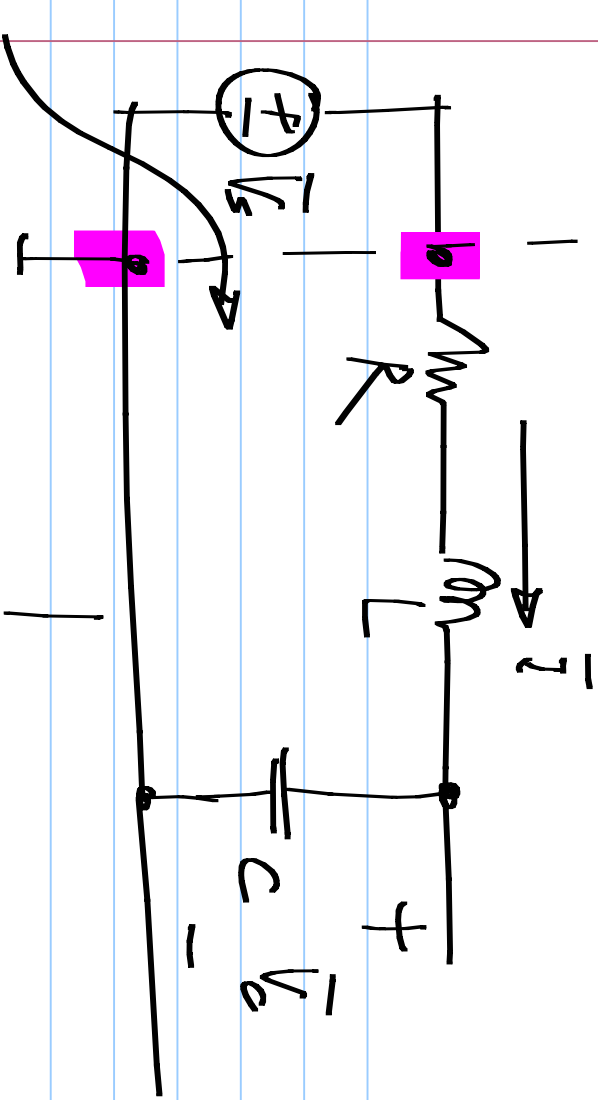


$$\frac{V_c}{V_s} = \frac{1}{(1 - \omega^2 LC) + j\omega CR}$$
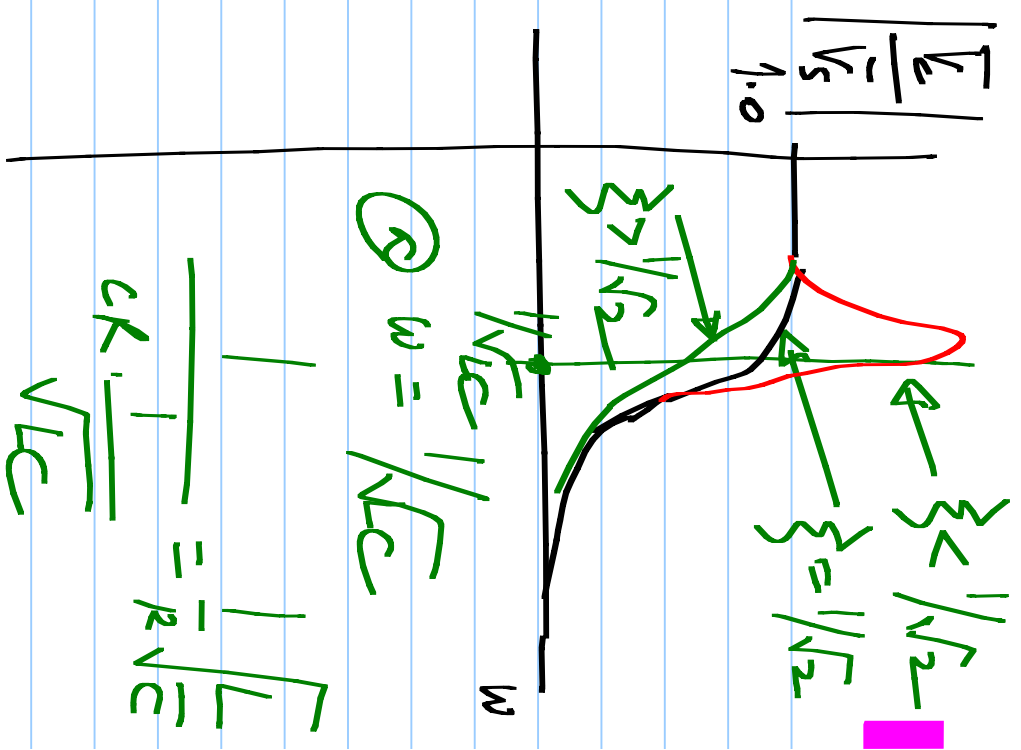
$$\frac{I}{V_s} = \frac{1}{R(1 - \omega^2 LC) + j\omega CR}$$



$$\frac{V_c}{V_s} = \frac{1}{(1 - \omega^2 L_c) + j\omega R_c}$$

~~$\sqrt{\frac{V_c}{V_s}}$~~

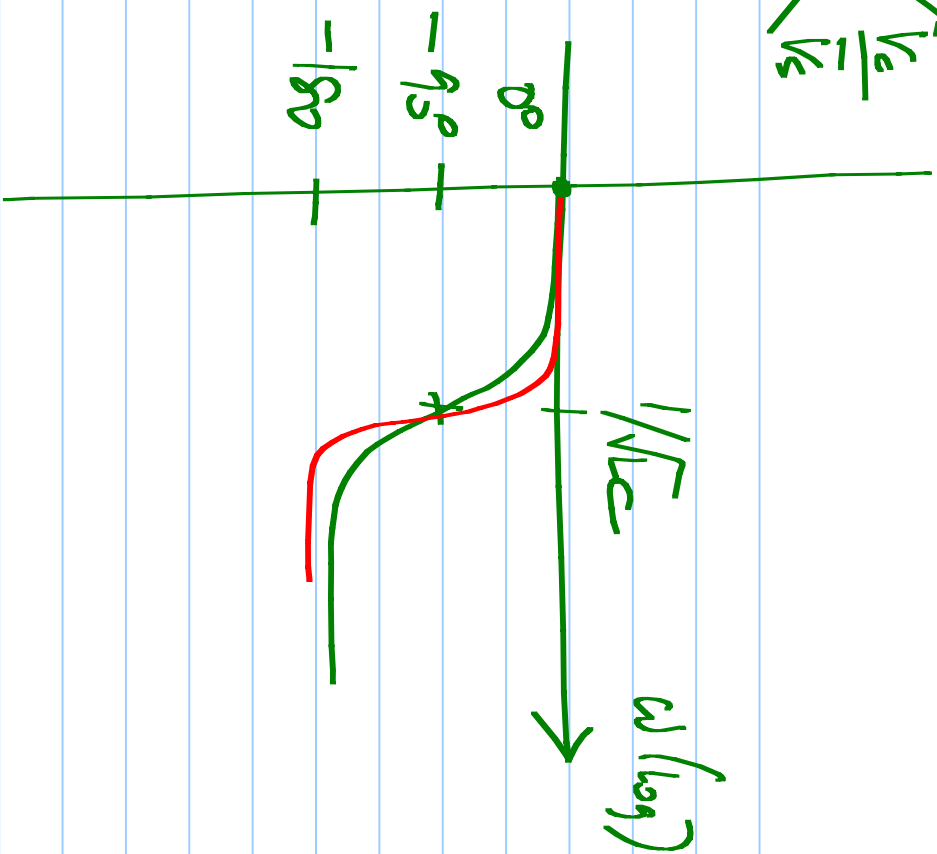

$$\underline{I} = \frac{j\omega C}{(1 - \omega^2 LC) + j\omega CR}$$

$$= \frac{1}{R} \frac{j\omega CR}{(1 - \omega^2 LC) + j\omega CR}$$

