
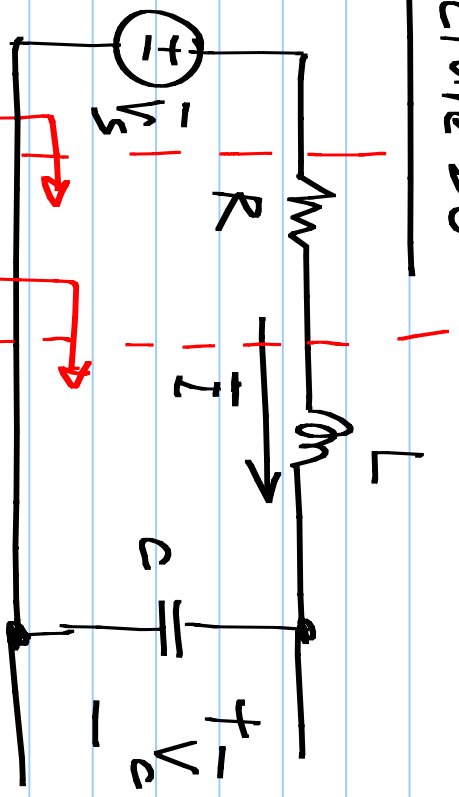



Lecture 30

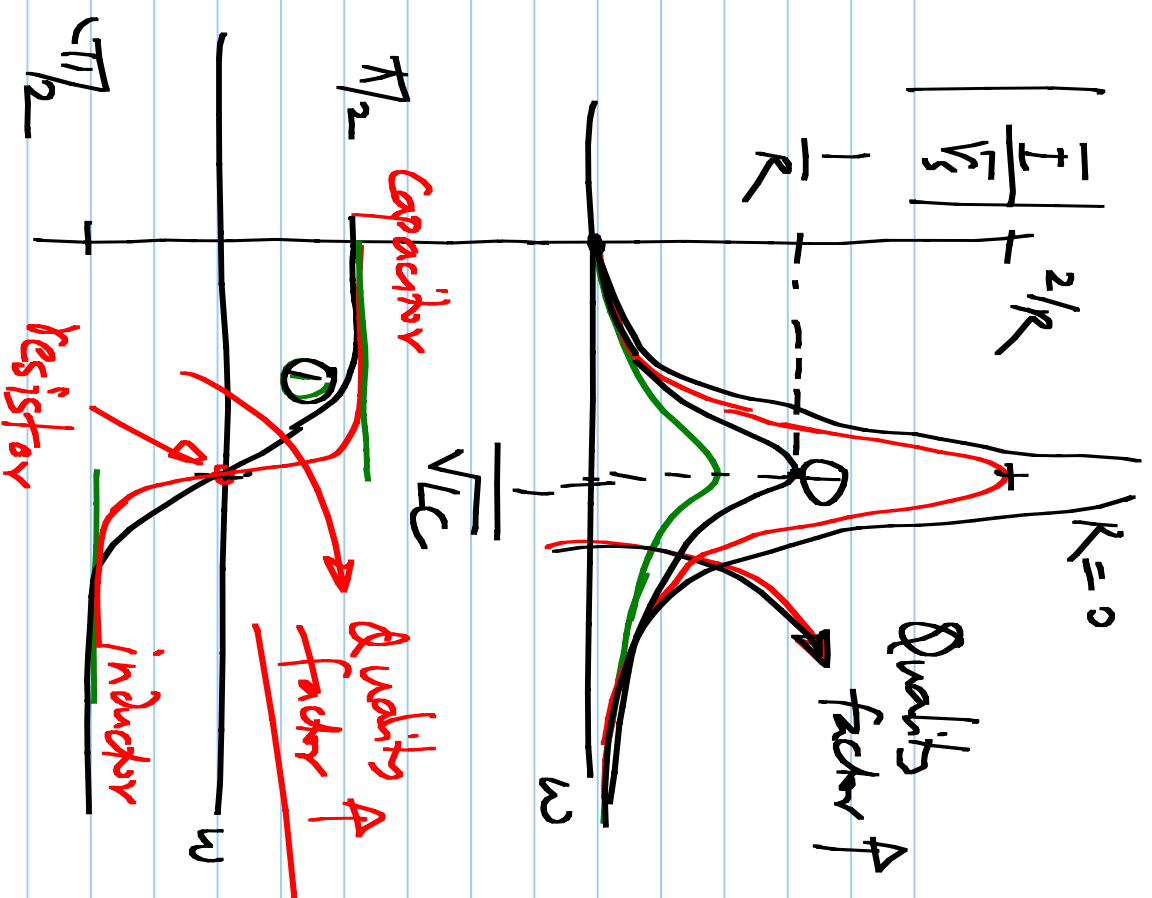

Short circuit

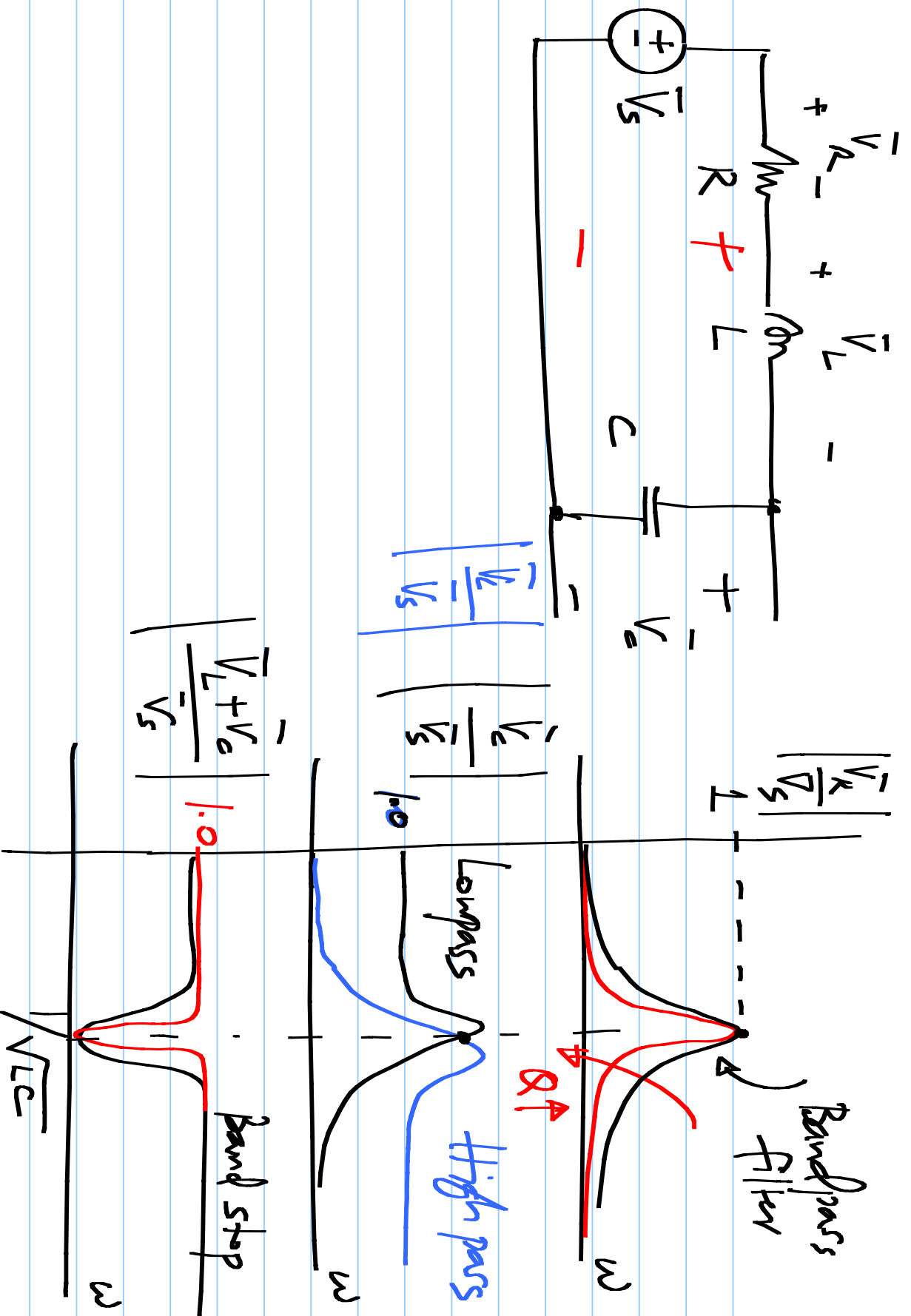$j\omega L + \frac{1}{j\omega C}$, resonance frequency





Nodal analysis:

$$[G] \cdot \underline{V} = \underline{I}$$

Mesh analysis:

$$[R] \cdot \underline{I} = \underline{V}$$

② a


particular
freq. ω

$$[Y]$$

Admittance
matrix


$$\underline{V} = \underline{I}$$

(n) source vector (phases)

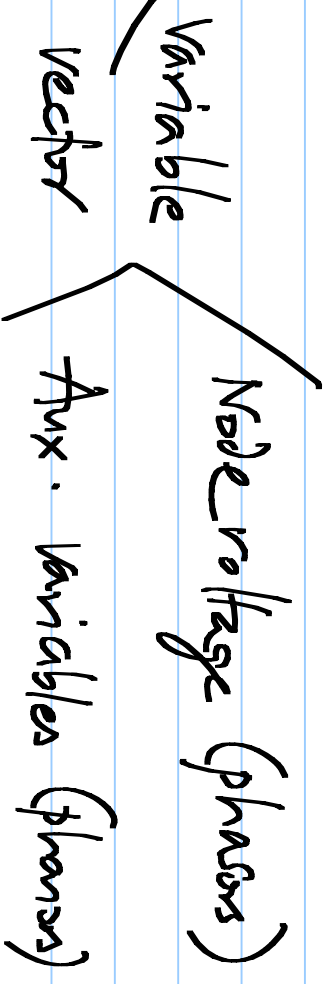

Substitution theorem: replace Z with \bar{V}_Z or \bar{I}_Z

Thevenin / Norton:

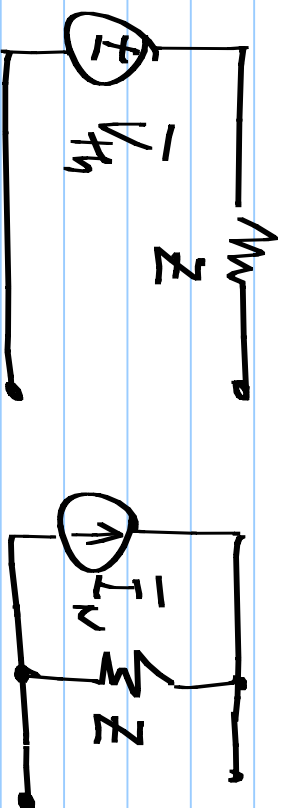

Tellegen's theorem: KVL/KCL ✓

Reciprocity theorem: works in the phasor domain

R, L, C



Compensation theorem: ✓

Two port parameters:

$$\underline{I} = [Y] \underline{V}$$

Complex parameters

$$v(t) = V_p \cos \omega t$$

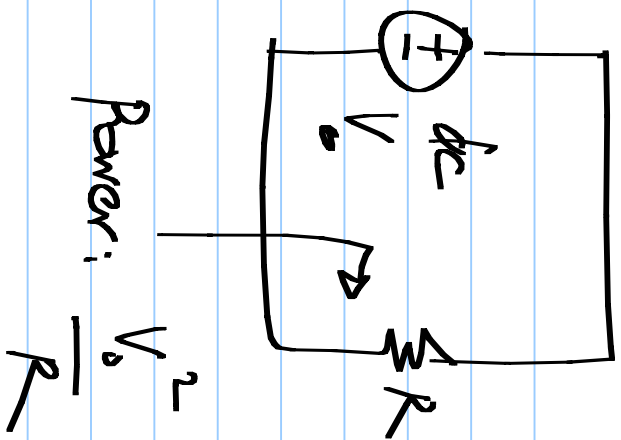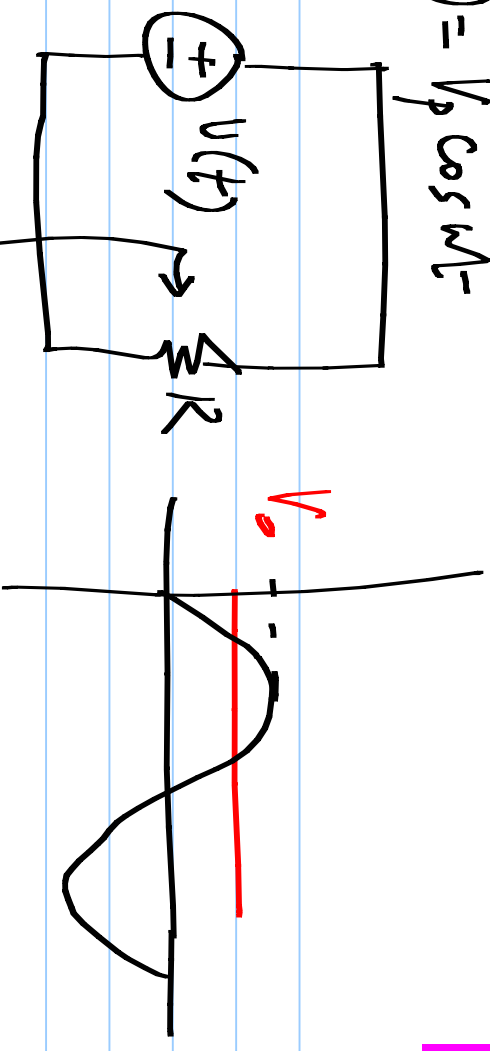

Power: $\frac{V_0^2}{R}$

Instantaneous power: $\frac{v(t)^2}{R}$

Equal average power:

$$\frac{V_0^2}{R} = \frac{V_p^2}{2R}$$

$$\frac{V_p}{\sqrt{2}} = V_0$$

$$\frac{V_p^2}{R} \cos^2 \omega t = \frac{V_p^2}{2R} (1 + \cos 2\omega t)$$

Average $\frac{V_p^2}{2R}$

Peak Amplitude

$\frac{V_p}{\sqrt{2}}$: rms value of the sinusoid. $V_p \cos \omega t$


Root mean squared

$U(t)$: period T Mean Squared Value : $\frac{1}{T} \int_0^T U^2(t) dt$


rms .



$$\sqrt{\frac{1}{T} \int_0^T U^2(t) dt}$$

Opamp!

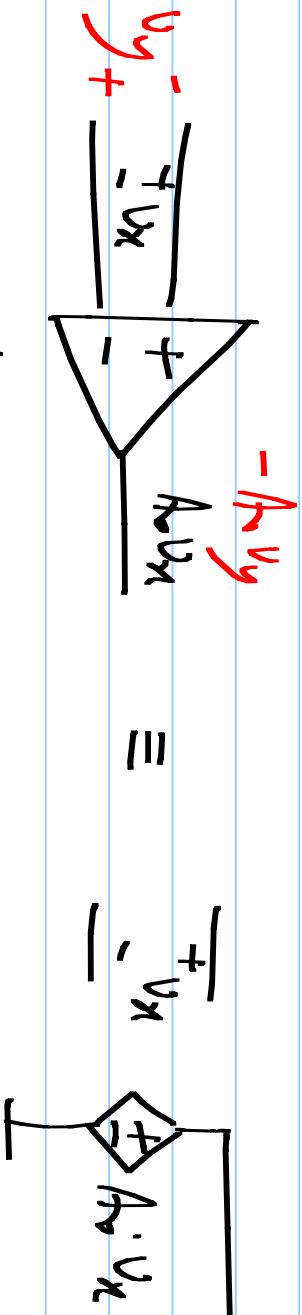

$$A_0 > 0$$

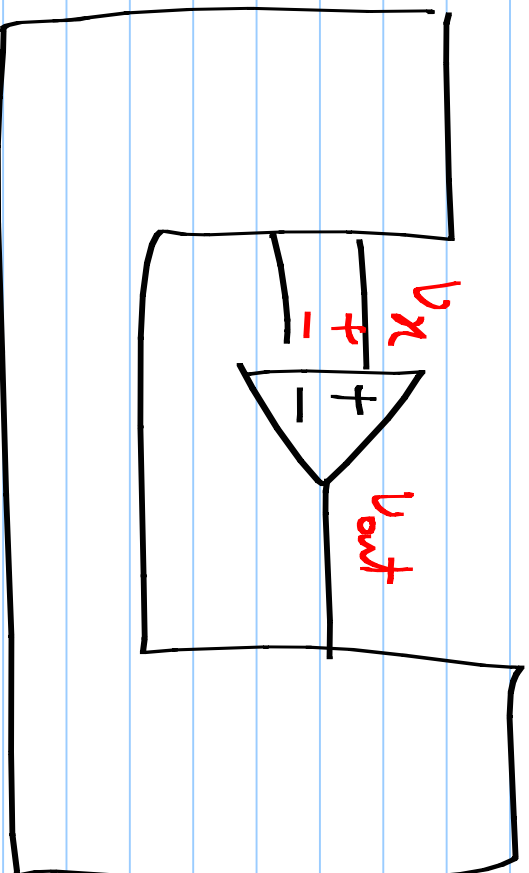

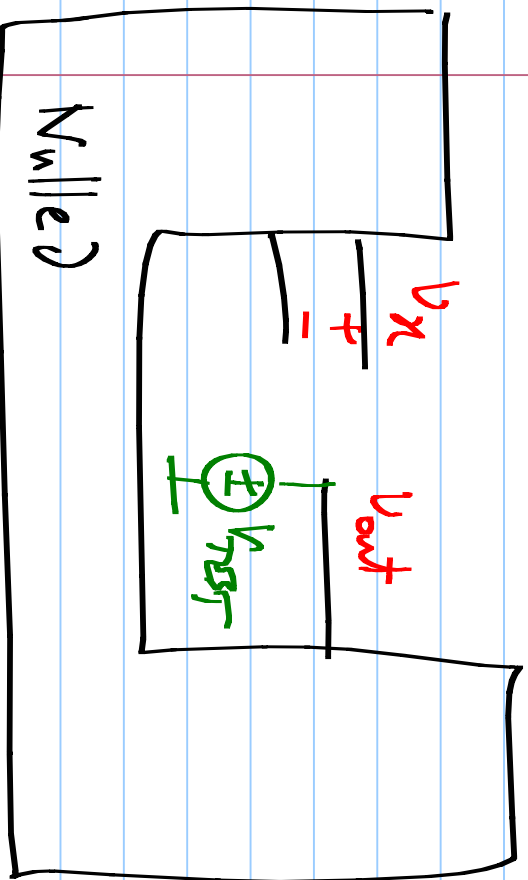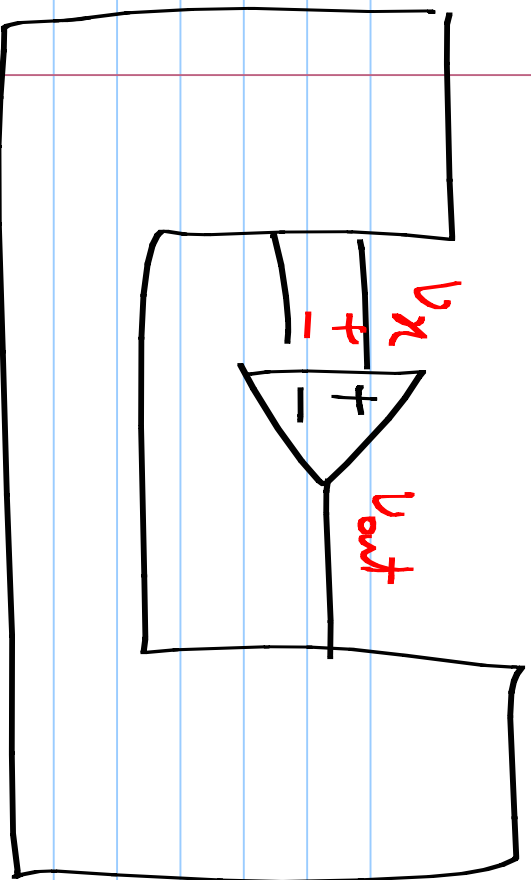

- * Assume the signs
- * Identify V_x & V_{out}
- * Remove the opamp & apply V_{test} at the o/p
- * Calculate $V_x = () \cdot V_{test}$
- ve sign if this number is negative