



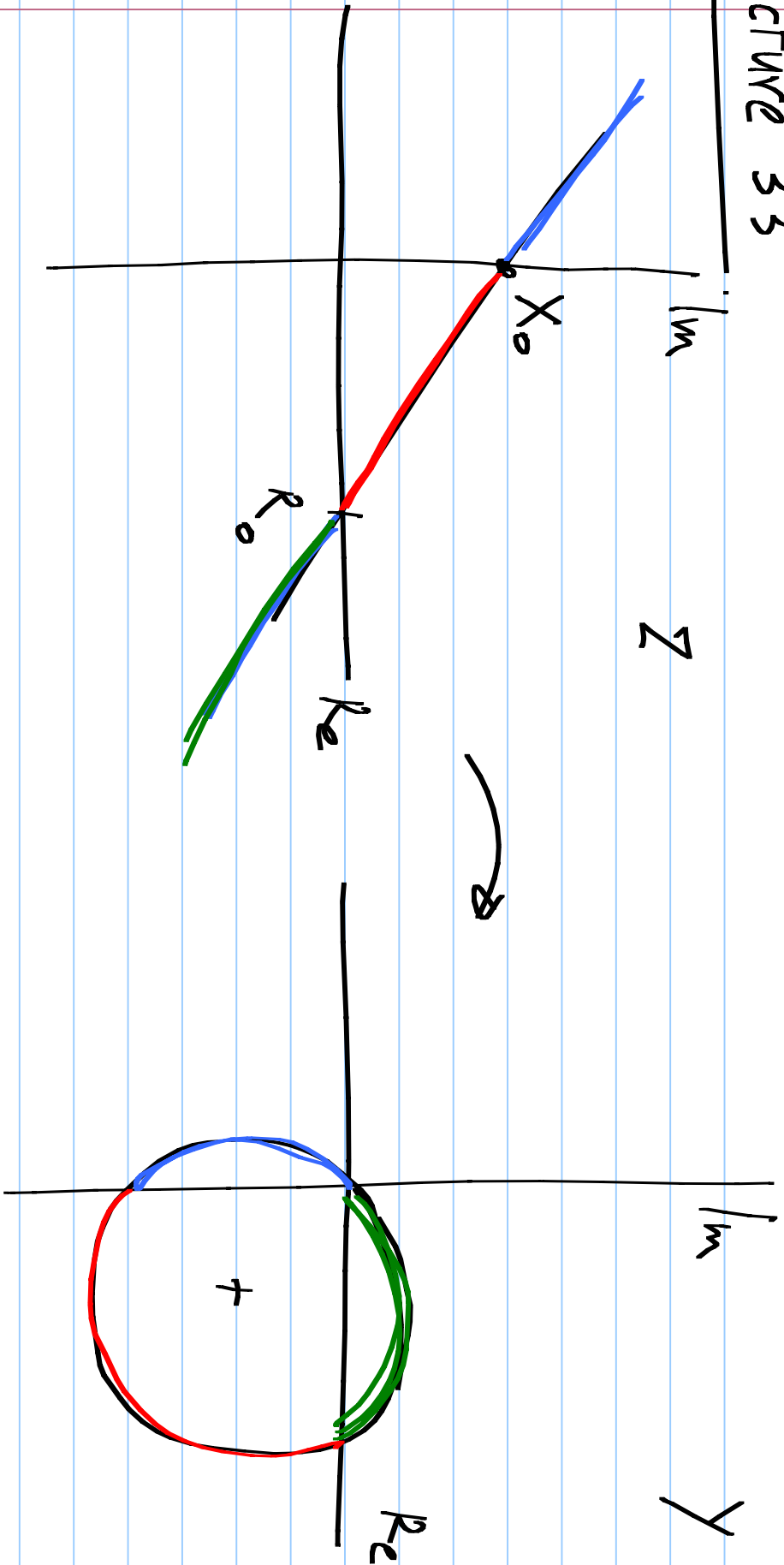
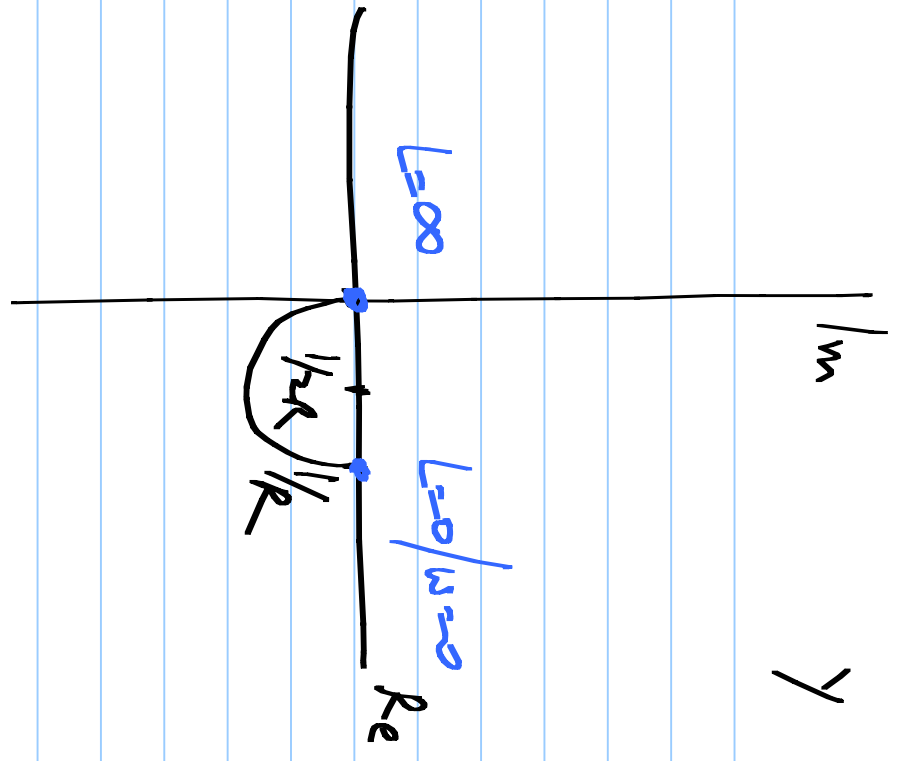
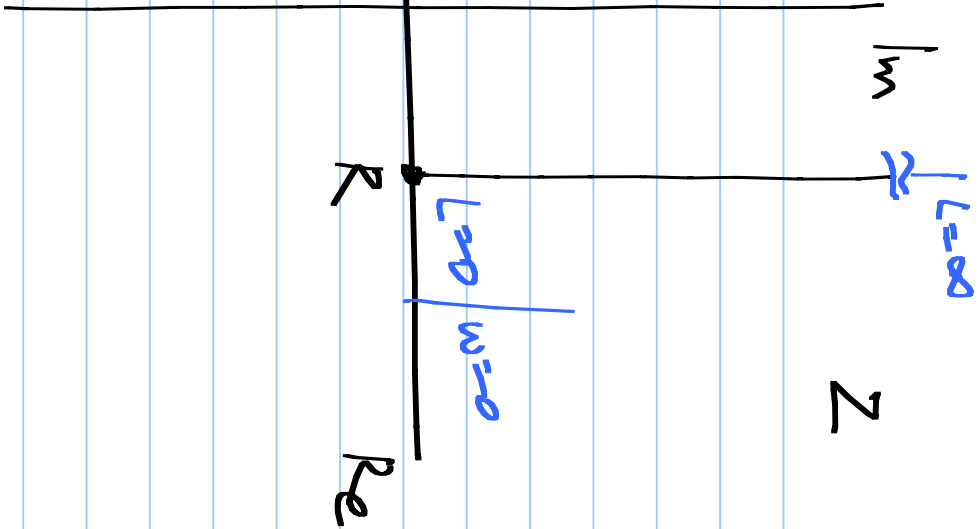


Lecture 33



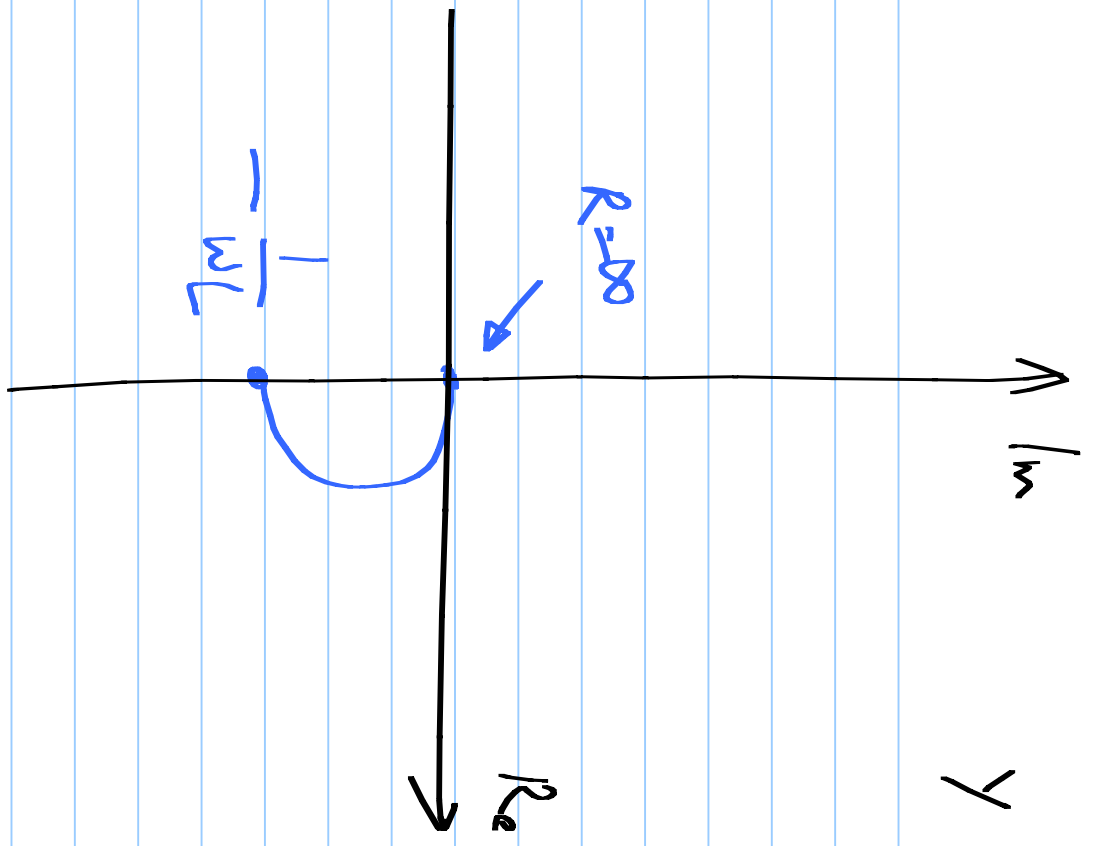


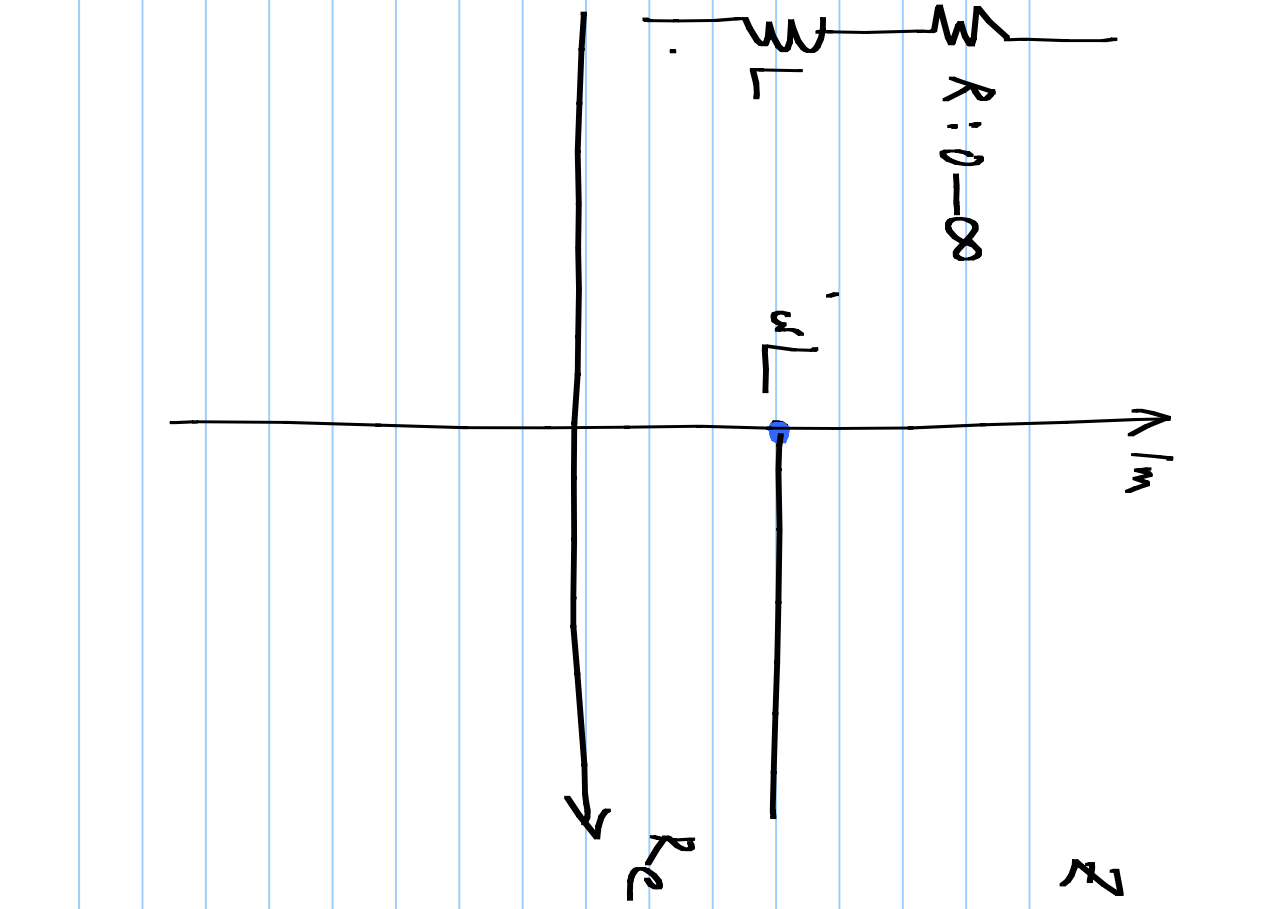

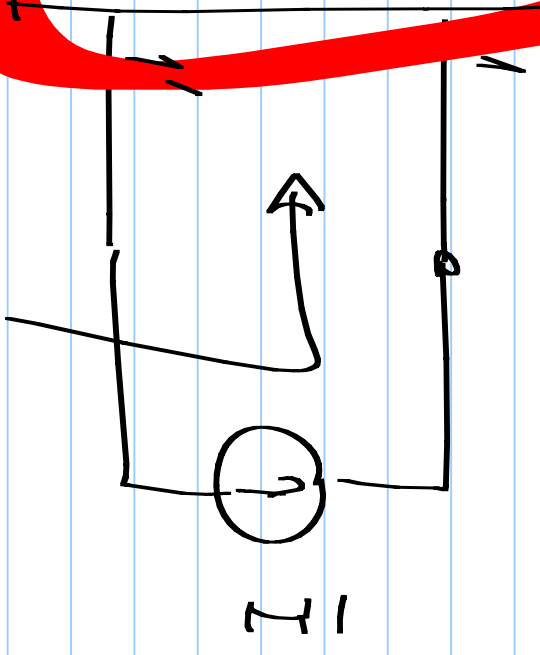

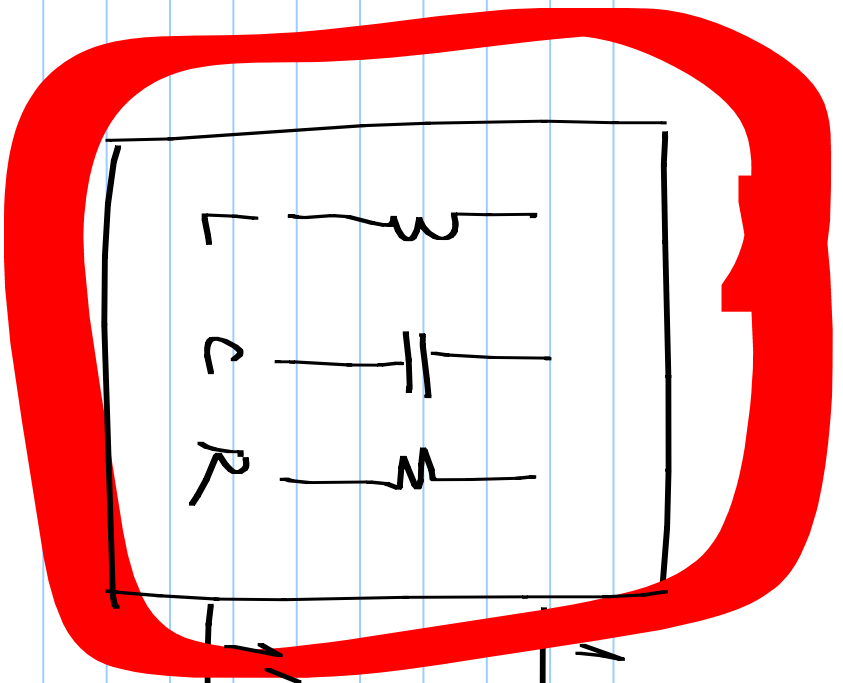

$$R_e \left\{ I \left(R_o + jX_o \right) I^* \right\} = \frac{|I|^2 R_o}{2}$$

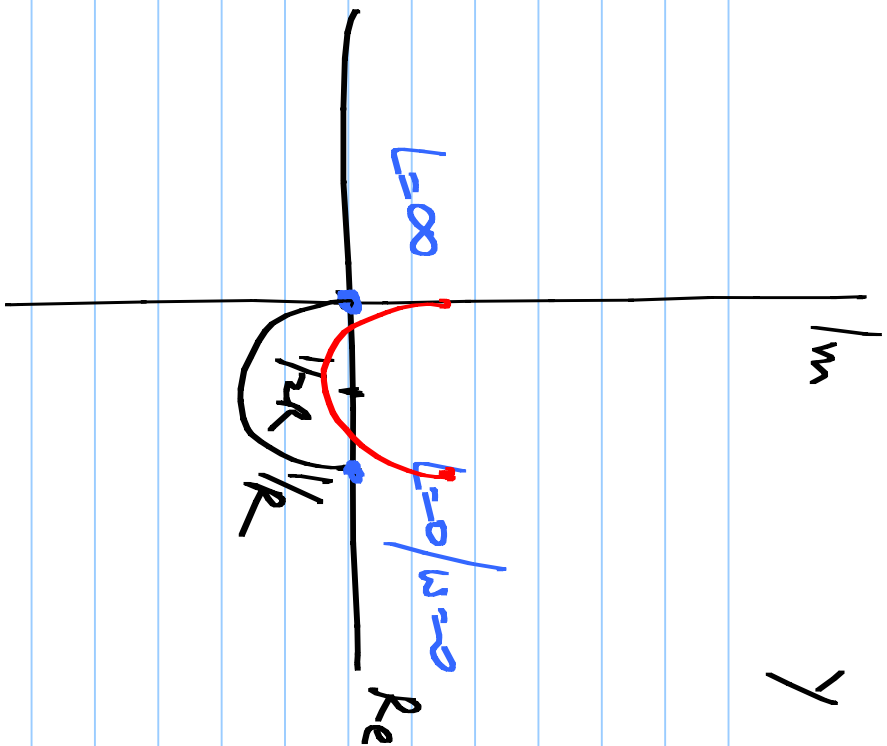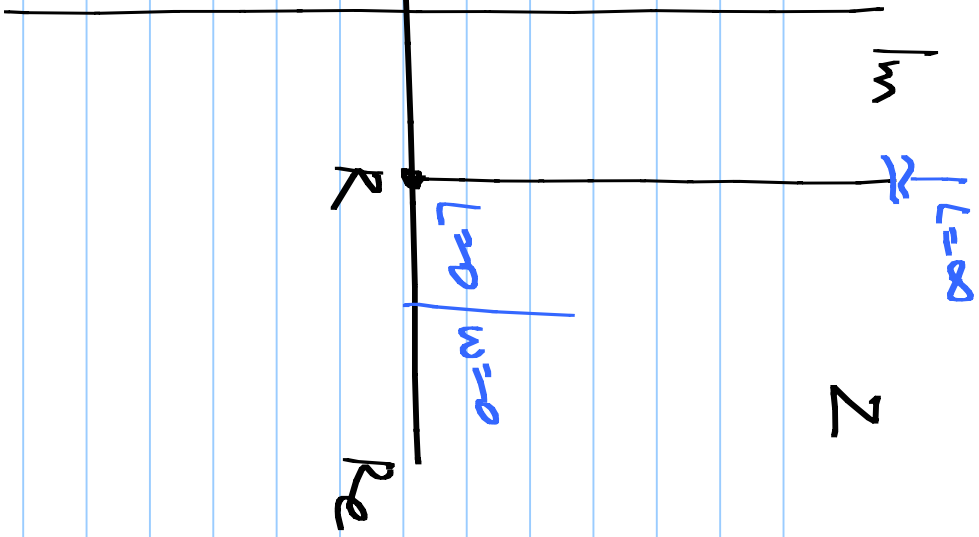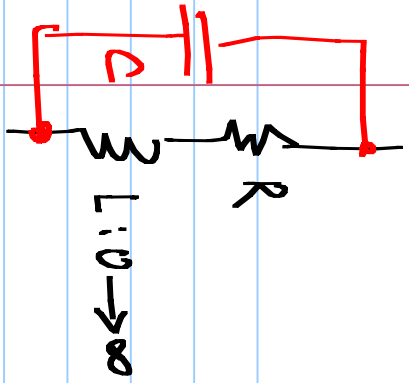

$$y = \frac{1}{z}$$


$$|z - z_0| = r_{z_0}$$

$$(z - z_0)(z^* - z_0^*) = r_{z_0}^2$$



$$\left(\frac{1}{y} - z_0\right)\left(\frac{1}{y^*} - z_0^*\right) = r_{z_0}^2$$



$$\left|y - \frac{1}{\alpha z_0}\right| = \frac{\sqrt{1 - \alpha}}{\alpha |z_0|}$$

$$\alpha = \left[1 - \frac{r_{z_0}^2}{|z_0|^2}\right]$$

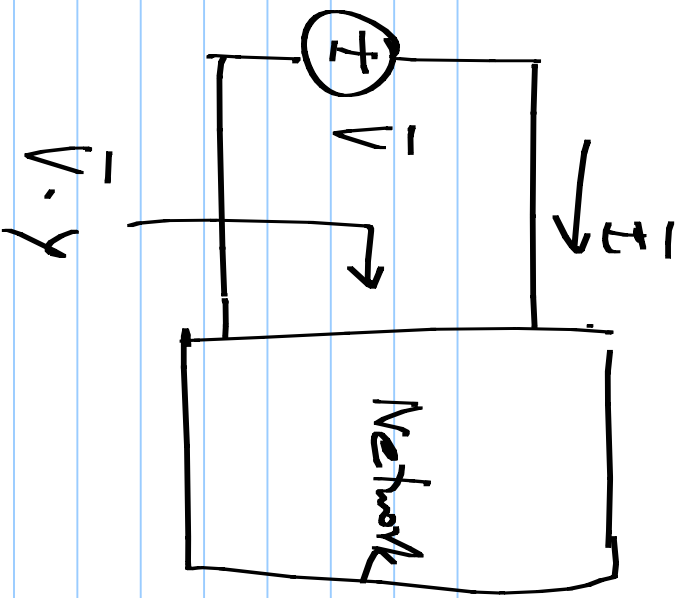

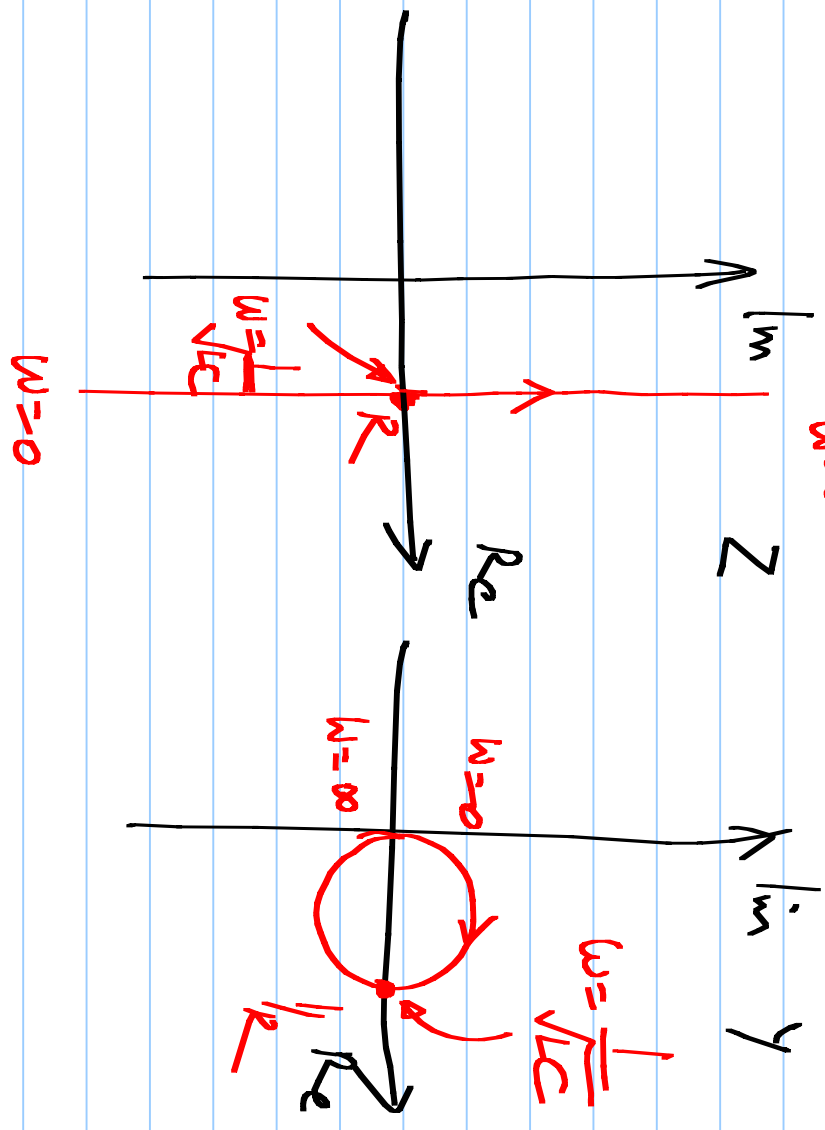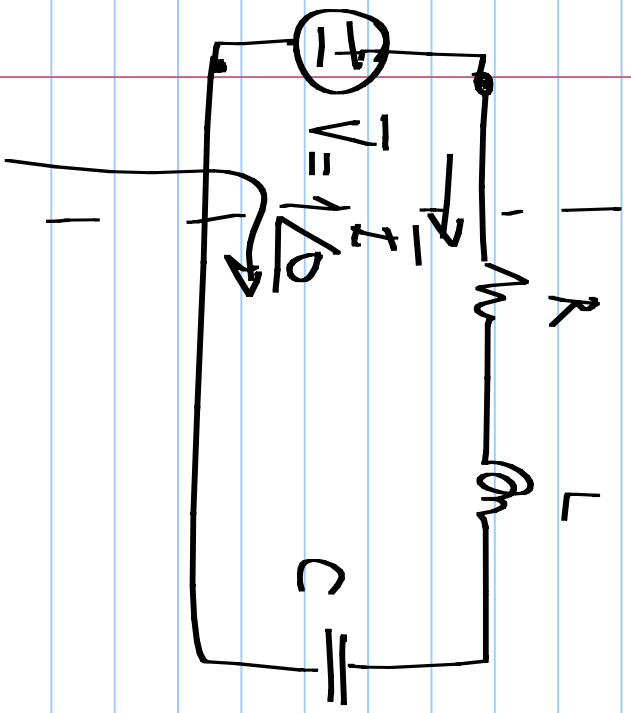
2nd order network: Series RLC $\omega: 0 - \infty$



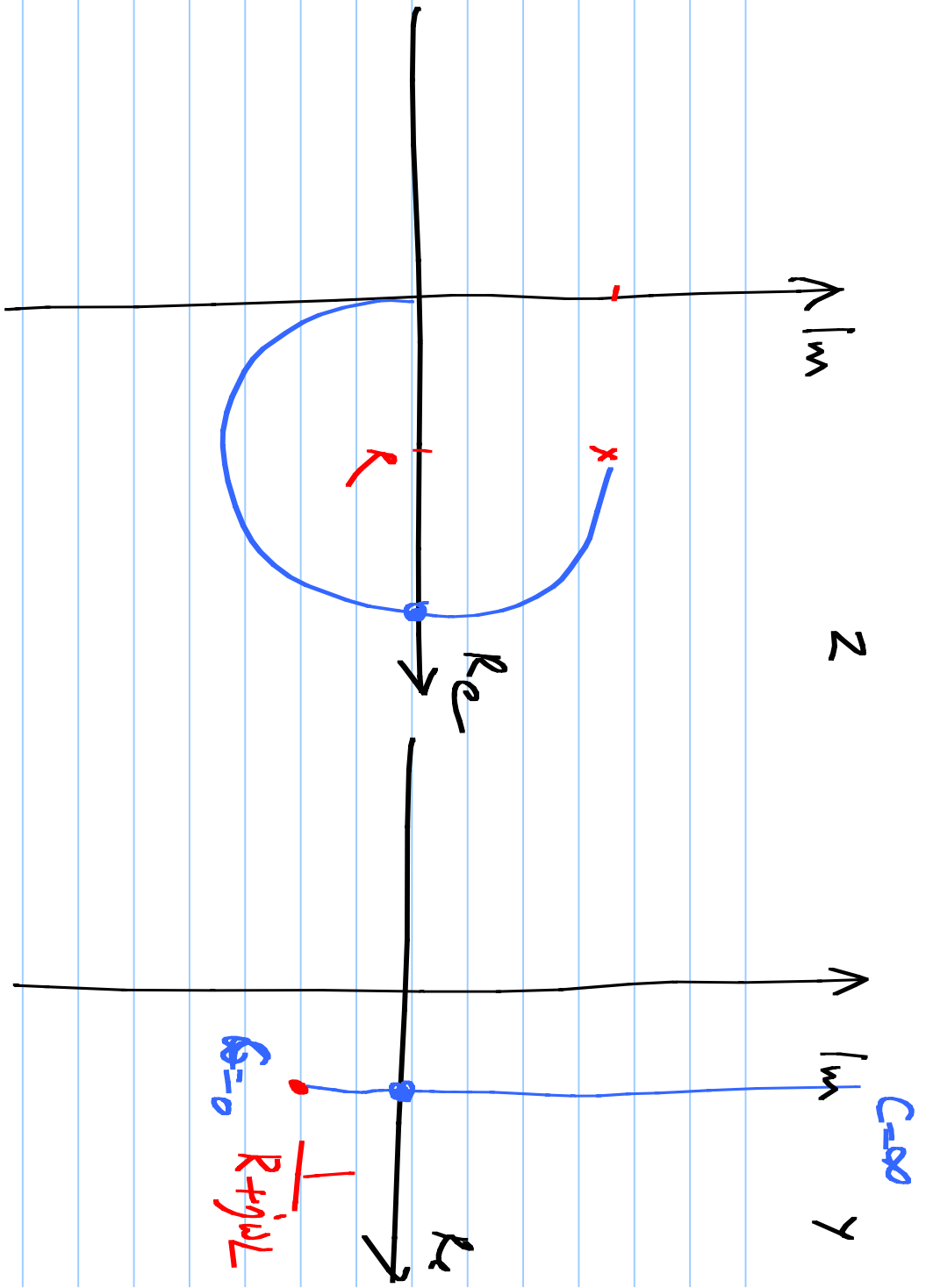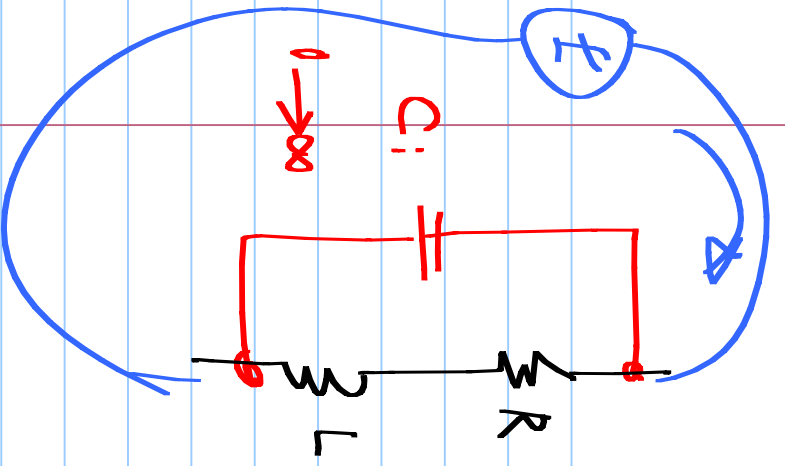

Mutual inductance
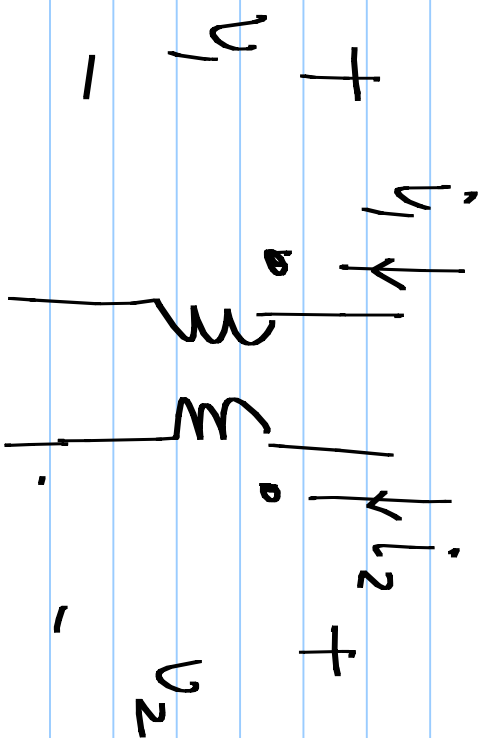
$$\underline{\underline{\begin{bmatrix} \bar{V}_1 & \bar{V}_2 \\ \bar{I}_1 & \bar{I}_2 \end{bmatrix}}}$$



$$\bar{V}_1 = \bar{V} \exp(j\omega t)$$

$$\bar{V}_2 = \bar{V}_2 \exp(j\omega t)$$

$$\bar{I}_1 = \bar{I}_1 \exp(j\omega t)$$

$$\bar{I}_2 = \bar{I}_2 \exp(j\omega t)$$

$$\begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \end{bmatrix}$$