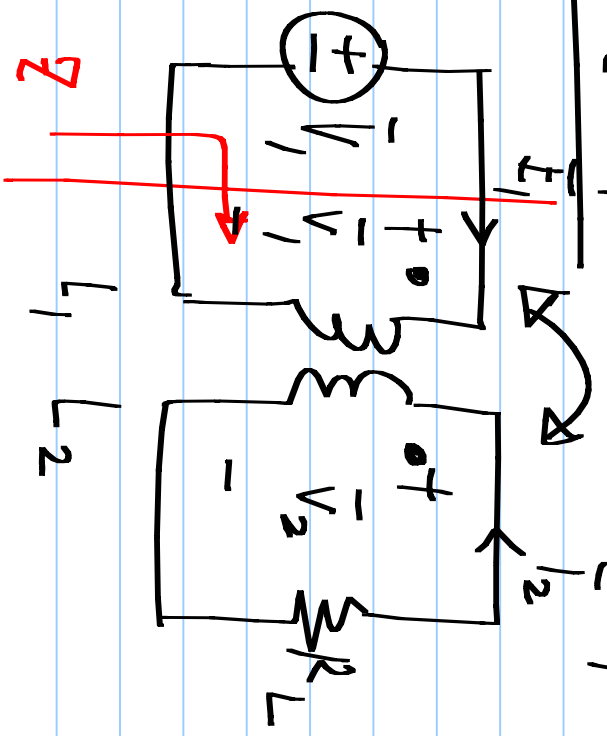


Lecture 34

$$M = k \sqrt{L_1 L_2}$$



$$\vec{V}_1 = j\omega L_1 \vec{I}_1 + j\omega M \vec{I}_2$$

$$\vec{V}_2 = j\omega M \vec{I}_1 + j\omega L_2 \vec{I}_2$$

$$\vec{V}_2 = -\vec{I}_2 \cdot R_L$$

$$\vec{I}_2 = - \frac{j\omega M \vec{I}_1}{j\omega L_2 + R_L}$$


$$Z = \frac{\vec{V}_1}{\vec{I}_1} = j\omega L_1 + \frac{k^2 L_1 L_2 \omega^2}{R_L + j\omega L_2} = \frac{j\omega L_1 R_L + \omega^2 L_1 L_2 (k^2 - 1)}{R_L + j\omega L_2}$$

$$Z = \frac{V_1}{I_1} = j\omega L_1 + \frac{k^2 L_1 L_2 \omega^2}{R_L + j\omega L_2} = \frac{j\omega L_1 R_L + \omega^2 L_1 L_2 (k^2 - 1)}{R_L + j\omega L_2}$$

$$= j\omega L_1 \cdot \left[1 + j \frac{\omega L_2}{R_L} (1 - k^2) \right]$$


$k = 1,$
 $L_1, L_2 \rightarrow \infty$
 $L_1/L_2 = \eta^2$

$$\frac{V_2}{V_1} = \frac{M/L_1}{1 + j \frac{\omega L_2}{R_L} (1 - k^2)}$$

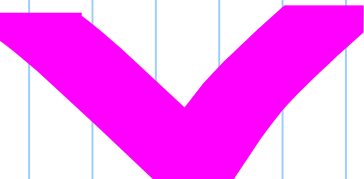
 $= \frac{1}{\eta}$

$$j\omega L_1 \cdot \left[1 + \frac{j\omega L_2}{R_L} \right] = R_L \cdot \frac{L_1}{L_2} = R_L \cdot \eta^2$$

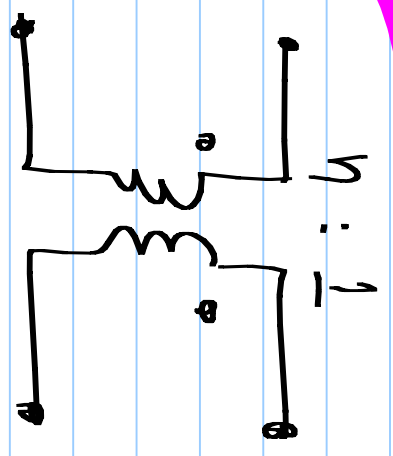
ideal transformer
 $\left\{ \begin{array}{l} k \rightarrow 1, \\ L_1, L_2 \rightarrow \infty \\ \frac{L_1}{L_2} = \eta^2 \end{array} \right.$




Ideal transformer:

Mutually coupled coils with $k \rightarrow 1$ & $L_1, L_2 \rightarrow \infty$
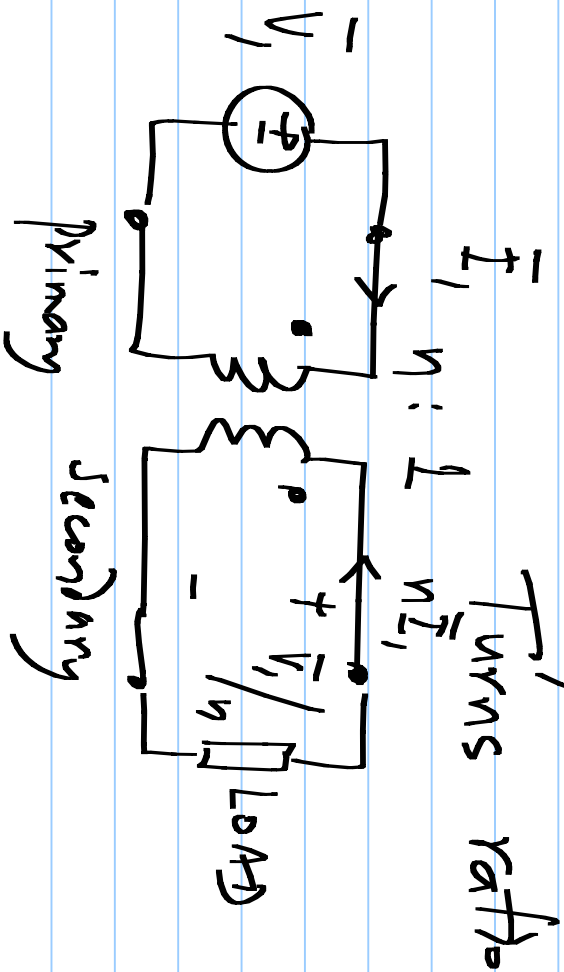
$$\frac{L_1}{L_2} = n^2 \quad \left\{ \begin{array}{l} n:1 \text{ transformer} \end{array} \right.$$



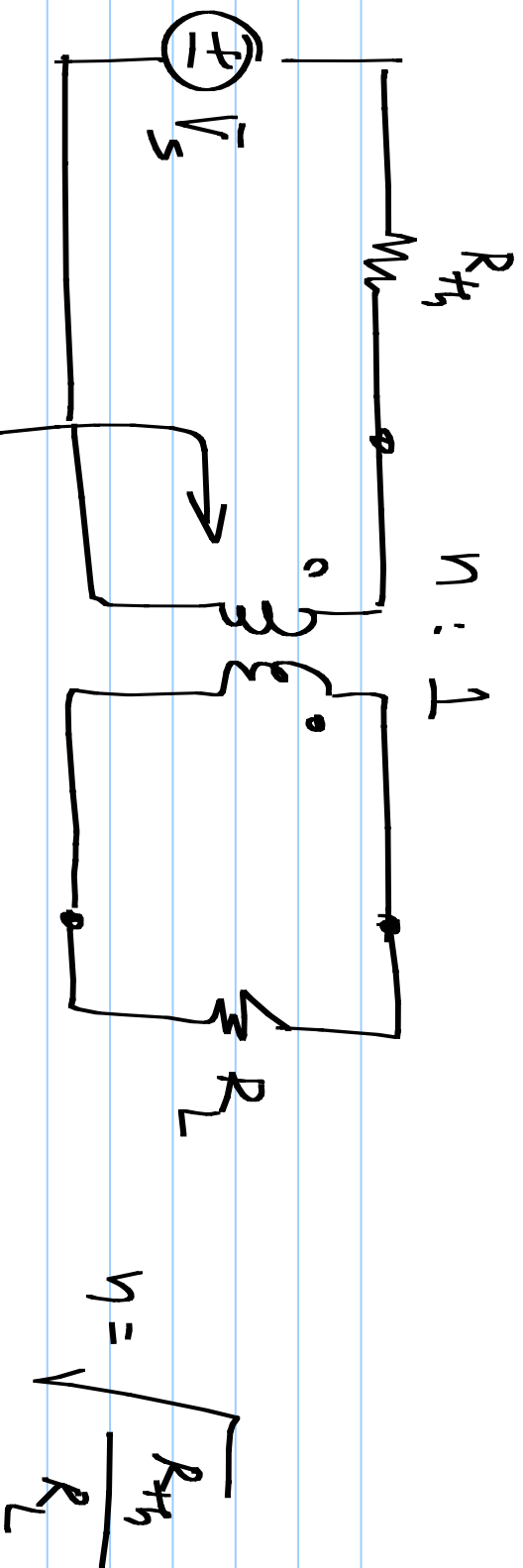

$$n^2 R_L = R_{H_s}$$

$$n^2 R_L$$

Transformers for impedance matching