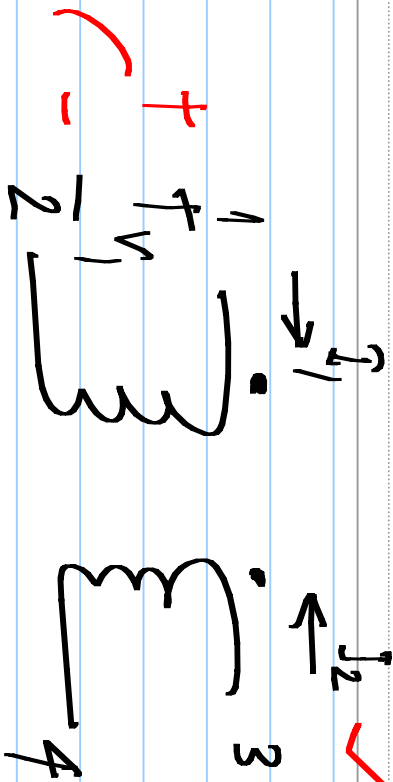




EC1010: Lecture 4


Note Title

1/22/2014





$-V_e$
Voltage
 L_1, L_2, M

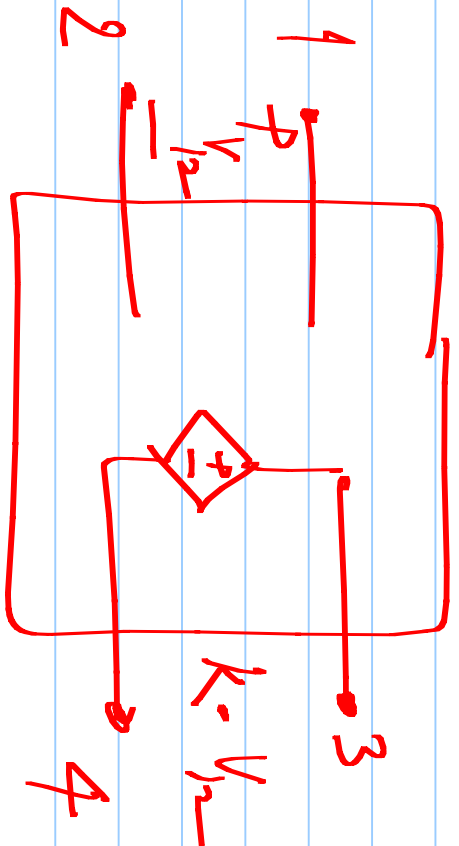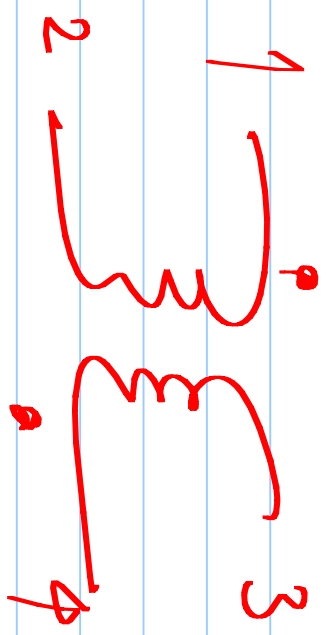

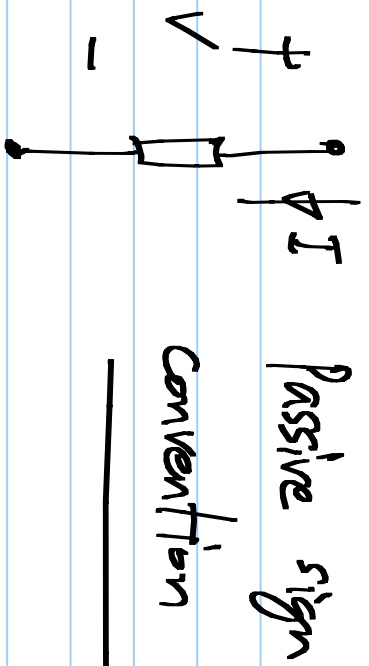


Passive elements:

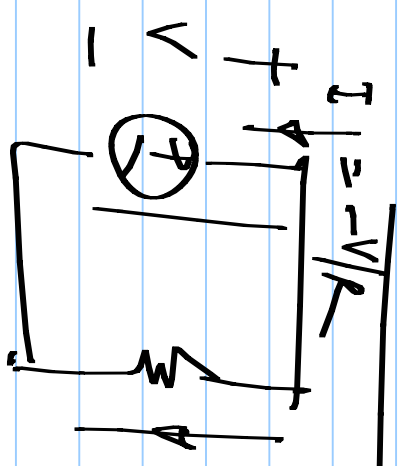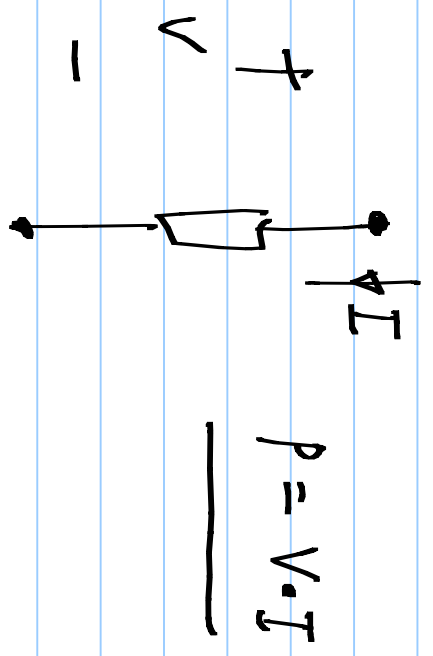Elements that do not generate power, only dissipate it



Resistor:

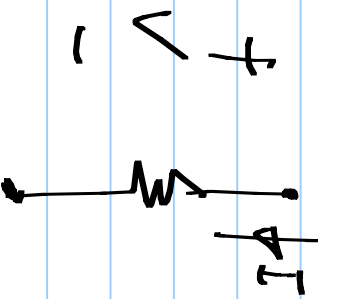

$$I = V/R$$

$$P = V \cdot I = \frac{V^2}{R} > 0$$

Power always dissipated in a resistor

$$E = \int_0^{T_0} P(t) dt > 0$$

Energy dissipated


Power flowing into the element
Energy flowing into the element

Capacitors:

Can only absorb energy (discharged capacitor)

$P(t) = V(t) \cdot I(t)$ either positive or

negative

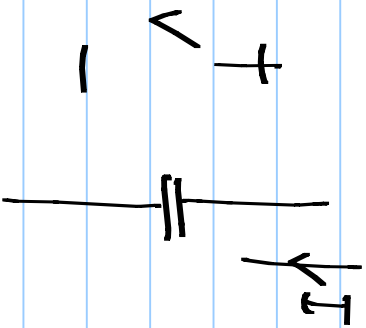


$$E = \int_0^{T_0} \underbrace{V(t)} \cdot C \underbrace{\frac{dV(t)}{dt}} \cdot dt$$

$$\frac{1}{2} \frac{d}{dt} V^2(t)$$

$$I = C \cdot \frac{dV}{dt}$$

$$= \frac{1}{2} C \left[\underbrace{V^2(T_0) - V^2(0)}_{V(0)=0} \right]$$

$$V(0)=0$$

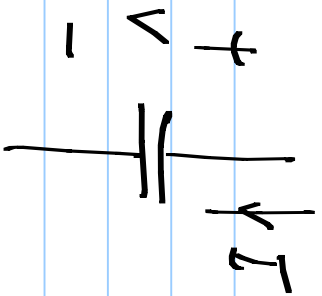


Instantaneous power: positive or negative

Energy: absorbed & stored

Dissipation: Zero

Inductor:

$P = V \cdot I$ either +ve or -ve

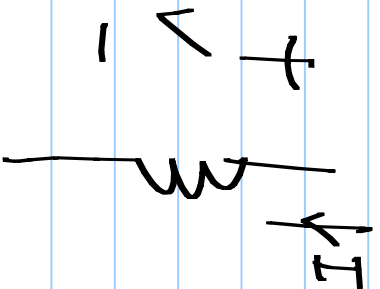



$$V = L \cdot \frac{dI}{dt}$$

$$E = \int_0^{T_0} L \cdot \frac{dI}{dt} \cdot I \cdot dt$$

$$= \frac{1}{2} L \left(I^2(T_0) - I^2(0) \right)$$

Stored energy = $\frac{1}{2} L I^2$

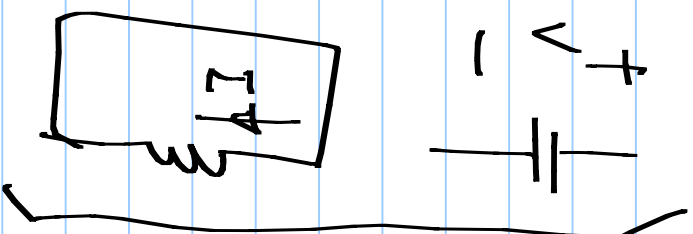

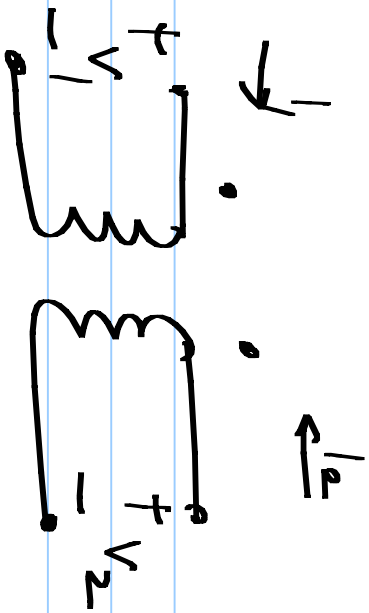

$$P = v_1 i_1 + v_2 i_2$$

$$P = L_1 i_1 \frac{di_1}{dt} + L_2 i_2 \frac{di_2}{dt} + M \left(i_1 \frac{di_2}{dt} \right)$$

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} + i_2 \frac{dM}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$


$$E = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2 \geq 0$$

Coupling coefficient

$$k < 1$$


$$M \leq \sqrt{L_1 L_2}$$

$$M = k \sqrt{L_1 L_2}$$

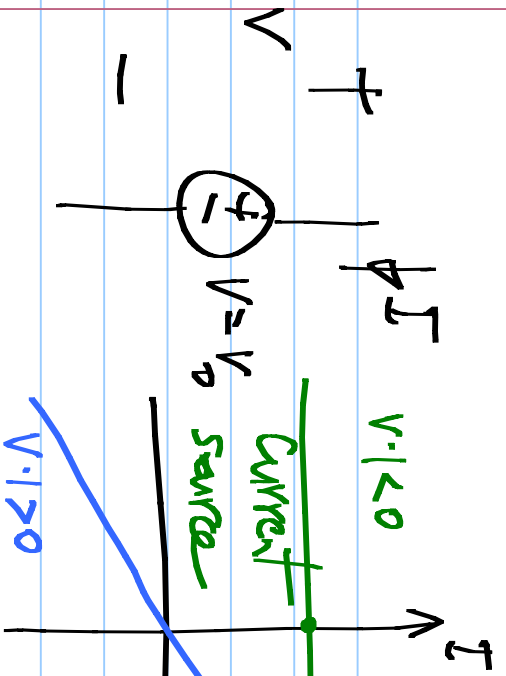

$P = V \cdot I$


dissipated in the
voltage source

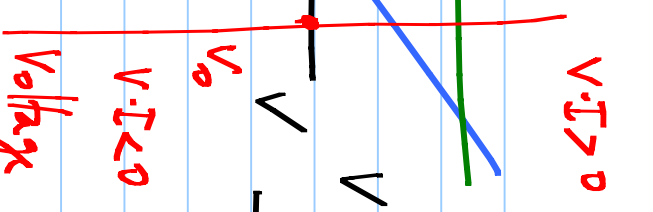

Source


$P = V \cdot I$

dissipated in
the current source

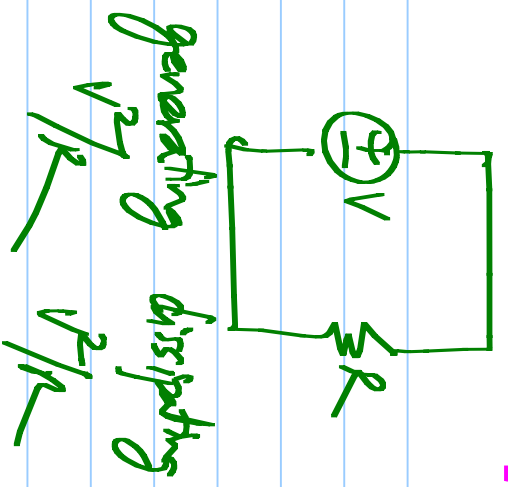

generating
dissipating

V^2/R

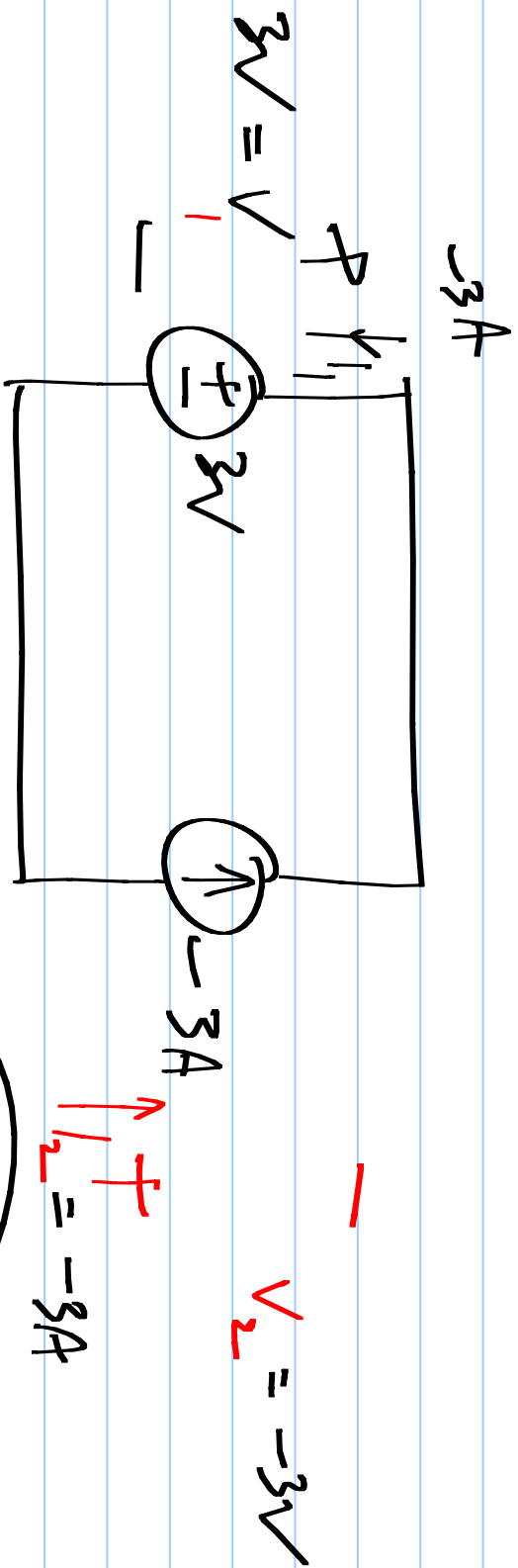

$V_{11} = -9W$

Watt

Take

$V_{212} = 9W$

$I_2 = -3A$

$V_2 = -3V$