


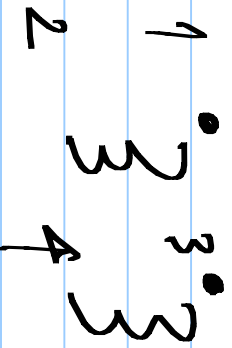
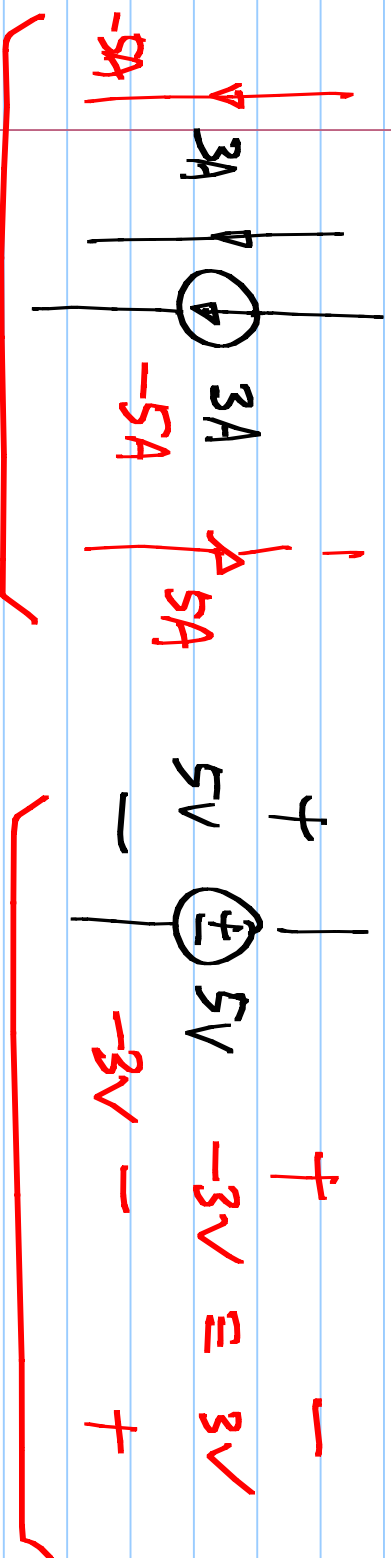
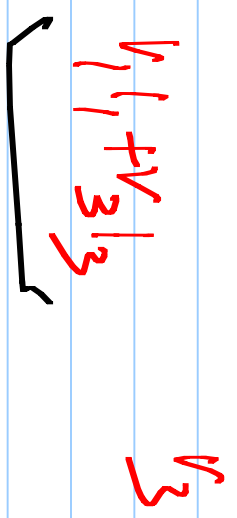
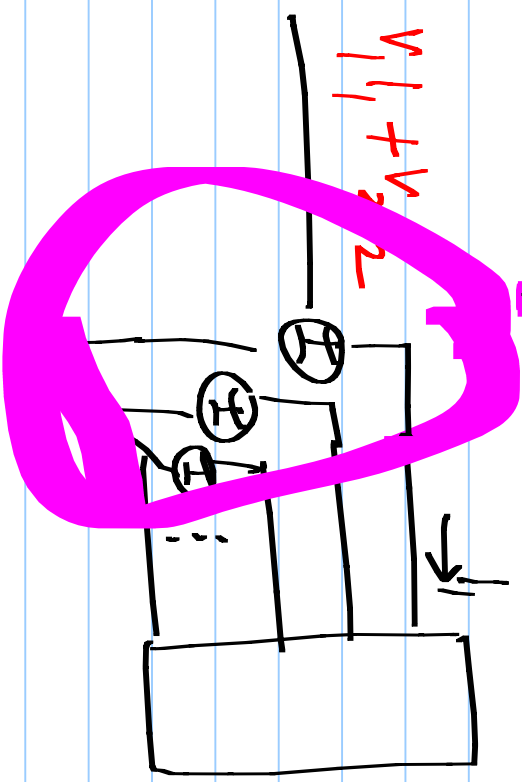


EC1010: Lecture 5


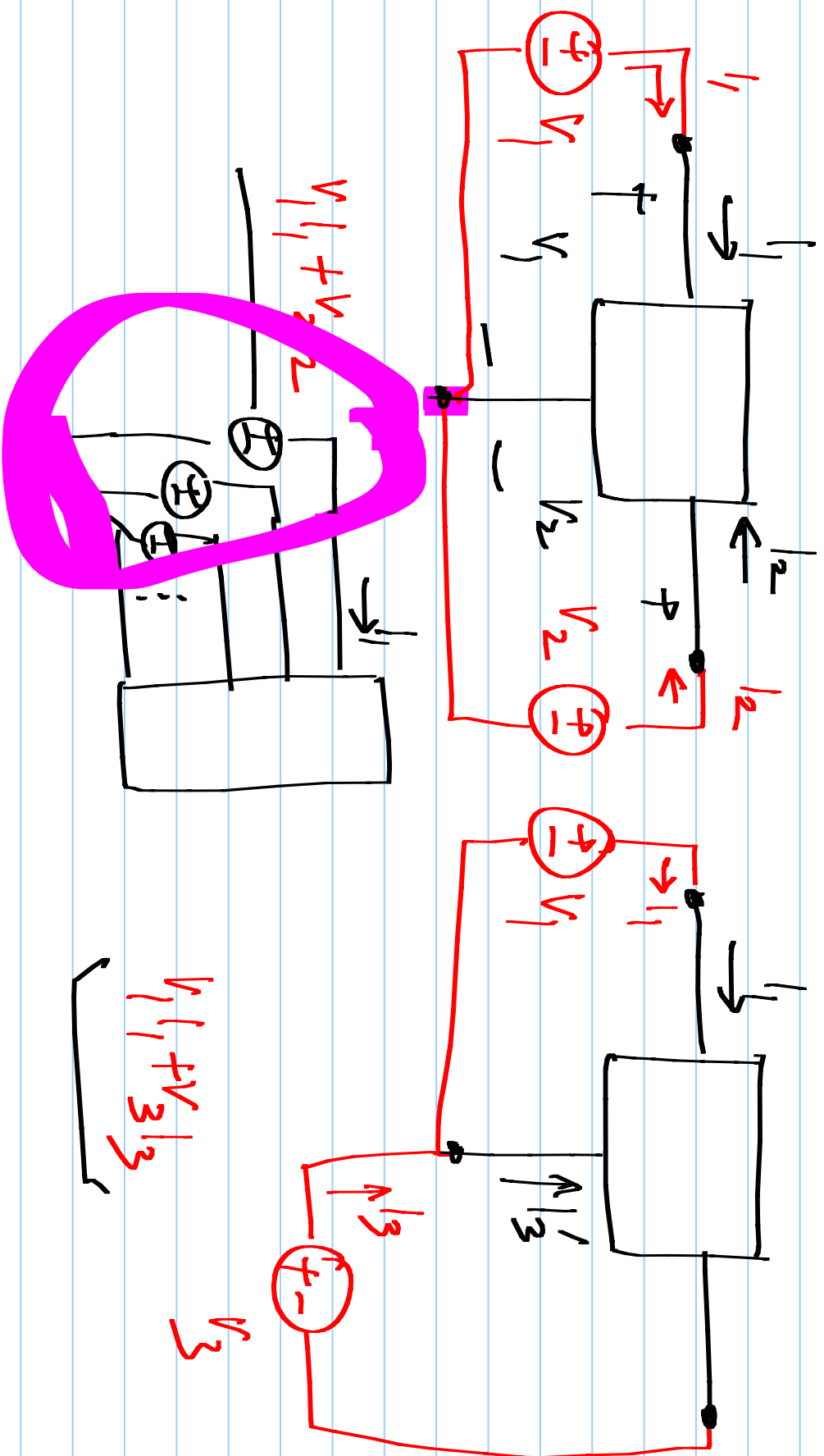


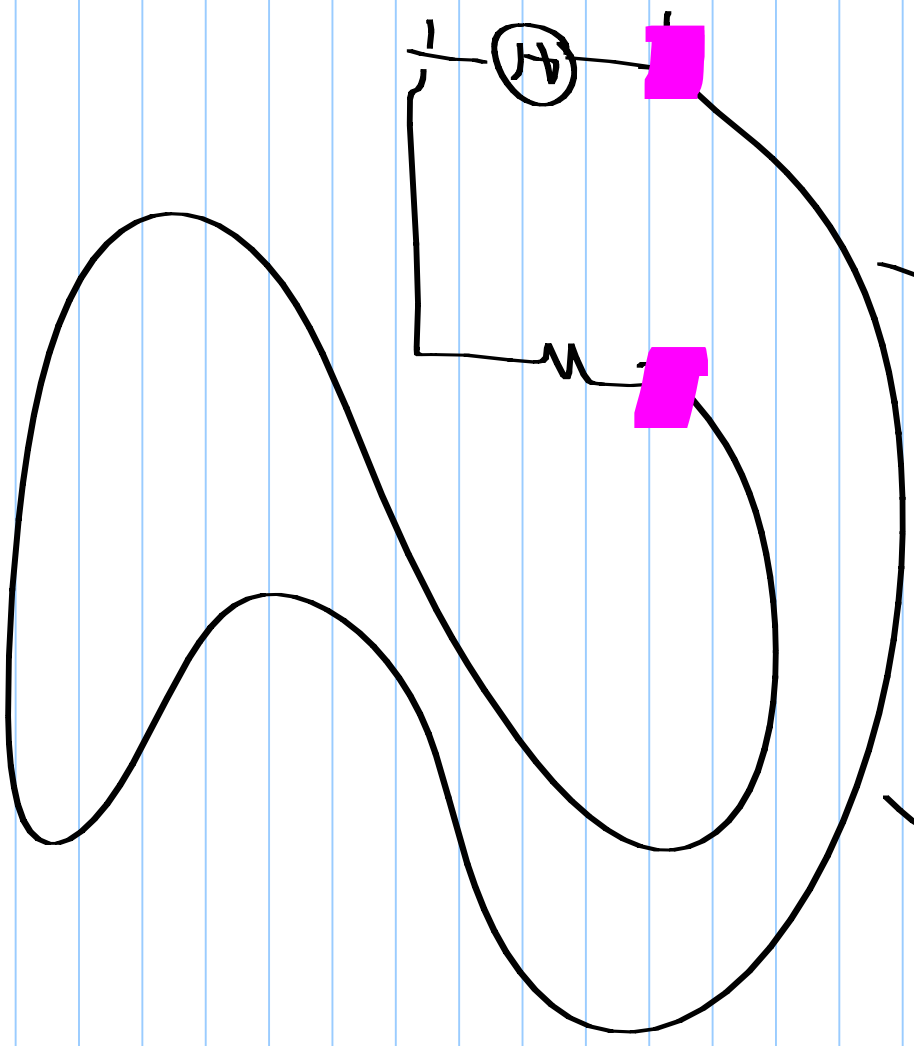

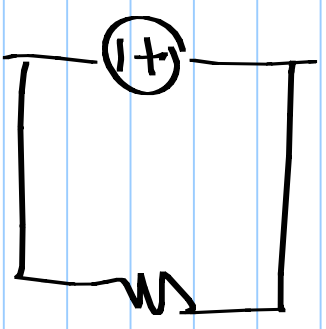
Wire: Ideal (zero resistance / short ckt ...)




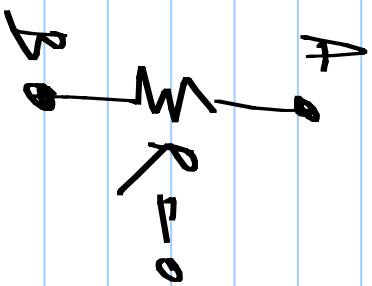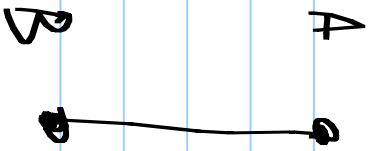Short circuit (between 2 nodes) \Rightarrow Voltage difference between those nodes $= 0$



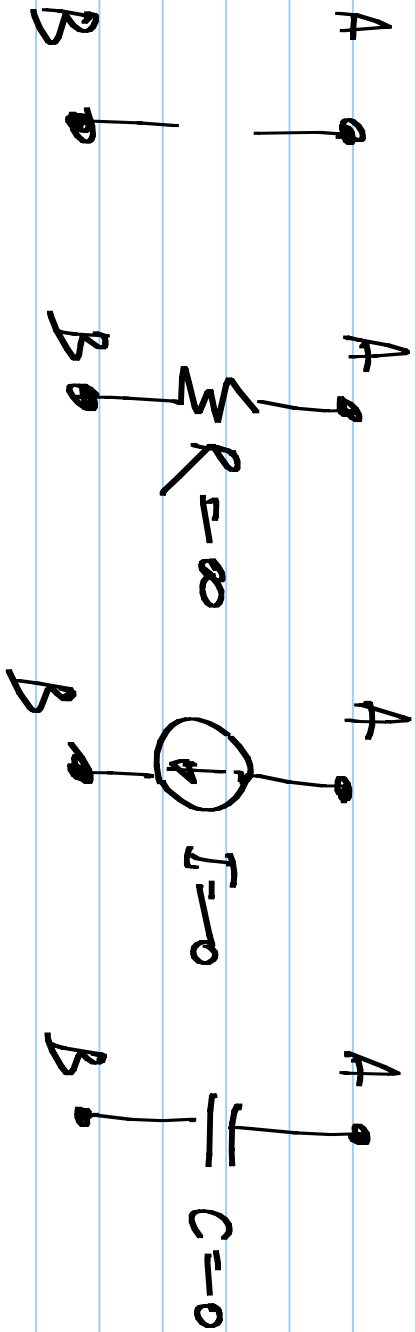open circuit: (along a branch) \Rightarrow current along that branch $= 0$




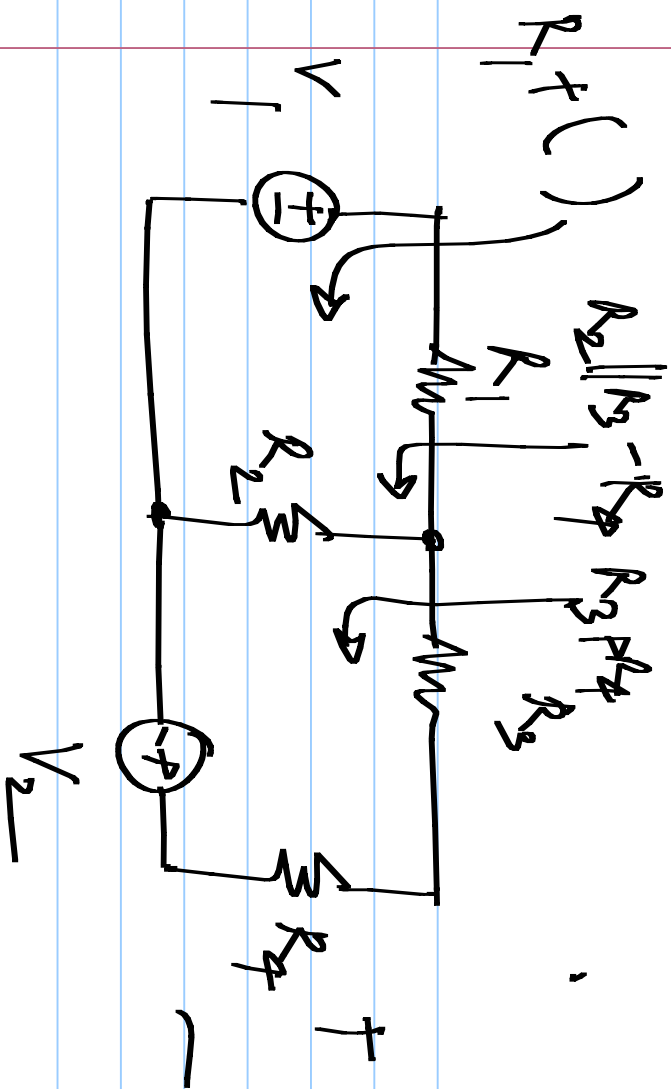

Node: point of interconnection of multiple elements
(Terminals)

Branches: Elements between nodes

2B variables

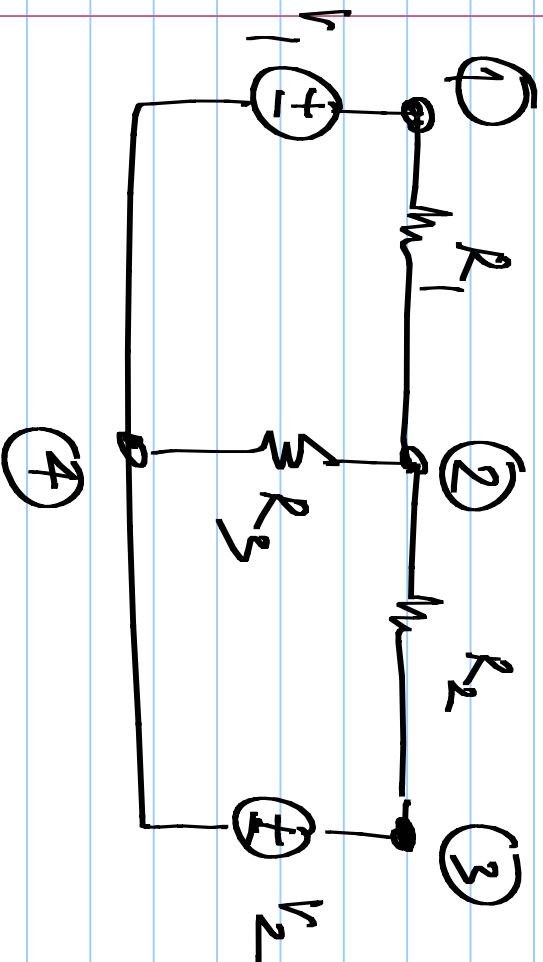


$N = 4$ nodes $N-1$

$B = 5$ branches

$B - N + 1$
KCL, KVL, B

Element relationships

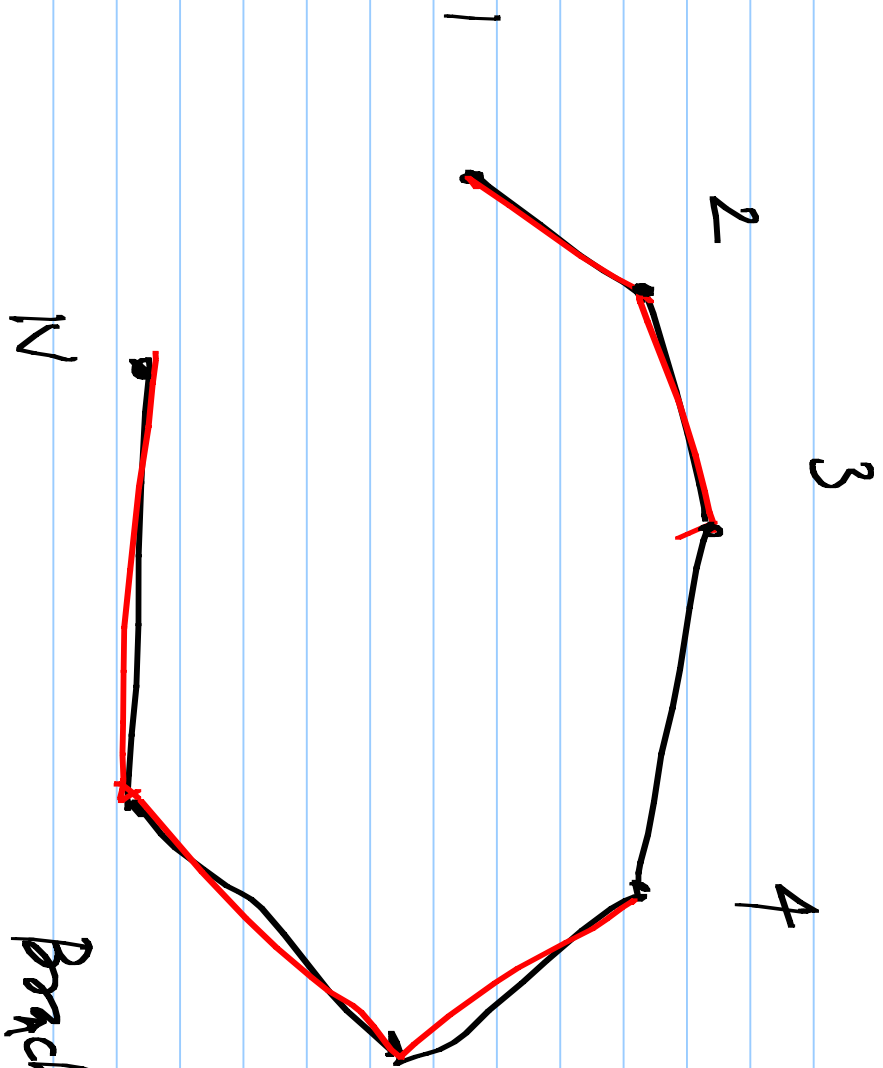

Sub-
Tree: Network
(of the original) N
connecting

nodes without

forming a


loop

(contains $N-1$




branches)


Branches not in a tree

\equiv links

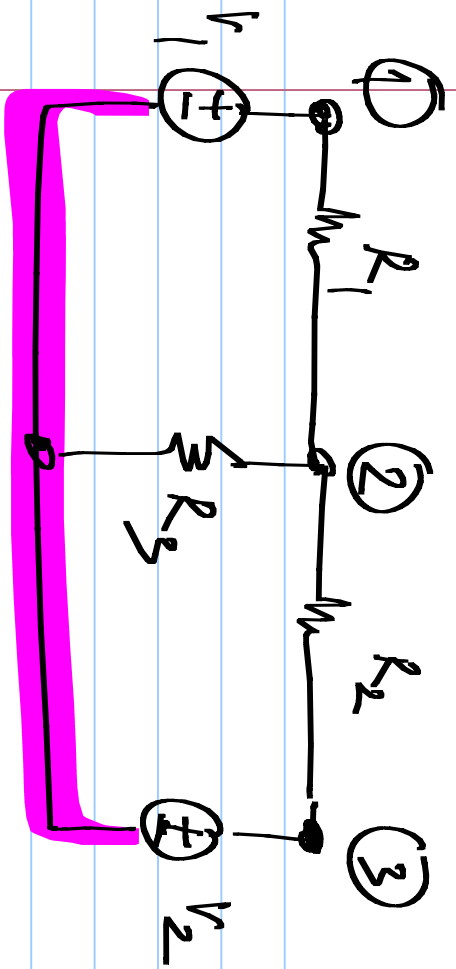


Trees

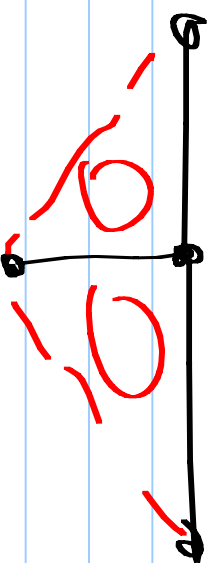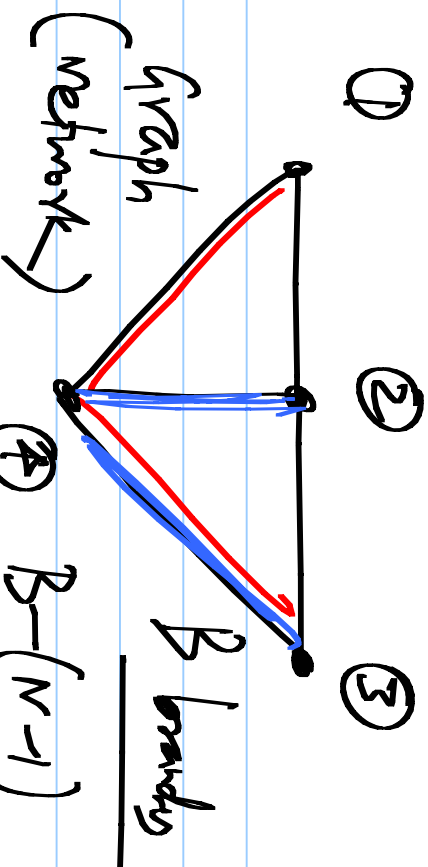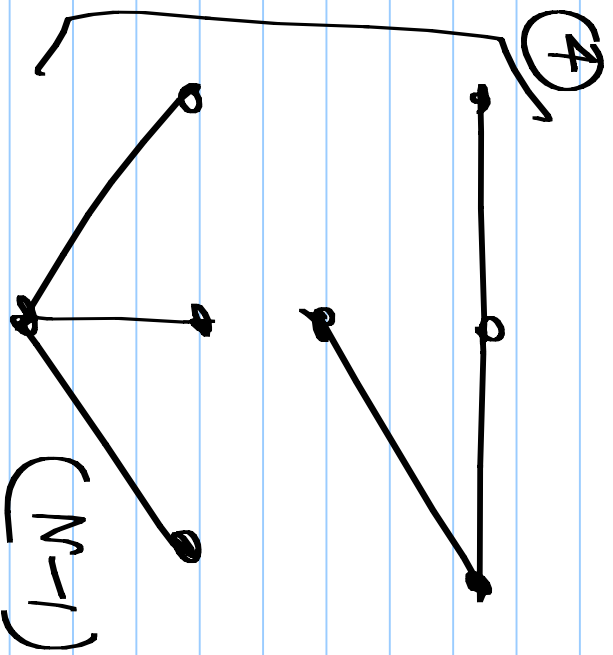


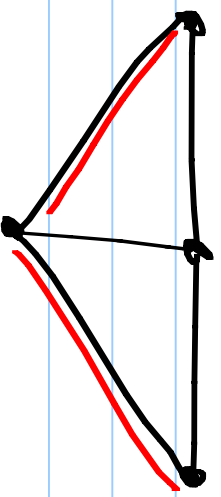

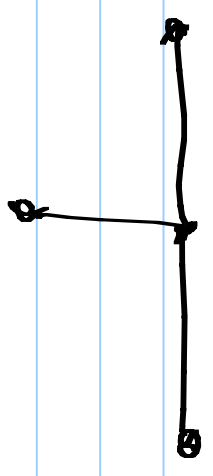
original $B (= 5)$ branches
network: $N (= 4)$ nodes





Tree: $N - 1$ branches

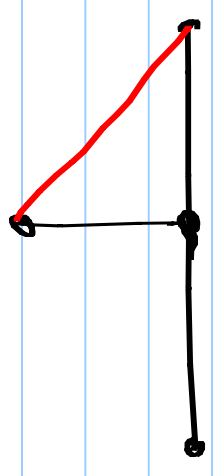

Links: $B - (N - 1)$ branches left out

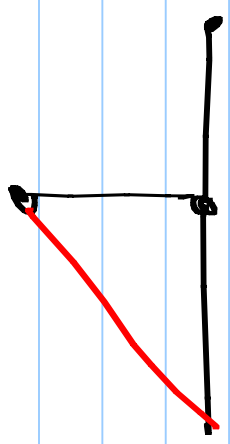

$B - N + 1$ loops

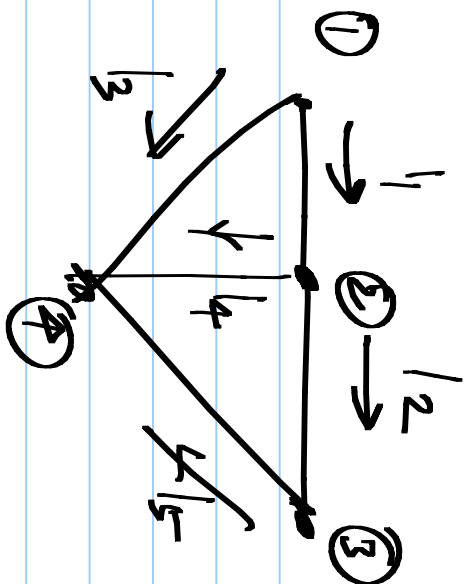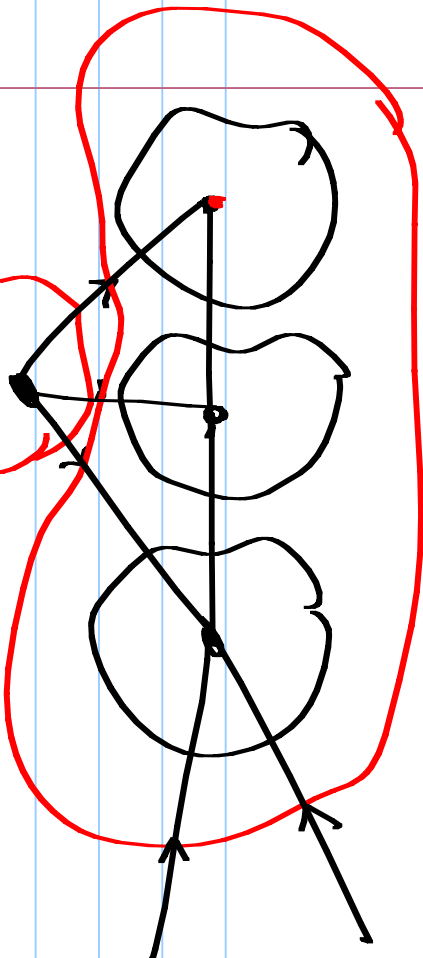

$$-1/3 - 1/4 - 1/5 = 0$$


N-1 KCL eq.

N-1 KCL eq.

$$\begin{cases} 1 + 1/3 = 0 \\ -1 + 1/2 + 1/4 = 0 \\ -1/2 + 1/5 = 0 \end{cases}$$

$$\underline{1/3 + 1/4 + 1/5 = 0}$$

Nodal analysis: KCL at $N-1$ nodes

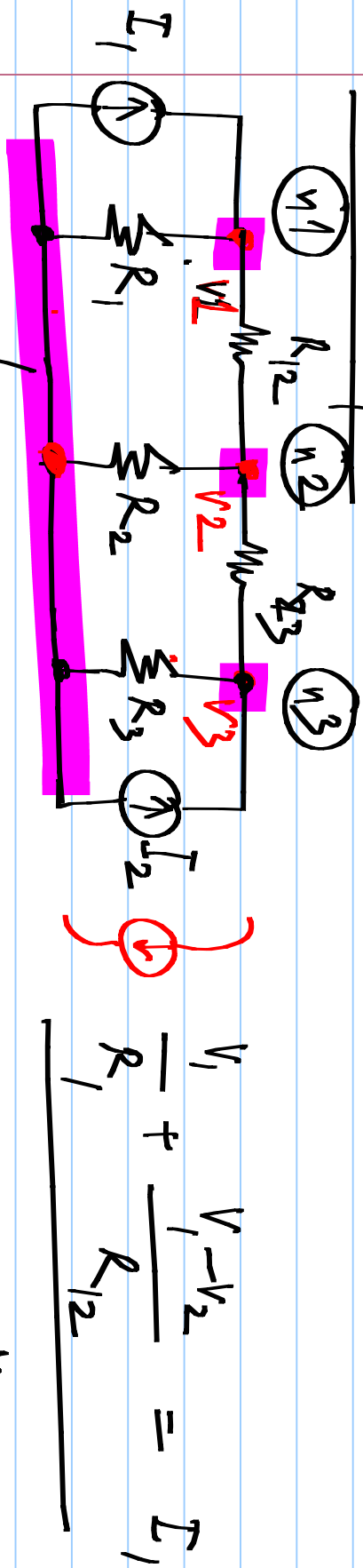

$$\frac{V_1}{R_1} + \frac{V_1 - V_2}{R_{1/2}} = I_1$$

$$\frac{V_2 - V_1}{R_{1/2}} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_{2/3}} = 0$$

$$\frac{V_3 - V_2}{R_2} + \frac{V_3}{R_3} = I_2$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_{1/2}} & -\frac{1}{R_{1/2}} & 0 \\ -\frac{1}{R_{1/2}} & \frac{1}{R_{1/2}} + \frac{1}{R_2} + \frac{1}{R_{2/3}} & -\frac{1}{R_{2/3}} \\ 0 & -\frac{1}{R_{2/3}} & \frac{1}{R_2} + \frac{1}{R_3} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ 0 \\ I_2 \end{bmatrix}$$

$-I_2$

