




EECE 1010 : Lecture 10

Loop analysis

N nodes

B branches


$B - N + 1$ KVL equations

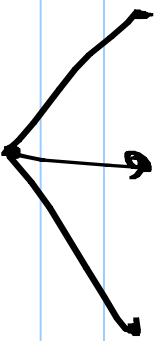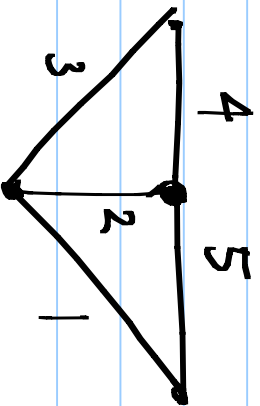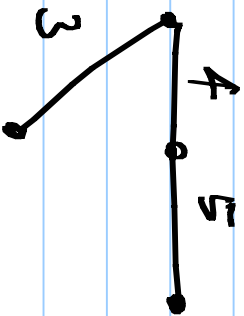


Tree: subset of branches which connect all N nodes without forming a loop.

Co-Tree: Graph - Tree




Branches: links

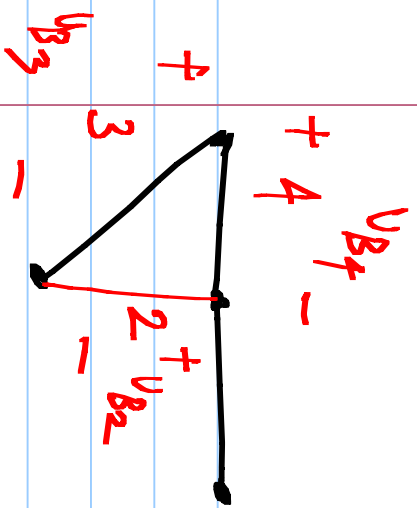


$$V_{B2} - V_{B3} + V_{B4} = 0$$

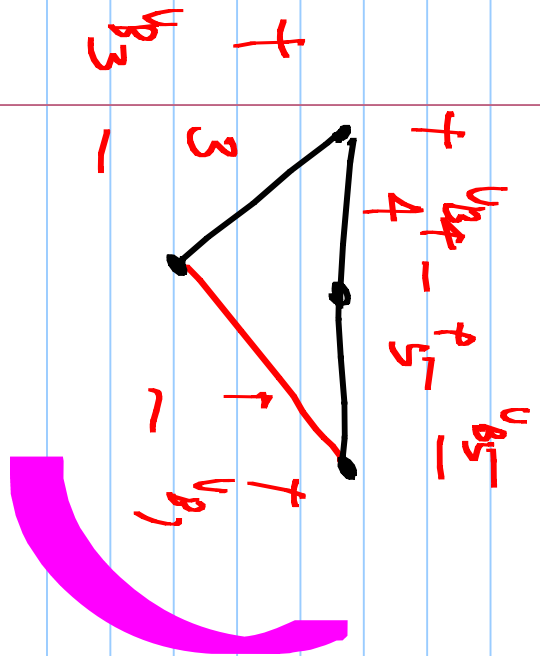
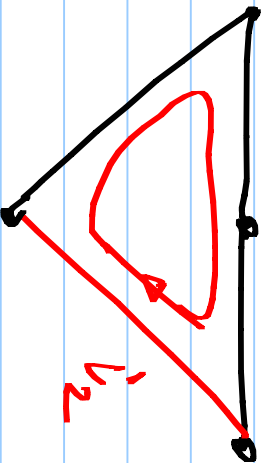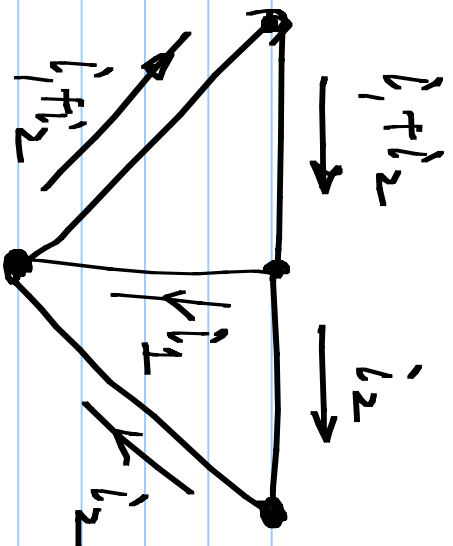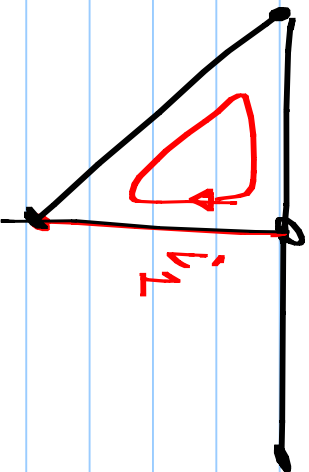
$$V_{B1} - V_{B3} + V_{B4} + V_{B5} = 0$$



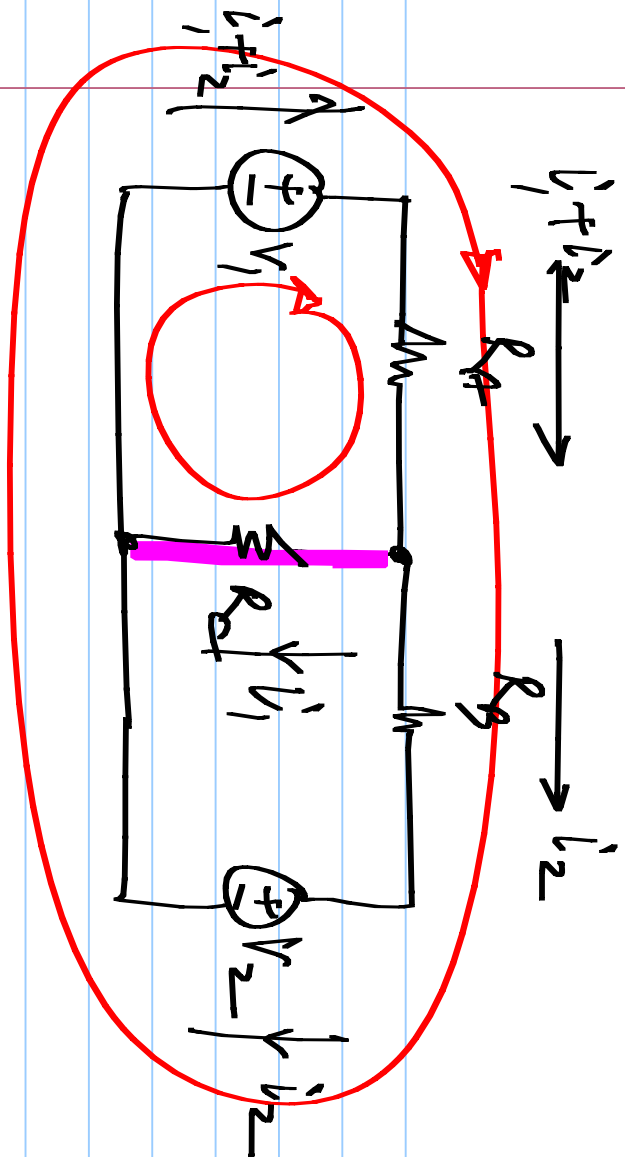

$$\begin{bmatrix} R_A + R_2 & R_A \\ R_A & R_A + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_1 - V_2 \end{bmatrix}$$

$$[R] \underline{i} = \underline{V}$$

$$V_{B2} - V_{B3} + V_{B4} = 0$$

$$V_{B1} - V_{B3} + V_{B4} + V_{B5} = 0$$


$$i_1 \cdot R_A - V_1 + (i_1 + i_2) R_A = 0$$

$$V_2 - V_1 + (i_1 + i_2) R_A + i_2 R_3 = 0$$

(Nodal) Nodal analysis → circuit simulators

N nodes


$N-1$ KCL equations

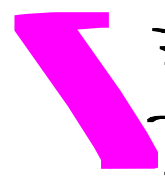

B branches

$B-N+1$ KVL equations

$$N \leq B \leq \frac{N(N-1)}{2}$$

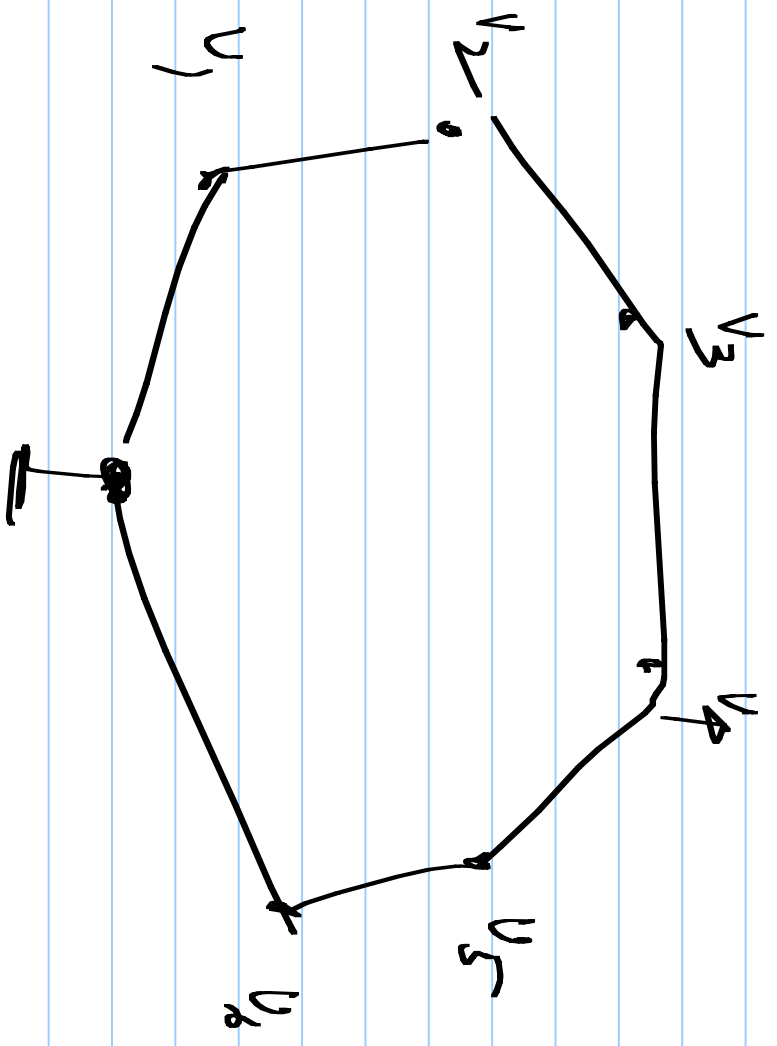

Solving a circuit: solve for all branch v, i

* Nodal analysis: node voltages wrt ref. node ✓

Branch voltages: $V_k - V_l$

Branch currents: Element relationship & branch voltage

* Loop analysis: link currents

Branch currents: $\sum_k i_k$

Branch voltages: Element relationship & branch currents,