
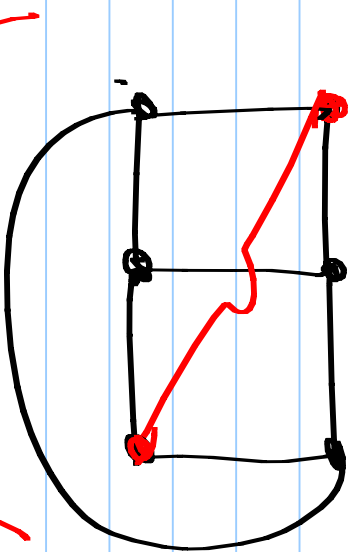
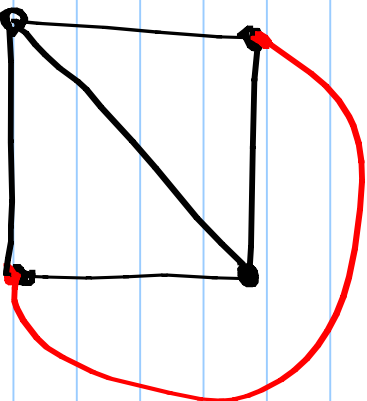


EECE 1010: Lecture 11


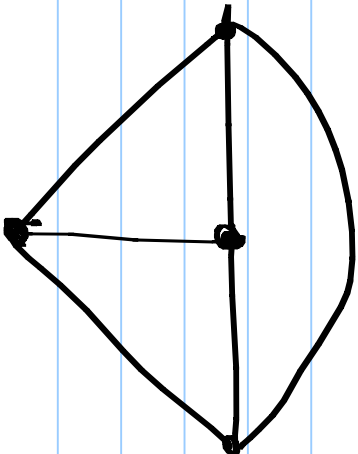
Mesh analysis (KVL based analysis for planar circuits)



Planar

X

Planar graphs / circuits

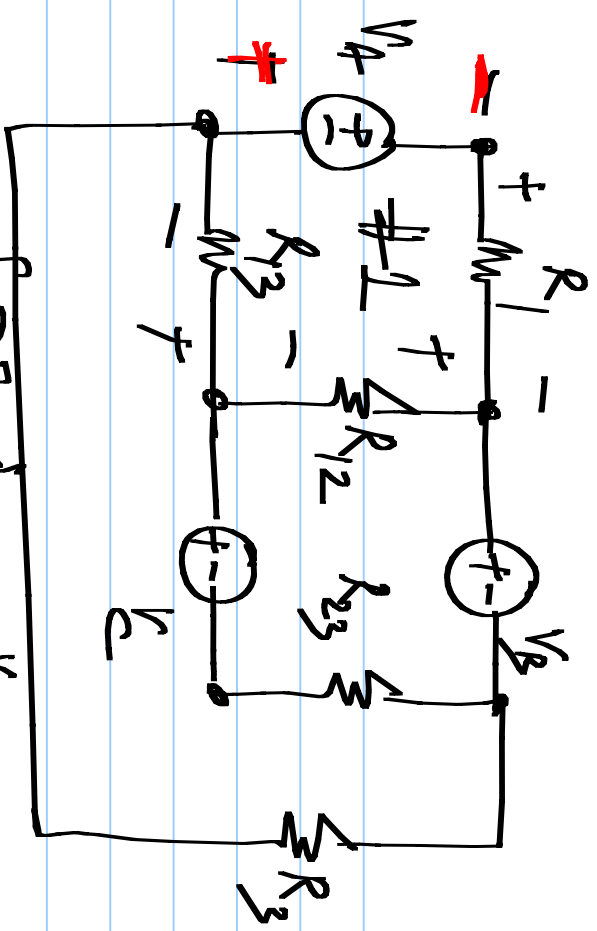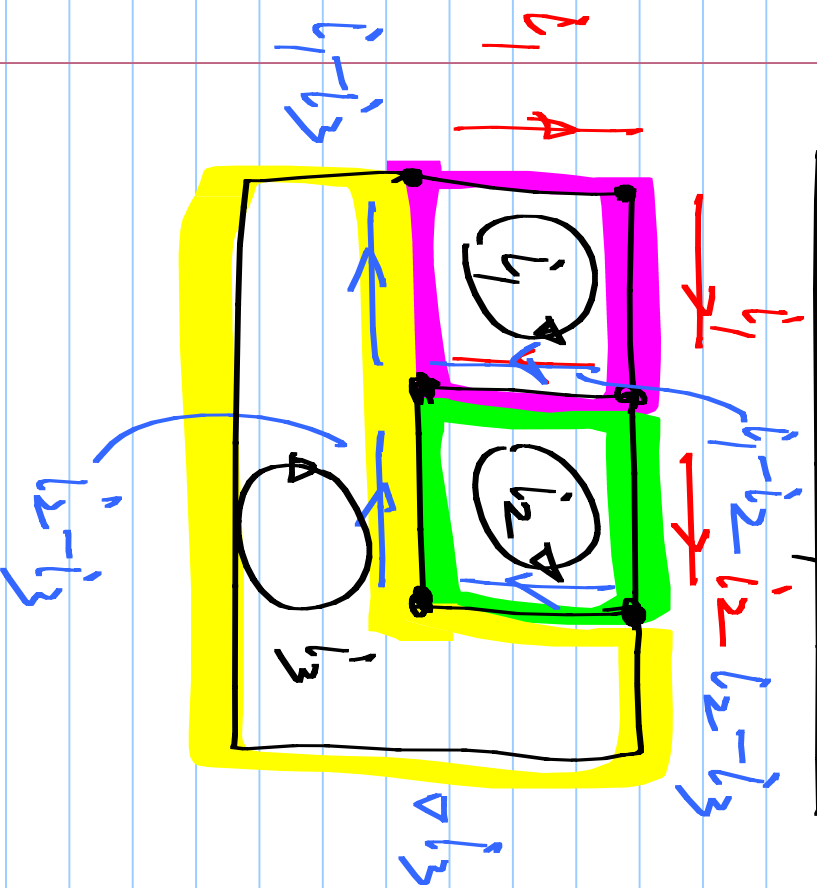

$$[R] \cdot \underline{i} = \underline{V}$$

$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_2 & -R_3 \\ -R_2 & R_2 + R_3 & R_3 \\ R_3 & -R_3 & R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} V_4 \\ V_4 - V_3 \\ -V_4 \end{bmatrix}$$

Super mesh.

Mesh #1:


$$V_{R_1} + V_{R_2} + V_{R_3} = V_A$$

$$V_{R_2} - V_{R_3} = V_C - V_B$$

$$V_{R_1} + V_{R_2} + V_{R_3} = V_A + V_C - V_B$$

$$i_1 R_1 + (i_1 - i_2) R_2 + (i_2 - i_3) R_3$$


$$i_1 - i_2 = 1$$

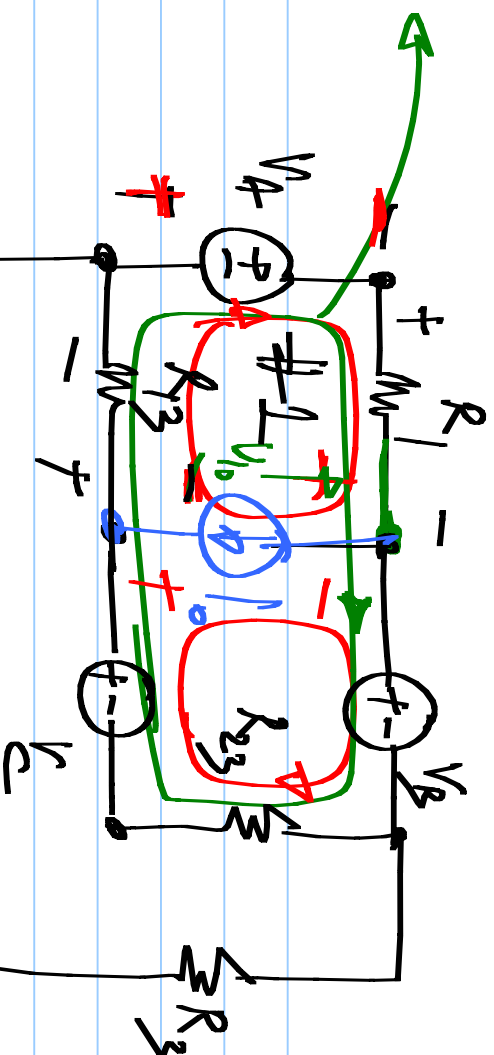

$$[R] \cdot i = V$$

$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_2 & -R_3 \\ -R_2 & R_2 + R_3 & -R_3 \\ R_1 & -R_2 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} V_A \\ V_C - V_B \\ -V_C \end{bmatrix}$$

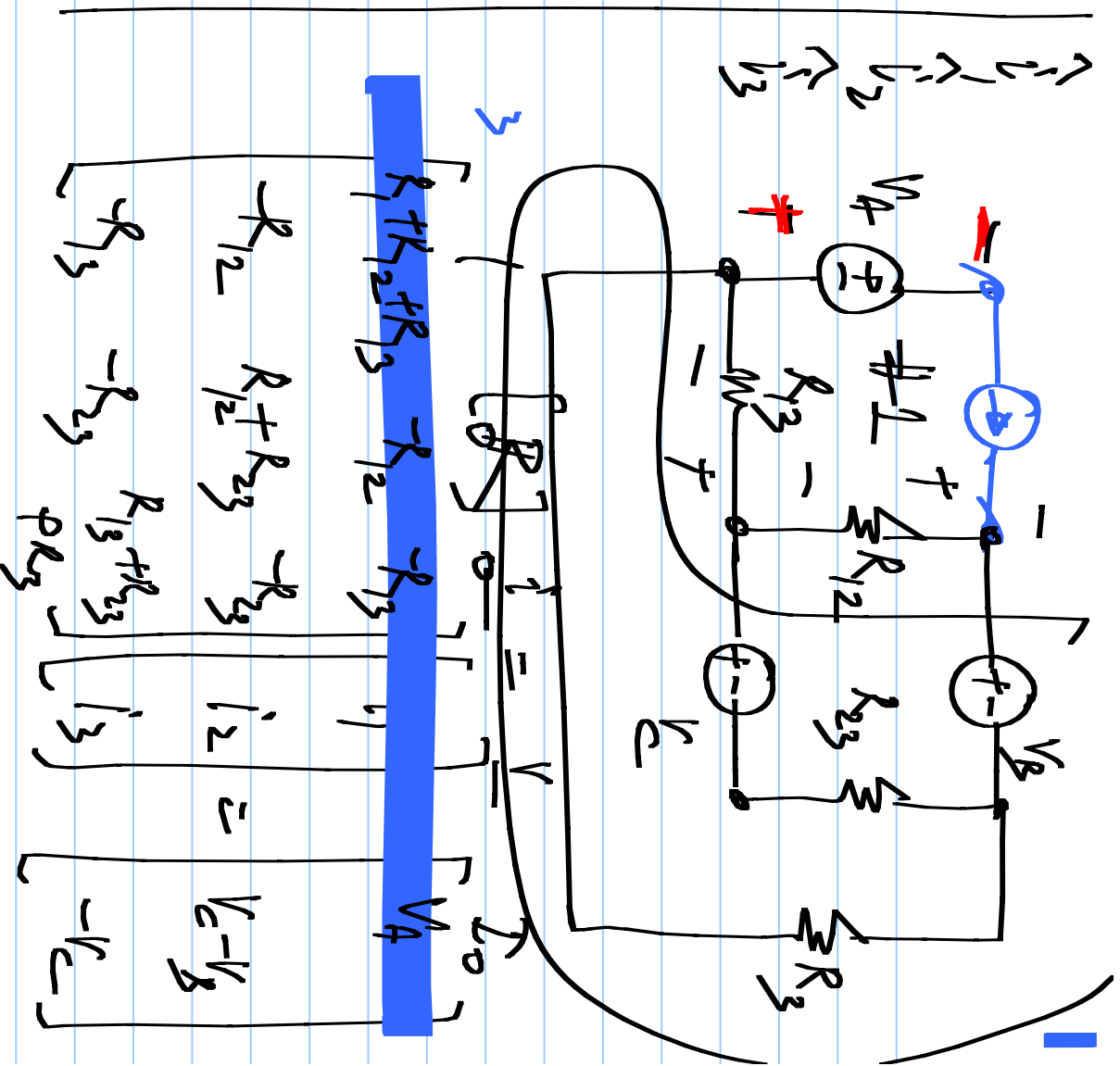- * CCVS
 - * CCCS
 - * $V_C V_S$
 - * $V_C V_S$
-
- mesh #



$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_2 & -R_3 \\ -R_2 & R_2 + R_3 & -R_3 \\ -R_3 & -R_3 & R_3 + R_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_A \\ V_C - V_B \\ -V_C \end{bmatrix}$$

$$\underline{\dot{v}} = [R]^{-1}$$

$$\begin{bmatrix} v_A \\ v_C - v_B \end{bmatrix}$$

$$[G] \underline{v} = \underline{I}$$

!

$$= [R^{-1}] \begin{bmatrix} v_A \\ v_C - v_B \end{bmatrix} + \begin{bmatrix} 0 \\ v_C \\ -v_C \end{bmatrix} + \begin{bmatrix} 0 \\ -v_B \\ 0 \end{bmatrix}$$

$\left[\begin{matrix} v_A \\ +v_C \\ -v_C \end{matrix} \right] + \left[\begin{matrix} 1 \\ -v_B \\ 0 \end{matrix} \right]$

MNA: V, I, R dependent sources.


$$V = I \cdot R$$

Superposition: Solution to a circuit excited

by multiple independent sources equals the sum of


solutions to the circuit with each ind. source acting

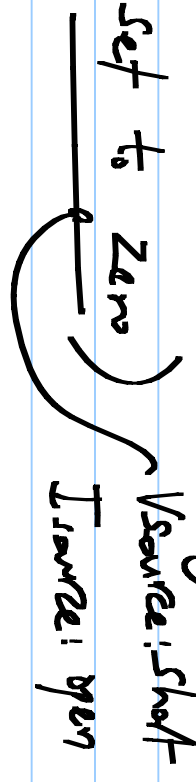by itself (and all other sources set to zero)





V_{source} : short


I_{source} : open

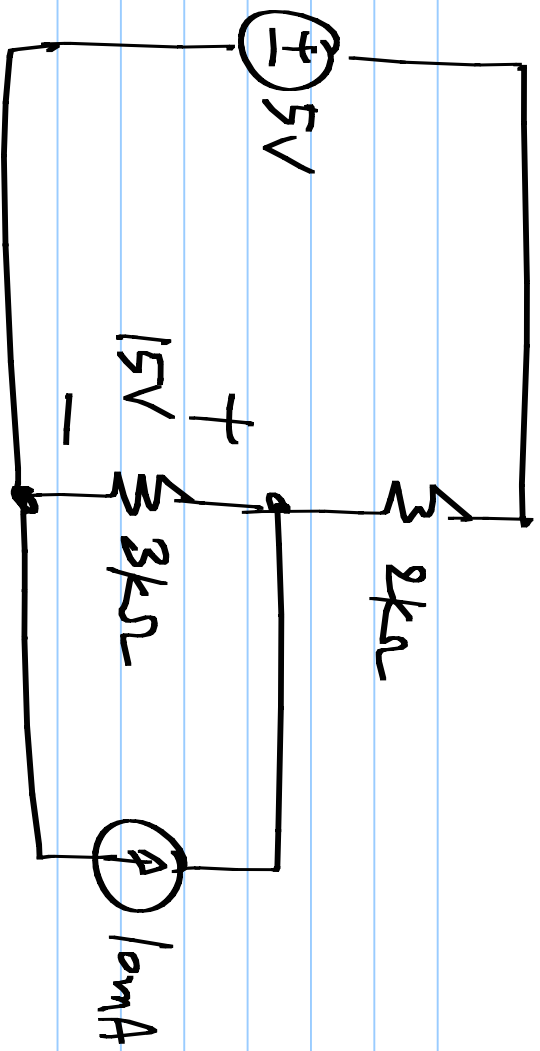


$$\frac{2k\Omega \cdot 3k\Omega}{2k\Omega + 3k\Omega}$$


$$= \frac{6}{5} k\Omega$$

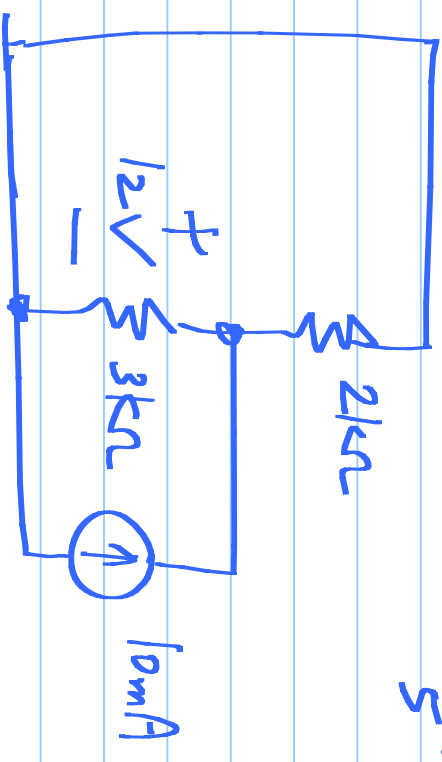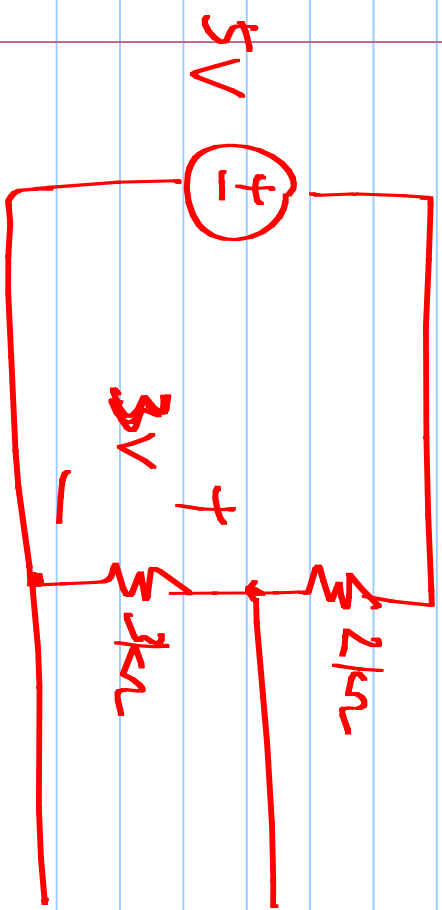

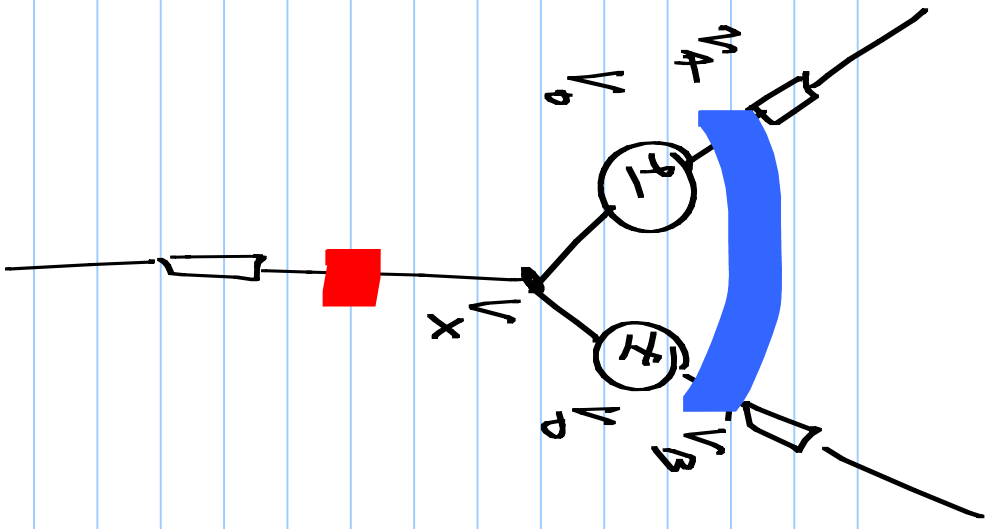

|||

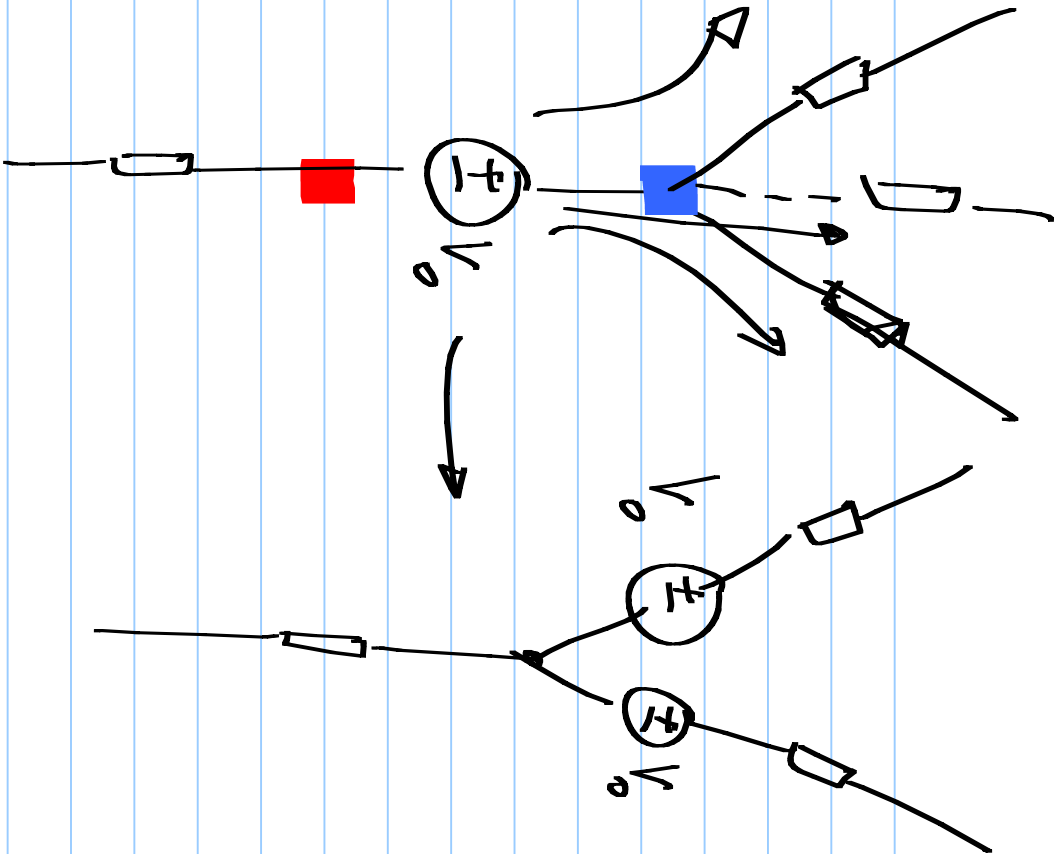

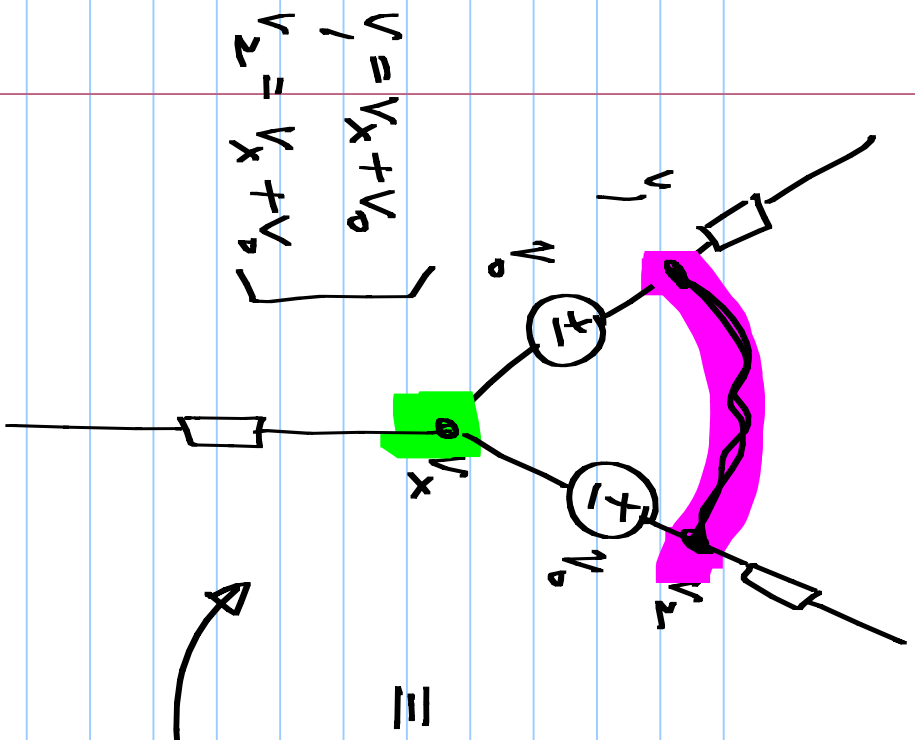

≡

