
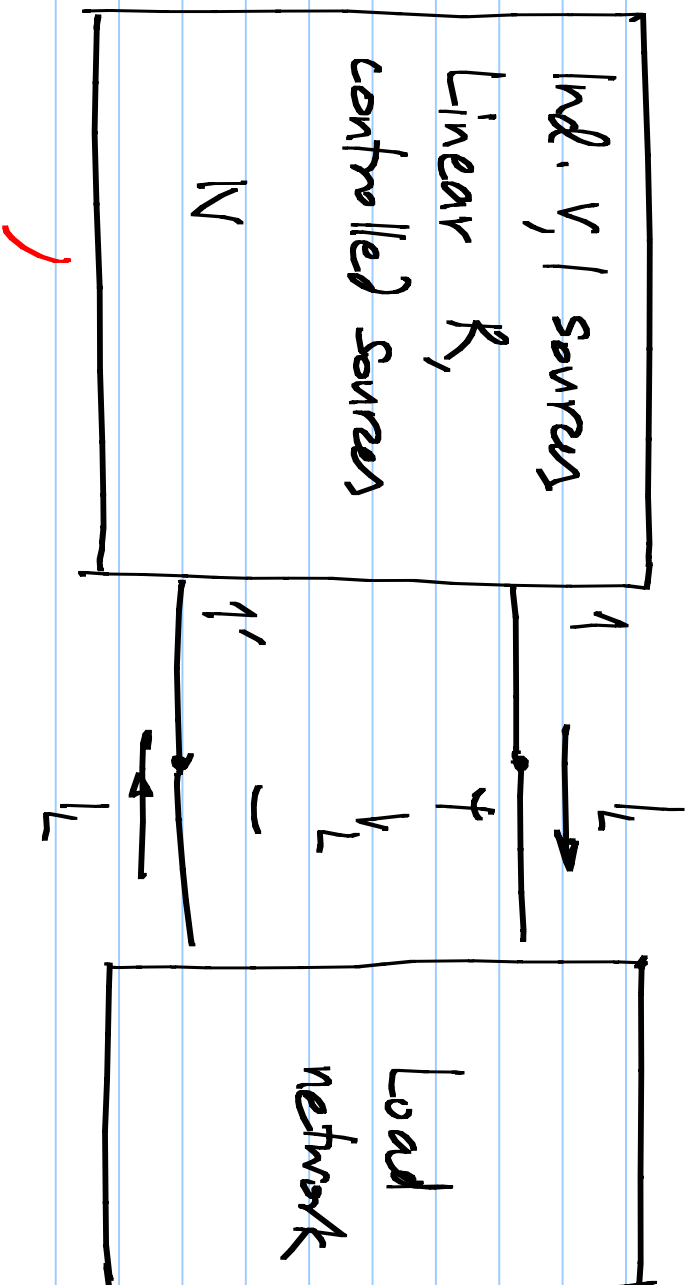




EECE 1010: Lecture 12

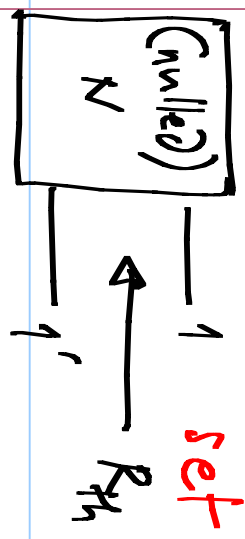


Simple model for this




set independent sources = 0

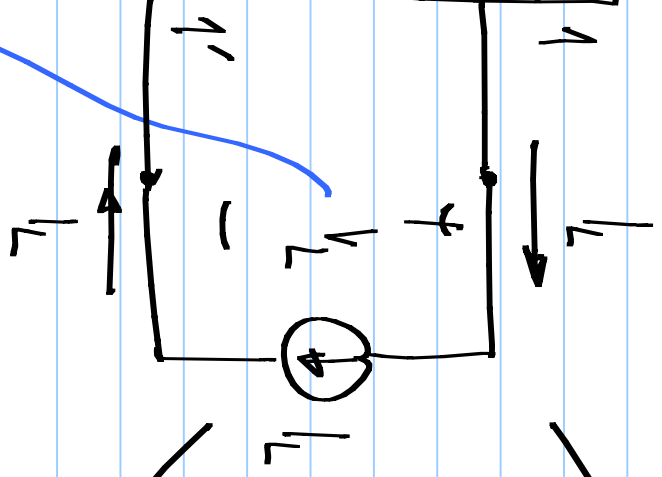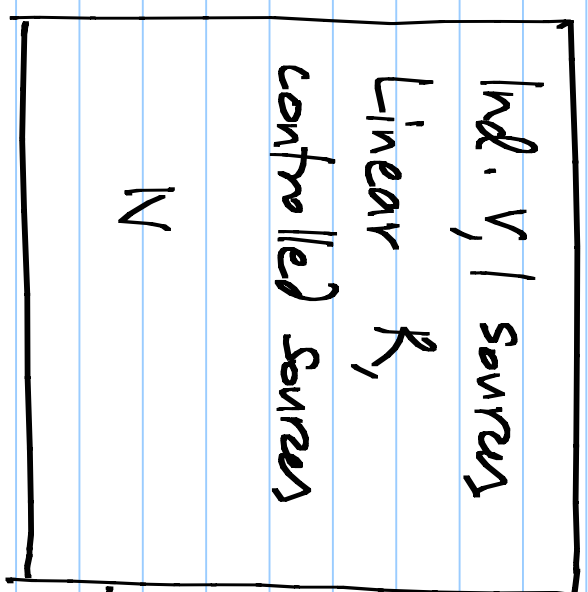


Superposition

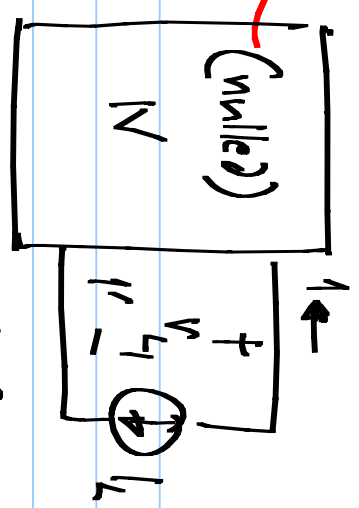

open circuit


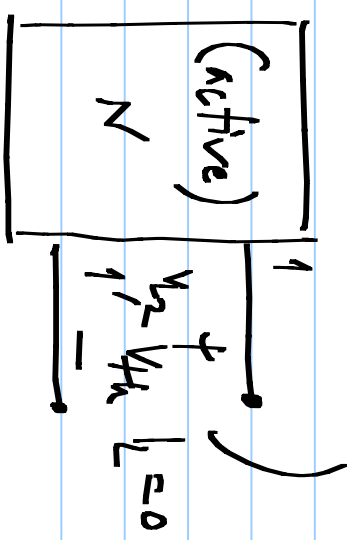


$$V_H = i_L \cdot R_H$$

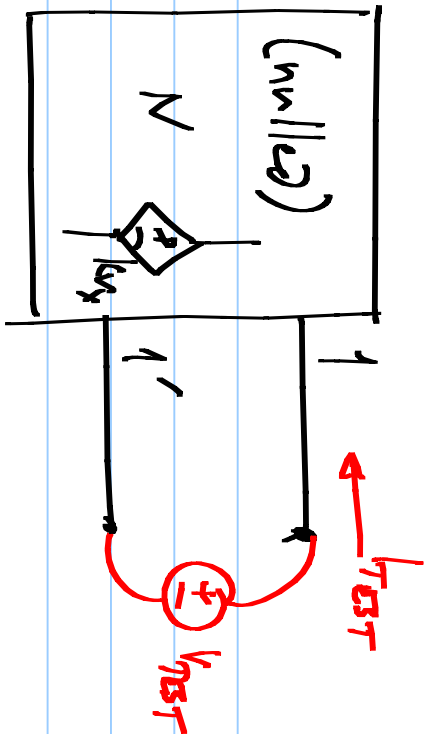

$$\frac{V_{test}}{I_{test}} = R_{th}$$

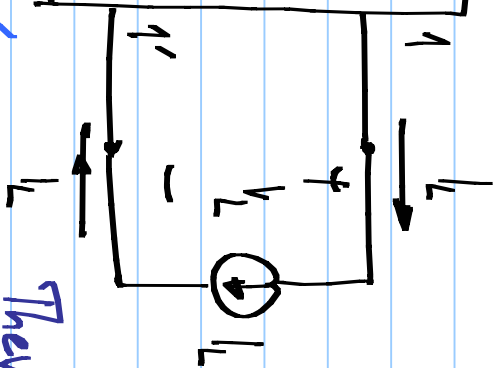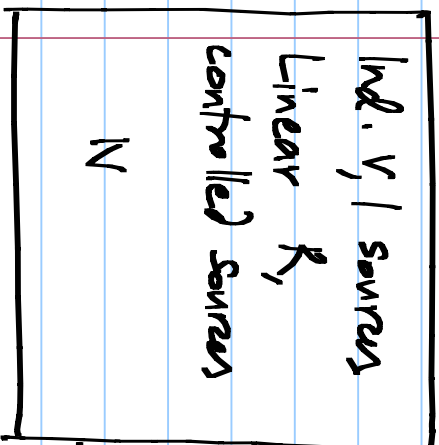Resistance looking into '1-1''
with ind. sources set to zero







Thevenin's voltage

$$\text{Thevenin's resistance } V_L = V_{th} - R_{th} \cdot I_L$$

Thevenin's theorem



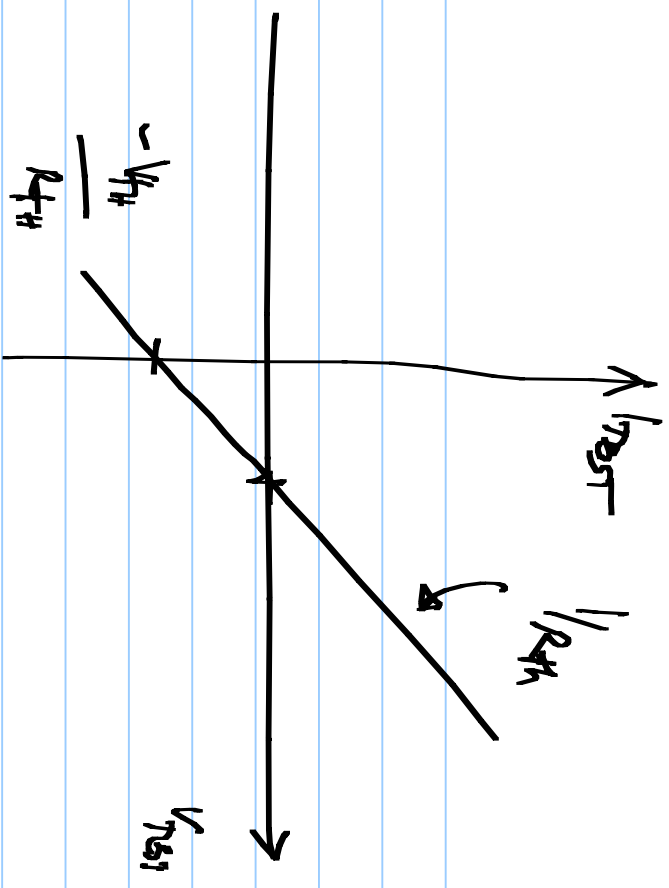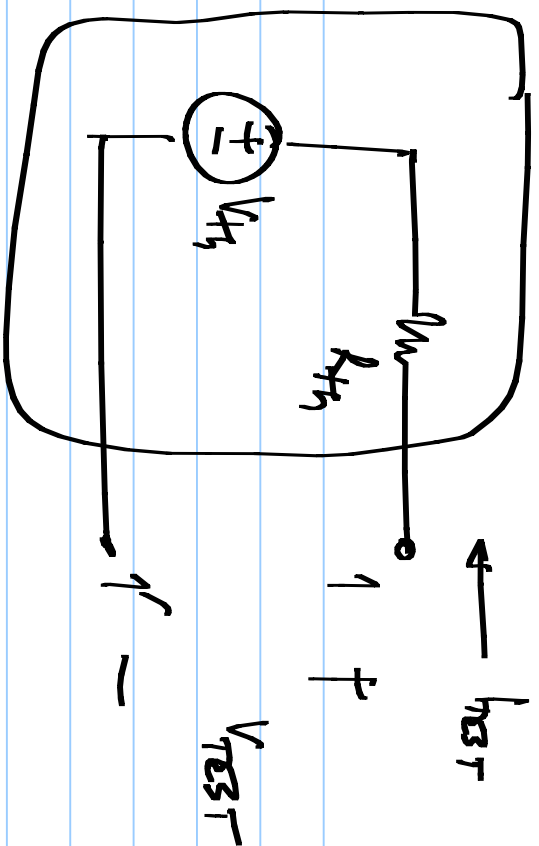

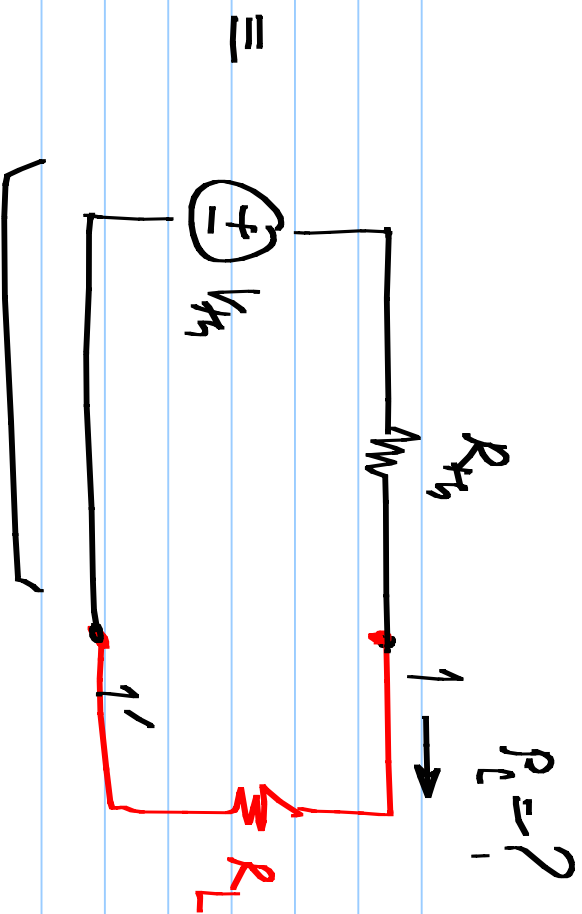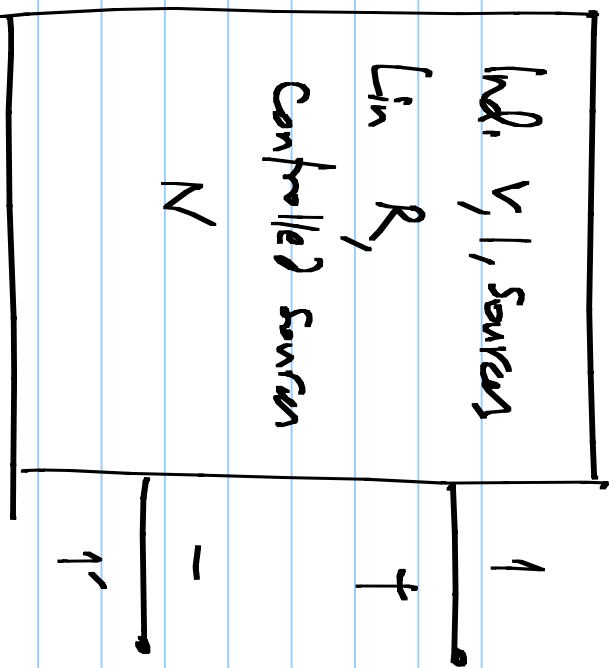

$$P_L = V_{th} \cdot \frac{R_L}{R_{th} + R_L} \cdot \frac{V_{th}}{R_{th} + R_L}$$

What is R_L such that the maximum power is drawn from $\{V_{th}, R_{th}\}$?

Maximum power transfer theorem:

$$P_L = V_{th}^2 \cdot \frac{R_L}{(R_{th} + R_L)^2} = \frac{V_{th}^2}{R_{th}} \cdot \frac{R_L R_{th}}{(R_{th} + R_L)^2}$$

$$P_L = P_{L, \max} = \frac{V_{th}^2}{R_{th}} \cdot \frac{1}{\left(\frac{R_{th} + R_L}{\sqrt{R_{th} R_L}} \right)^2} = \frac{V_{th}^2}{R_{th}} \cdot \frac{1}{\left(\sqrt{\frac{R_{th}}{R_L}} + \sqrt{\frac{R_L}{R_{th}}} \right)^2}$$

When $R_L = R_{th}$

(matching the load to the source)


$$P_{L, \max} = \frac{V_{th}^2}{4R_{th}}$$

Available

power of the source

minimum when
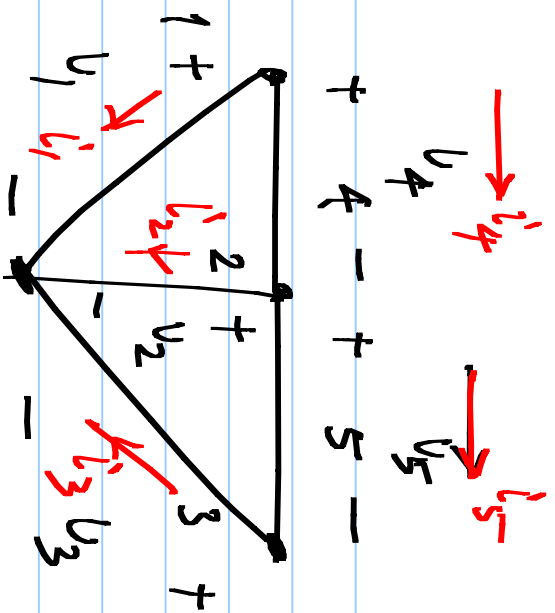
$$\sqrt{\frac{R_{th}}{R_L}} = 1, R_L = R_{th}$$





$$\sum_{\text{all branches}} v_k i_k = 0$$

Prove it

KVL, KCL





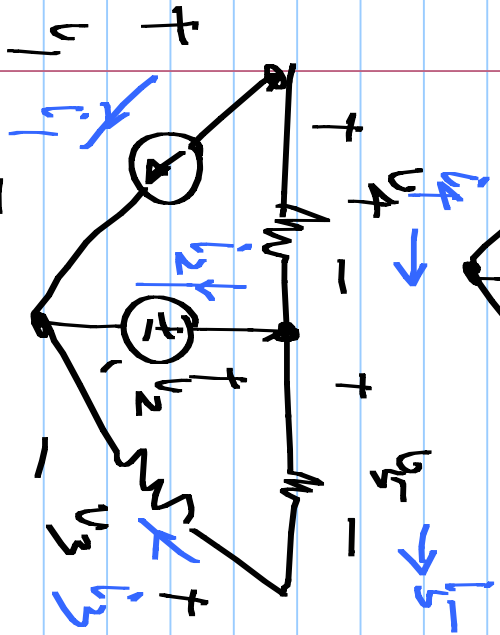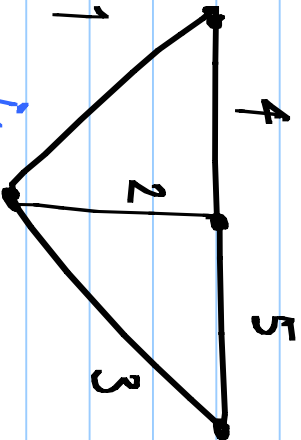

$$\sum v_k i_k = 0$$


all branches

$$\sum v_k i_k$$

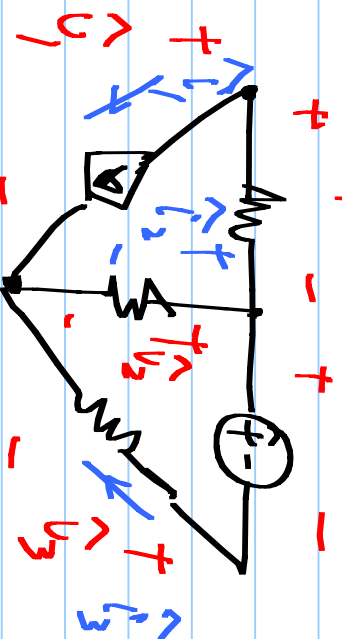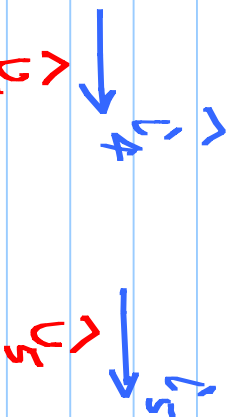


$$\sum v_k i_k = 0$$

$$\sum v_k i_k = 0$$

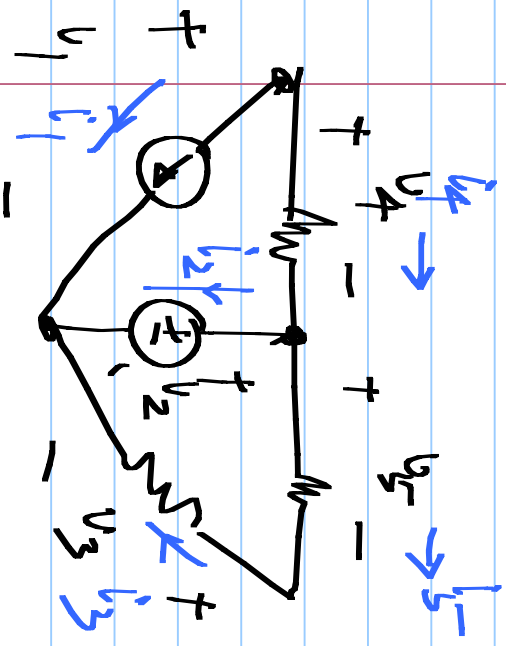

$$\sum v_k (i_k + i_k^{\rightarrow}) = 0$$

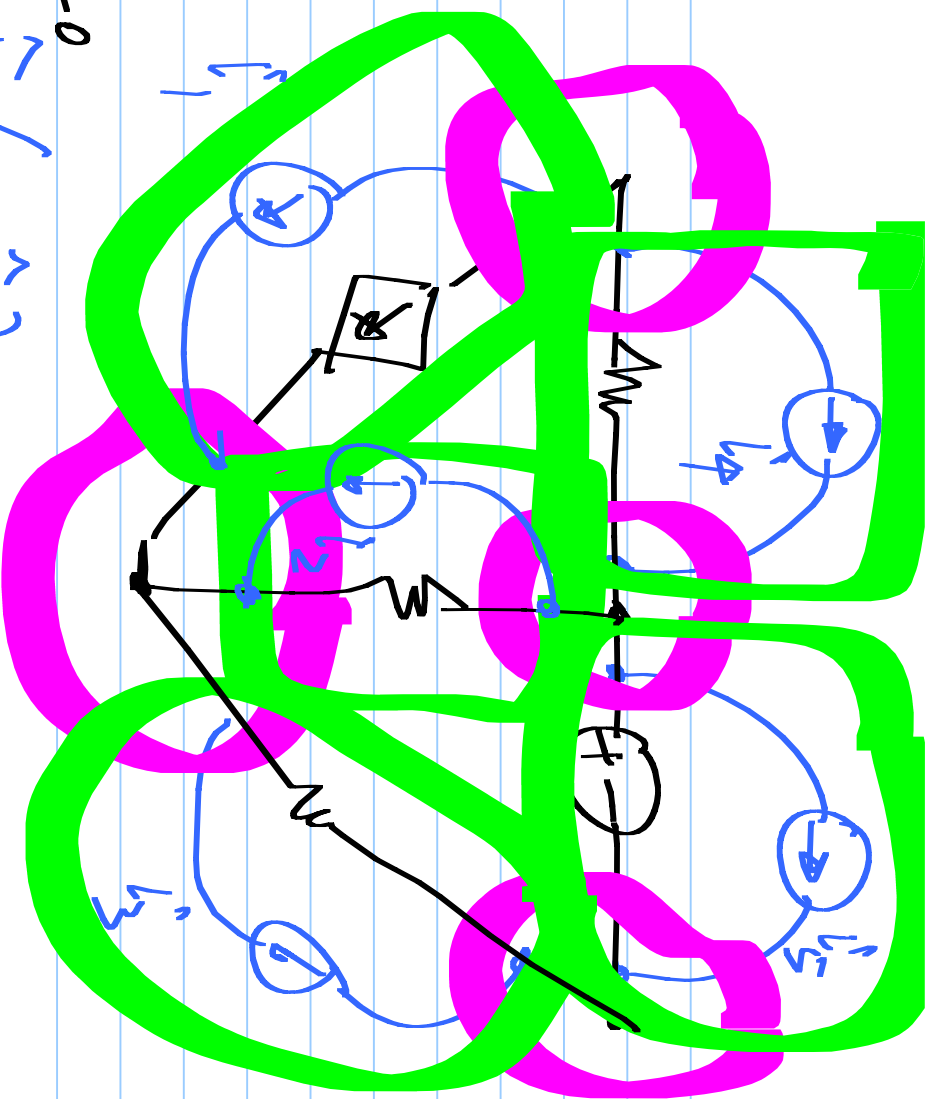all branches $\sum v_k i_k^{\rightarrow} = 0$



Kirchhoff's theorem

Exercises:

1: Prove $\sum_{k=0}^{\infty} v_k y_k = 0$
all branches

2: Derive eq. det with a current source