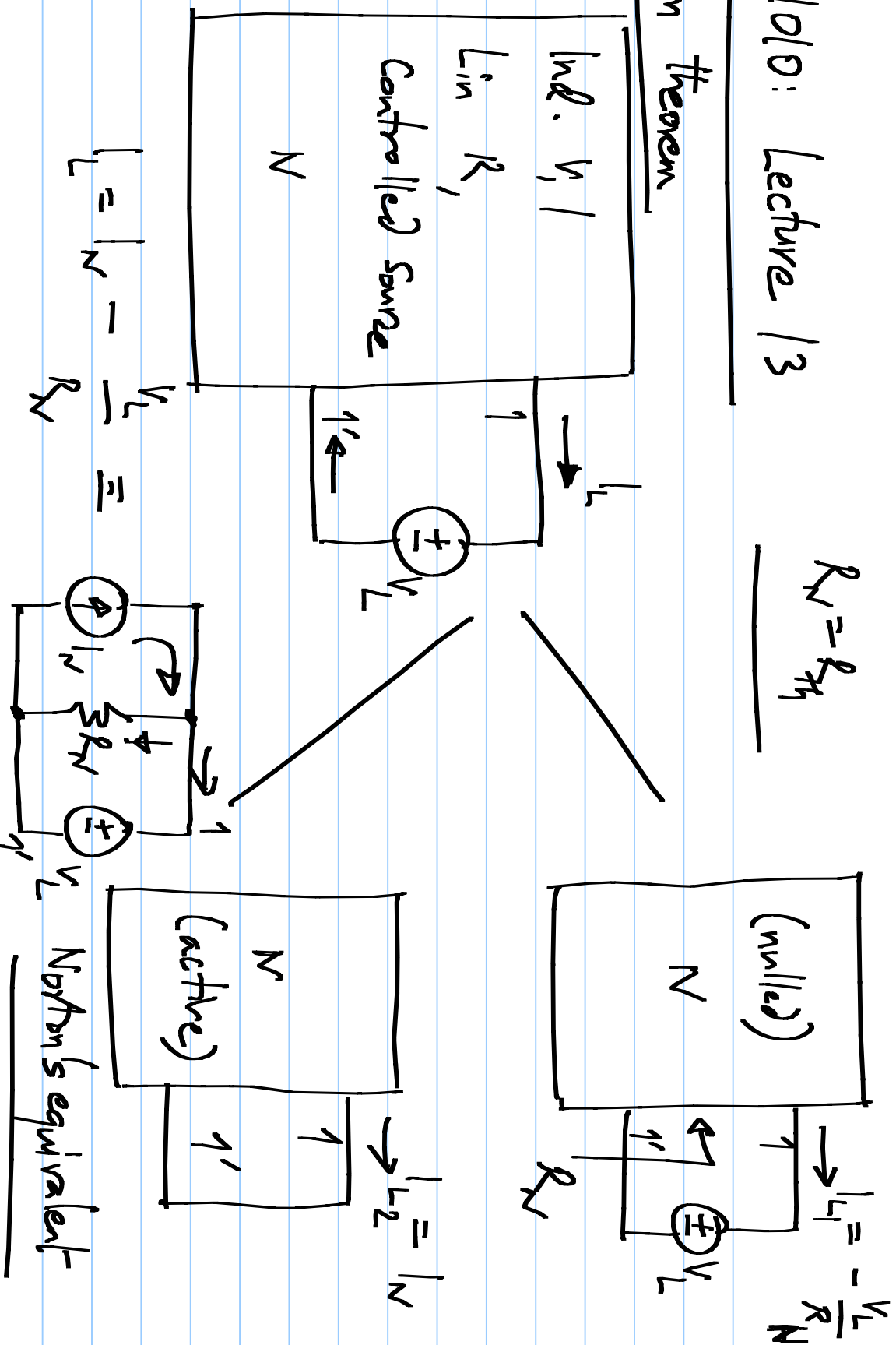




# EC 1010: Lecture 13

$$R_N = R_{Th}$$

## Norton theorem






$R_N = R_{th}$  : Looking in resistance |  $V_{th}$ : open ckt. voltage at 1-1'  
 $I_N$ : short ckt. current from 1-1'

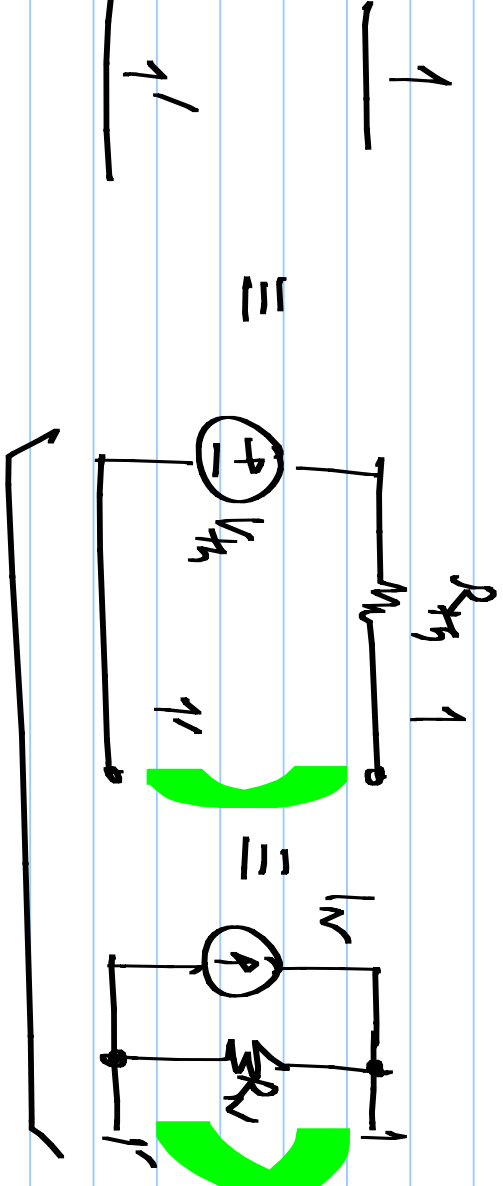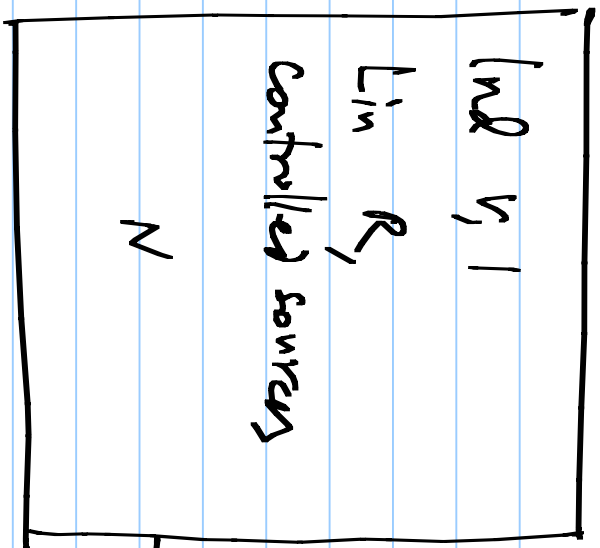


$$V_{th} = I_N \cdot R_{th}$$

$$\frac{V}{I} = R_N = R_{th}$$

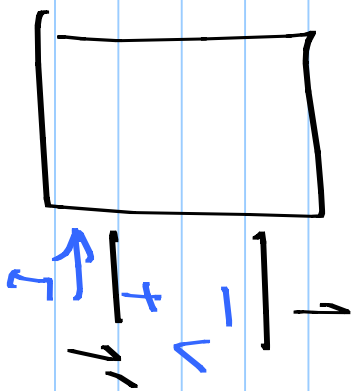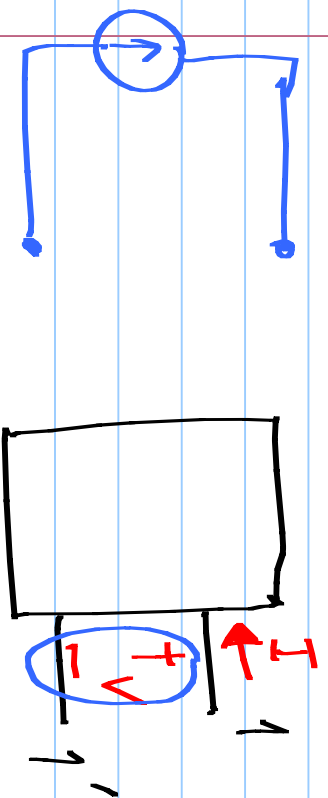


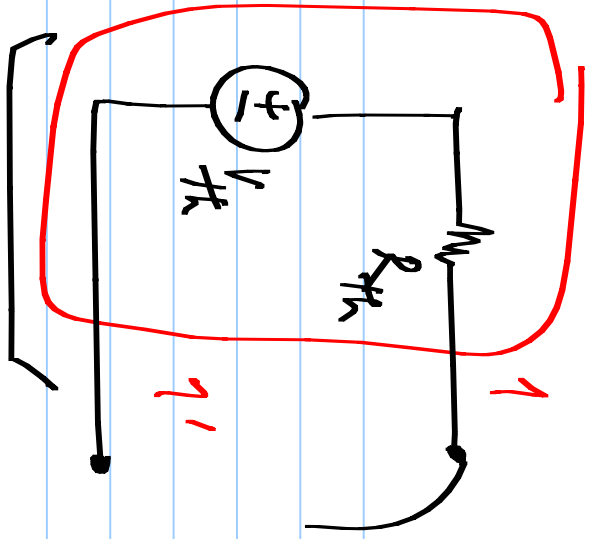

≡

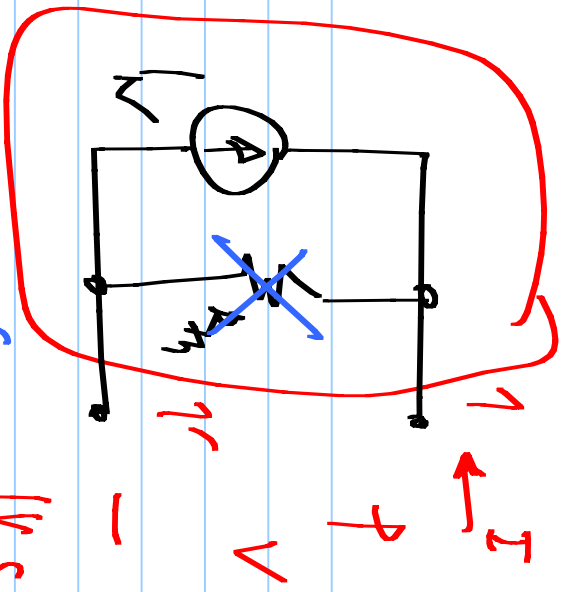

Battery  
I

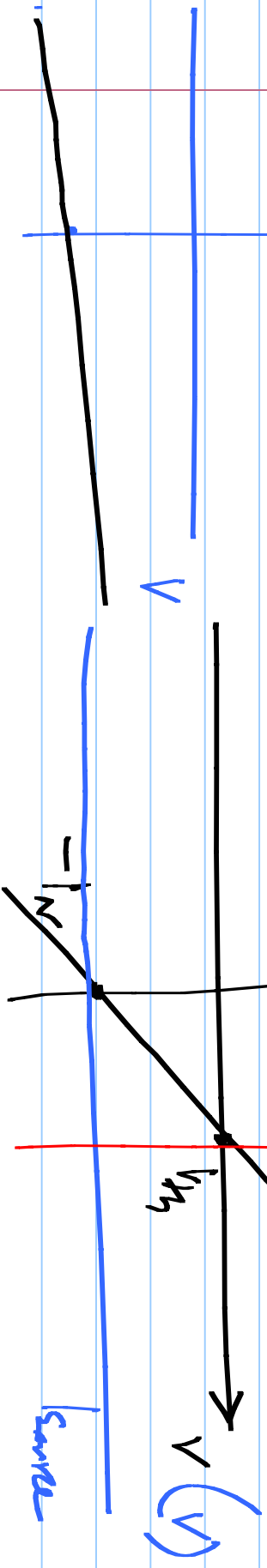



$I_{RL}$

$V_{Source}$


$I_{RL}$

$I_{Source}$

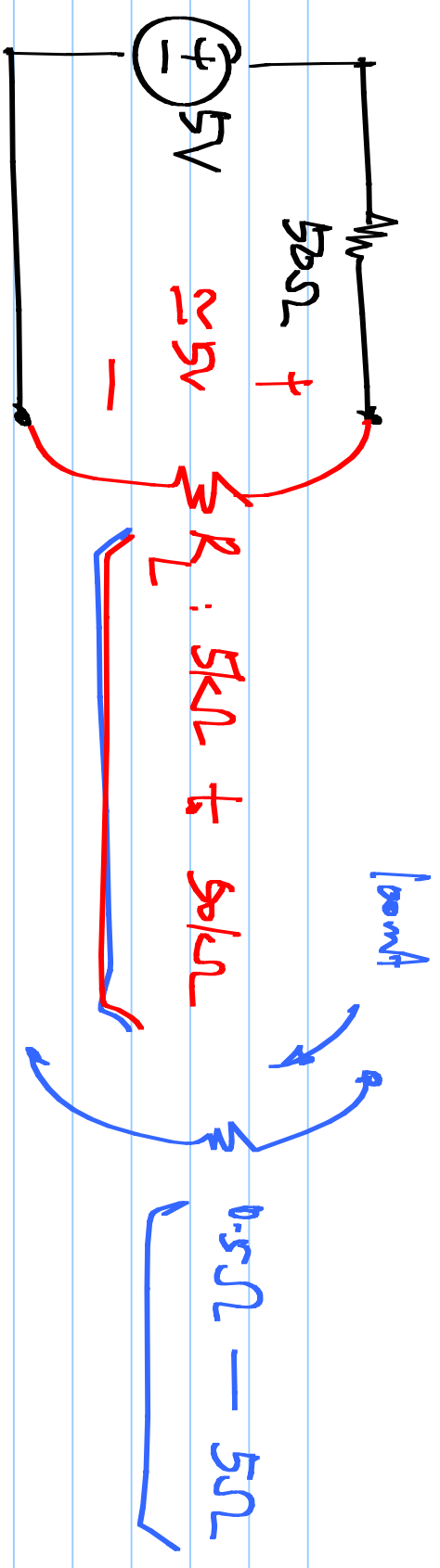

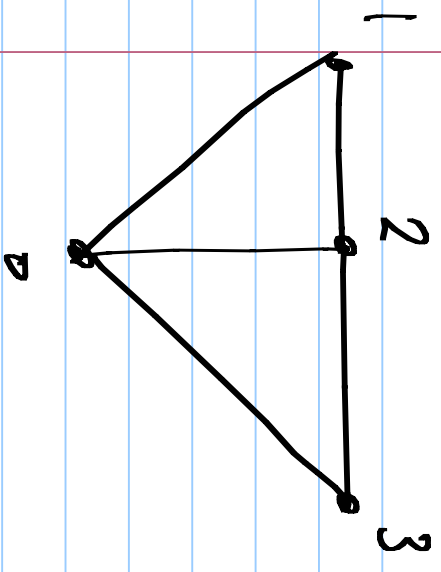
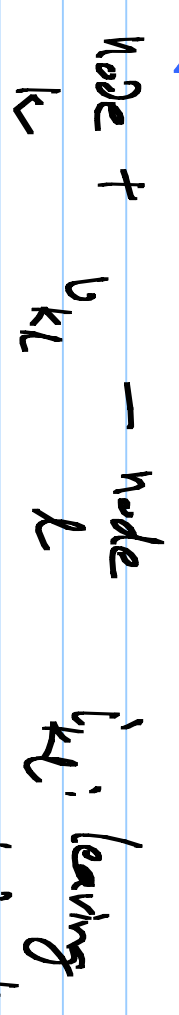
$$\sum_{\text{branches}} v_{kl} i_{kl} = 0$$



$$\sum (v_k - v_l) i_{kl}$$

entering node k & leaving node l

$$\sum_{\text{nodes}} v_m \left( \sum_{\text{branches}} i_{mn} - \sum_{\text{branches}} i_{nm} \right) = 0$$

node m:   
 nodes   
 currents leaving node m   
 currents entering node m

Tellegen's theorem:

$$\sum v_k \hat{i}_k = 0$$

all branches

$$\textcircled{1} \sum v_k \cdot i_k = 0$$

all branches  
of a circuit:-

$N, \hat{N}$ : Same graph

$v_k, i_k$ : branch voltages &

$$\textcircled{2} \sum v_k \hat{i}_k = 0$$



all branches



currents of  $N$

$\hat{v}_k, \hat{i}_k$ : branch voltages &

currents of  $\hat{N}$
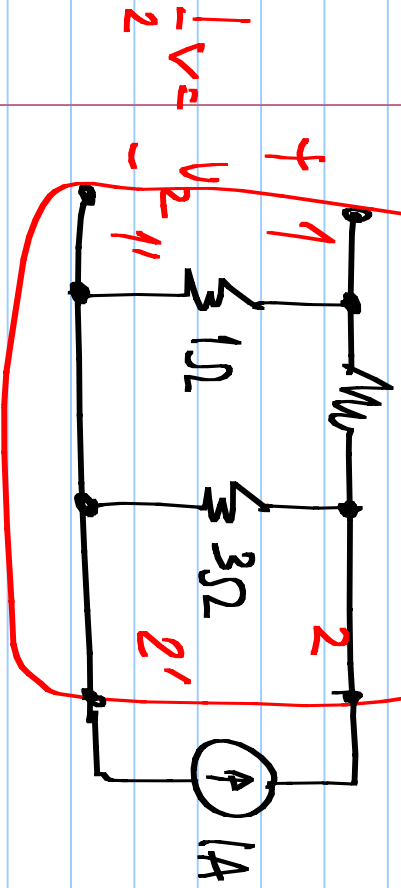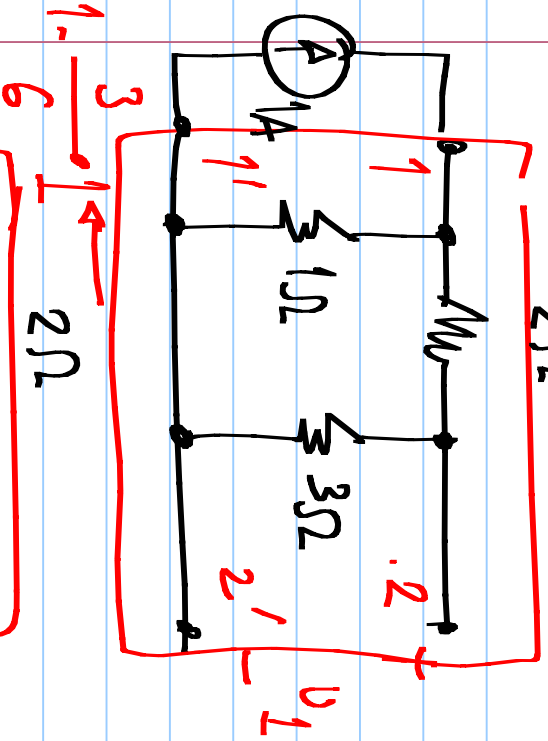
$$2\Omega \rightarrow 1 + \frac{1}{\frac{1}{6} + \frac{1}{3\Omega}} = \frac{1}{2}$$



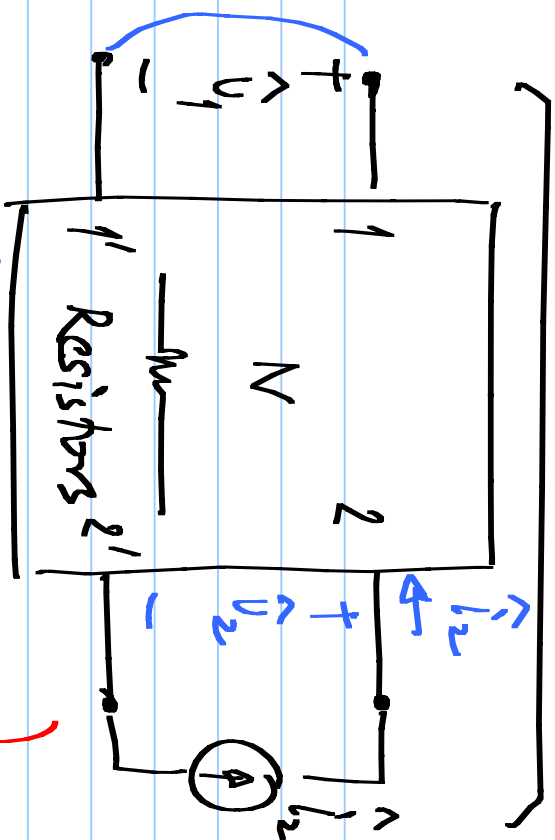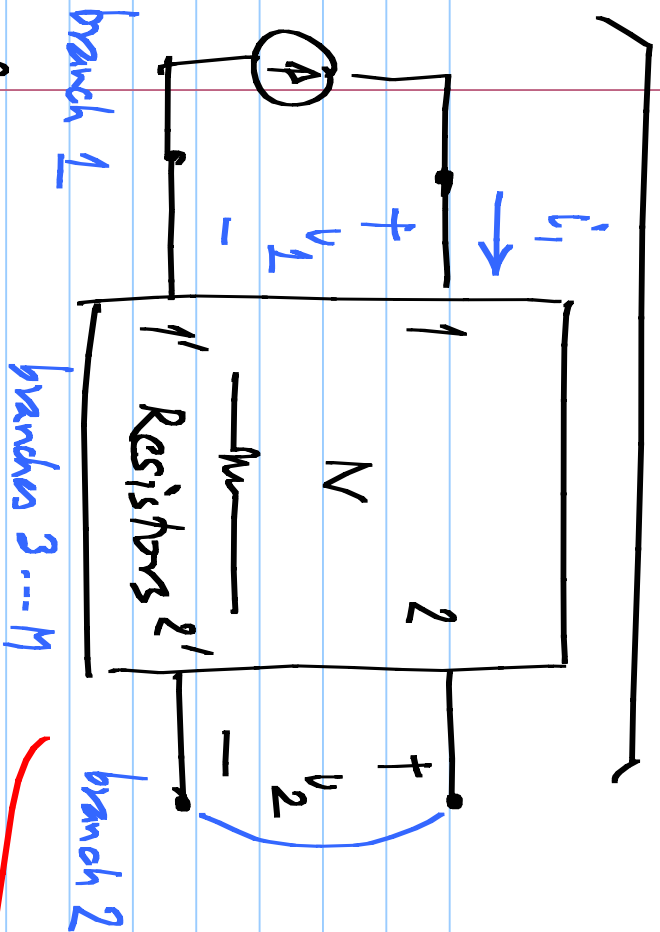

Voltages

currents:

$$R_k \cdot i_k$$

currents

voltages

$$v_1 \cdot 0 + v_2(-i_2) + \sum_{k=3}^M v_k i_k = 0$$

$$(-i_1)v_1 + (0)v_2 + \sum_{k=3}^M v_k i_k = 0$$