
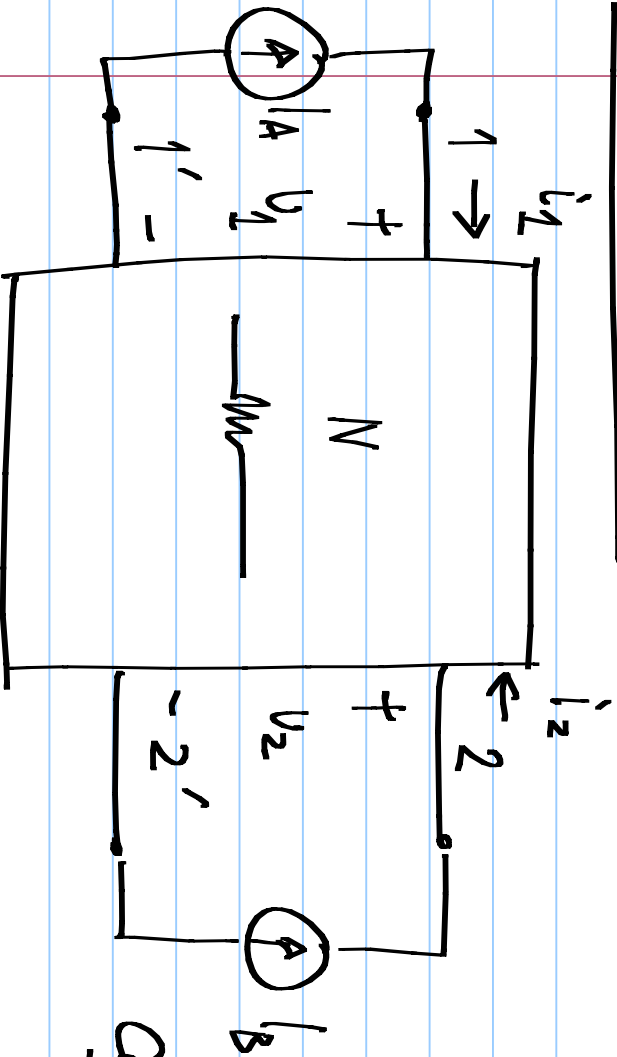


EC1010: Lecture 14

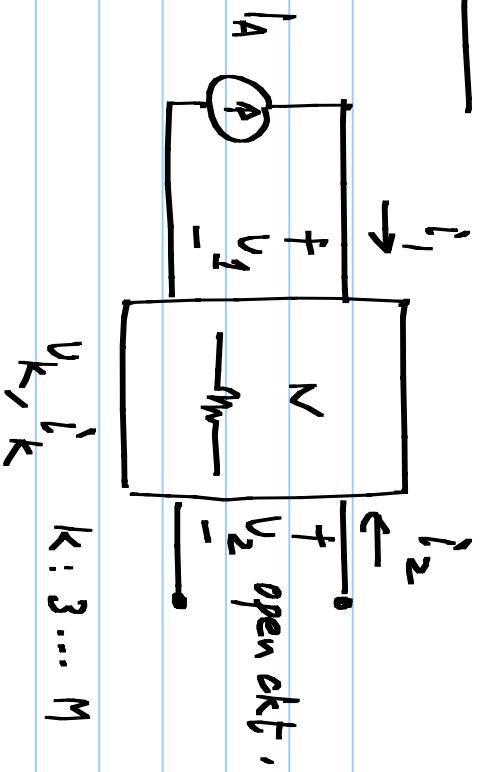


Two port network

Case 1: $i_B = 0$



Case 2: $i_A = 0$

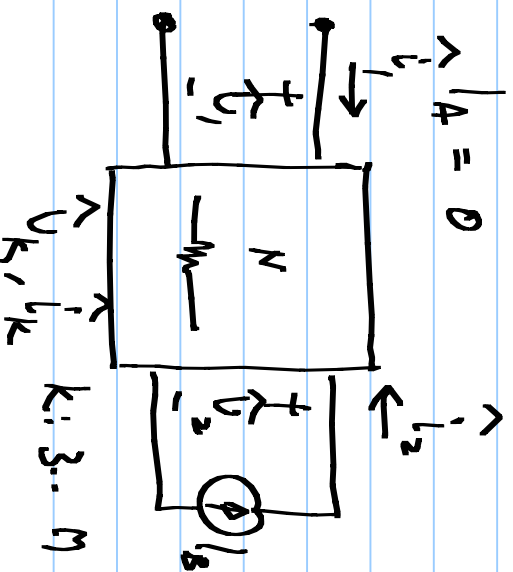


Tellegen's theorem: $\{v_k, i_k\}$

$$v_1 \cdot 0 + v_2(-i_b) + \sum_3^M v_k \cdot i_k = 0$$

Resistive network $\Rightarrow \sum_3^M R_k i_k i_k = R_k i_k^2$

Case 1: $i_b = 0$

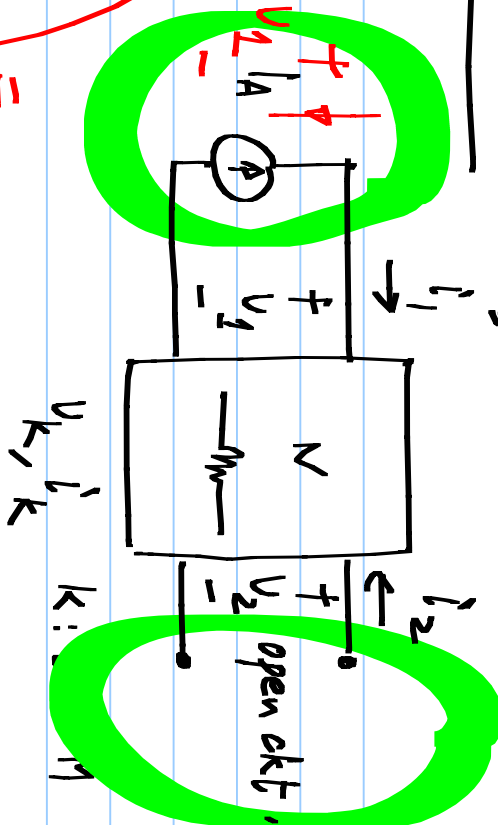


Tellegen's theorem: $\{v_k, i_k\}$

$$\hat{v}_1(-i_A) + \hat{v}_2(0) + \sum_3^M \hat{v}_k i_k = 0$$

$$\hat{v}_k = R_k \cdot \hat{i}_k$$


$$\sum_3^M R_k i_k i_k$$

Case 2: $i_A = 0$

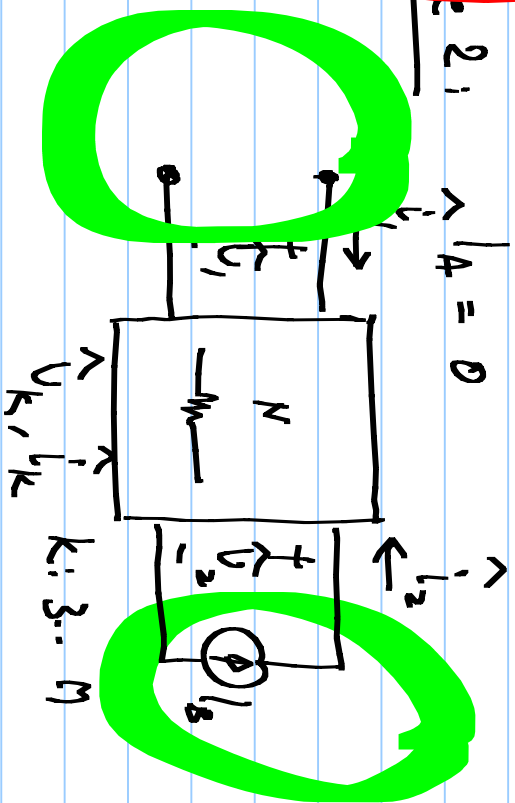

$$\hat{V}_1(-I_A) = V_2(-I_B)$$

Case 1: $I_B = 0$

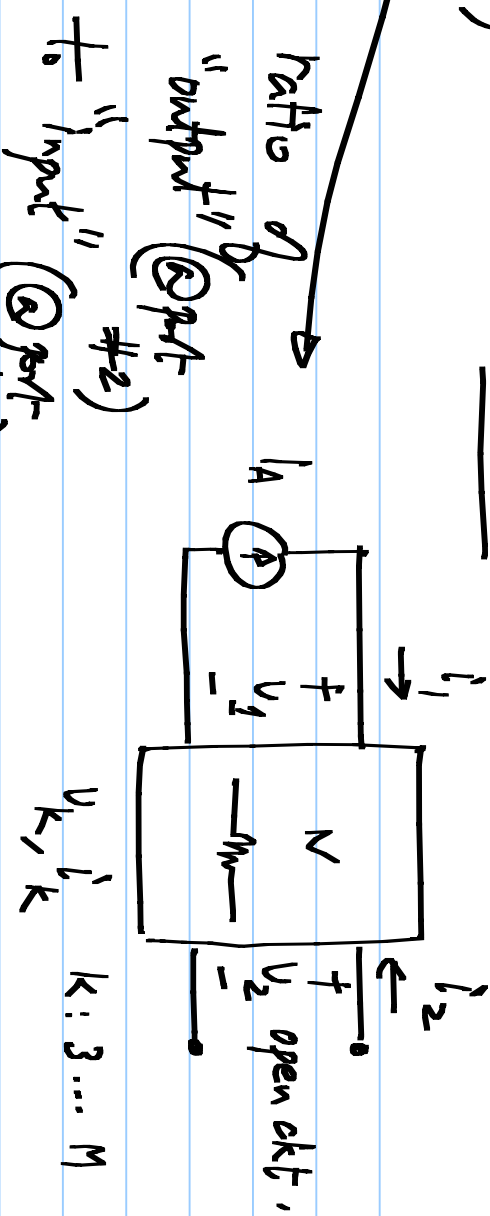


$$\frac{V_2}{I_A} = \frac{\hat{V}_1}{I_B}$$


Reciprocity theorem


Reciprocal networks

Case 2:

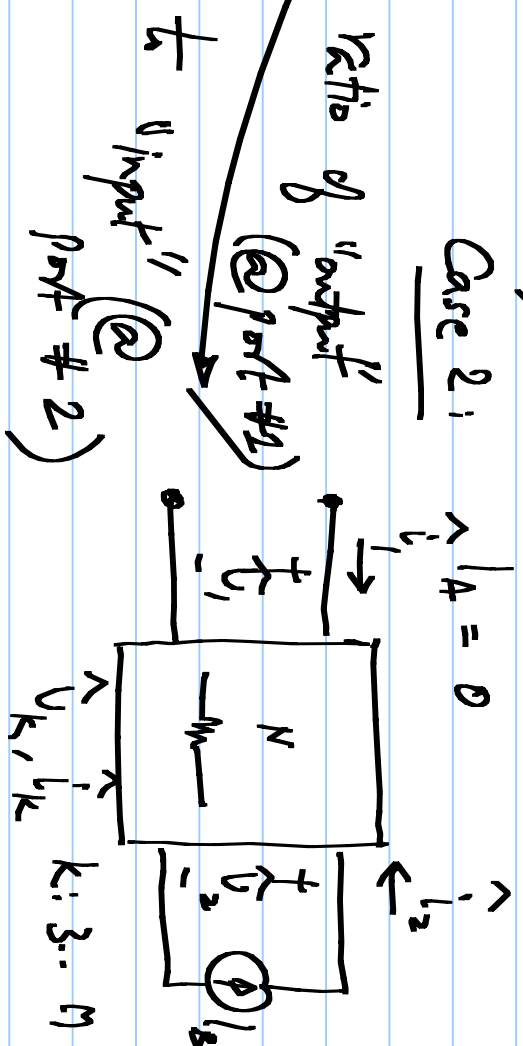


$$\hat{I}_A = 0$$

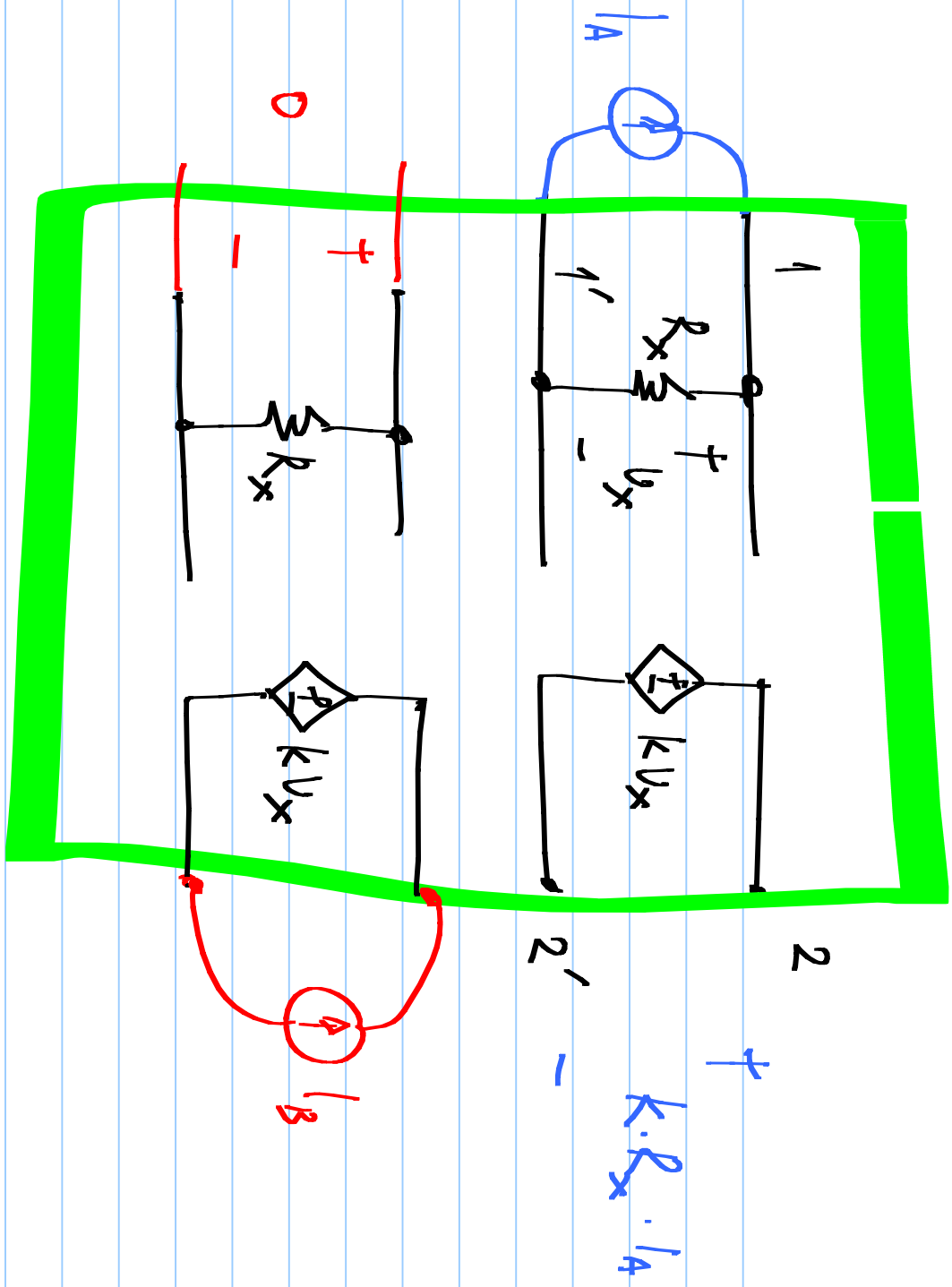


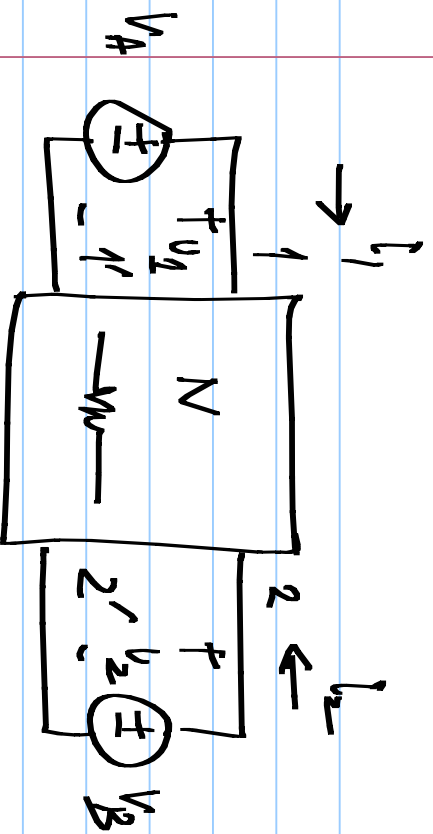

Case 1: $V_B = 0$

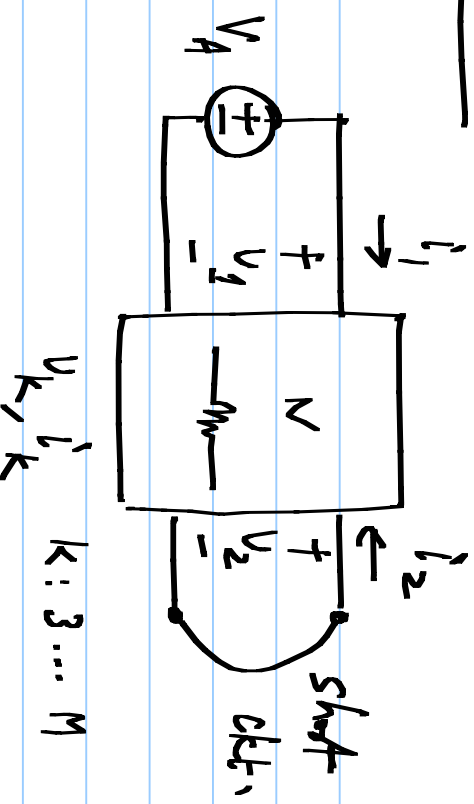

Case 2: $V_A = 0$

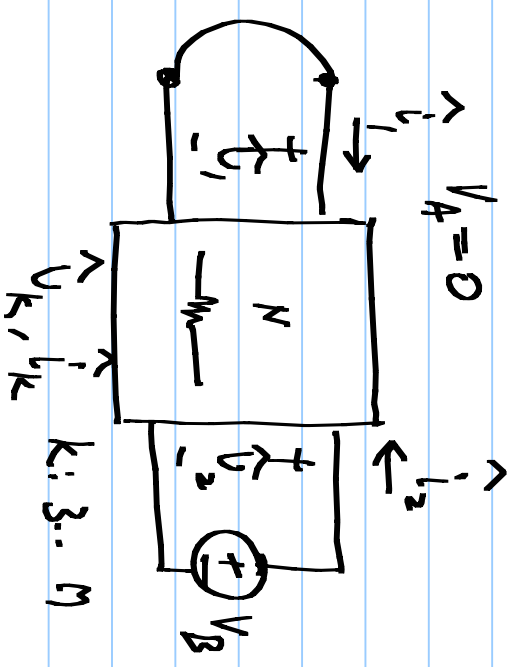


Tellegen's theorem:

$\{v_k, i_k\}$

Case 1:

$v_B = 0$
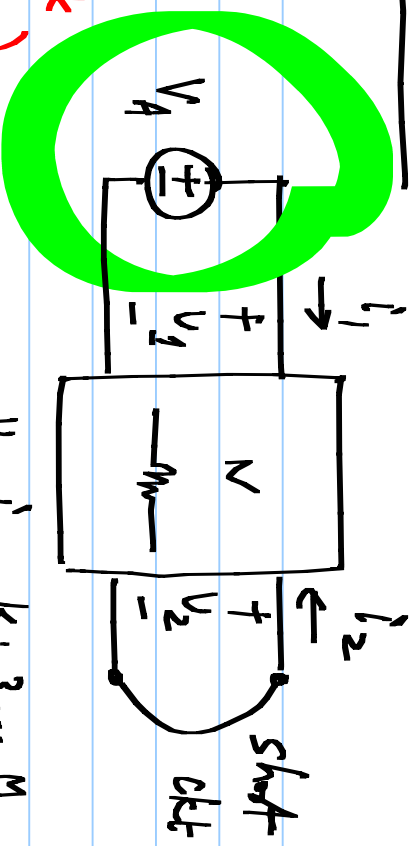
$$v_A(-i_1) + 0(-i_2) + \sum_{k=3}^M v_k i_k = 0$$



$$0(-i_1) + v_B(-i_2) + \sum_{k=3}^M v_k i_k = 0$$



Case 2:

$v_A = 0$

$$v_A(-i_1) = v_B(-i_2)$$


$$\frac{i_2}{v_A} = \frac{i_1}{v_B}$$

Reciprocity theorem

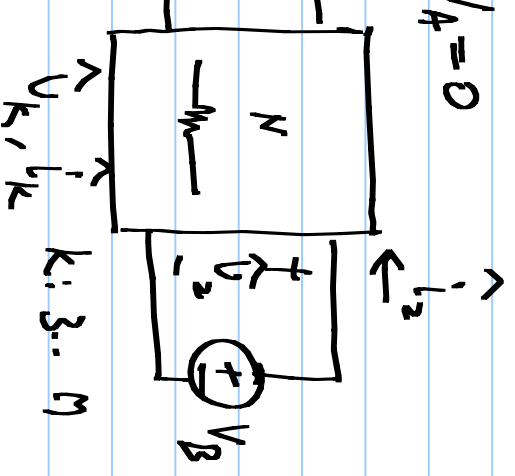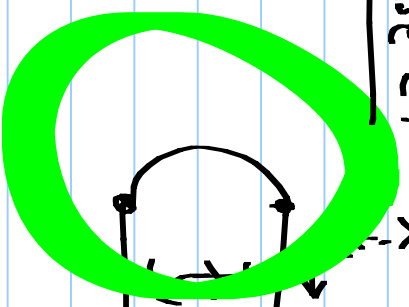

Case # 1 : $I_B = 0$, v_k, i_k

Case # 2 : $V_A = 0$, v_k, i_k

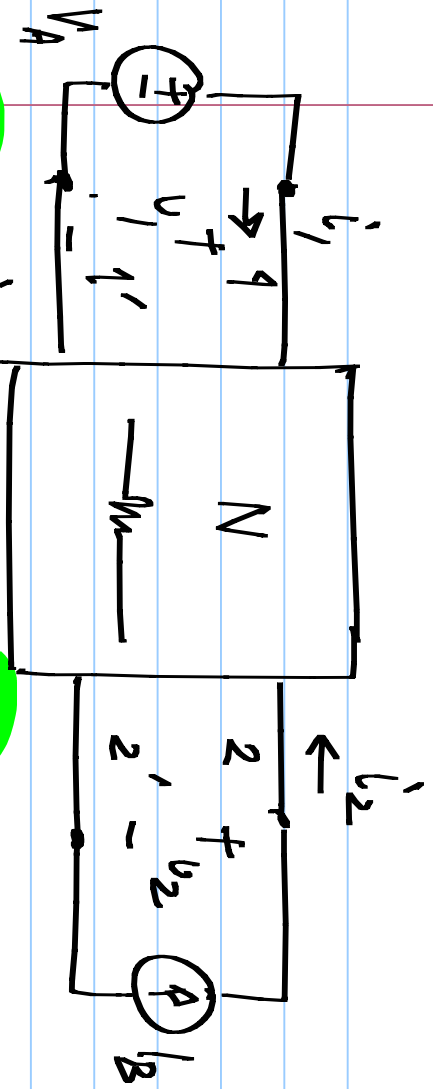


Tellegen's theorem $\{v_k, i_k\}$



$$v_A(-i_1) + v_2(-I_B) + \sum_{k=3}^M v_k i_k = 0$$

$\{v_k, i_k\}$: $\neq R_{k,i_k}$

$$0(-i_1) + v_2(0) + \sum_{k=3}^M v_k i_k = 0$$
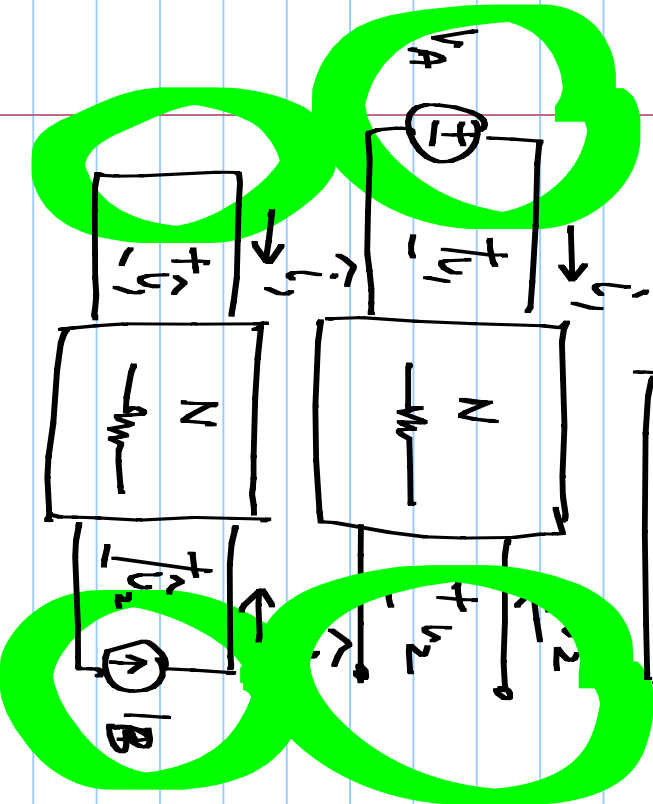
$$\left\{ \frac{v_2}{V_A} = -\frac{i_1}{I_B} \right\}$$



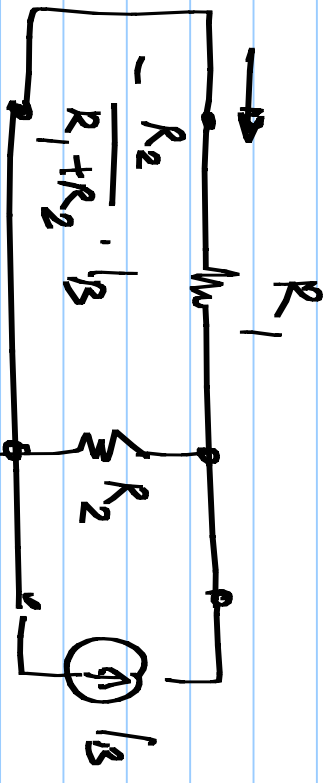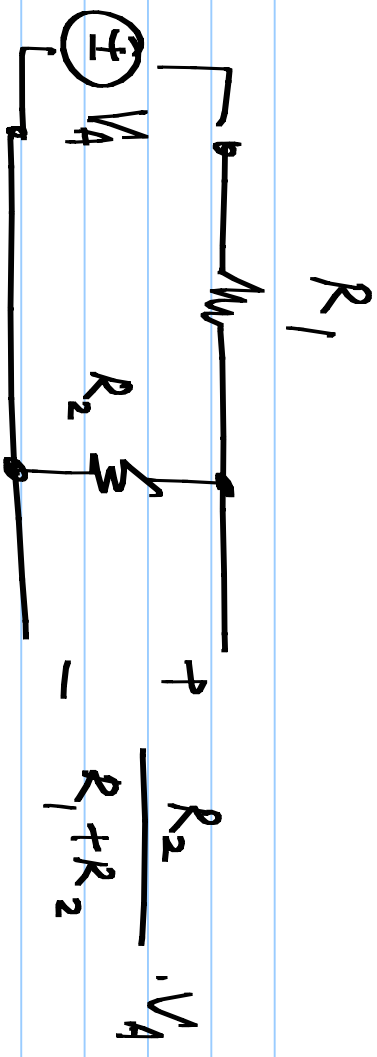

Two port networks:

