
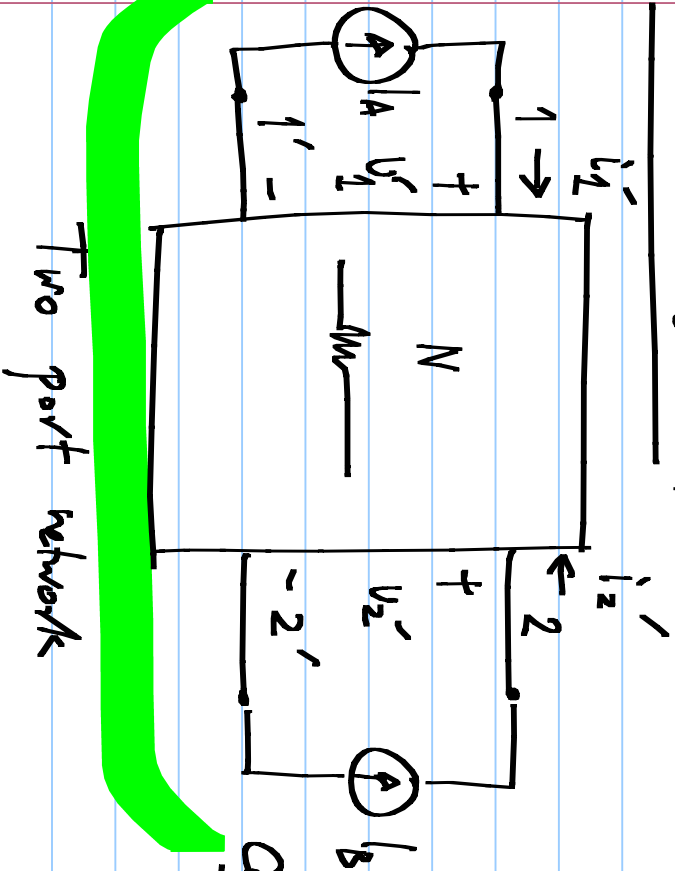


# EC1D10: Lecture 15


## EC1D10: Lecture 14

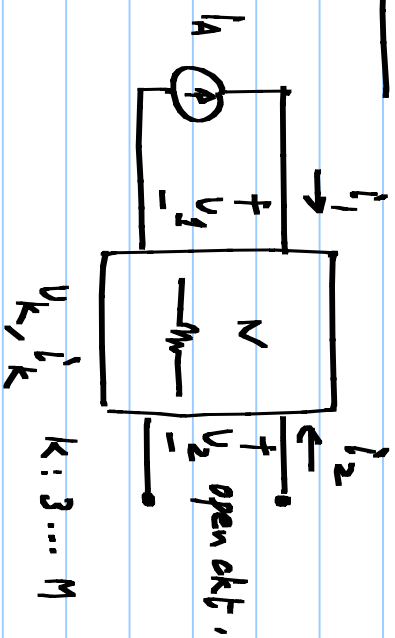


Case 1:  $I_B = 0$



Case 2:  $I_A = 0$

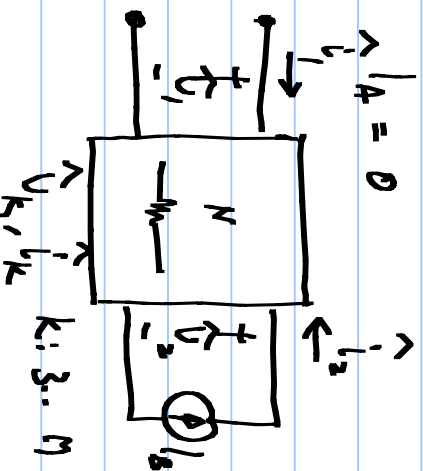

Two port network:

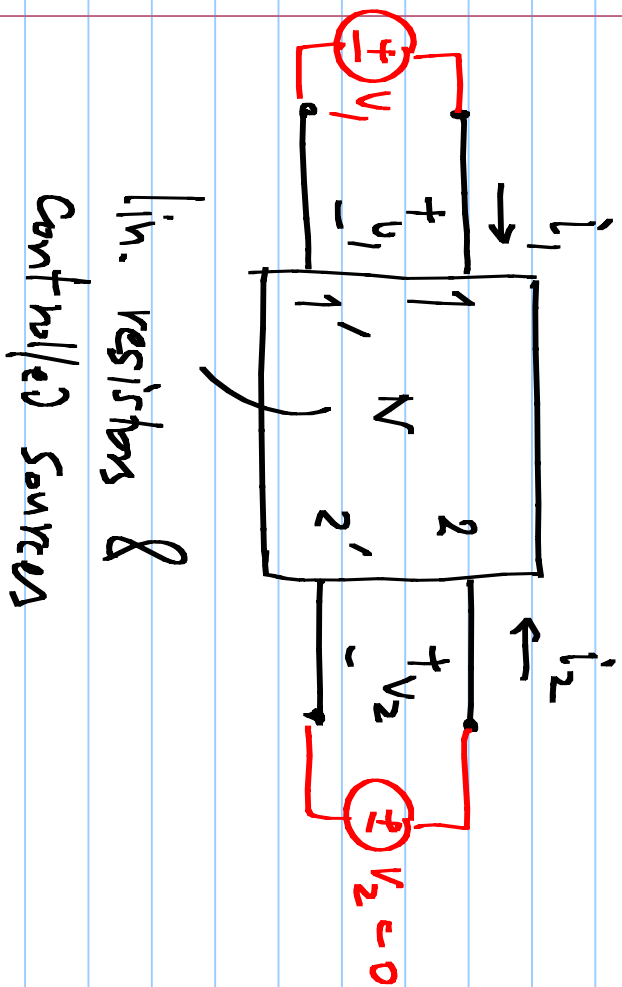

$$i_1 = y_{11} \cdot V_1 + y_{12} \cdot V_2$$

effect


cause

$$i_2 = y_{21} \cdot V_1 + y_{22} \cdot V_2$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

y-parameters of the two port
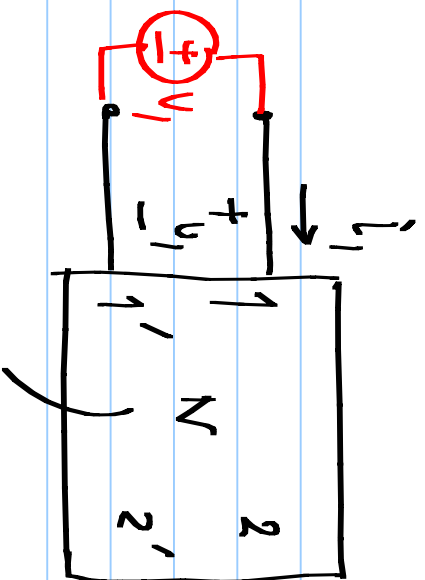
$$i_1 = y_{11} \cdot v_1 + y_{12} \cdot v_2$$




$$i_2 = y_{21} \cdot v_1 + y_{22} \cdot v_2$$

$$y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0} \quad y_{12} = \frac{i_1}{v_2} \Big|_{v_1=0} \quad y_{21} = \frac{i_2}{v_1} \Big|_{v_2=0} \quad y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}$$


Short circuit parameters





$$y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}$$


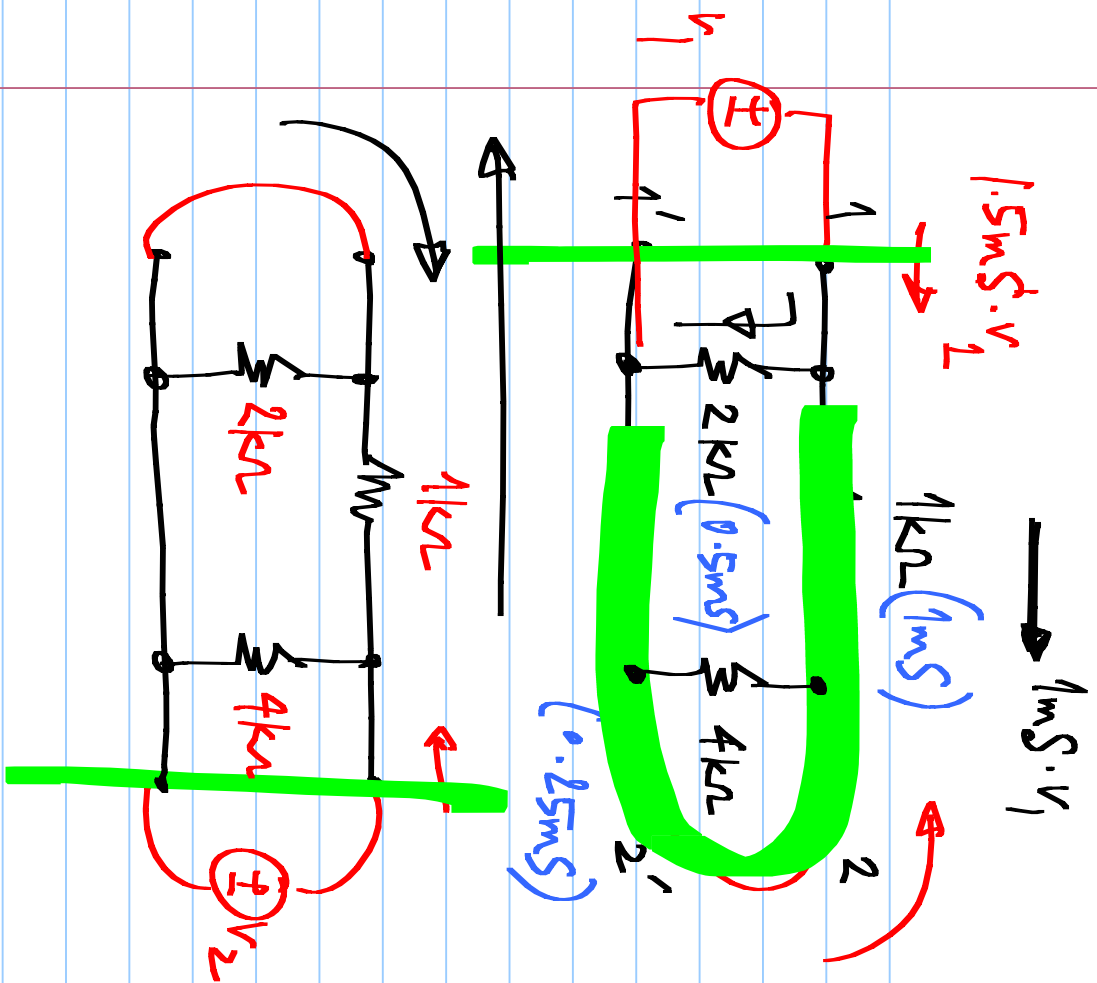



$y_{12} = y_{21}$  for a resistive (reciprocal)
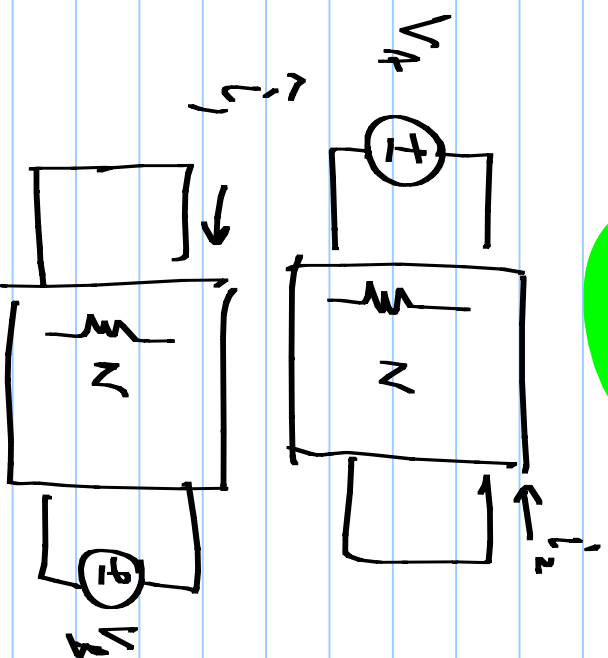
$$[Y] = \begin{bmatrix} 1.5 \text{mS} & 1 \text{mS} \\ -1 \text{mS} & 0.25 \text{mS} \end{bmatrix}$$



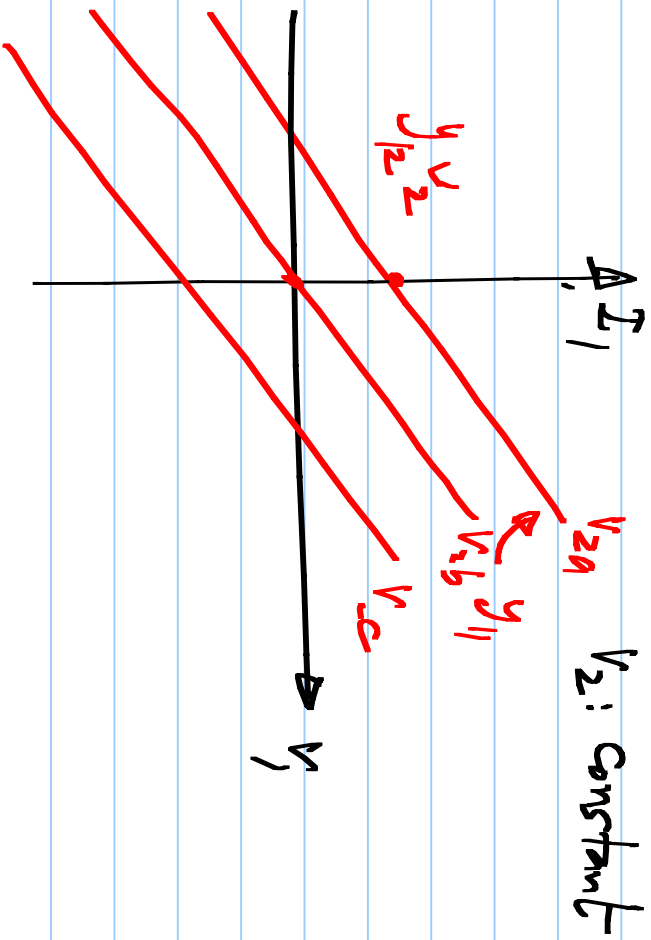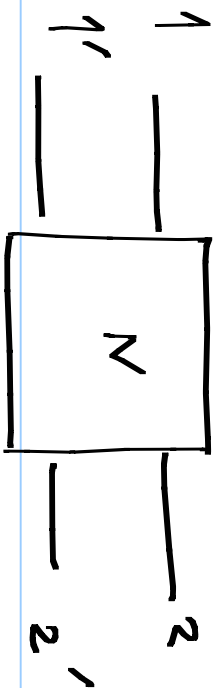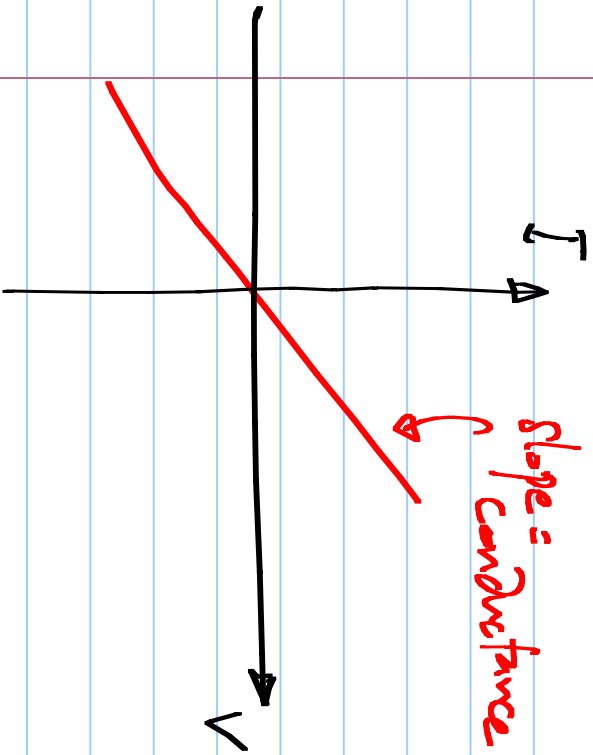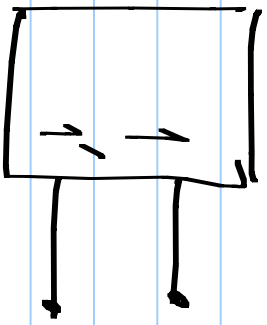


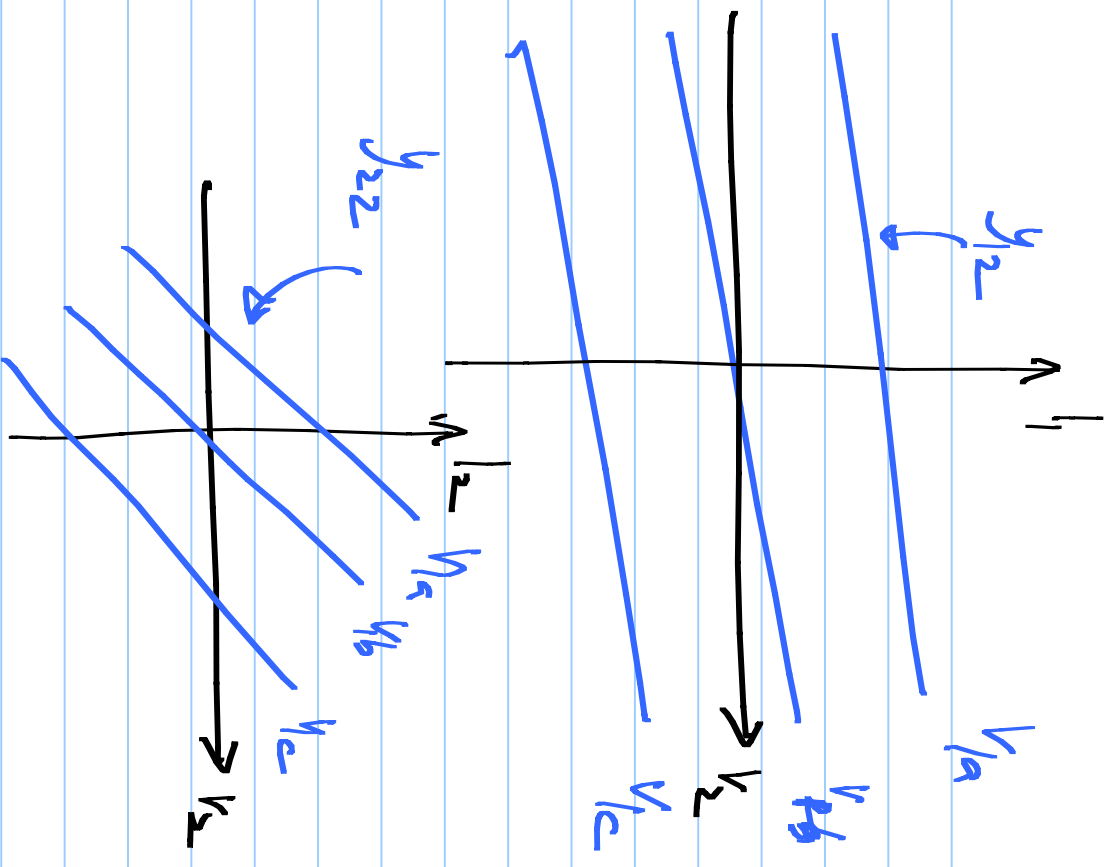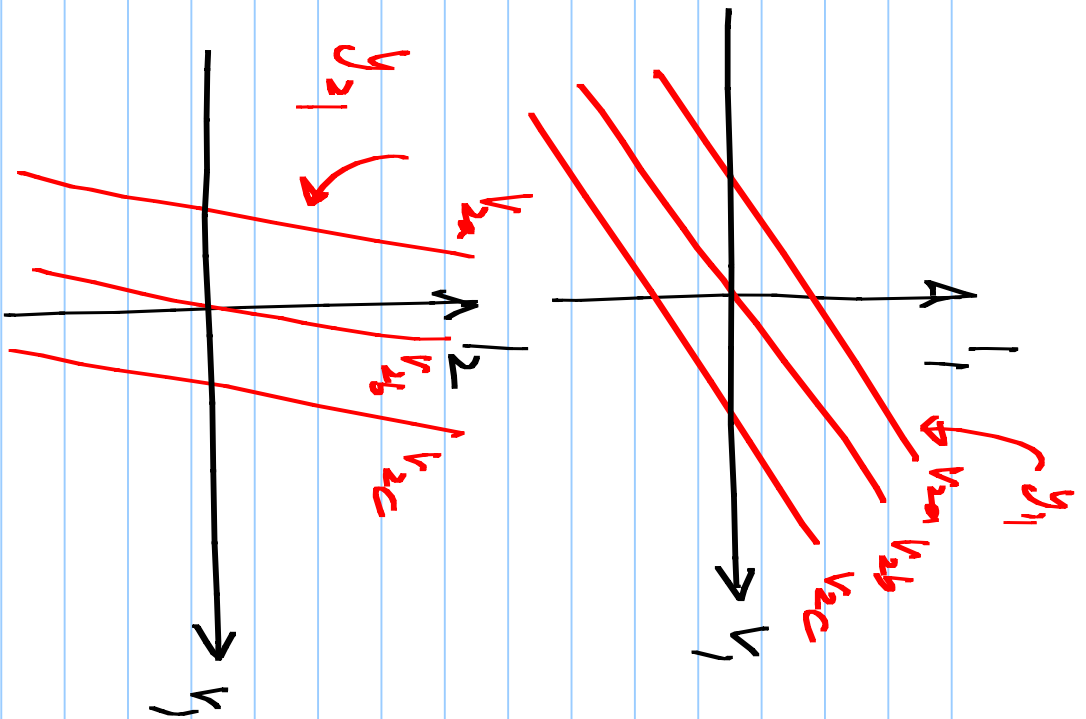

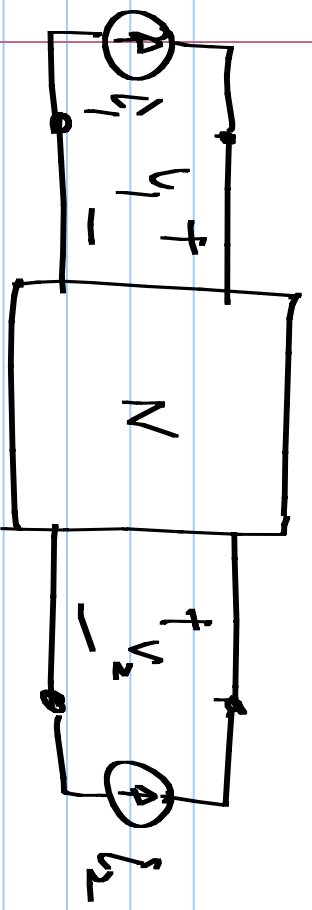

$$v_1 = Z_{11} \cdot i_1 + Z_{12} i_2$$

$$v_2 = Z_{21} i_1 + Z_{22} i_2$$

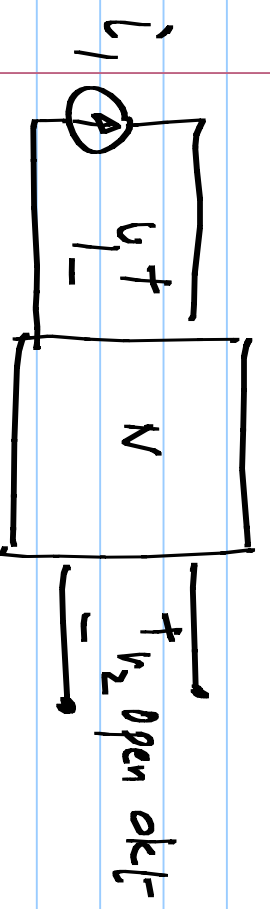

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Z-parameters


open-circuit parameters

$$\left. \frac{v_1}{i_1} \right|_{i_2=0} = Z_{11}$$

$$\left. \frac{v_2}{i_1} \right|_{i_2=0} = Z_{21}$$

$$\left. \frac{i_1}{v_1} \right|_{v_2=0} = y_{11}$$
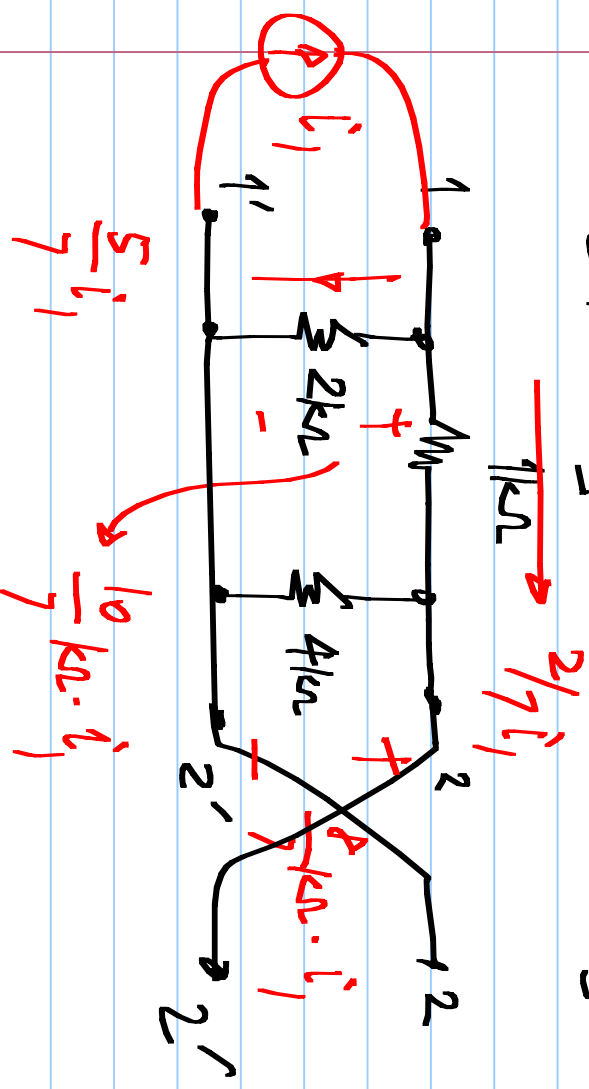
$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}^{-1}$$



$$\begin{bmatrix} \frac{10}{7}k\Omega & \frac{8}{7}k\Omega \\ \frac{8}{7}k\Omega & \frac{12}{7}k\Omega \end{bmatrix}$$





→ hybrid parameters.

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

h-parameters  
Reciprocity?

inverse-hybrid

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

g-parameters