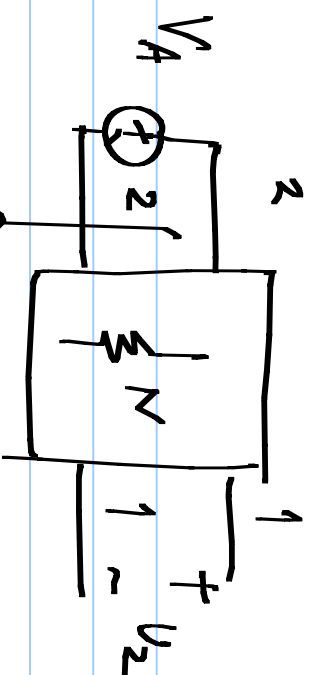


# EC1010: Lecture 16


$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



$$y_{12} = y_{21}$$


$$z_{12} = z_{21}$$

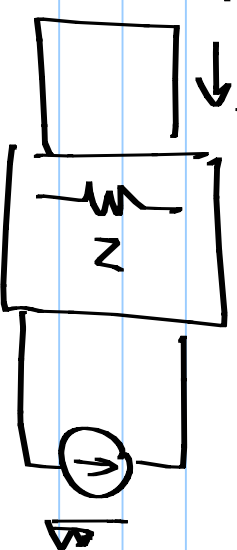

$$h_{21} = -h_{12} \frac{v_1}{v_2}$$


$$\frac{v_2}{v_A} = -\frac{I_B}{g_{21}}$$

$$g_{21} = -g_{12}$$

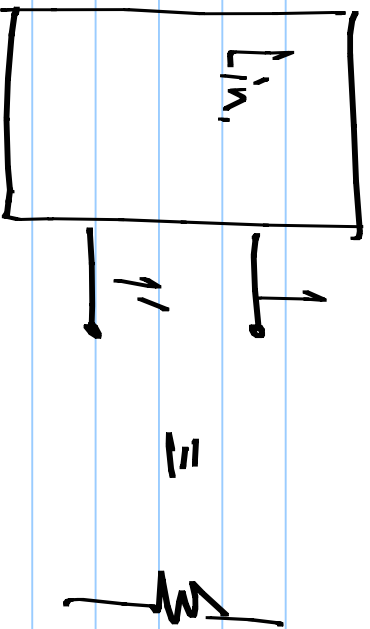


$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

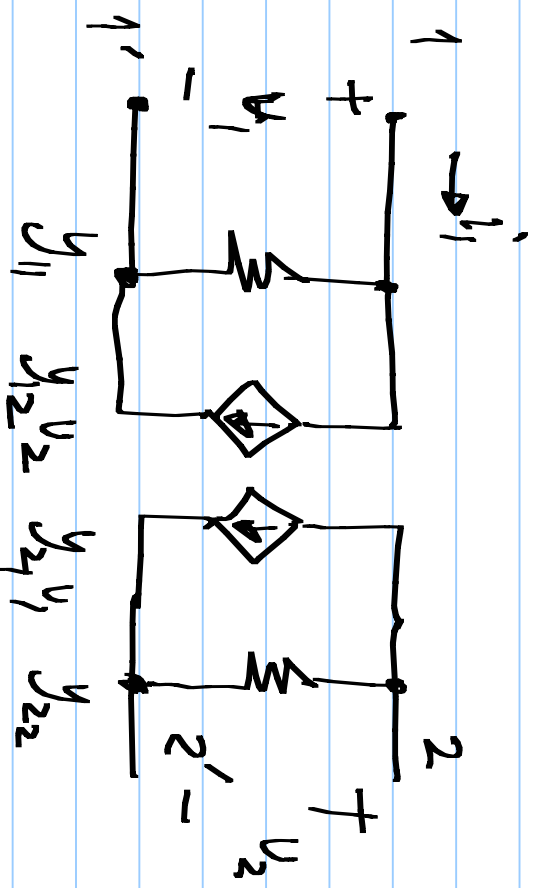
$$\underline{i} = \underline{y}_{11} v_1 + \underline{y}_{12} v_2$$





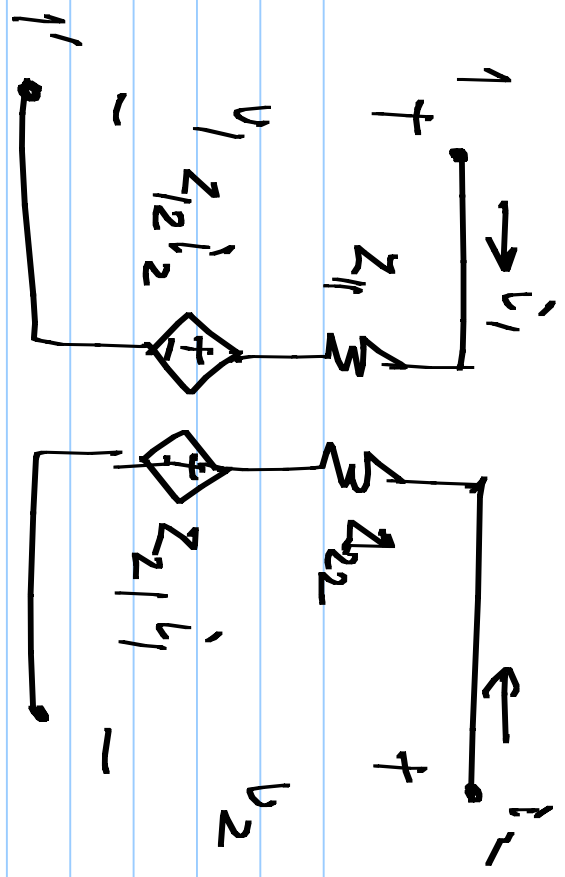
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


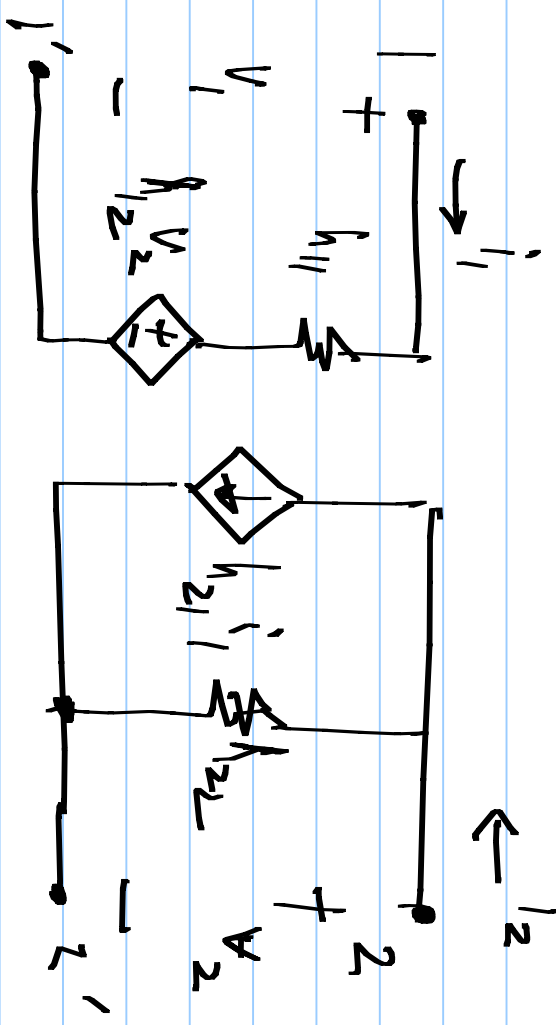
$$\begin{bmatrix} A \\ I_1 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$




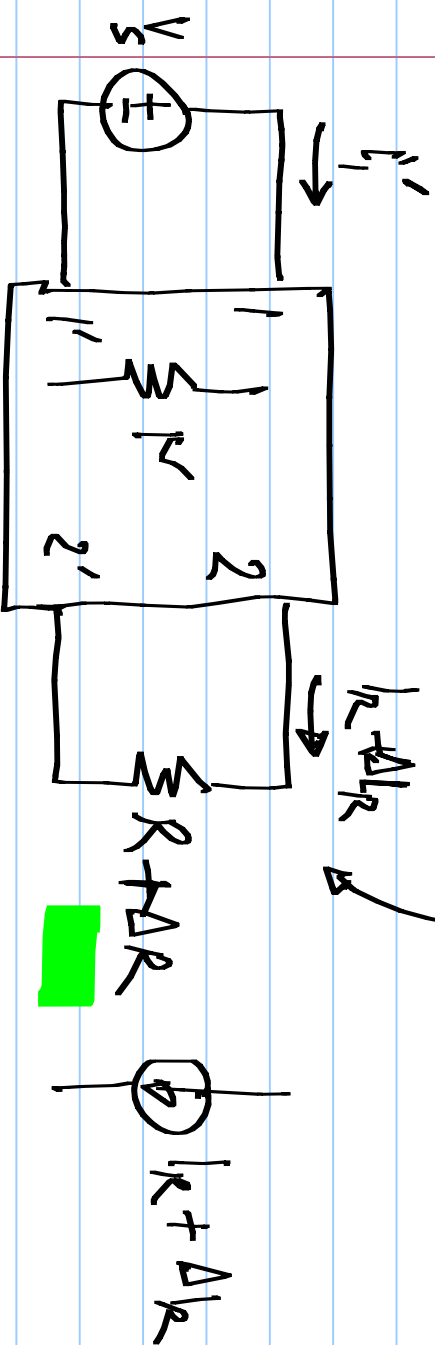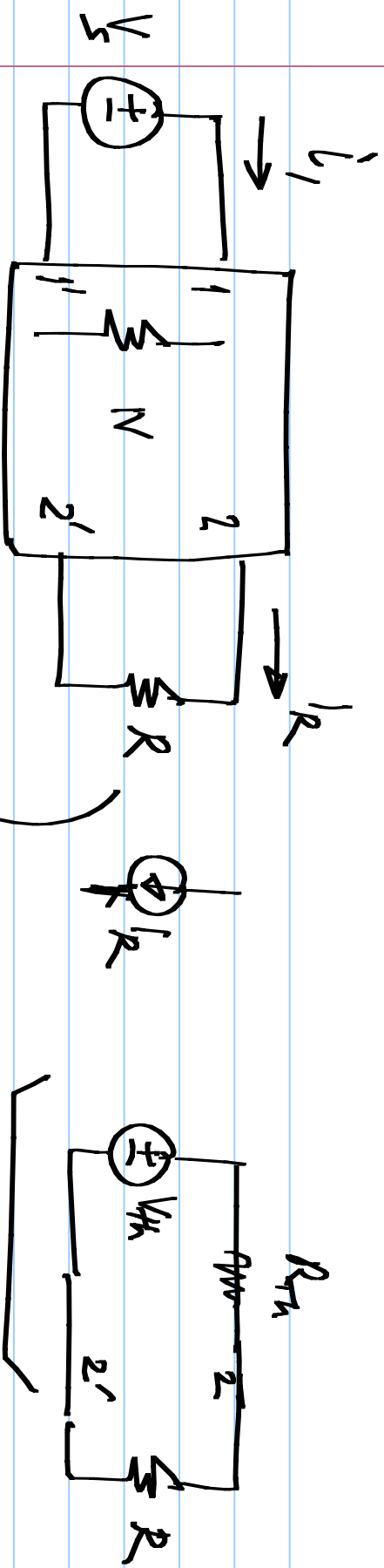

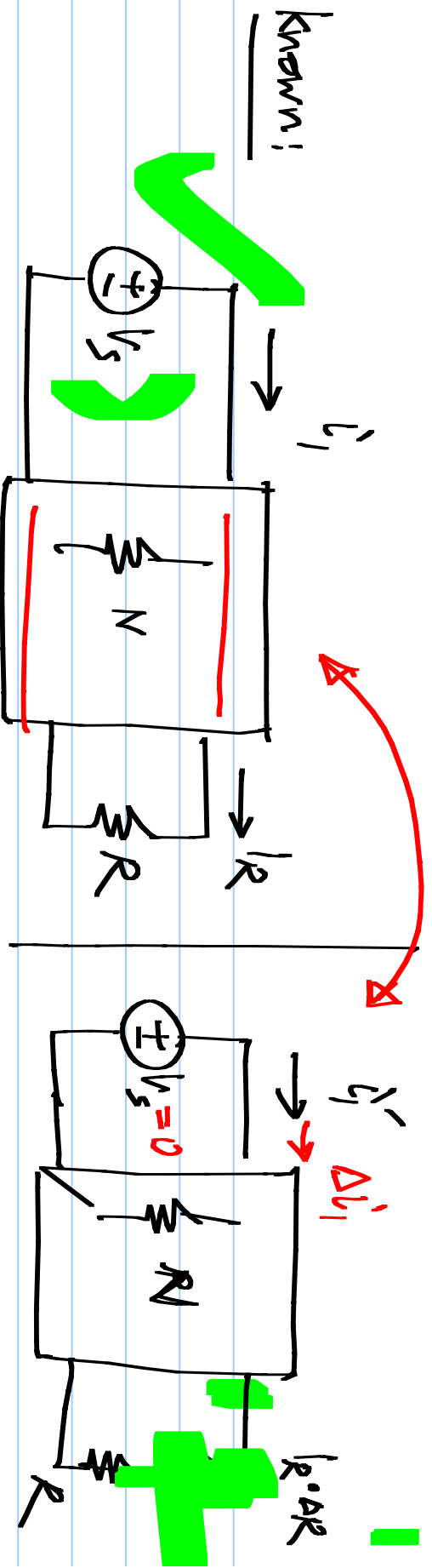

$$\frac{\Delta V_1}{r_1 \cdot \Delta R} = \frac{-i_1}{V_s}$$
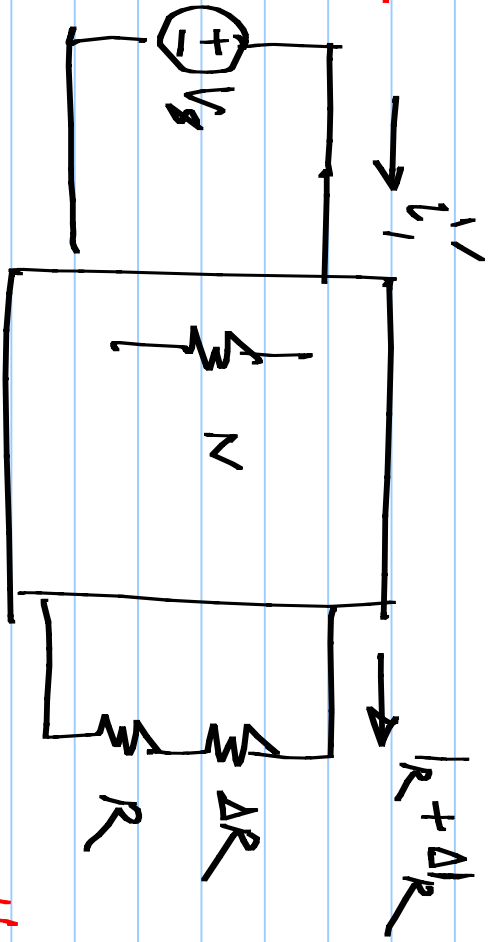
$$\Delta V_1 = -\frac{r_1}{V_s} \cdot \Delta R$$




$$(r_1 + \Delta r) \cdot \Delta R \approx r_1 \cdot \Delta R$$

Compensation theorem

## EC1010: Lecture 17


Reciprocity theorem :

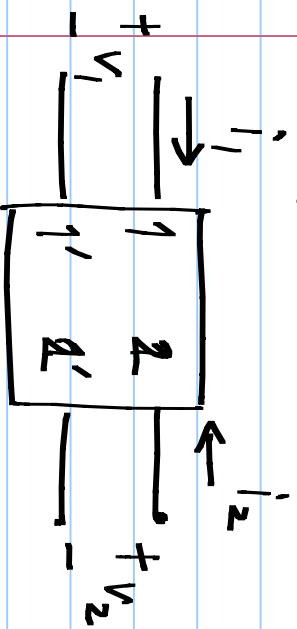

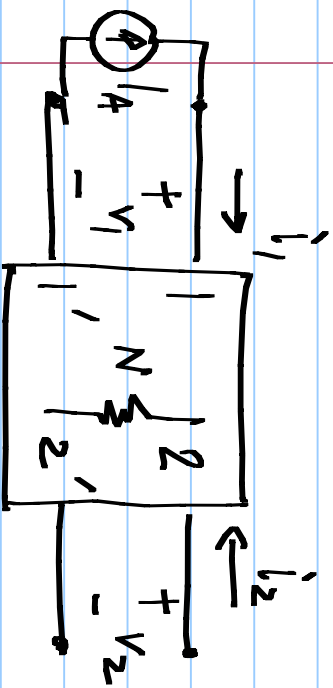- (i) Excitation at port 1 & response @ port 2
- (ii) Excitation at port 2 & response @ port 1


For reciprocal 2 port networks  
(resistive networks are reciprocal)

Excite port 1 with a current &  
leave port 2 open circuited




$$\frac{V_2}{I_A} = \frac{V_1}{I_B}$$

$$Z_{21} = Z_{12}$$

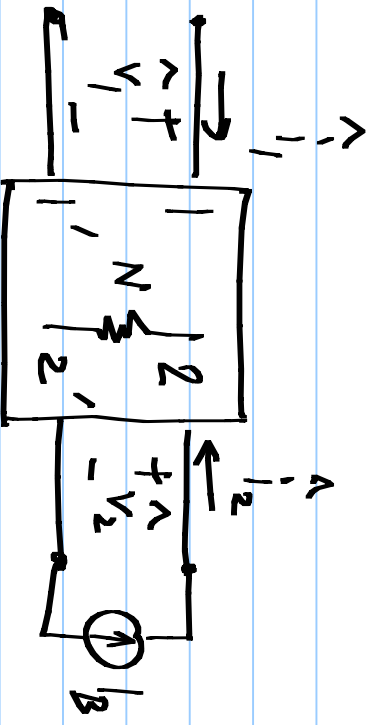

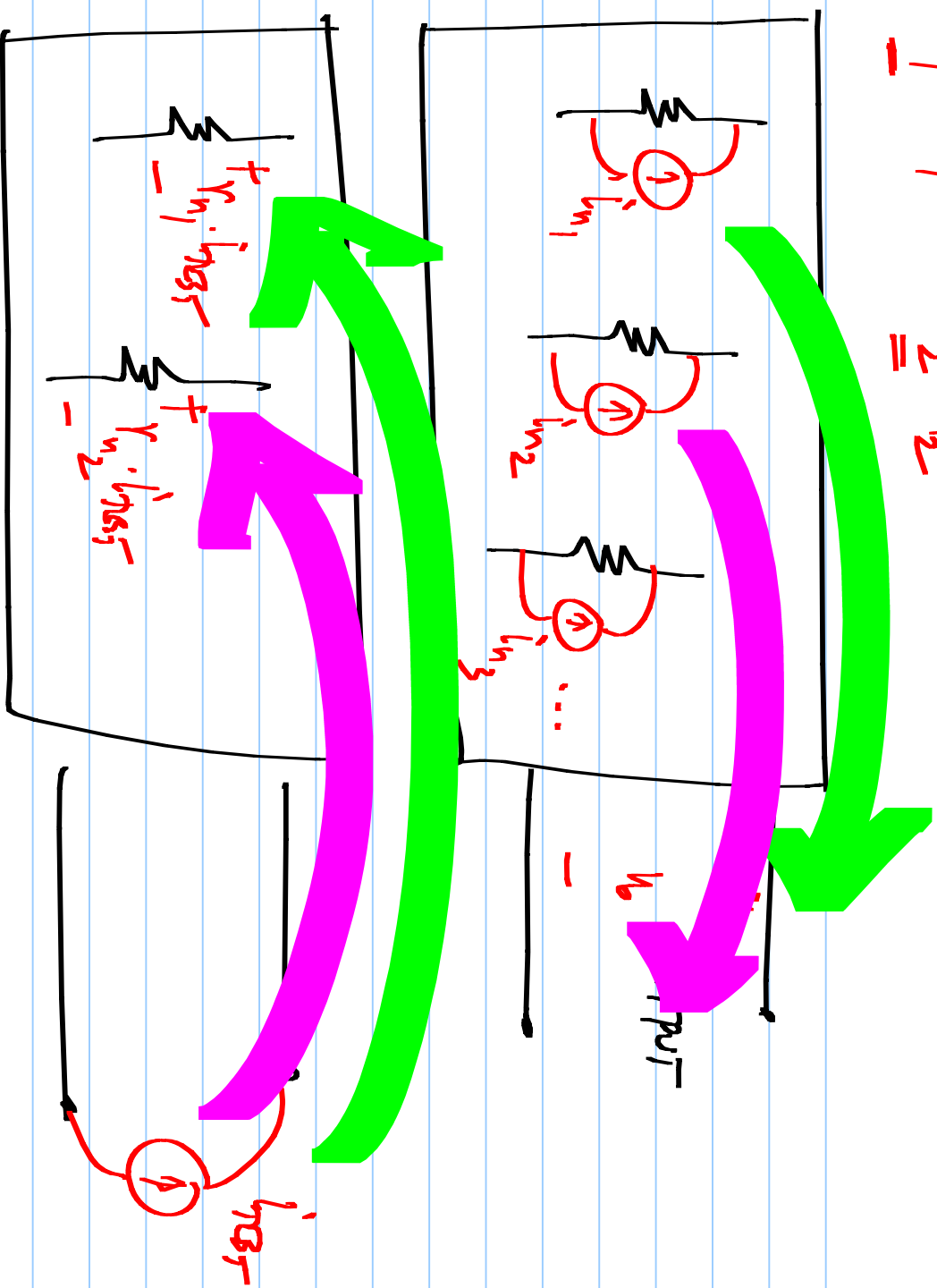
$$V_o = R_{n1} \cdot i_{n1} + R_{n2} \cdot i_{n2} + \dots$$





$$y_{11}V_A + y_{12}V_B$$

$$y_{21}V_A + y_{22}V_B$$

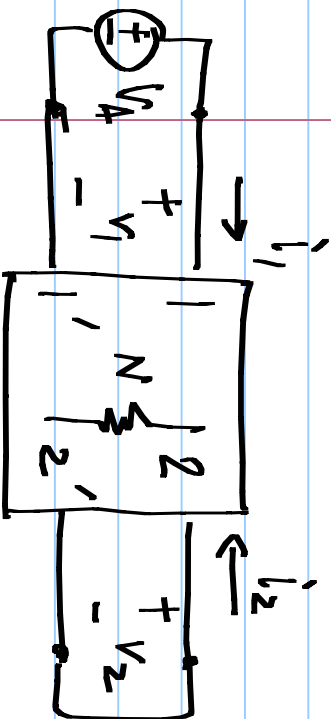


Excite port 1 with a voltage & leave port 2 short circuited (port 2)

$$i_2 = \frac{i_1}{V_A}$$

$$y_{21} = y_{12}$$



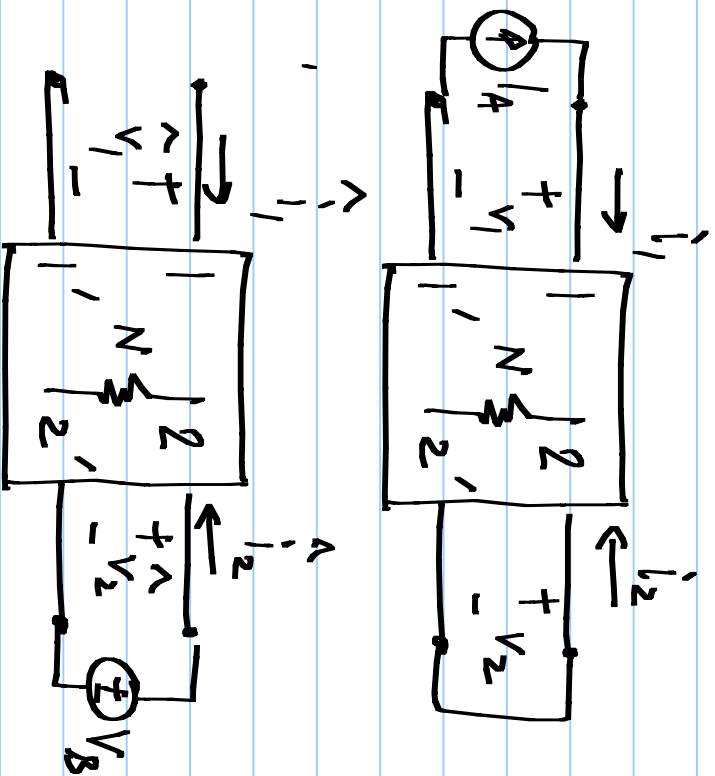
Excite port 1 with a current & leave port 2 short circuited




$$h_{21} = -\frac{I_2}{I_1} = -\frac{V_1}{V_2}$$

$$h_{21} = -h_{12}$$

$$g_{21} = -g_{12}$$

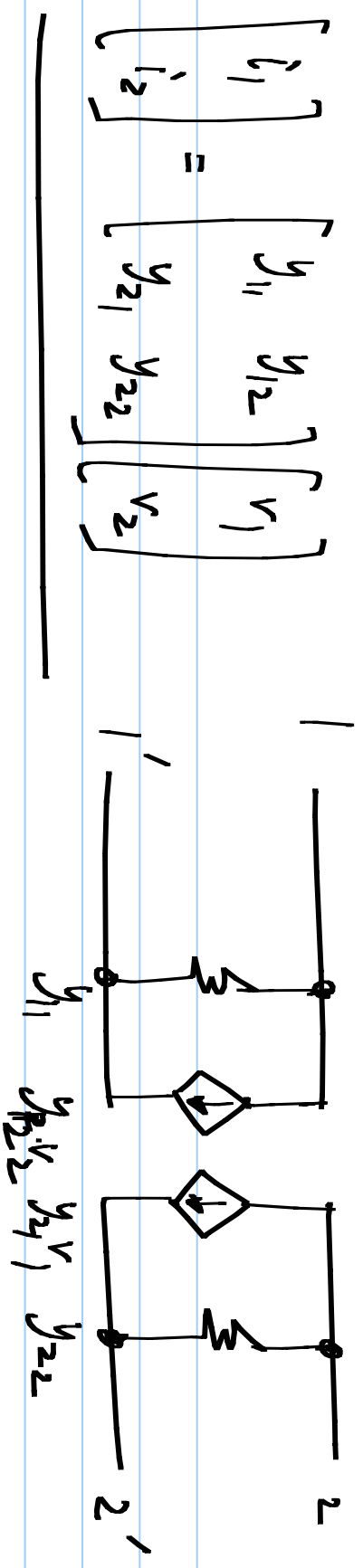

Ideal VCVS

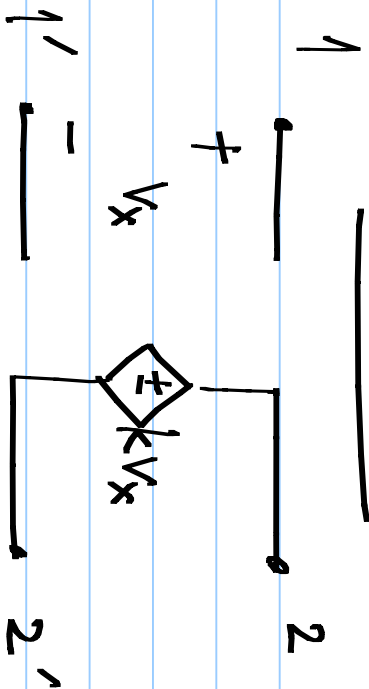

g-Parameters


$$\begin{bmatrix} 0 & 0 \\ k & 0 \end{bmatrix}$$

Unilateral


$$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$


VCCS

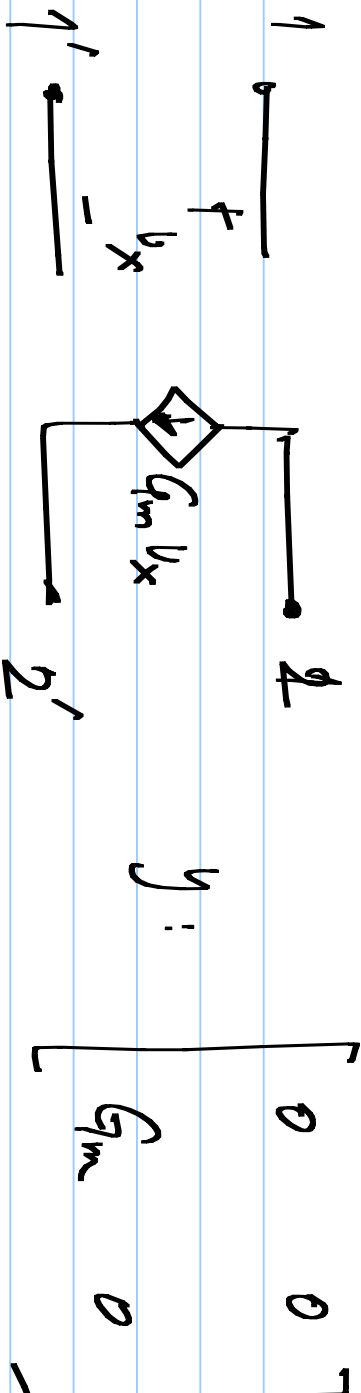

CCVS

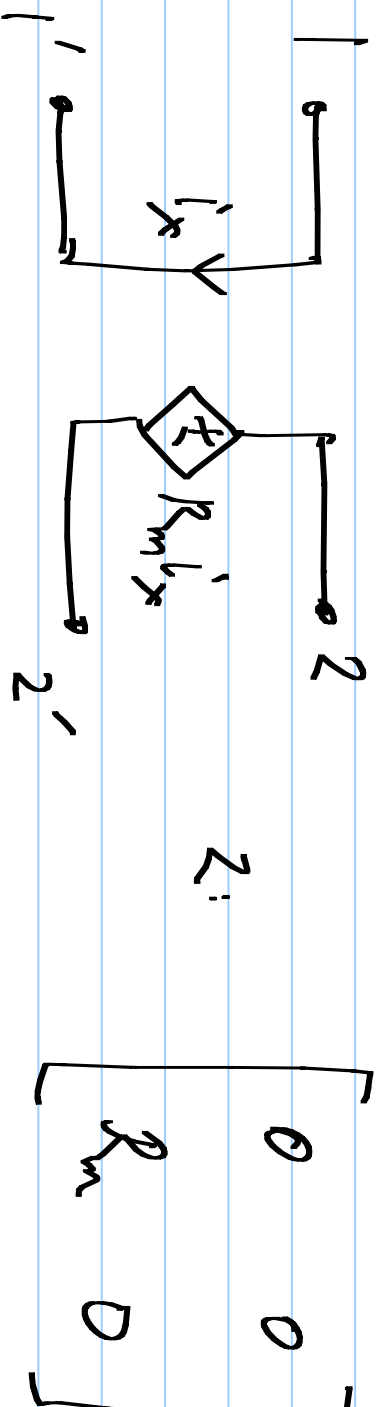

CCCS

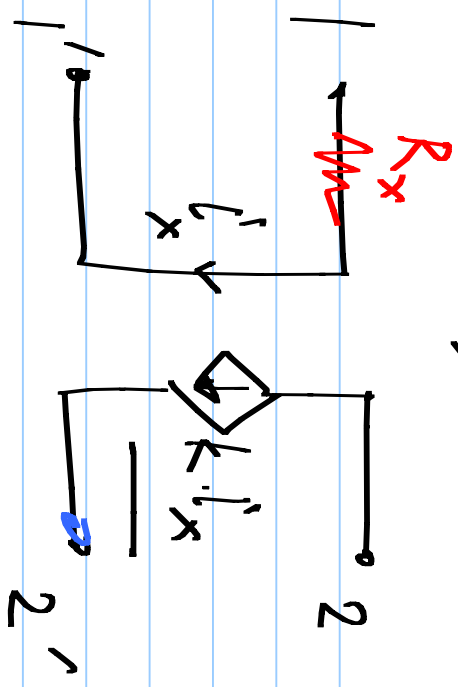


$h_i$

$$\begin{bmatrix} 0 & R_x \\ k & 0 \end{bmatrix}$$

$$[Z]^T = [y]$$

$$\begin{bmatrix} 1/R_x & 0 \\ k/R_x & 0 \end{bmatrix}$$

$y:$

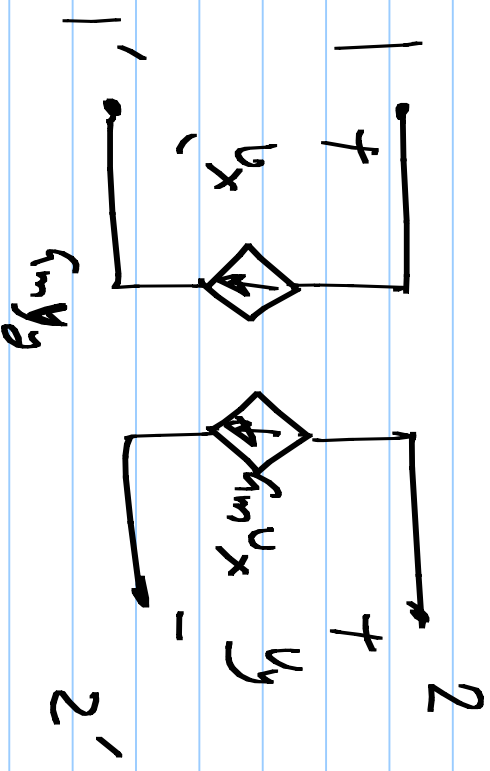

$$\begin{bmatrix} 0 & g_m \\ g_m & 0 \end{bmatrix}$$