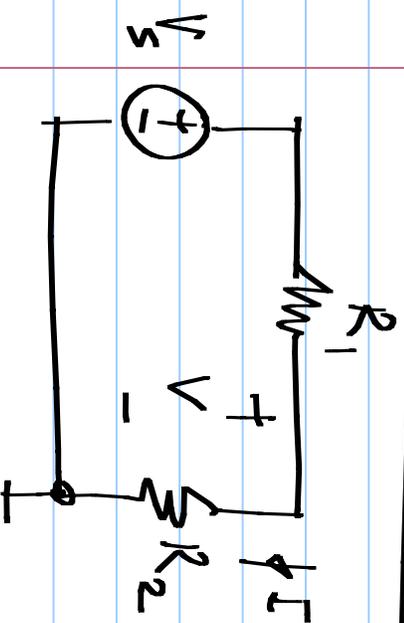



# EECE1010: Lecture 18

## Nonlinear circuits



$$I = V/R_2$$

$$I = \frac{V_s - V}{R_1}$$

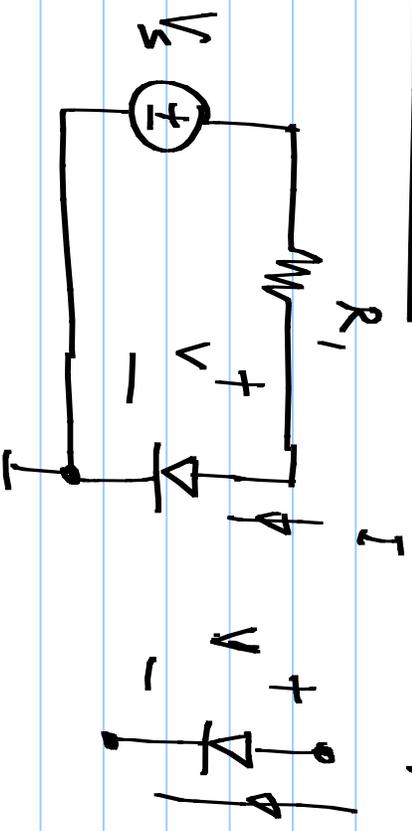


$$I = f(V)$$

$$I = f(V)$$

$$I = \frac{V_s - V}{R_1}$$
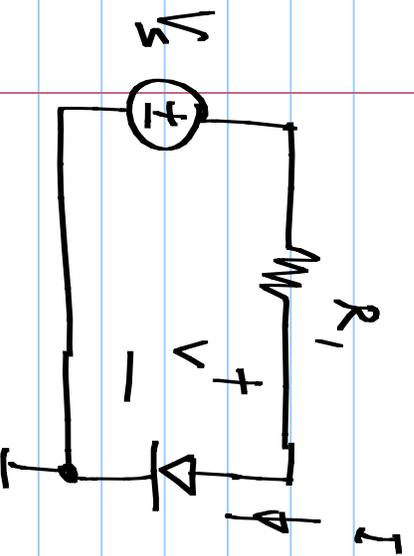
$$\underline{V_s - V - R_1 \cdot f(V) = 0}$$



$$I = f(V)$$

Diode:

$$I = f(V) = I_s \left( \exp\left(\frac{V}{V_T}\right) - 1 \right)$$

$I_s$ : Saturation current

$V_T$ : Thermal voltage

300k

$$I = f(V)$$

$$\approx 4 \times 10^{-21} \text{ A}$$

@ 300k

$$I = \frac{V_s - V}{R_1}$$

25.9 mV @ 300k

26 mV @ Room temp.

Absolute temperature


Electron charge

Boltzmann's constant

$$1.38 \times 10^{-23} \text{ J/K}$$

$$\frac{kT}{q} \quad 1.6 \times 10^{-19} \text{ C}$$

# Diode characteristics:

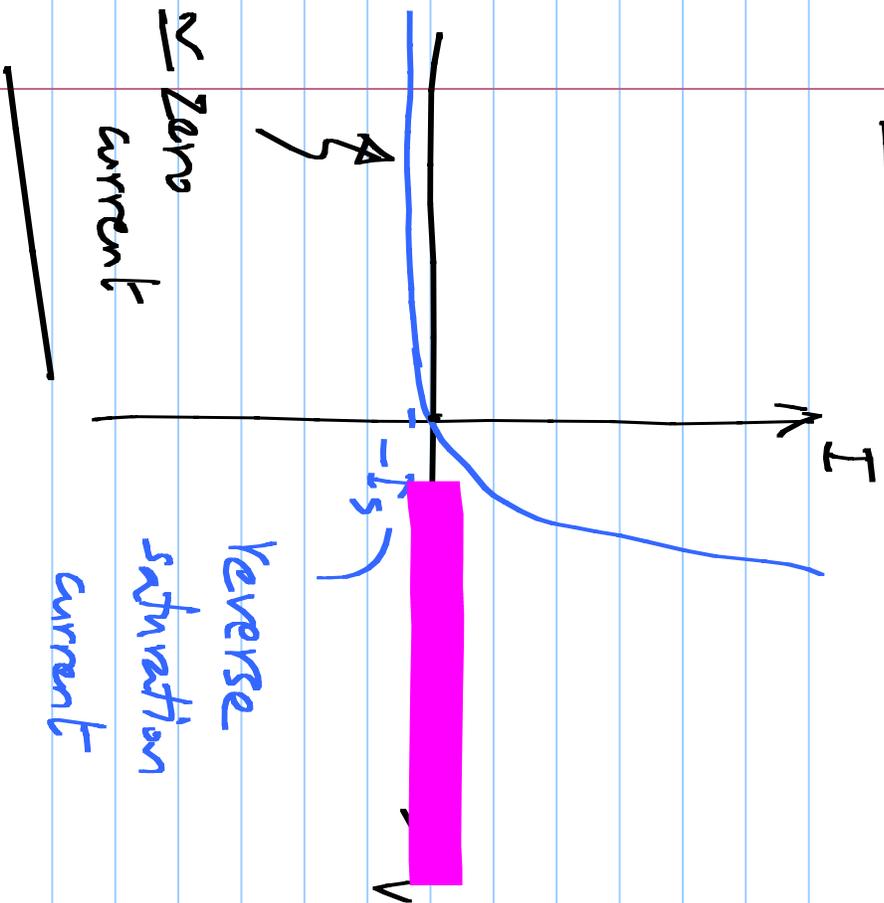

$$I = I_s \left( \exp\left(\frac{V}{V_T}\right) - 1 \right) \approx I_s \exp\left(\frac{V}{V_T}\right)$$


$$I_s : 10^{-15} \text{ A}$$


$$I = 1 \text{ mA} \sim V : ?$$

I	V	$V_T \approx 25 \text{ mV}$
$100 \mu\text{A}$	$63 \text{ mV}$	}
$1 \text{ mA}$	$69 \text{ mV}$	
$10 \text{ mA}$	$75 \text{ mV}$	

$$I = I_s \exp(V/V_t)$$

Diode

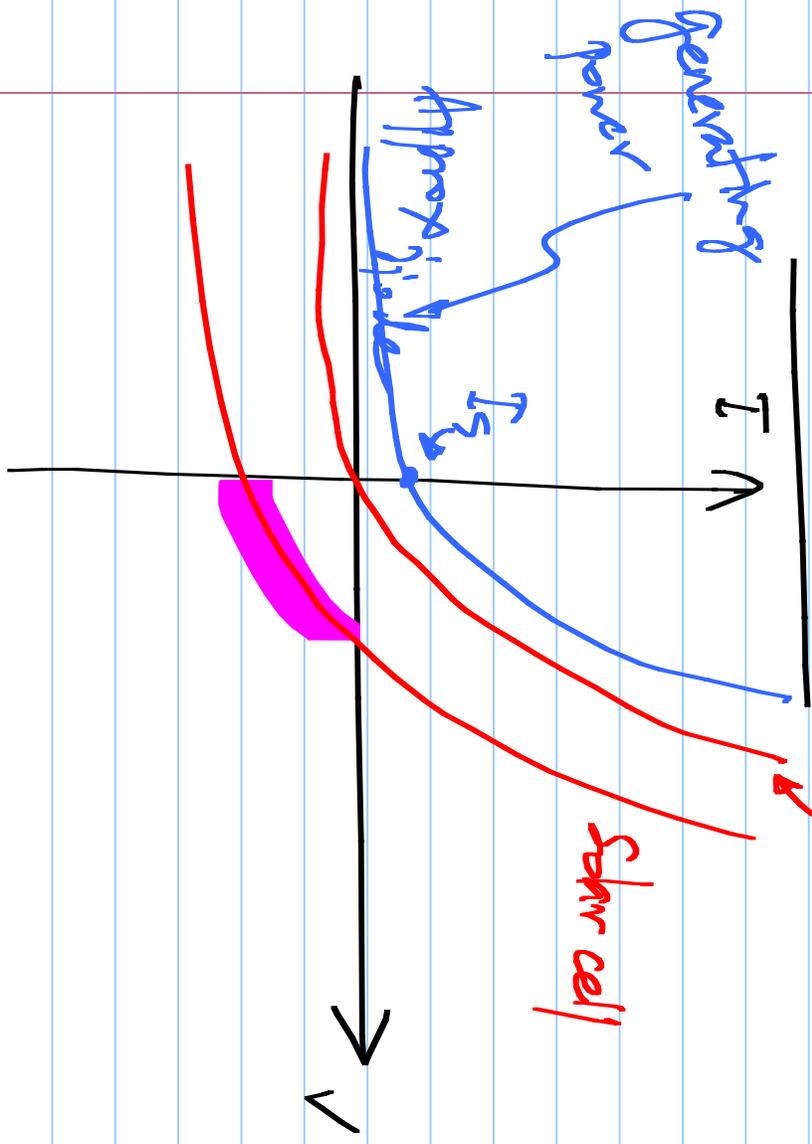

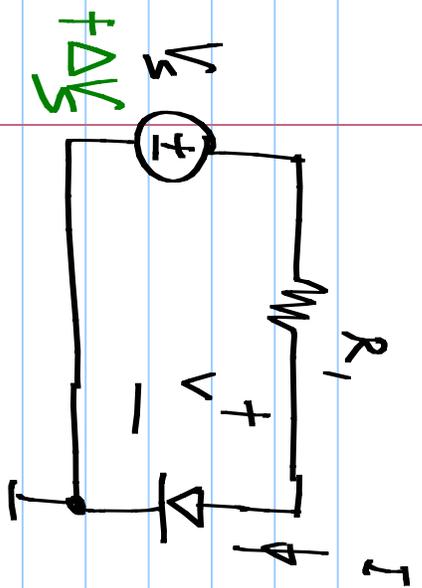


$$I = f(V)$$


$$I = f(V) \quad \textcircled{1}$$

$$I = \frac{V_s - V}{R_1} \quad \textcircled{2}$$


$V_o$ : operating point  
 { First case for which

the solution was calculated

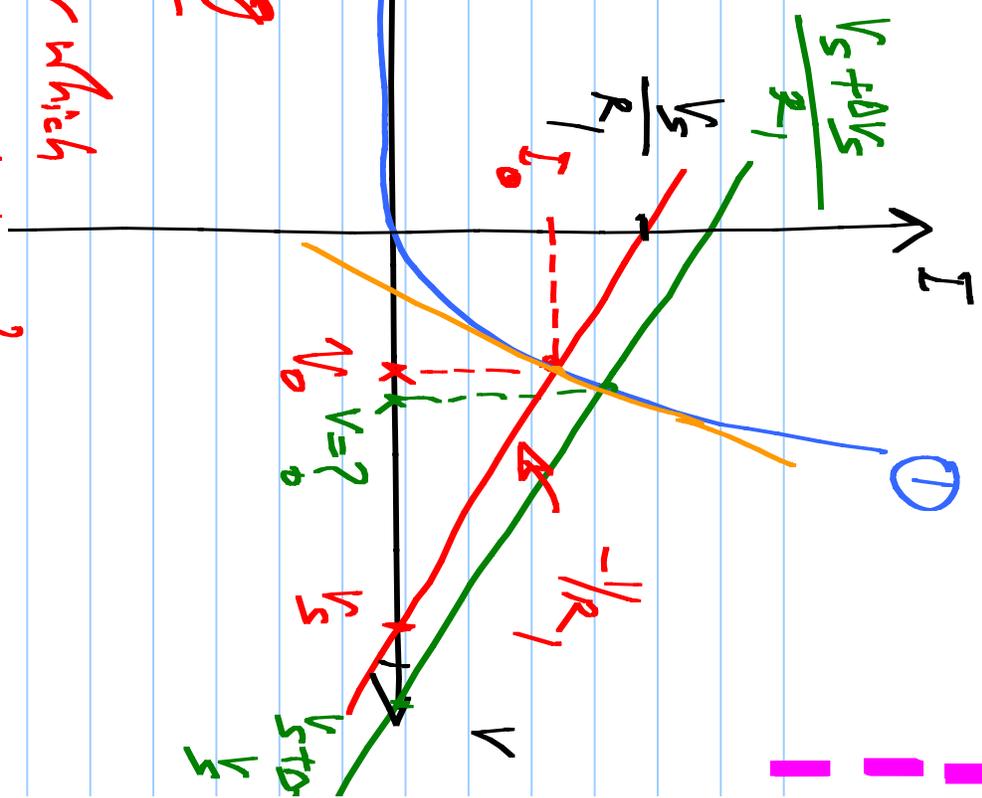

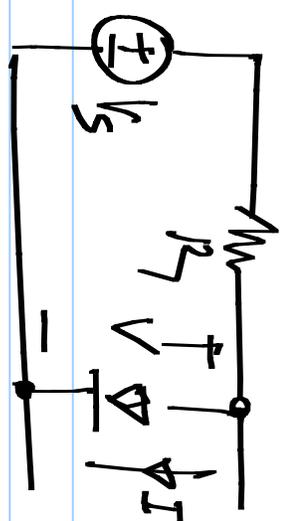


$I = f(V)$

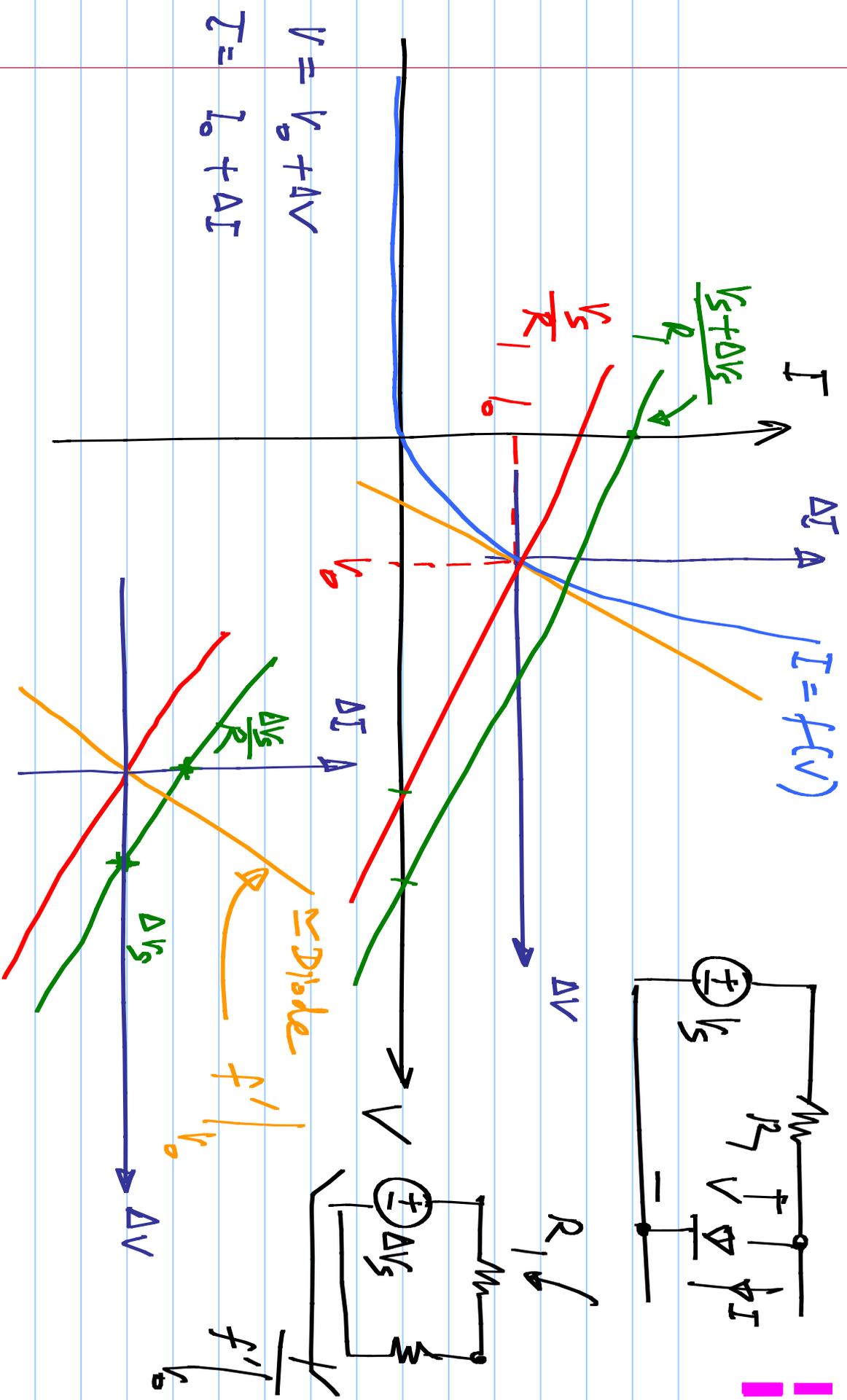


$V = V_0 + \Delta V$   
 $I = I_0 + \Delta I$

$\approx$  Diode

$f'(V_0)$

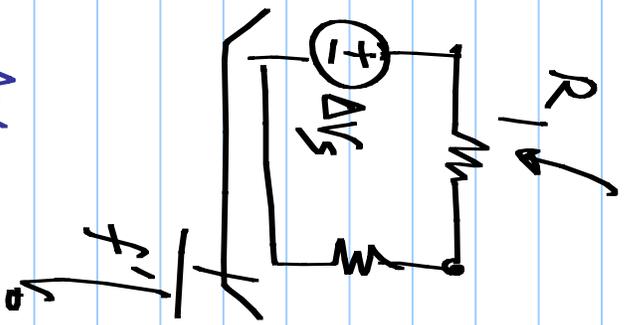


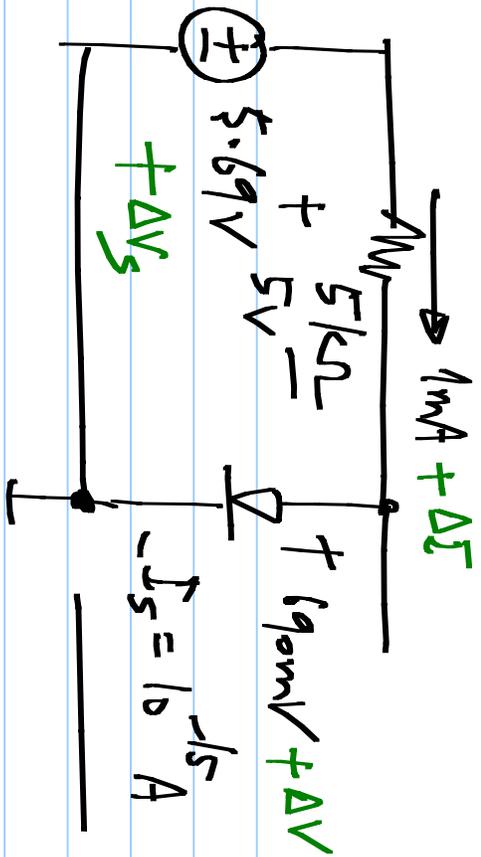

$V_D = 690\text{mV}$   
 $I_D = 1\text{mA}$   
 $\frac{1}{f' \left| \frac{V_D}{V_0} \right.}$  incremental resistance

I	V
100μA	630mV
1mA	690mV
10mA	750mV

Incremental conductance  $f' \left| \frac{V_0}{V_D} \right.$

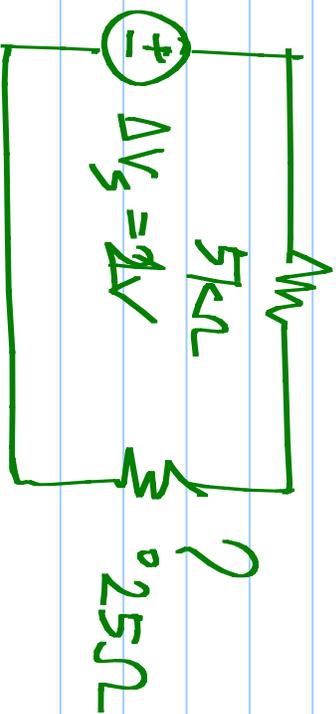

$$f(V) = I_s \left[ \exp\left(\frac{V}{V_T}\right) - 1 \right] \approx I_s \exp\left(\frac{V}{V_T}\right)$$

$$\frac{1}{f' \left| \frac{V_0}{V_D} \right.} = \frac{1}{I_s} \frac{V_T}{V_D}$$