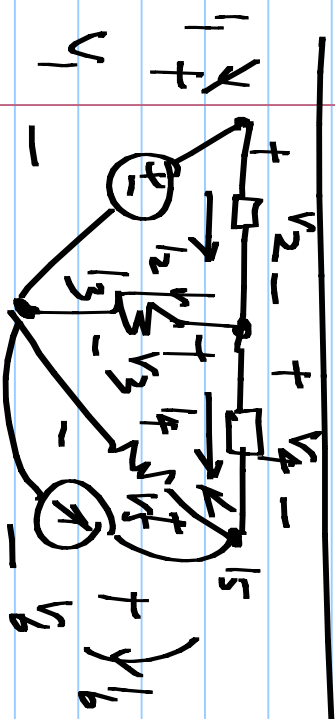


EECE 1010: Lecture 19

Newton-Raphson / Fixed point iteration /

Bisection

* Nodal analysis / MNA: Nonlinear



(circuit analysis) equations

$$[G] \underline{v} = \underline{I_s} + \underline{\Delta I_s}$$


$$\underline{h}(\underline{v}) = \underline{I_s} + \underline{\Delta I_s}$$

Solve nonlinear equations

Solution: V_{k0}, I_{k0} operating point

* Changed input $V_k = V_{k0} + \Delta V_k$

$$I_k = I_{k0} + \Delta I_k$$

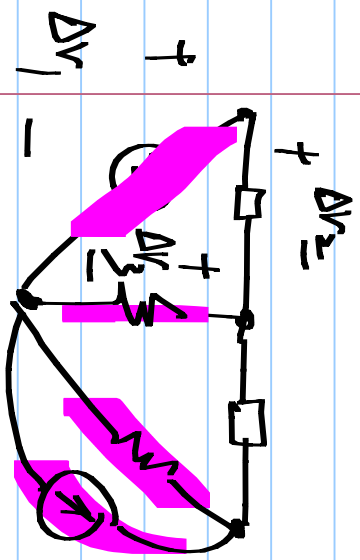

$$\frac{V_k}{I_k} = R_k$$

$$\frac{\Delta V_k}{\Delta I_k} = R_k$$

* Incremental equivalent circuit: circuit with the same graph as the original. Branch voltages: ΔV_k

currents: ΔI_k

— Linear elements: remain the same


— Independent sources: replaced by source of the same type & value = change in value

Nonlinear elements: For small increments, relationship

$I = f(V)$

between ΔV_k & ΔI_k is linear $\rightarrow \Delta I_k = f'(V_0) \cdot \Delta V_k$


replaced by resistances

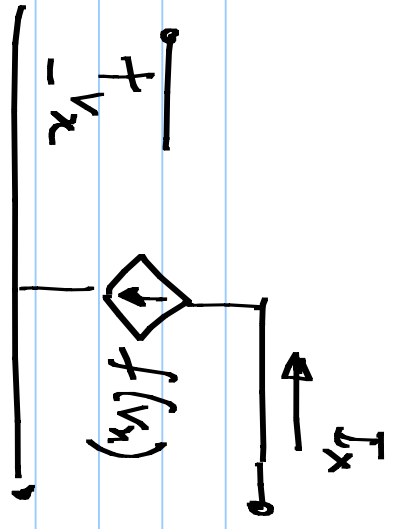

$$I_x = f(V_x)$$


$$I_{x_0} = f(V_{x_0})$$

op. point

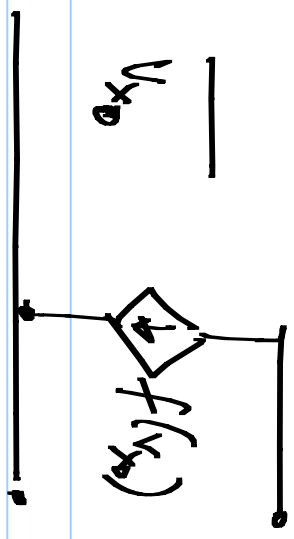

incremental

$$\Delta V_x$$

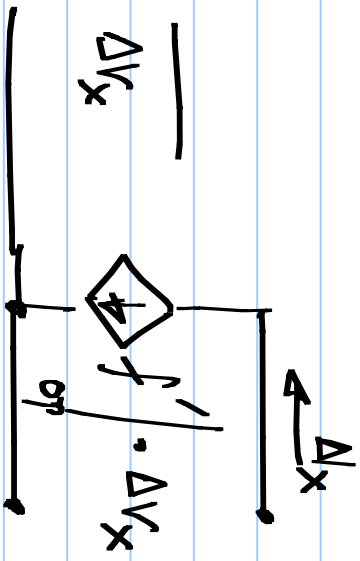


$$I_{x_0} + \Delta I_x = f(V_{x_0} + \Delta V_x) \approx f(V_{x_0}) + f'(V_{x_0}) \cdot \Delta V_x + \dots$$

$$I = I_s \exp\left(\frac{V}{V_T}\right)$$

$$I_0 + \Delta I = I_s \exp\left(\frac{V_0 + \Delta V}{V_T}\right)$$

$$= I_s \exp\left(\frac{V_0}{V_T}\right) \left[1 + \frac{\Delta V}{V_T} \right]$$
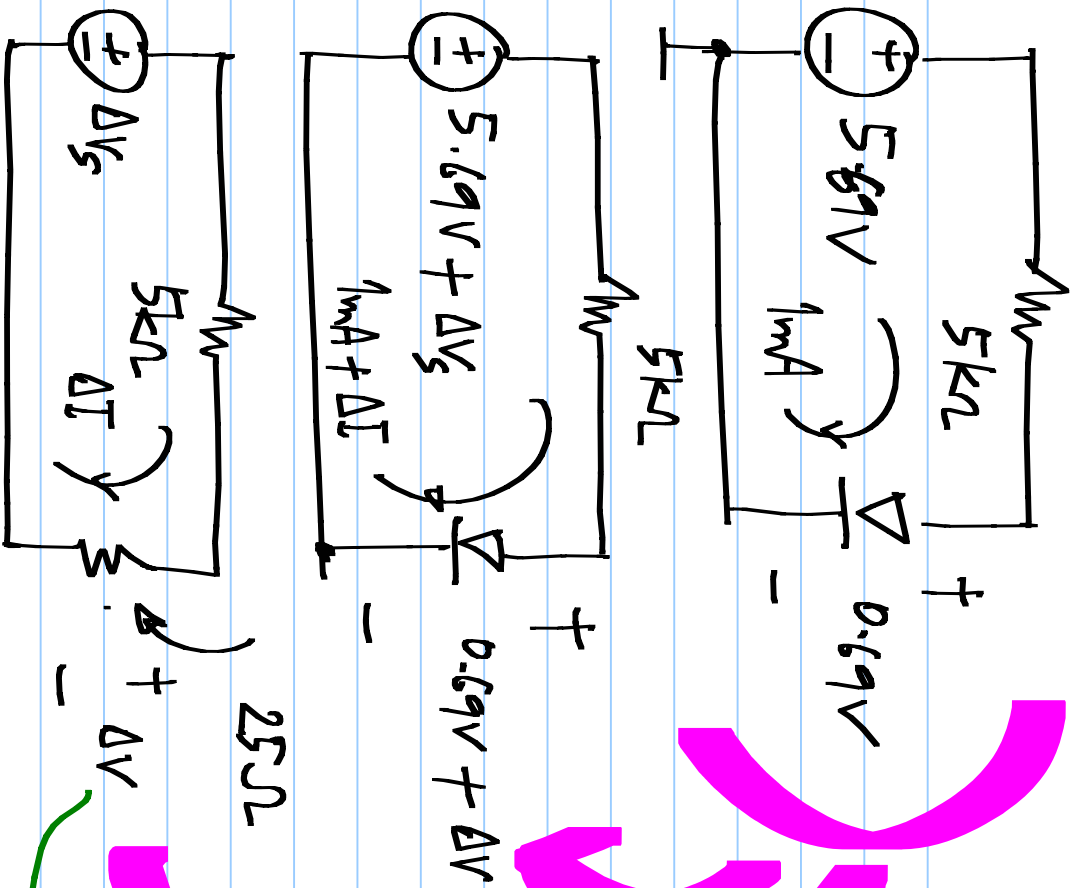
$$\frac{9.5}{25} + \frac{1}{21} \left(\frac{\Delta V}{V_T}\right)^2 + \frac{1}{3} \left(\frac{\Delta V}{V_T}\right)^3 + \dots$$



9.5 mV

$$I_s = 10^{-15} \text{ A}$$

I	V
100 μA	630 mV
1 mA	690 mV
10 mA	750 mV

$\approx 0.7 \text{ V}$

