

EC1010: Lecture 21

Negative feedback amplifier: $V_o = KV_i$

$$V_c = V_i - \frac{V_o}{K}$$

$$\int V_c dt = \frac{1}{3} V$$

$$Integrate \text{ the error (difference)} \\ \text{to drive the output}$$


Operations amplifier (op-amp)

$$V_o = 2V$$

$$V_i = \frac{V_o}{K}$$

$$V_o = KV_i$$


@ same voltage

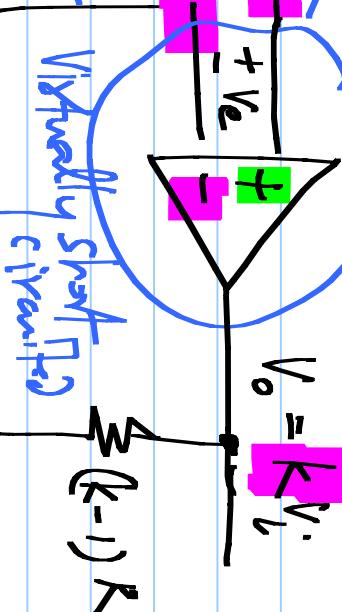


Non-inverting amplifier ($gain K > R$)

$$R$$

$$(k-1)R$$

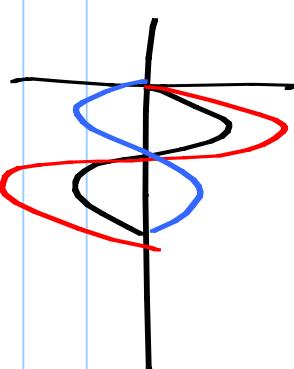


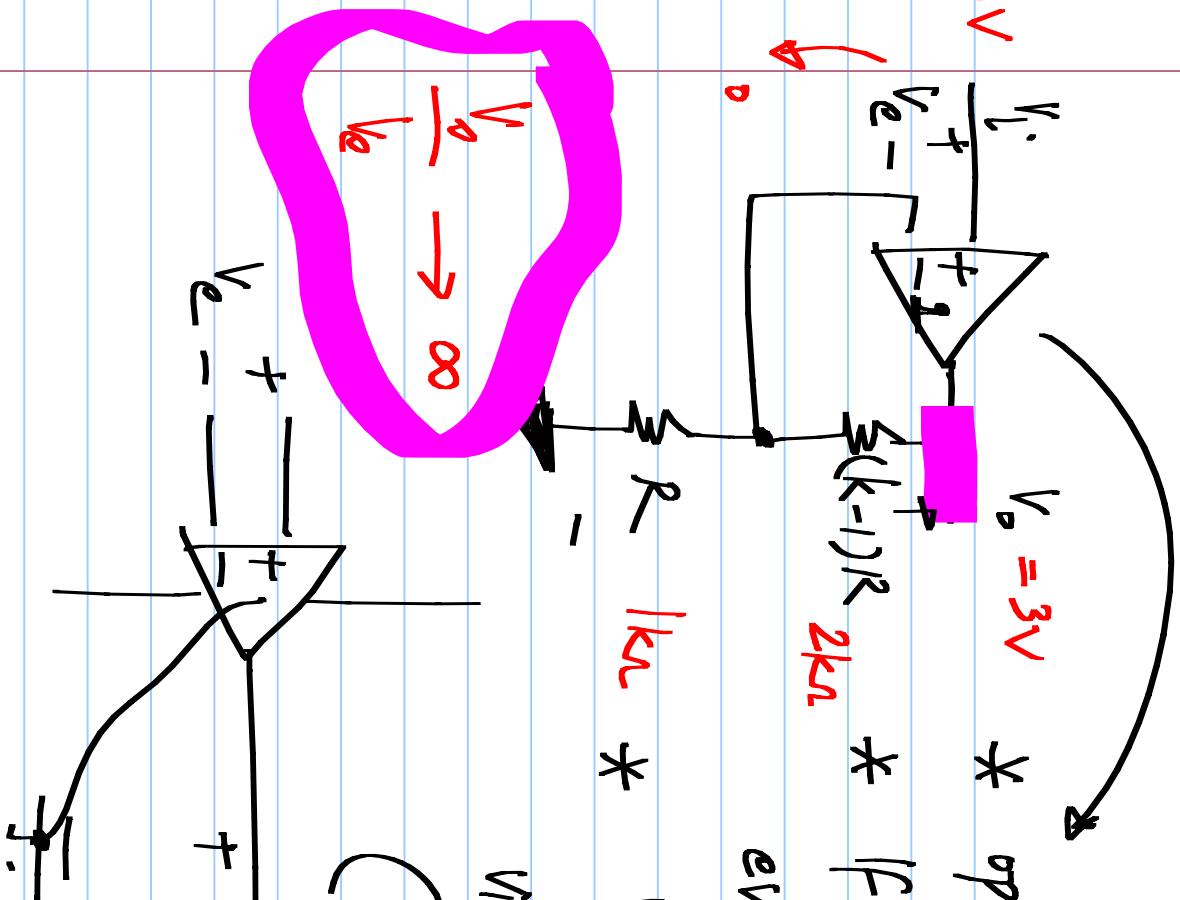


* op amp: "integrates" the error V_e
 * if it is in negative feedback,
 eventually V_e reaches zero


$|k| \cdot V_e = 0 \Rightarrow$ opamp inputs are
 virtually shorted to each other

(Negative feedback essential for this!)

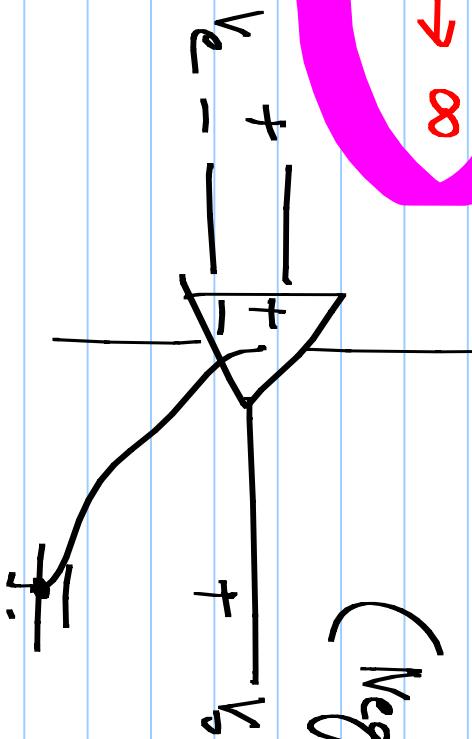

opamp modeled as $V_C V_S$ of gain A

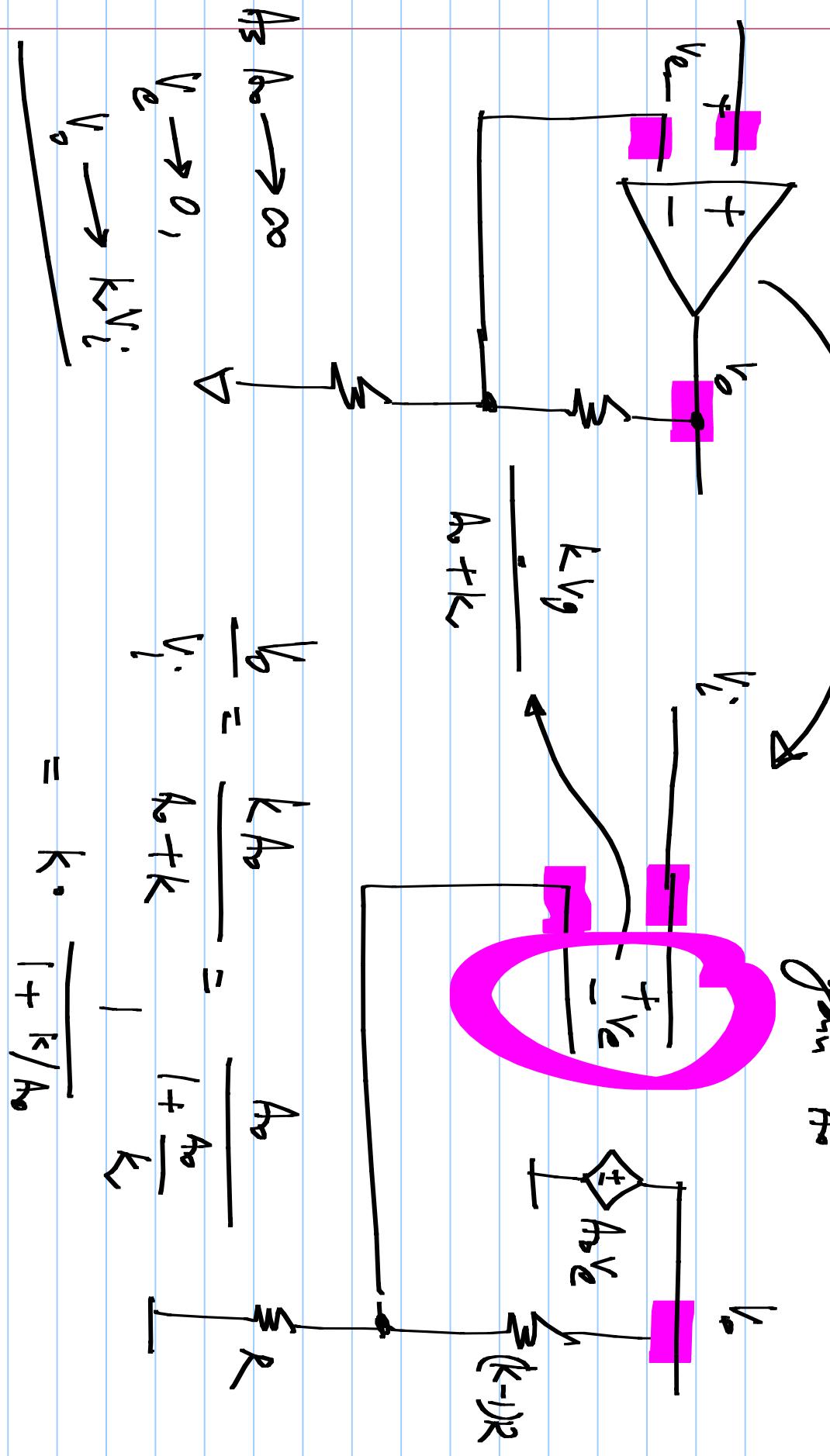


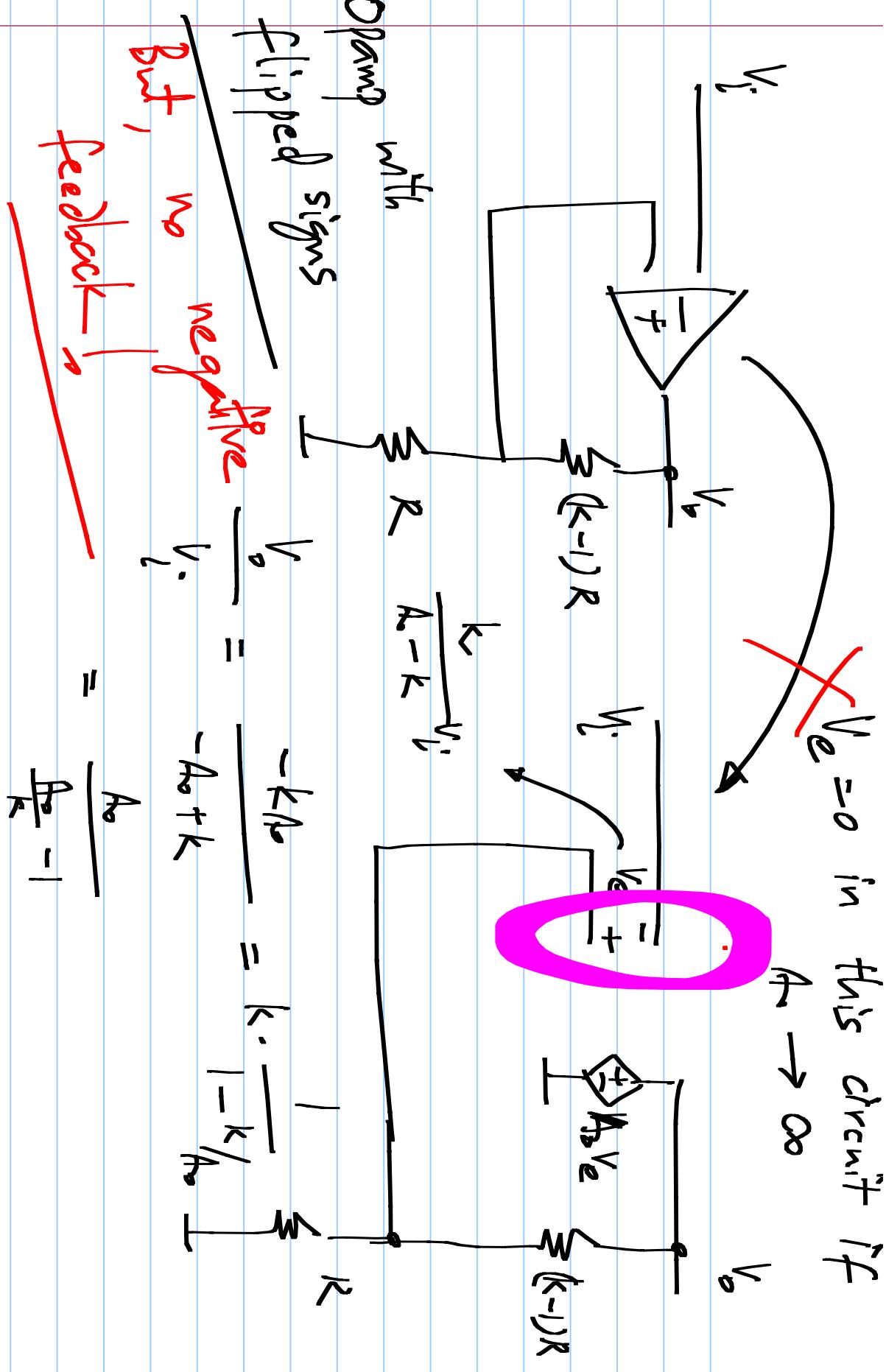

Testing for negative feedback

* Set inputs to the circuit

to zero

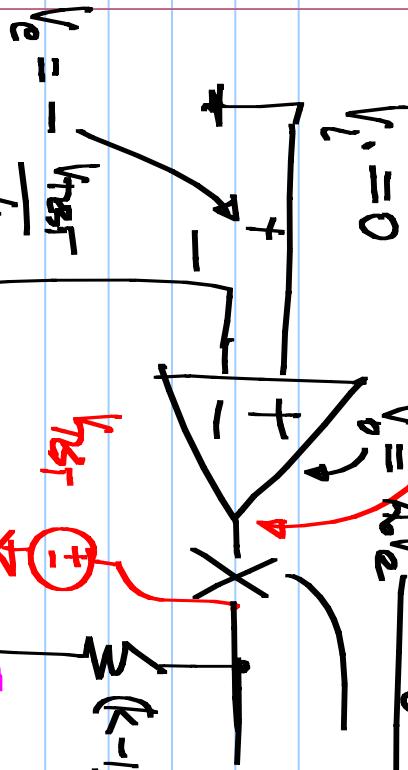

$\leq (k-1)R$
* Break the loop at the
output of the opamp

$$V_e = -\frac{V_{test}}{k}$$

$$V_{return} = -\frac{A_{v'e}}{k} V_{test}$$