
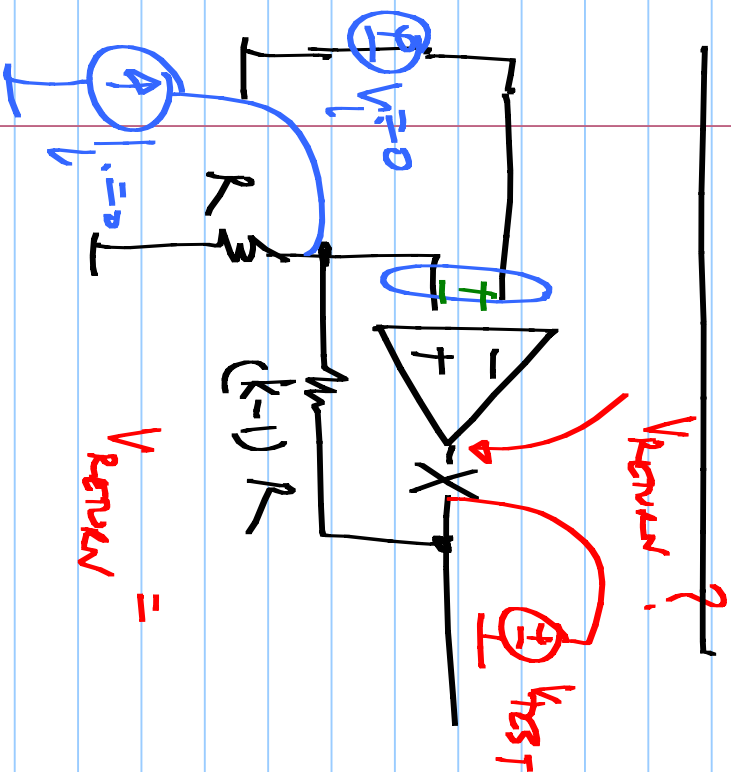


EC 1010: Lecture 22

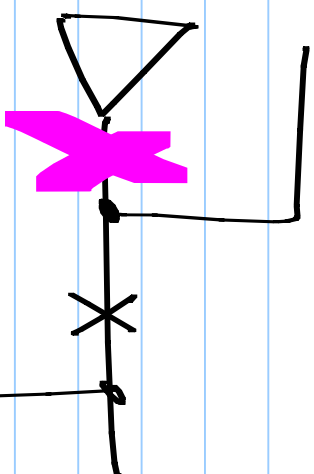


$V_{out} =$

$\frac{A_o}{k} > 0$
 $(k) \cdot V_{out}$



opamp is in the feedback



If this factor < 0

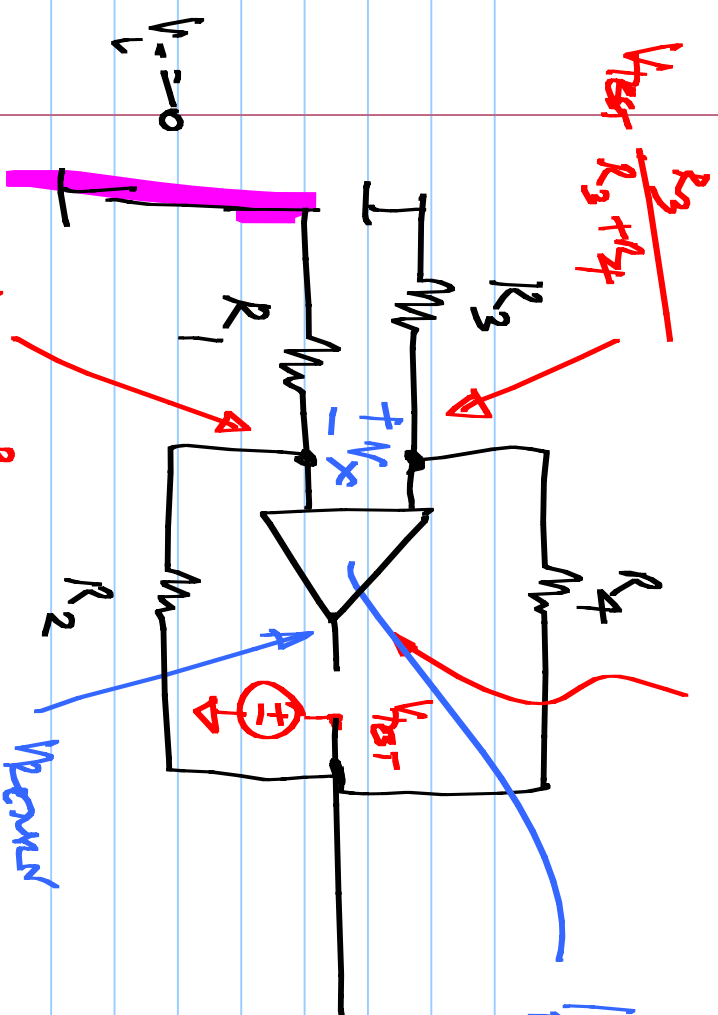

$$V_{test} \frac{R_3}{R_3 + R_4}$$

$$V_{test} \cdot \frac{R_1}{R_1 + R_2}$$
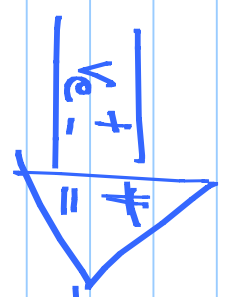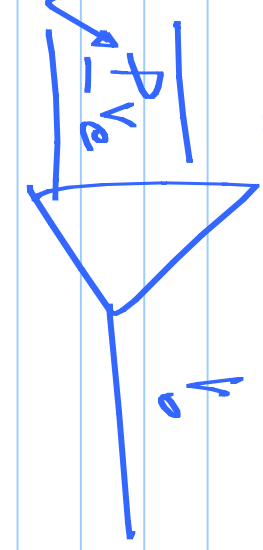
$$\left(\frac{R_3}{R_3 + R_4} > \frac{R_1}{R_2} \right) \Rightarrow -A_o \left(\frac{R_3}{R_3 + R_4} - \frac{R_1}{R_2} \right)$$





$$V_{test} \rightarrow V_{in} \rightarrow V_{out} = \alpha \cdot V_{test}$$


$$V_{test} = 0: V_{out} = \beta V_{in} + \alpha V_{test}$$
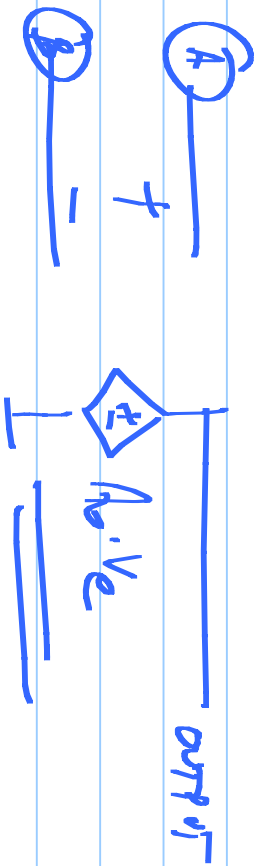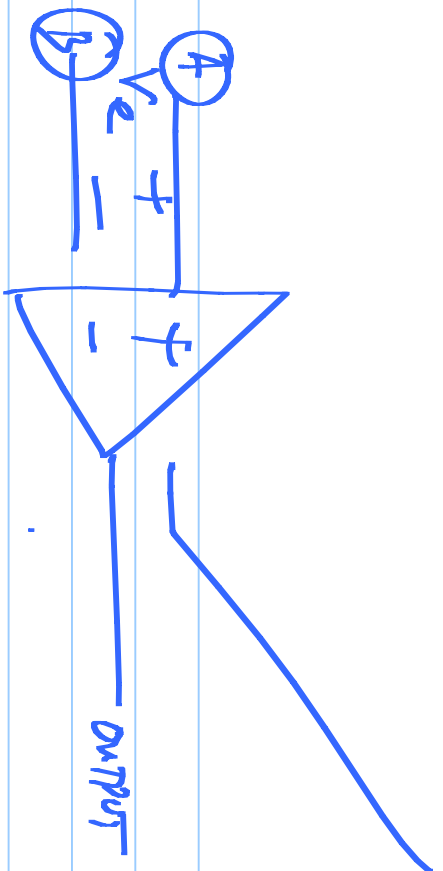
$$V_A > V_B \text{ if } \frac{R_3}{R_4} > \frac{R_1}{R_2}$$






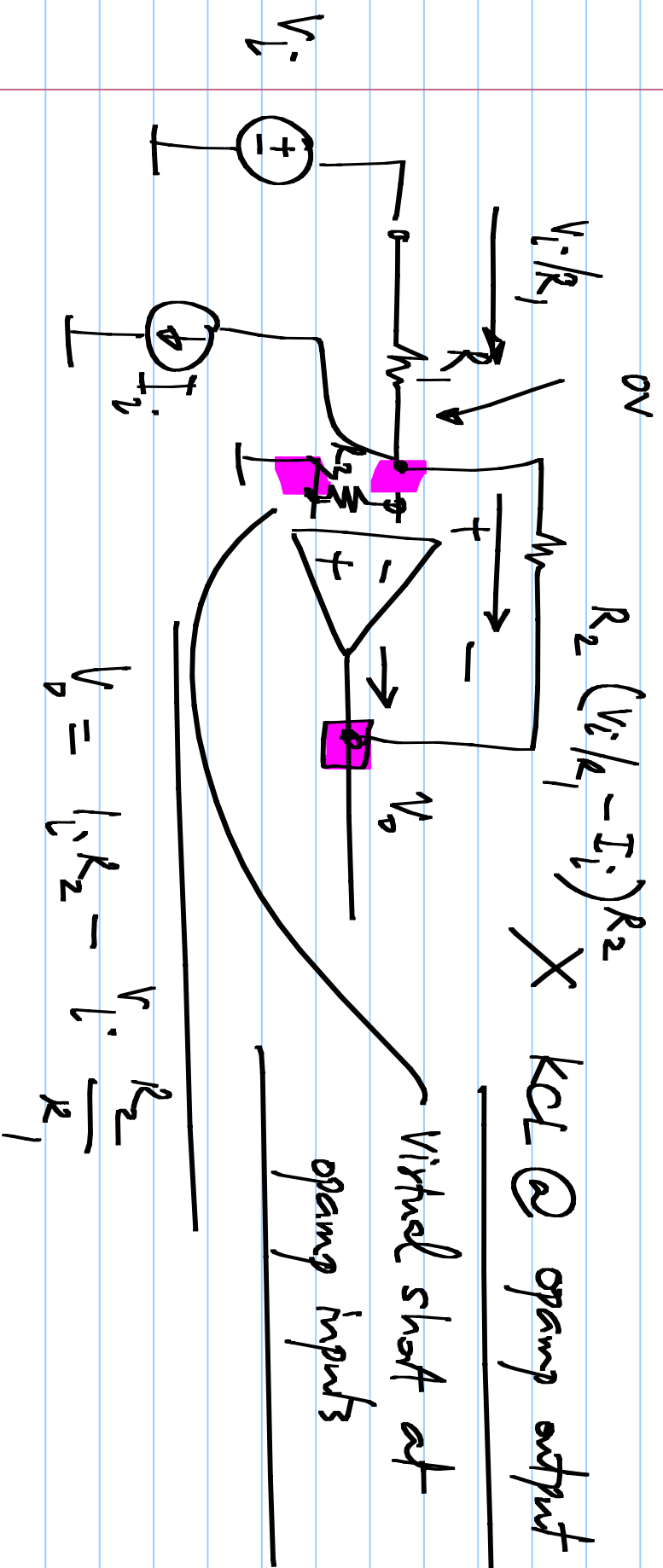Ideal
Analysis of circuits with opamps in negative feedback


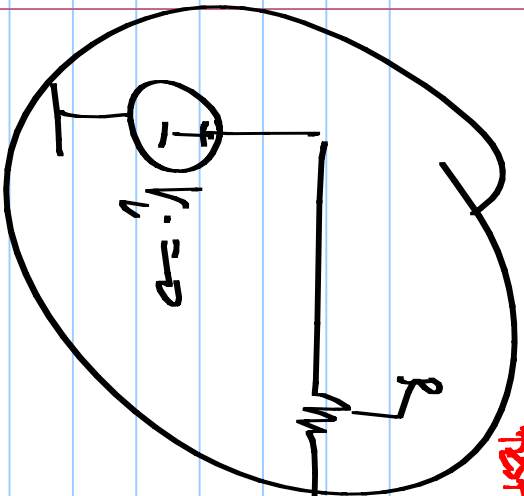
$$V_o = I_i R_2 - V_i \cdot \frac{R_2}{R_1}$$




$$I_1 = \frac{V_1}{R_1 + R_2}$$



$$V_{res} = \frac{I_1 \cdot R_2}{R_1 + R_2}$$



$$I_1 = \frac{V_1}{R_1 + R_2}$$

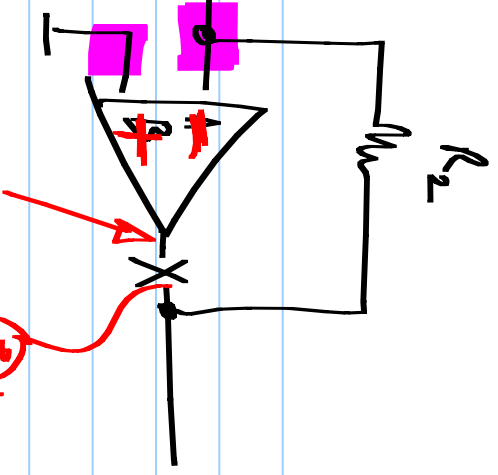


$$I_1 = \frac{V_{res}}{R_1 + R_2}$$

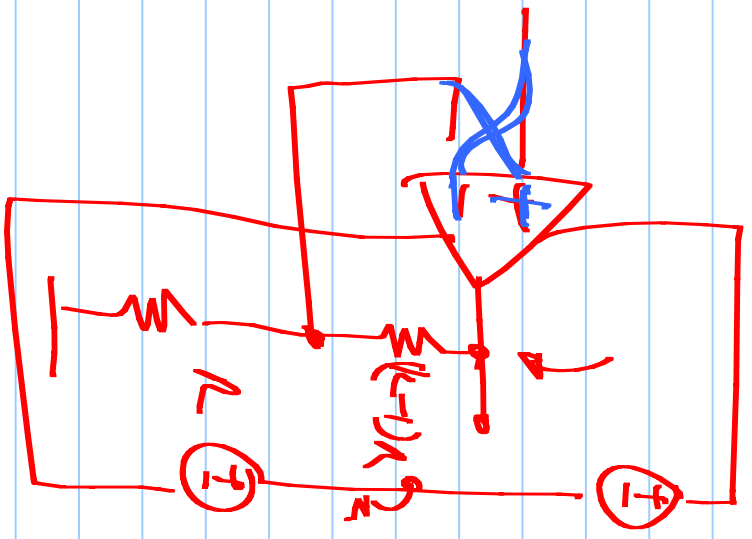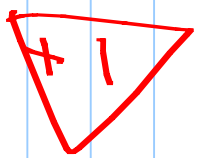


$$I_1 = \frac{V_1}{R_1 + R_2}$$

CCVS : using an opamp

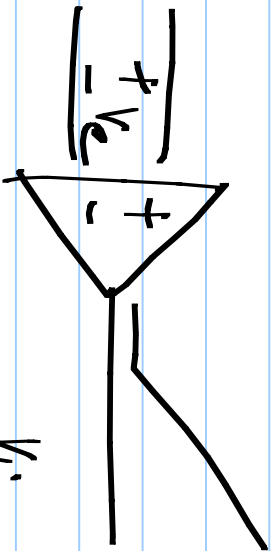

CCVS: $V_o = kV_i$

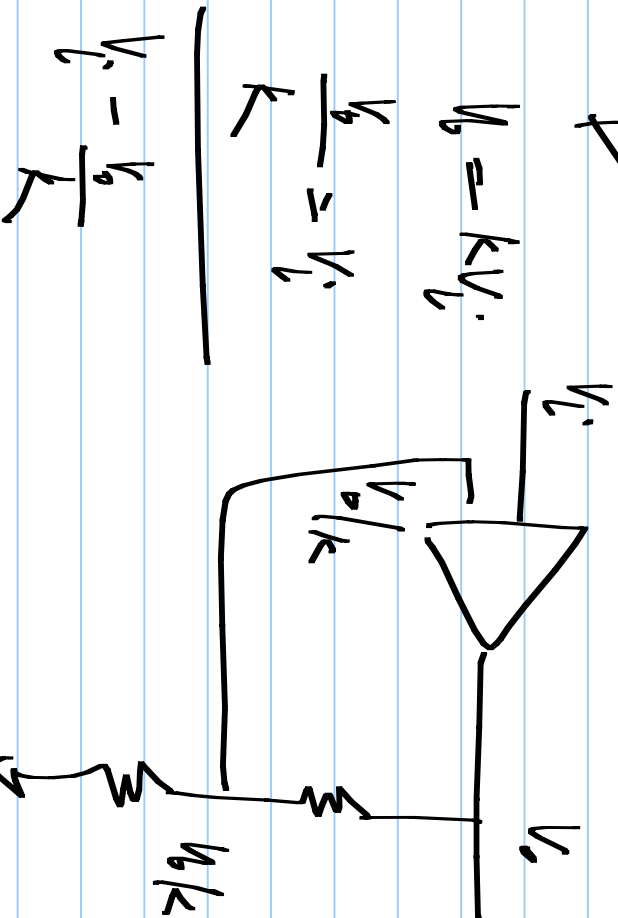

$$\frac{V_o}{k} = V_i$$

$$V_o = k V_i$$

$$V_o = I_i \cdot R_m$$

$$V_o - I_i \cdot R_m = 0$$

