
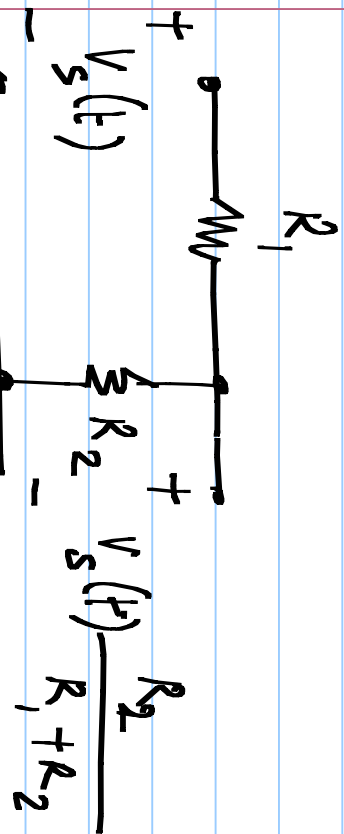


EC 1010 : Lecture 23

direct current (dc)

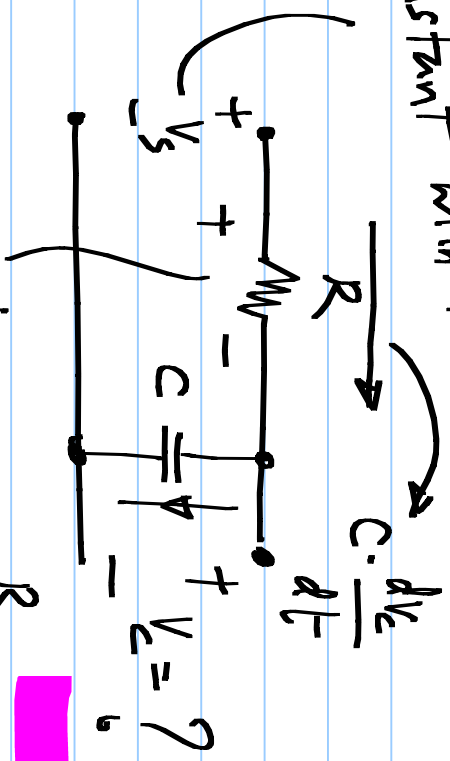


constant with time



$$RC \cdot \frac{dV_c}{dt}$$

$$V_s = 0$$

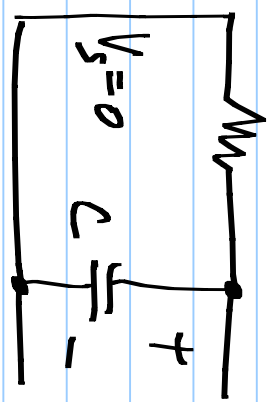

$$RC \cdot \frac{dV_c}{dt} + V_c = V_s$$


$$RC \frac{dV_c}{dt} + V_c = 0$$

First order diff. equation

linear

$$RC \cdot \frac{dV_c}{dt} + V_c = V_s$$

$$V_s = 0$$

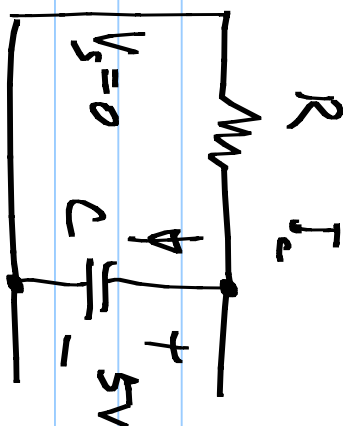


$$RC \frac{dV_c}{dt} + V_c = 0$$

homogeneous eq.

$$\exp(\alpha x)$$

$$\frac{dy}{dx} = \alpha y$$
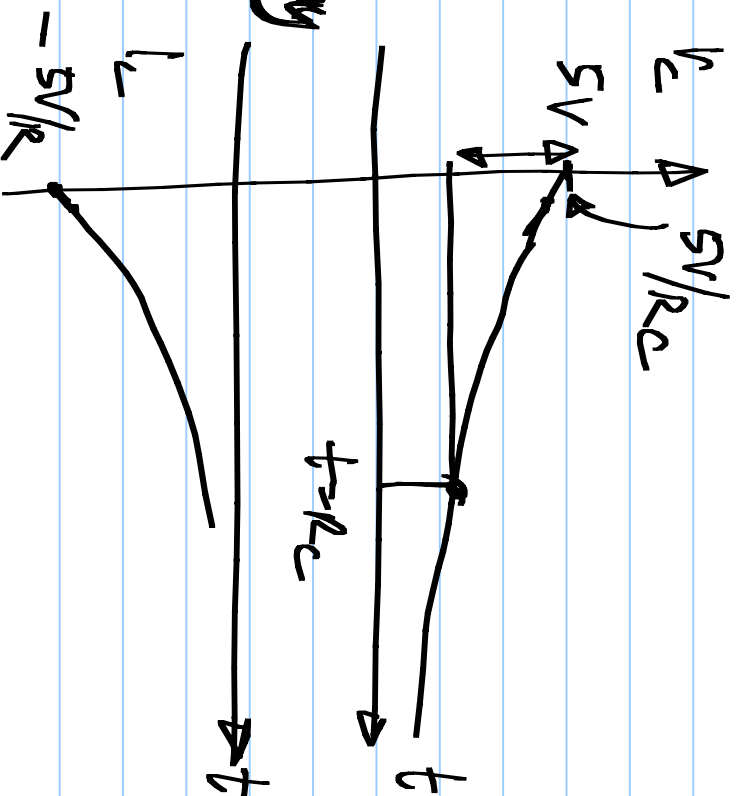
$$\frac{dV_c}{dt} = -\left(\frac{1}{RC}\right) \cdot V_c$$




$$[A] \begin{bmatrix} x_0 \\ y_0 \end{bmatrix} = \begin{bmatrix} x_1 \\ y_1 \end{bmatrix}$$


A green arrow points from the 2×2 matrix $[A]$ to the 2×1 vector $\begin{bmatrix} x_0 \\ y_0 \end{bmatrix}$.

$$\propto \begin{bmatrix} x_0 \\ y_0 \end{bmatrix}$$

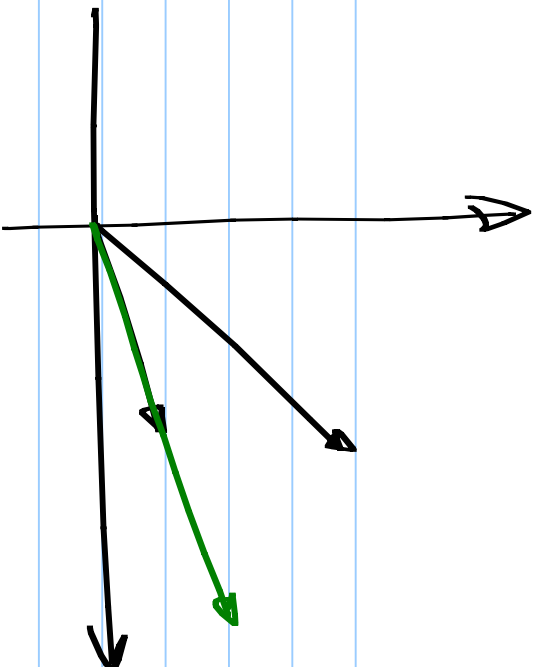The vector $\begin{bmatrix} x_0 \\ y_0 \end{bmatrix}$ is underlined in green.


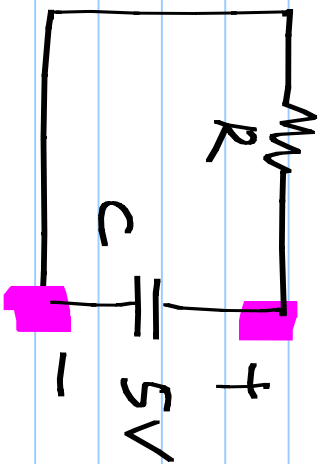
$$\frac{dV_C}{dt} = -\frac{1}{RC} \cdot V_C$$



$$\frac{dV_C}{dt} = -\frac{V_0}{RC} \exp\left(-\frac{t}{RC}\right)$$


$$V_C = V_0 \exp\left(-\frac{t}{RC}\right)$$

$V_0 = 5V$

$V_C(t=0)$

?

...

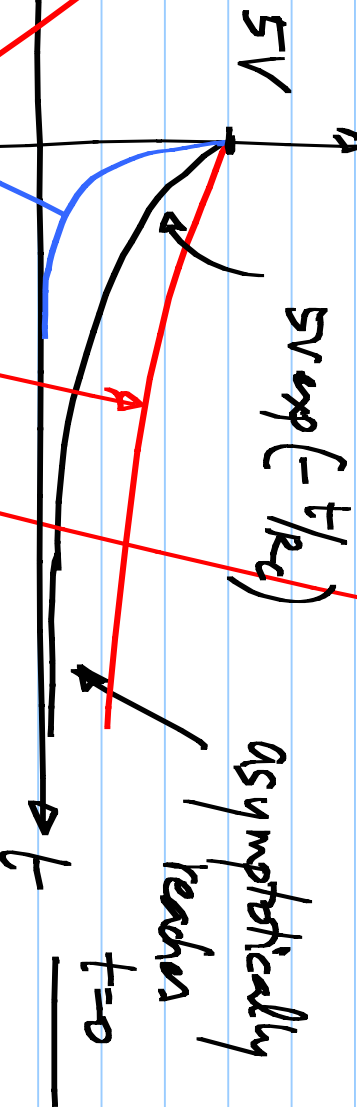


Short time constant t

long time constant t

time constant RC
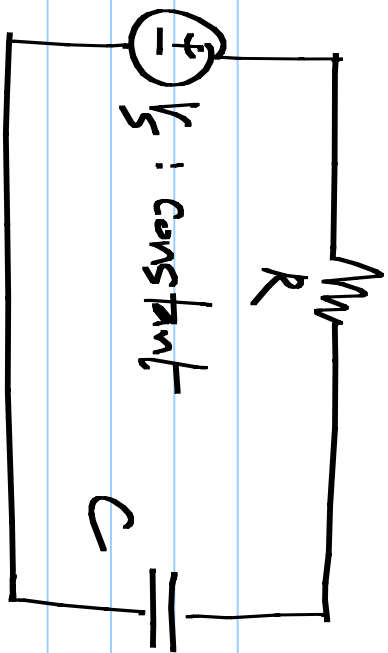
$$\text{long time constant } t \exp\left(-\frac{t}{RC}\right)$$



$$RC \frac{dV_c}{dt} + V_c = V_s$$

$$\frac{dV_c}{dt} + \frac{V_c}{RC} = \frac{V_s}{RC}$$


$$RC \frac{dV_c}{dt} + (V_c - V_s) = 0$$

$$RC \frac{dV_c}{dt} + V_c = 0$$

$$V_c = V_{c10} \cdot \exp\left(-\frac{t}{RC}\right)$$

$$V_c = V_c - V_s \quad V_c = V_s + V_{c10} \exp\left(-\frac{t}{RC}\right)$$

$$\frac{dV_c}{dt} = \frac{dV_c}{dt}$$

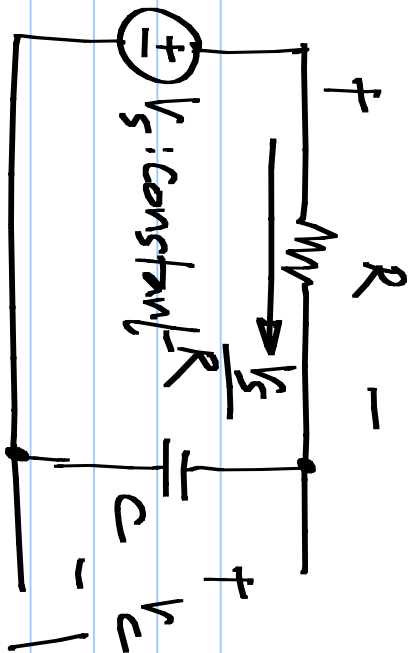

$$RC \frac{dV_c}{dt} + V_c = V_s$$


$$V_c(t) = V_s + V_{c10} \cdot \exp\left(-\frac{t}{RC}\right)$$


$$V_c(t) = V_s + (V_{c10} - V_s) \exp\left(-\frac{t}{RC}\right) \quad V_c(0) = V_s + V_{c10}$$

$$V_c(0) = 0 : \quad V_{c10} = V_c(0) - V_s$$

$$V_c(t) = V_s - V_s \exp\left(-\frac{t}{RC}\right)$$
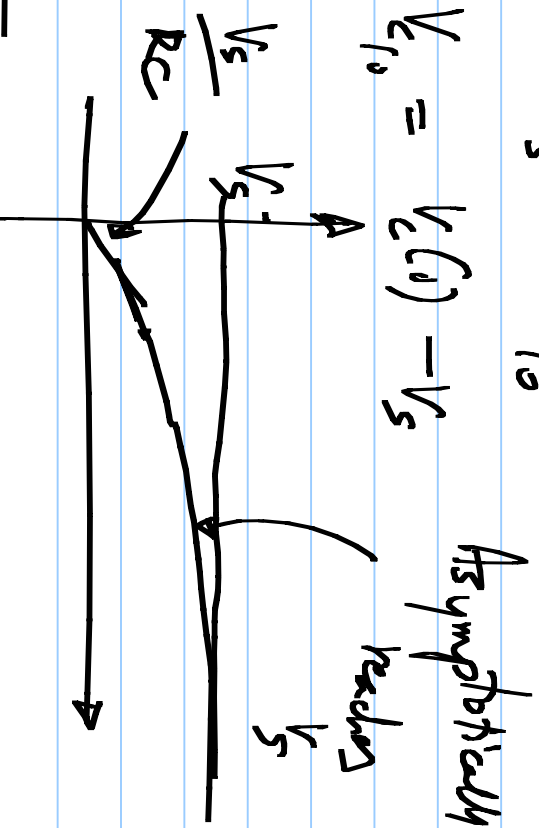
$$= V_s \left(1 - \exp\left(-\frac{t}{RC}\right)\right)$$




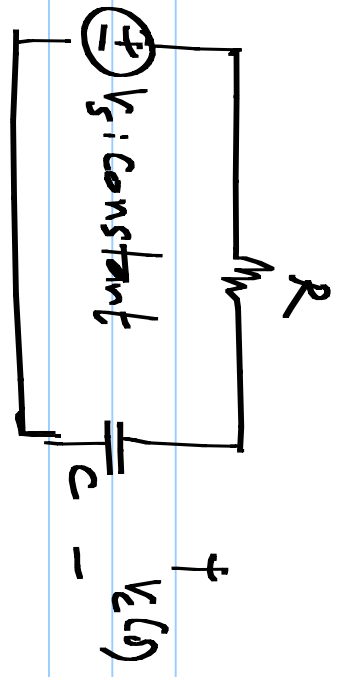

$$V_s \left(1 - \frac{1}{e}\right) \approx 0.63$$

$$V_C(t) = V_s + (V_C(0) - V_s) \exp\left(-\frac{t}{R_c}\right)$$

t = R_c ?

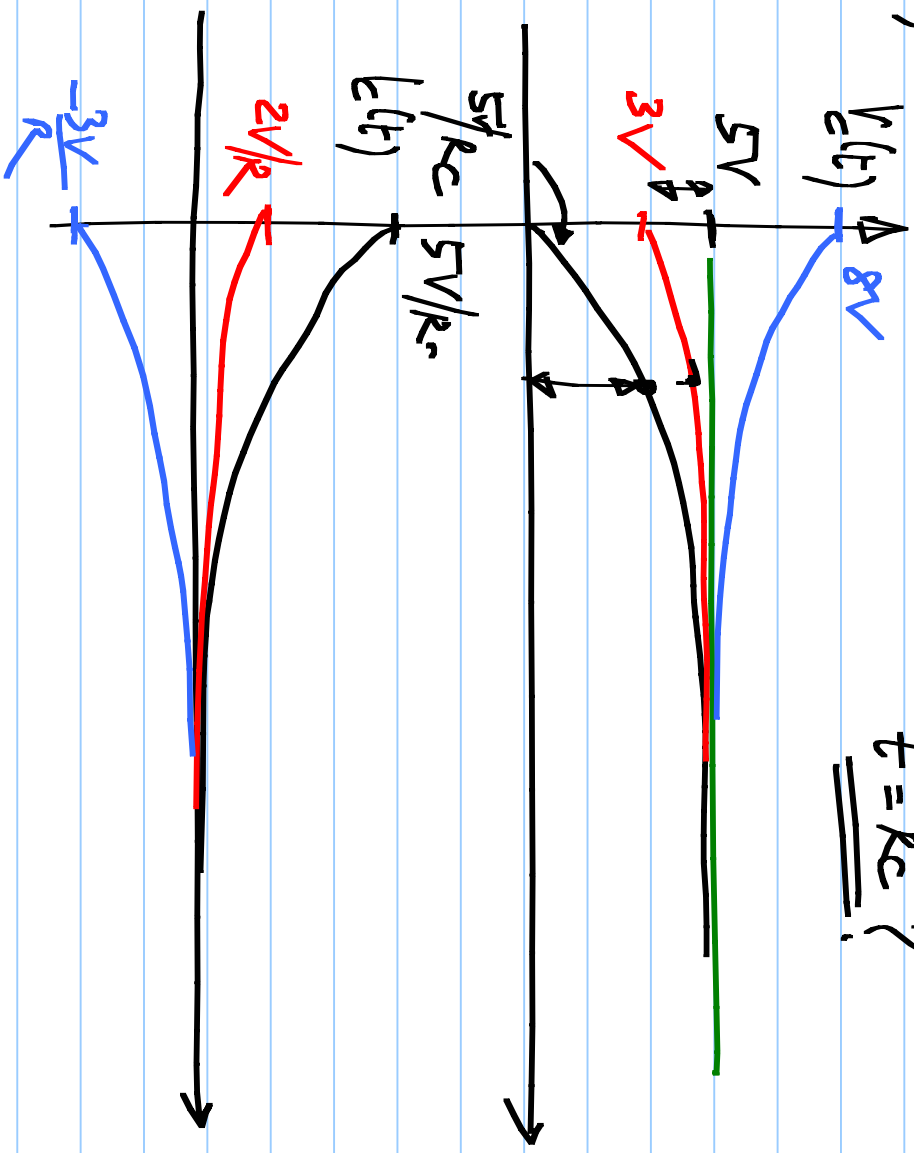

$$RC \frac{dV_c}{dt} + V_c = V_s$$

$$: \quad V_c(t) =$$

$$V_s$$

+

$$(V_c(0) - V_s) \exp\left(-\frac{t}{RC}\right)$$

Steady state response

+ Transient response

Forced response + Natural response

Particular solution + Solution to homogeneous equation

$$RC \frac{dV_c}{dt} + V_c = 0$$

$$V_c(t) = V_c(0) \exp\left(-\frac{t}{RC}\right)$$

Forcing function

$$V_s \left(1 - \exp\left(-\frac{t}{RC}\right)\right) + V_c(0) \exp\left(-\frac{t}{RC}\right)$$

Zero state response

Zero input response