

EC1010: Lecture 24

Total response: (constant input)

Procedure

$$V_C(t) = V_s + (V_s - V_c) \exp\left(-\frac{t}{R_c C}\right)$$


Steady-state Transient

Forced


Natural

Particular
solution

Homogeneous
solution

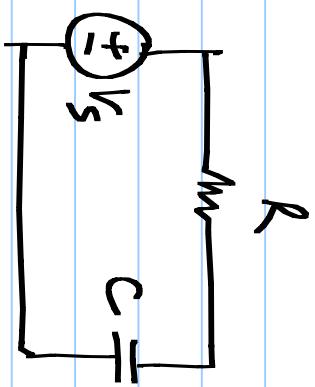

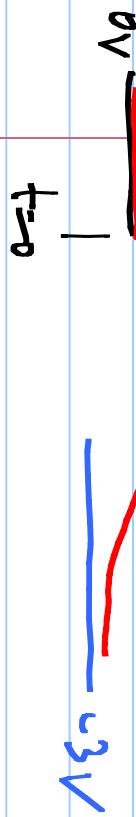
$$= V_s \left(1 - \exp\left(-\frac{t}{R_c C}\right)\right) + V_c \exp\left(-\frac{t}{R_c C}\right)$$




Zero-state response

Zero input response

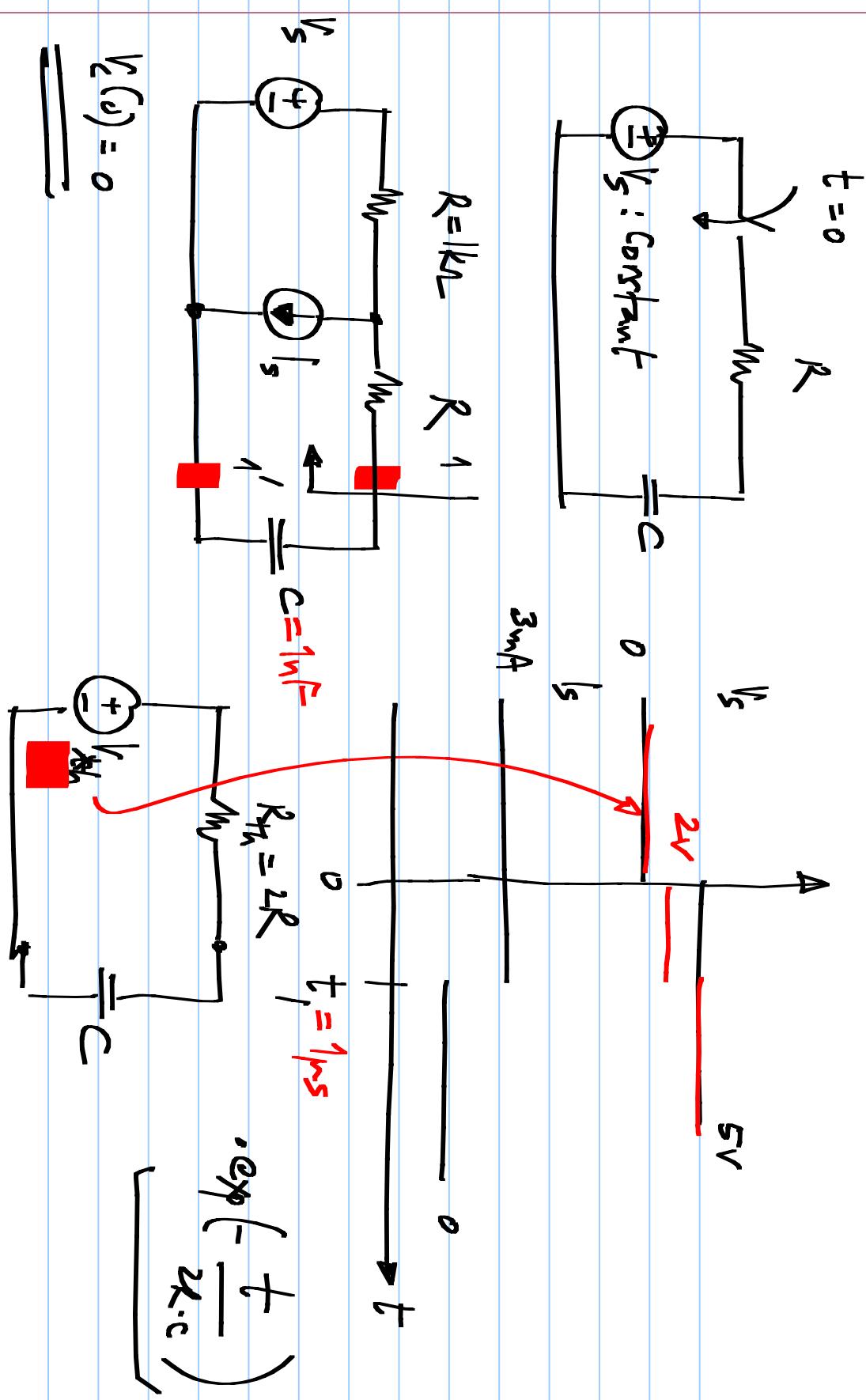

$$R_K \approx 2k\Omega$$
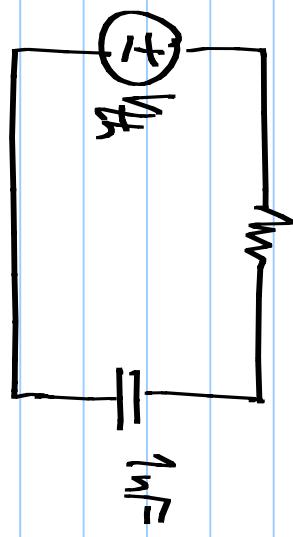
$$\frac{\text{final value}}{\text{initial - final value}} + \left(V_c(0) - \frac{V_A}{R_K} \right) e^{-t/R_K C}$$




$$\#1: \quad 2V + (-2V) e^{-t/2\mu s}$$


$$\textcircled{C} \quad t = 1\mu s \quad 2V - 2V e^{-t/2\mu s}$$

$$= 0.7869 V$$

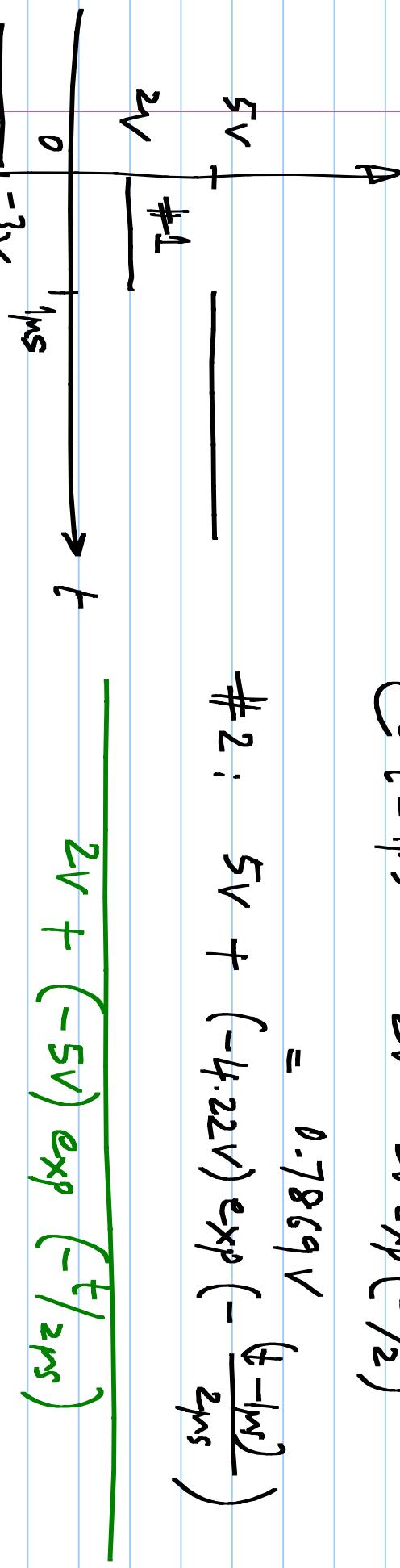
$$\#2: \quad 5V + (-4.22V) e^{-\frac{(t-1\mu s)}{2\mu s}}$$



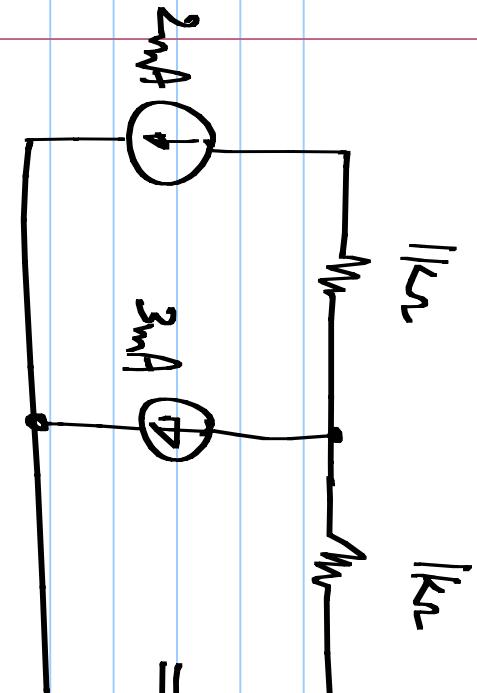
$$2V - 5V e^{-\frac{t}{2\mu s}} = -1.003 V$$



$\frac{1}{1nF}$?

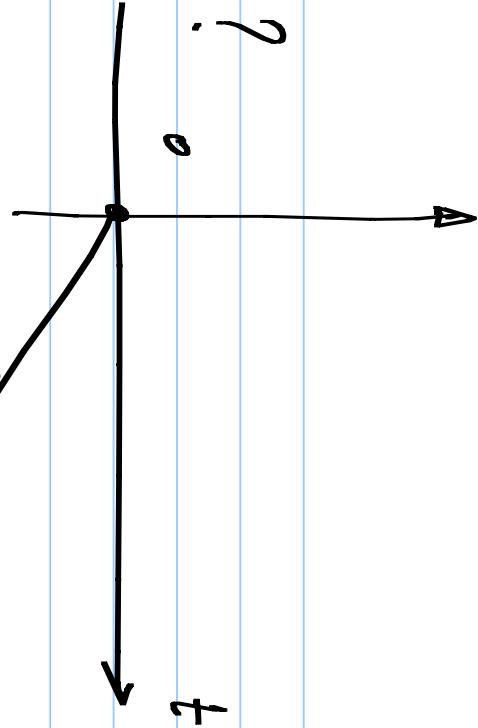

$$\frac{5mA}{1nF} = \frac{5V}{1s}$$

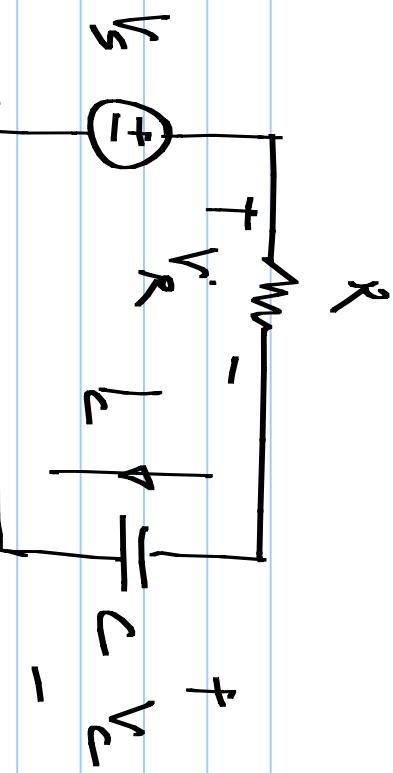

$$RC \frac{dV_c}{dt} + V_c = V_s$$

$$RC \frac{dI_c}{dt} + I_c = C \frac{dV_s}{dt}$$

$$RC \frac{dV_c}{dt} + V_c = RC \frac{dV_s}{dt}$$

V_R

$$V_c = (V_s - I_c R) e^{-t/RC}$$


Piecewise constant input:

$$V_s : V_s + (I_c(0) - I_c(\infty)) e^{-t/RC}$$

$$I_c = (V_s - V_c) e^{-t/RC}$$

$$I_c : I_c(\infty) + (I_c(0) - I_c(\infty)) e^{-t/RC}$$

Natural response

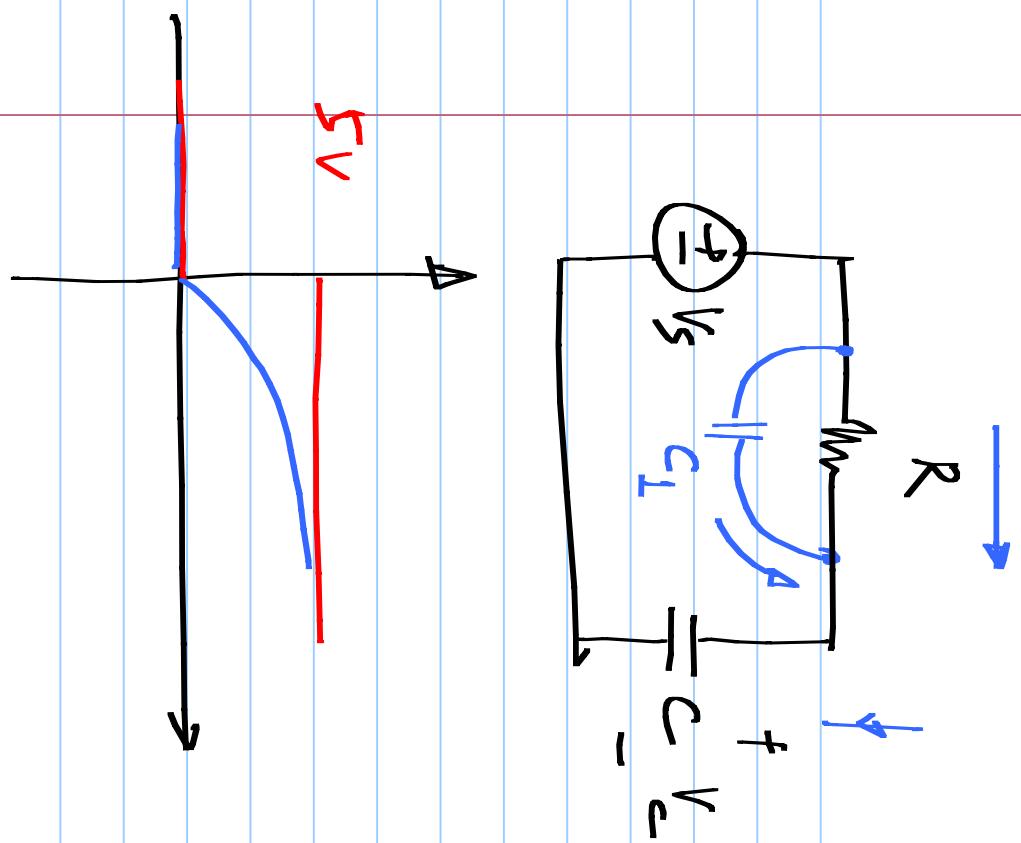

$$RC \frac{d\nu_c}{dt} + \nu_c = \nu_s$$

$$C \cdot \frac{d\nu_c}{dt} = \frac{\nu_s - \nu_c}{R} + C_1 \frac{1}{dt} (\nu_s - \nu_c)$$

$$R(C_1 + C) \frac{d\nu_c}{dt} + \nu_c = \nu_s + RC_1 \frac{d\nu_s}{dt}$$