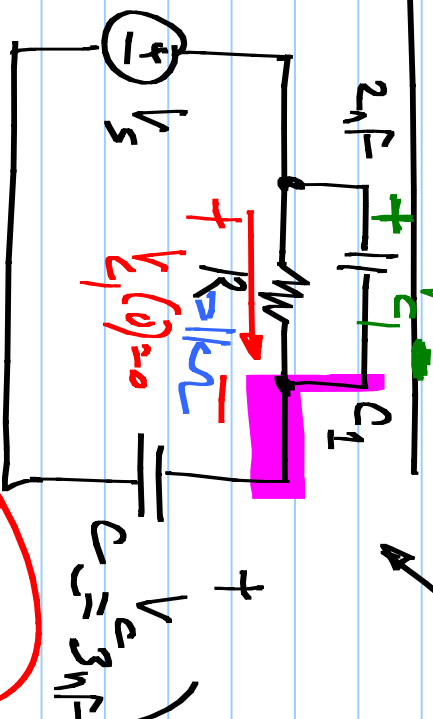


EC 1010: Lecture 25




1st order circuit =

1st order diff. eqn.


$$R(C + C_1) \cdot \frac{dV_c}{dt} + V_c = V_s + RC_1 \cdot \frac{dV_s}{dt}$$

$$3V \cdot \exp(-t/5\mu s)$$

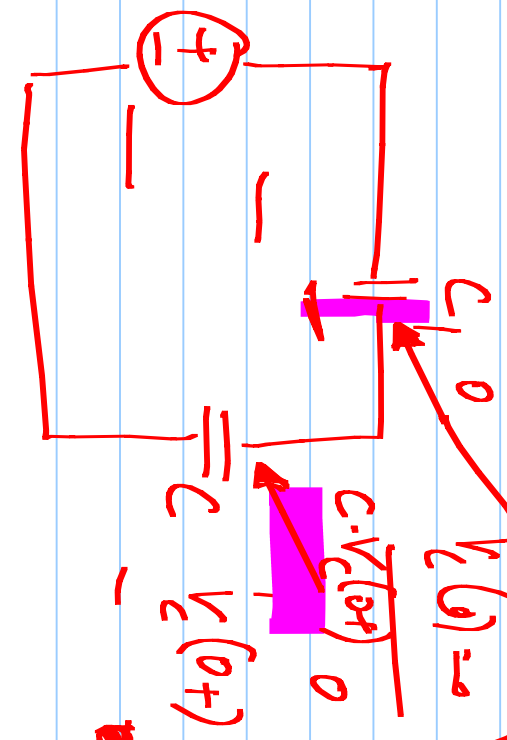


$$V_c(t) = V_s \cdot \frac{C_1}{C_1 + C_2}$$

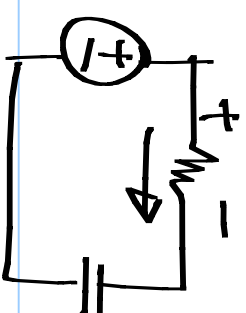Q: Instant of the step
Step response of a first order circuit-



Step input

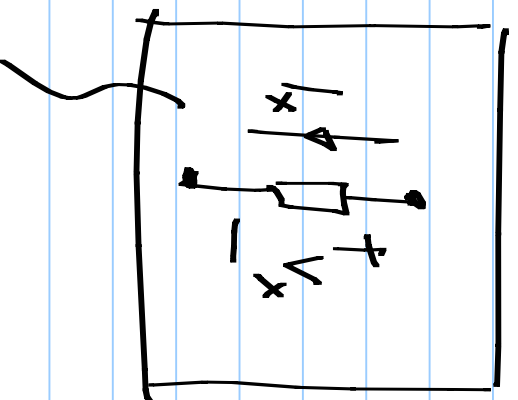


First order circuit-

$$V_x =$$

$$V_{x,final} + (V_x(0+) - V_{x,final}) \cdot \exp\left(-\frac{t}{\tau}\right) \\ V_x(\infty) + (V_x(0+) - V_x(\infty)) \cdot \exp\left(-\frac{t}{\tau}\right)$$

Initial condition given: $V_c(0-)$

Input source known: $V_s(0-)$

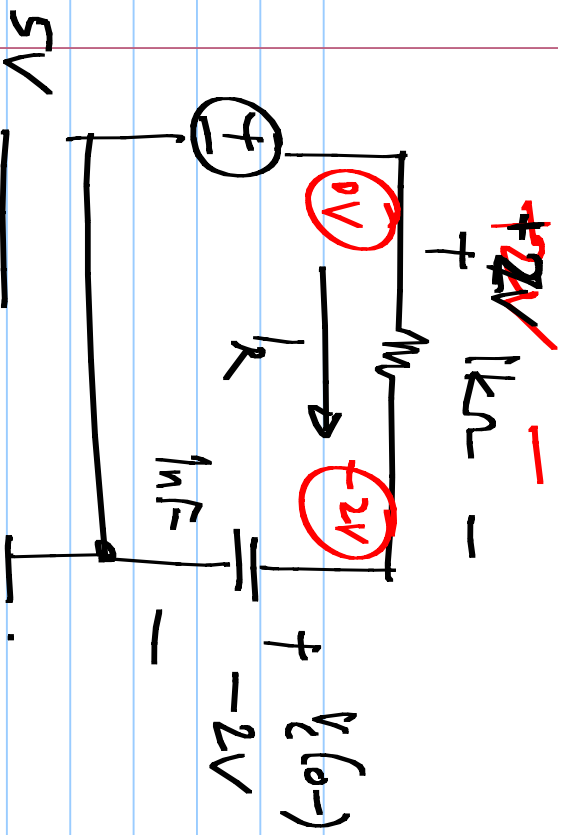


$$i_R(t) = 7mA \cdot \exp(-t/1\mu s) \quad (t > 0)$$

$$i_R(0^-) = +2mA$$

$$i_R(0^+) = 7mA$$

$$i_R(\infty) = 0$$

$$\tau = 1\mu s$$

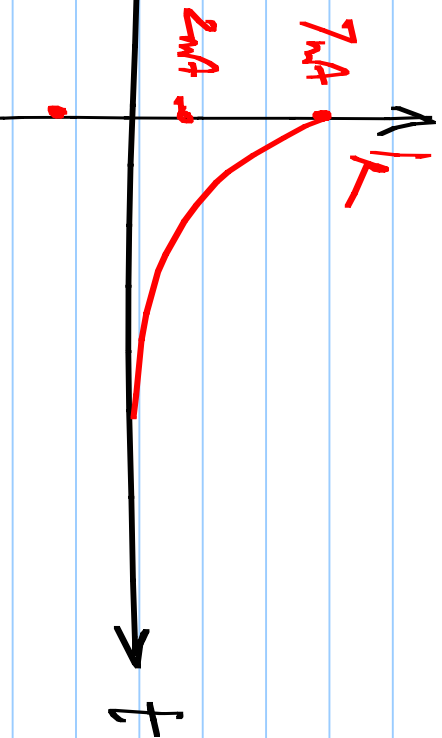

Step response of a first-order circuit-

Final

* Determine the time constant

- set source = 0

$$- C_{\text{eff}} \cdot R_{\text{th}} = \tau$$

* Determine the values at $t = 0^-$

- From initial conditions & ckt. analysis

* Determine discontinuities in cap. voltages at $t = 0$

- Voltage source - capacitor loops


- open circuit all resistors & determine cap. voltages

* Determine values at $t = 0^+$


* Determine values

(open circuiting all capacitors)

$$+ L \frac{di}{dt} = V_s - iR$$

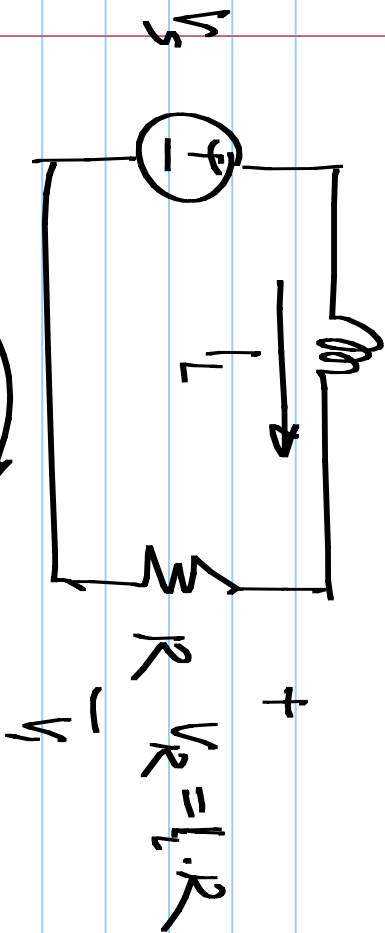

$$V_s - iR = L \cdot \frac{di}{dt}$$

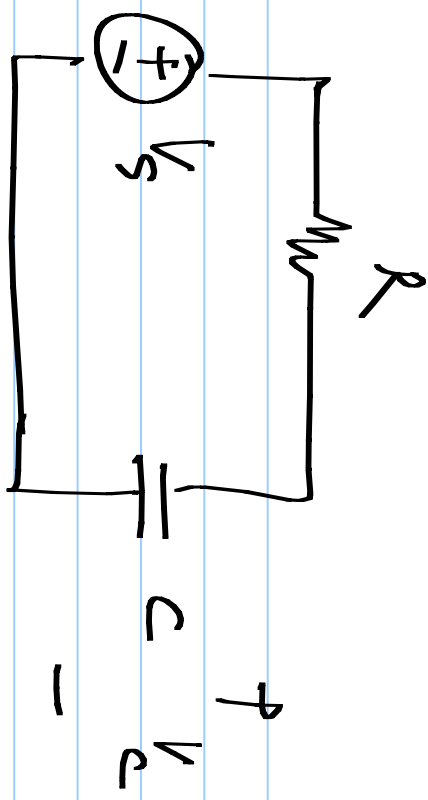

$$R \frac{dV_c}{dt} + V_c = V_s$$

$$L \frac{di}{dt} + iR = \frac{V_s}{R}$$

$$L \frac{dV_R}{dt} + V_R = V_s$$