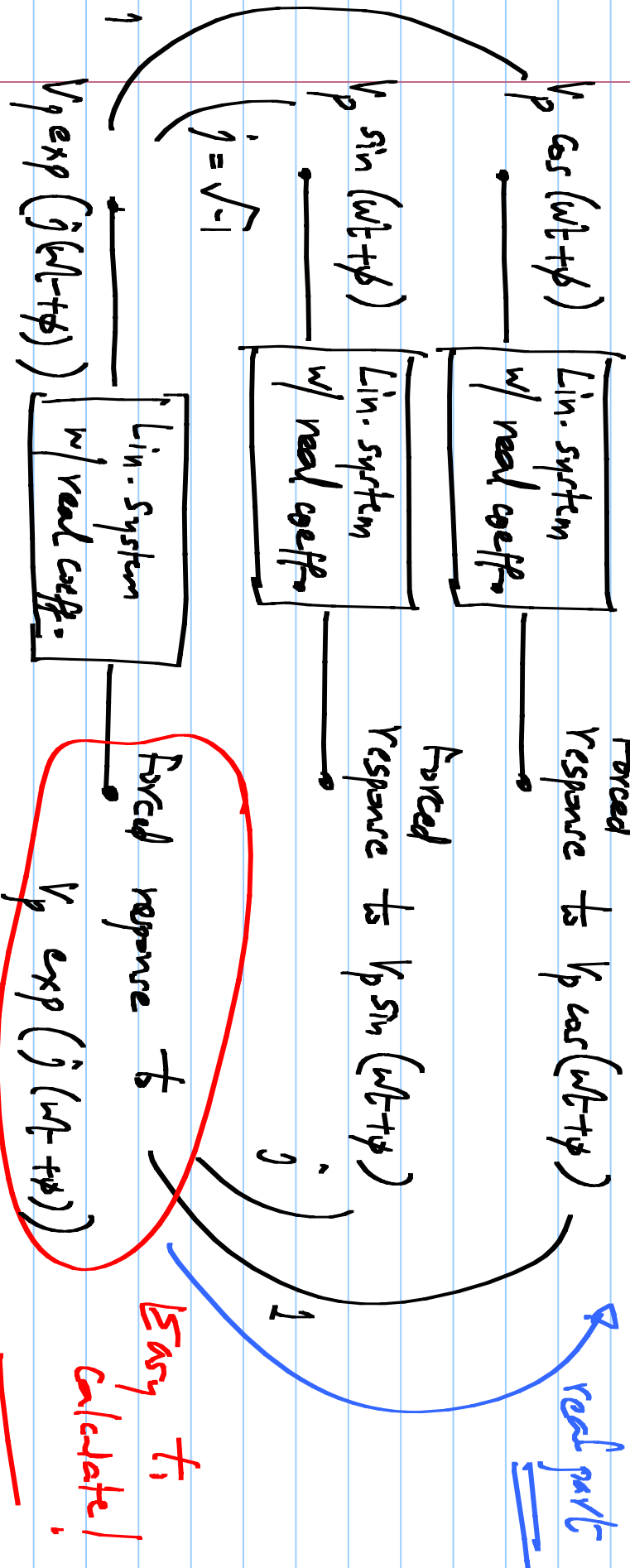



EC1010: Lecture 27

Forced response to $V_p \cos(\omega t + \phi)$



Sinusoidal steady state response

Forced resp.

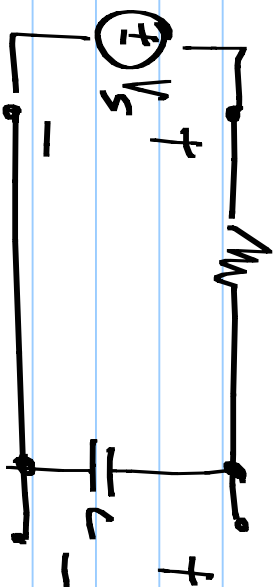

$$\frac{V_p \exp(st)}{1 + sCR}$$


$$V_p \exp(j(\omega t + \phi))$$

$$x + jy = A \exp(j\theta) = V_p \exp(j\phi) \cdot \exp(j\omega t) = \frac{V_p \exp(j\phi)}{1 + j\omega CR} \exp(j\omega t)$$






$$\frac{1}{1 + j\omega CR} = \frac{1}{\sqrt{1 + (\omega CR)^2}} \cdot \exp(j \tan^{-1}(\omega CR)) = \frac{V_p \exp(j(\omega t + \phi))}{(1 + j\omega CR)}$$

$$\frac{V_p}{\sqrt{1 + (\omega CR)^2}} \cdot \cos(\omega t + \phi - \tan^{-1}(\omega CR)) \quad V_p \cos(\omega t + \phi) \quad \text{Re} \left[\right]$$

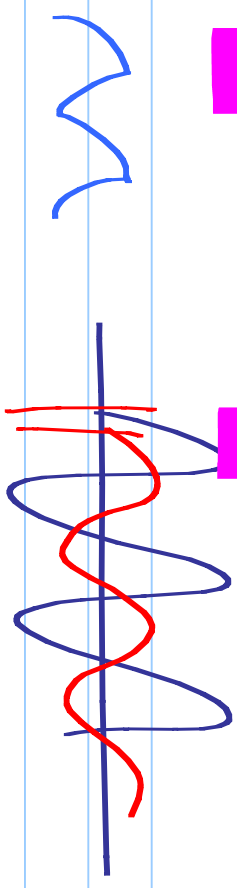
$$V(\infty) + (V(0) - V(\infty)) \exp(-t/\tau_c)$$




exp(st)

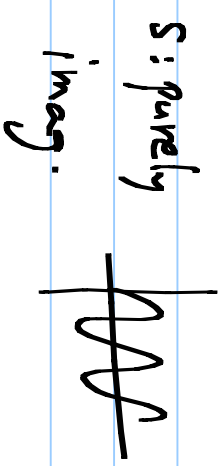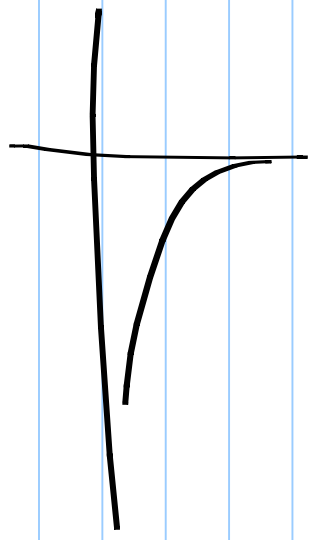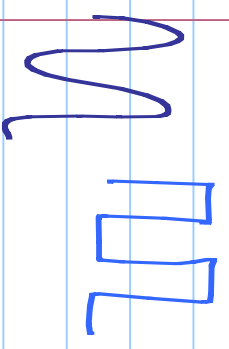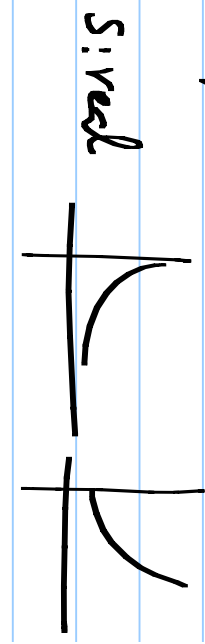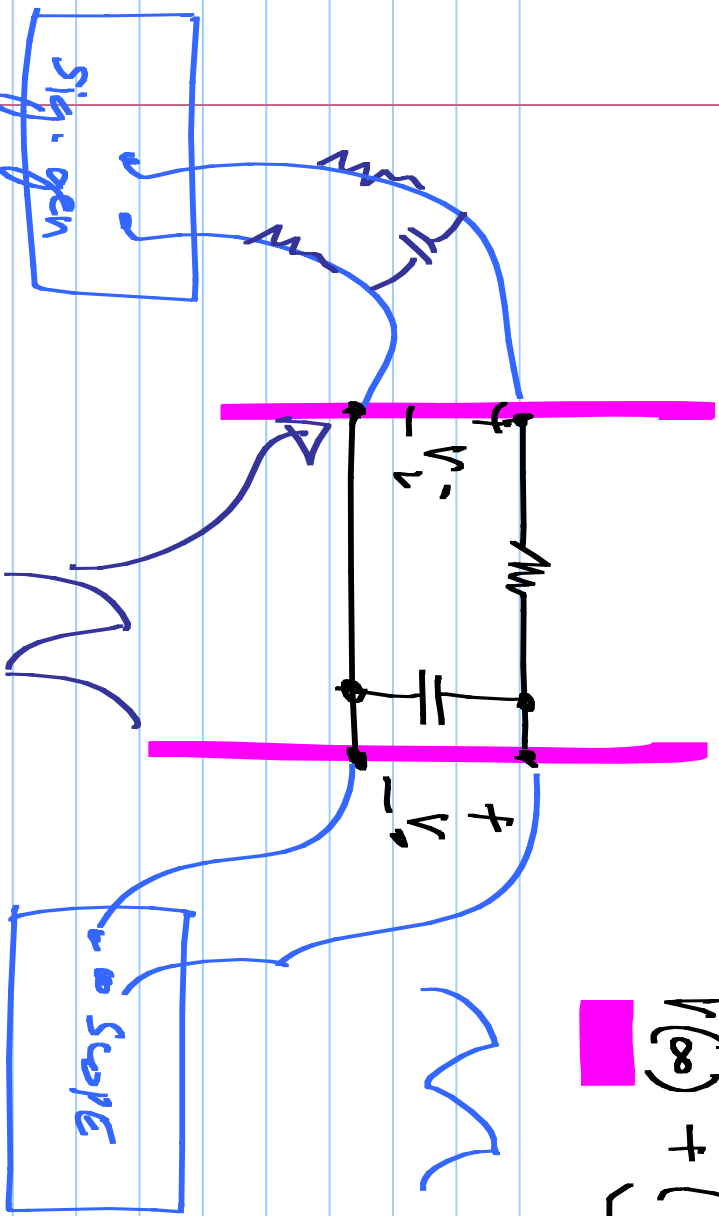

s: complex

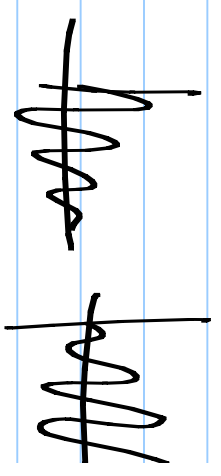

Second order circuits: e.g: RLC

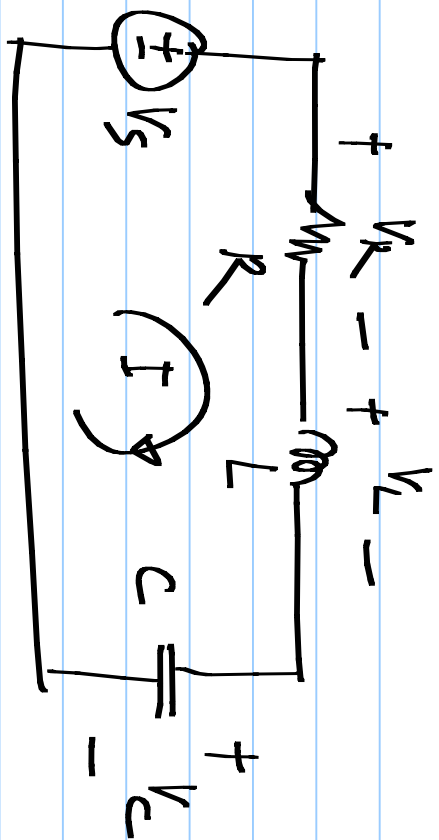

Diff. equation in terms of V_C

$$LC \frac{d^2 V_C}{dt^2} + RC \frac{dV_C}{dt} + V_C = V_S$$

Natural response: $V_S = 0$

$$LC \frac{d^2 V_C}{dt^2} + RC \frac{dV_C}{dt} + V_C = 0$$

$$V_C = V_0 \exp(qt) \quad (LC \cdot p^2 + RC \cdot p + 1) V_0 \exp(qt) = 0$$

Characteristic eq. of the D.E

$$RC \frac{dV_c}{dt} + V_c = 0$$

$$p = -\frac{1}{RC}$$

First order
circuit

$$V_c = V_0 \exp(pt)$$

$$(RC \cdot p + 1) \cdot V_0 \exp(pt) = 0$$

$$\underbrace{(LC \cdot p^2 + RC \cdot p + 1)}_{\text{Characteristic eq. of the D.E.}} V_0 \exp(pt) = 0$$

Second order
circuit

$$p = \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Two possible solutions: p_1, p_2 $\exp(p_1 t)$ & $\exp(p_2 t)$ are possible solutions.

In general: Solution (Natural response) = $A_1 \exp(p_1 t) + A_2 \exp(p_2 t)$

$$LC p^2 + RC \cdot p + 1 = 0$$

$$p_{1,2} = \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$p_{1,2}$: real & distinct:

$$(RC)^2 > 4LC \quad R > \frac{4L}{C}$$

$$A_1 \exp(p_1 t) + A_2 \exp(p_2 t)$$

$p_{1,2}$: real & identical

$$(A_1 + A_2 t) \exp(p_1 t)$$

$$R^2 = \frac{4L}{C}$$

Forced response to $\exp(st)$ of an RC circuit-

$$sCR + 1 = 0$$

$$\frac{(V_c(0) - \frac{V_p R}{1+sCR})}{V_c(0)}$$

$$\lim_{s \rightarrow 0} \frac{V_p \exp(st)}{1+sCR} + V_0 \exp(-t/\tau_c) = V_c(t)$$

$$s = 1+sCR$$

$$\frac{V_p}{(1+sCR)} \left[\exp(st) - \exp(-t/\tau_c) \right] + V_c(0) \exp(-t/\tau_c) = V_c$$

$$\frac{1}{s} \left[\exp\left(\frac{s-1}{R_C} \cdot t\right) - \exp\left(-\frac{t}{R_C}\right) \right] + V_C(0) \exp\left(-\frac{t}{R_C}\right)$$

$$\lim_{s \rightarrow 0} \frac{1}{s} \left[\exp\left(\frac{dt}{R_C}\right) - 1 \right] \exp\left(-\frac{t}{R_C}\right) + V_C(0) \exp\left(-\frac{t}{R_C}\right)$$

$$\frac{1}{s} \left[\cancel{1} + \frac{dt}{R_C} + \left(\frac{dt}{R_C}\right)^2 \cdot \frac{1}{2} + \dots - 1 \right]$$

$$V_p \cdot \frac{t}{R_C} \cdot \exp\left(-\frac{t}{R_C}\right) + V_C(0) \exp\left(-\frac{t}{R_C}\right)$$

$$(k_1 + k_2 t) \exp\left(-\frac{t}{R_C}\right)$$

$p_{1,2}$: complex conjugates of each other

$$R^2 < \frac{4L}{C}$$

$$p_{1,2} = -\frac{R}{2L} \pm j \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} = p_1 \pm j\omega_1$$

$$A_1 \exp(p_1 t) + A_2 \exp(p_2 t) \quad A_2 = A_1^*$$

$$v_c(t) = \underline{A_1 \exp(p_1 t)} + \underline{A_1^* \exp(p_2 t)}$$

$$A_1 \exp(\gamma_1 t) \exp(j\omega_1 t) + A_1^* \exp(\gamma_2 t) \exp(j\omega_2 t)$$

$$\cos(\quad) \cdot \exp(\quad)$$