

# EC 1010: Lecture 28

$$V_c = V_0 \exp(\rho t) \quad \leftarrow \text{homogeneous eq.}$$

$$LC \frac{d^2 V_c}{dt^2} + RC \frac{dV_c}{dt} + V_c = V_s$$

Natural response:  $\exp(\rho t)$

$$A_1 \exp(\rho_1 t) + A_2 \exp(\rho_2 t) \quad \checkmark$$

$$(A_1 + A_2 t) \exp(\rho t) \quad \checkmark$$


$$p_{1,2} : LC \cdot \rho^2 + RC \cdot \rho + 1 = 0$$


$$A_1 \exp(\rho_1 t) \exp(j\rho_1 t) + A_1^* \exp(\rho_1 t) \quad \checkmark$$

$$A_1 = A_0 \exp(j\phi_1) \quad \leftarrow \exp(j\rho_1 t)$$

$$2A_0 \exp(\rho_1 t) \cdot \cos(\rho_1 t + \phi_1) \quad \checkmark$$

$$p_{1,2} : \rho_r \pm j\rho_i$$

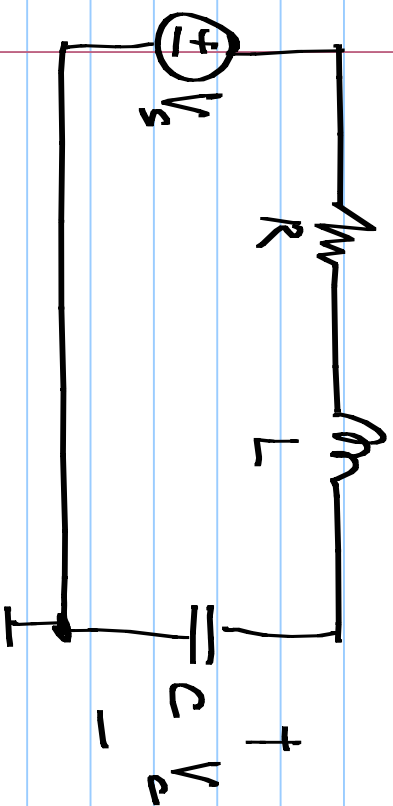

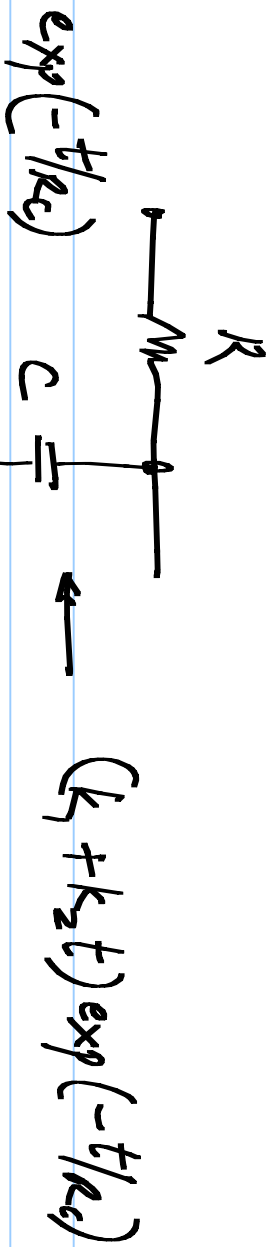

$$C) \exp(-t/RC)$$


$$\frac{(-\frac{1}{p_1} - \frac{1}{p_2}) (b_1 c_1)}{a_2} \frac{d^2 v_c}{dt^2} + a_1 \frac{dv_c}{dt} + k_c = v_s$$

$$\cancel{\left( -\frac{1}{p_1} + \frac{1}{p_2} \right)}$$

$p_{1,2}:$

$$a_2 p^2 + a_1 p + 1 = 0$$

$$\frac{b_1 c_1}{(b_1 + c_1)}$$

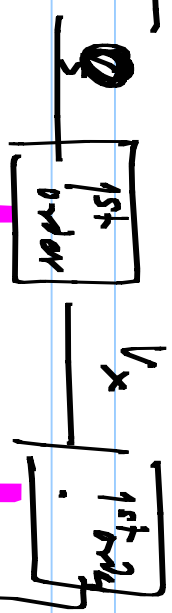

$$\exp(p_2 t)$$

$$\frac{-\frac{1}{p_1} \frac{dv_x}{dt} + v_x = v_s}{-\frac{1}{p_2} \frac{dv_c}{dt} + v_c = v_x}$$

Diff. equation:

$$\omega_n^2 = \frac{1}{LC} \quad \left| \frac{1}{\sqrt{LC}} \right.$$

$\omega_n$ : natural frequency

$\zeta$ : zeta: damping factor

$Q$ : Quality factor

$$Q: \frac{1}{2\zeta} ; \zeta = \frac{1}{2Q}$$

$$LC \cdot \frac{d^2 V_C}{dt^2} + RC \frac{dV_C}{dt} + V_C = V_S$$

$p_1, p_2$

$$\frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{V_C}{LC} = \frac{V_S}{LC}$$

$$\frac{d^2 V_C}{dt^2} + 2\zeta \omega_n \frac{dV_C}{dt} + \omega_n^2 V_C = \omega_n^2 V_S$$

zeta

$$\frac{d^2 V_C}{dt^2} + \frac{\omega_n}{Q} \frac{dV_C}{dt} + \omega_n^2 V_C = \omega_n^2 V_S$$

Characteristic Polynomial:

$$LC \cdot p^2 + RC \cdot p + 1 = 0$$

$$p_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$p^2 + 2\zeta \cdot \omega_n \cdot p + \omega_n^2 = 0$$

$$p^2 + \frac{\omega_n}{Q} \cdot p + \omega_n^2 = 0$$

$$: -\frac{\omega_n}{2Q} \pm \sqrt{\left(\frac{\omega_n}{2Q}\right)^2 - \omega_n^2}$$



$$Q: \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$\omega_n \left[ -\frac{1}{2Q} \pm \sqrt{\left(\frac{1}{2Q}\right)^2 - 1} \right]$$

$$\omega_n \left[ -\zeta \pm \sqrt{\zeta^2 - 1} \right]$$

Real & distinct	$Q < 1/2, \zeta > 1$	$A_1 \exp(p_1 t) + A_2 \exp(p_2 t)$	Overdamped
Real, repeated	$Q = 1/2, \zeta = 1$	$(A_1 + A_2 t) \exp(p_1 t)$	Critically damped
Complex conj	$Q > 1/2, \zeta < 1$	$(2A_0) \exp(p_1 t) \cos(p_1 t + \phi)$	Underdamped

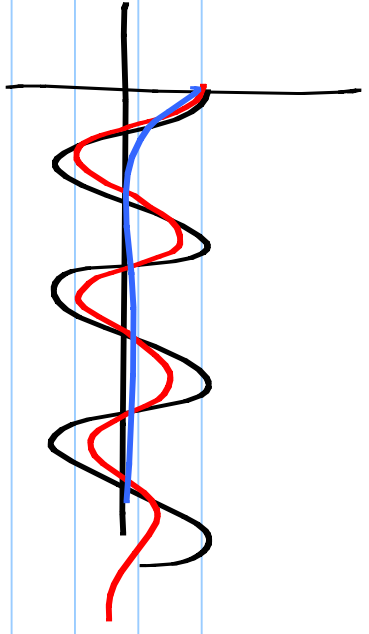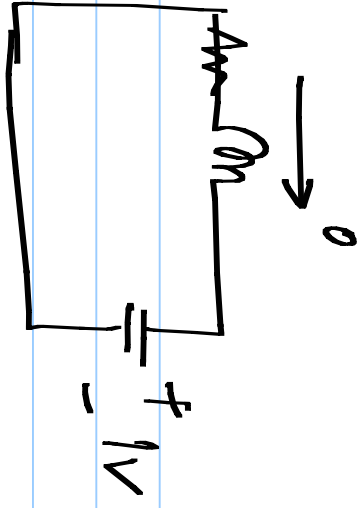


# Forced response of a 2<sup>nd</sup> order system

500, 20Ω, 2Ω

5mA: final value: 0 Final values: short circuit L

open circuit C

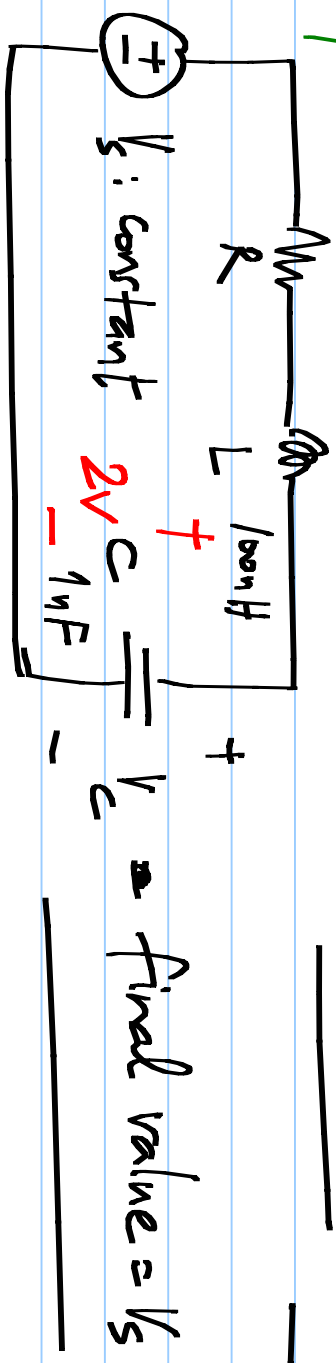

$$\zeta = 1/10$$

$$Q = 5$$

Steady state response + natural response

$$V_C(t) = V_s + A_1 \exp(p_1 t) \cos(p_1 t + \phi)$$

$$C \cdot \left. \frac{dV_C}{dt} \right|_{t=0} = 5 \mu A$$

$$V_C(0) = 2V = V_s + A_1 \cos(\phi)$$