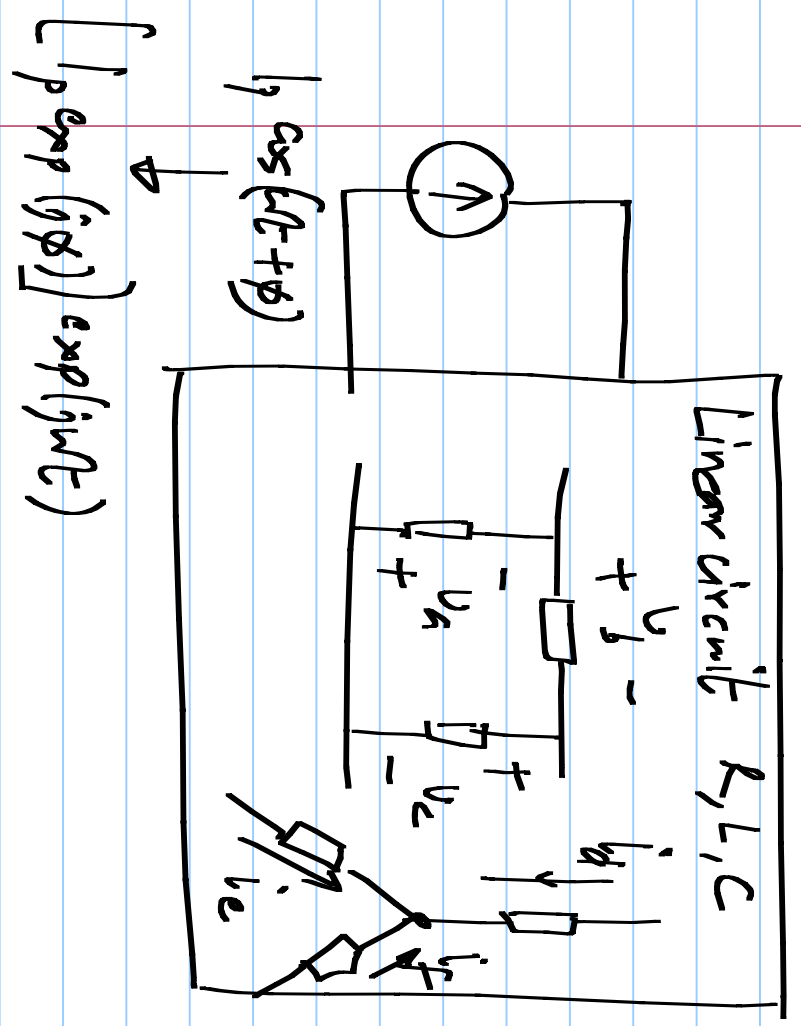


EC1010: Lecture 30.

Phasors

Sinusoidal steady state analysis at a frequency  $\omega$






$$\begin{aligned}
 v_a &= \bar{v}_a \cdot \exp(j\omega t) \\
 v_b &= \bar{v}_b \cdot \exp(j\omega t) \\
 v_c &= \bar{v}_c \cdot \exp(j\omega t)
 \end{aligned}
 \left. \vphantom{\begin{aligned} v_a \\ v_b \\ v_c \end{aligned}} \right\} \begin{aligned} &v_a + v_b + v_c \\ &= 0 \\ &\bar{v}_a + \bar{v}_b + \bar{v}_c \\ &= 0 \end{aligned}$$

$$\begin{aligned}
 i_b &= \bar{i}_b \cdot \exp(j\omega t) \\
 i_c &= \bar{i}_c \cdot \exp(j\omega t) \\
 i_p &= \bar{i}_p \cdot \exp(j\omega t)
 \end{aligned}
 \left. \vphantom{\begin{aligned} i_b \\ i_c \\ i_p \end{aligned}} \right\} \begin{aligned} &\text{KCL} \\ &\bar{i}_b + \bar{i}_c + \bar{i}_p = 0 \\ &\bar{i}_b + \bar{i}_c + \bar{i}_p = 0 \end{aligned}$$

KVL

KCL

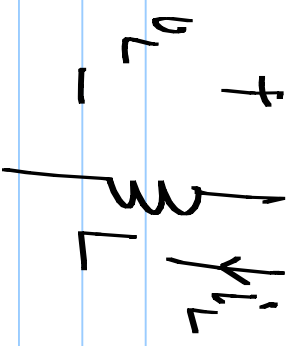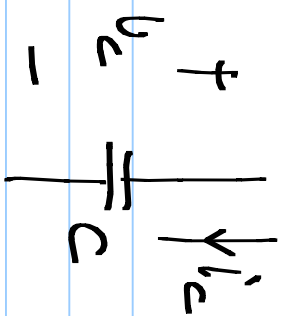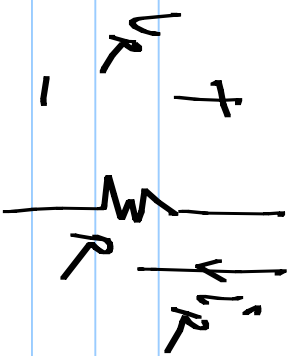

Voltage  $V_R = \bar{V}_R \cdot \exp(j\omega t)$

Current  $i_R = \bar{I}_R \cdot \exp(j\omega t)$

$$\frac{V_R}{i_R} = R$$

$$\bar{V}_R / \bar{I}_R = R$$

$$V_C = \bar{V}_C \cdot \exp(j\omega t)$$

$$i_C = \bar{I}_C \cdot \exp(j\omega t)$$

$$i_C = C \cdot \frac{dV_C}{dt}$$

$$V_C = L \cdot \frac{di_C}{dt}$$

$$\bar{I}_C \cdot \exp(j\omega t) = j\omega C \cdot \bar{V}_C \cdot \exp(j\omega t)$$

$$\bar{V}_C / \bar{I}_C = 1 / j\omega C$$

$$\bar{V}_C / \bar{I}_L = j\omega L$$

$$\text{Impedance } Z = \frac{\underline{V}}{\underline{I}}$$

Resistor  $R$

Capacitor  $\frac{1}{j\omega C} = -j \frac{1}{\omega C}$


Inductor  $j\omega L$

$$\text{Admittance } Y = \frac{\underline{I}}{\underline{V}}$$

$$G = \frac{1}{R}$$

$$j\omega C$$
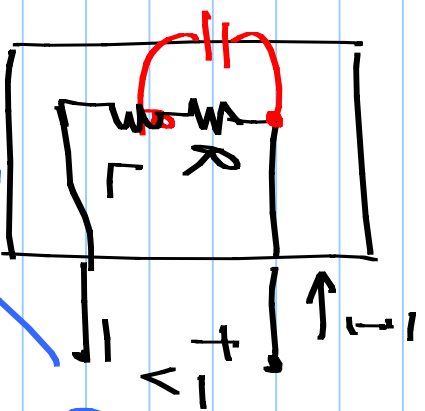
$$\frac{1}{j\omega L} = -j \frac{1}{\omega L}$$



$$Z = \frac{\underline{V}}{\underline{I}} = R + j\omega L$$

$R + jX$

$G_2$  Conductance  $= g_2 [Y]$

resistance  $Re[Z]$

reactance

$Im[Z]$

$$\underline{Y} = \frac{\underline{I}}{\underline{V}} =$$

$$\frac{R}{R^2 + \omega^2 L^2}$$

$$- \frac{j\omega L}{R^2 + \omega^2 L^2}$$

$$= G + jB$$


$Im[Y]$ : Susceptance

$$Z = R + jX = R_1 + j\omega L_1$$


$$R = R_1$$

$$X = \omega L_1$$

Re[Z]      Im[Z]

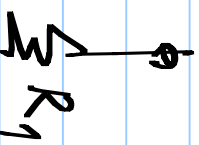

$$Y = G + jB$$

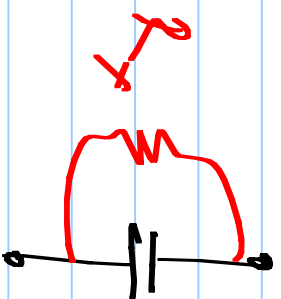


$$Y = \frac{1}{R_2} + j\omega C$$

$$G = \frac{R_1}{R_1^2 + \omega^2 L_1^2}$$

$$B = \frac{-\omega L_1}{R_1^2 + \omega L_1^2}$$

$$V_p \sin \omega t \rightarrow V_p \sqrt{\frac{1}{2}}$$

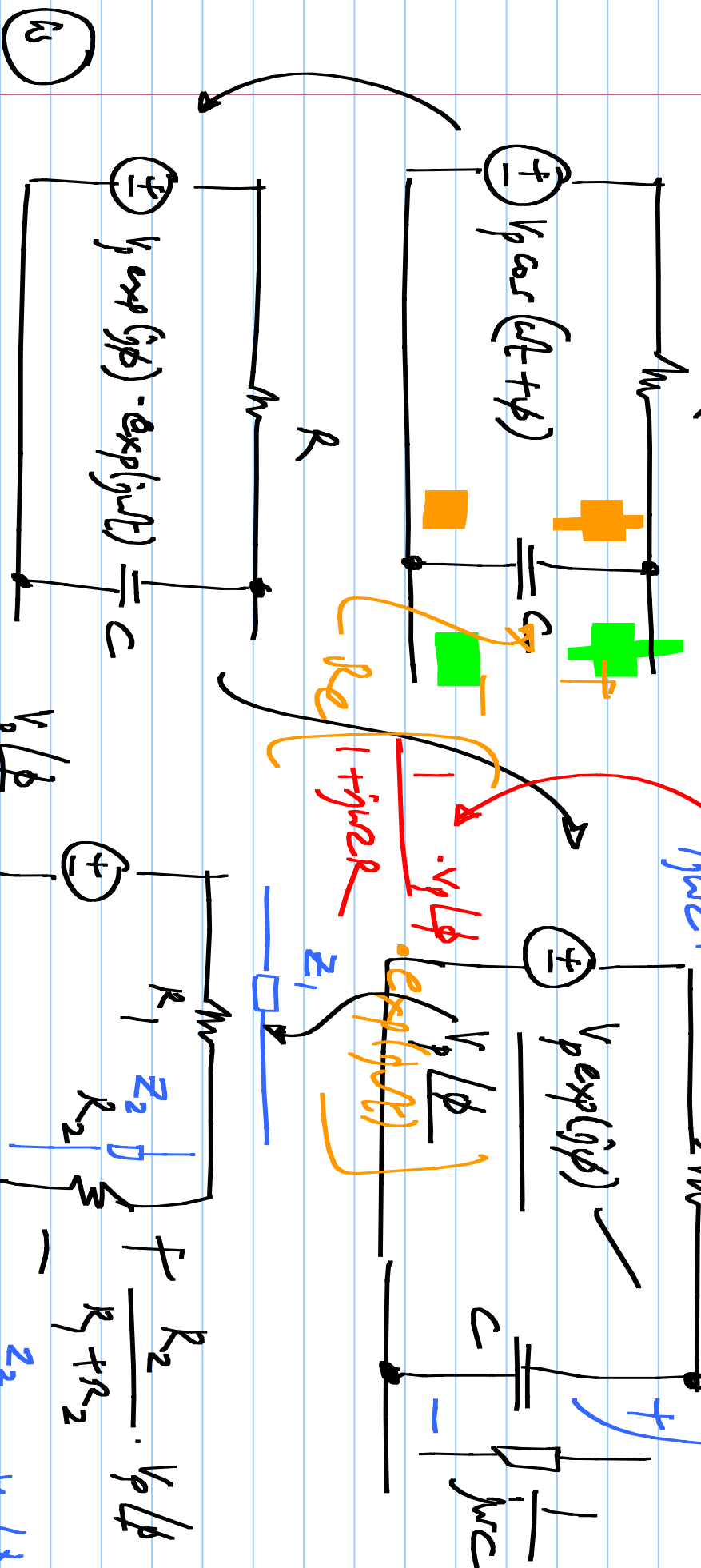
$$\frac{1/j\omega C}{j\omega C + R} \cdot V_p \sqrt{\frac{1}{2}}$$



(13)

$$V_{exp(j\omega t)} - \text{explicit} = C$$


$$V_p \sqrt{\frac{1}{2}}$$

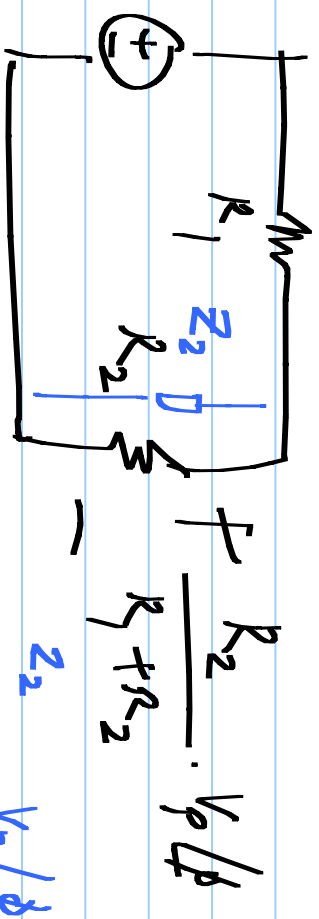

$$\frac{R_2}{R_1 + R_2} \cdot V_p \sqrt{\frac{1}{2}}$$

$$\frac{Z_2}{Z_1 + Z_2} \cdot V_p \sqrt{\frac{1}{2}}$$


Set up MNA eqs.

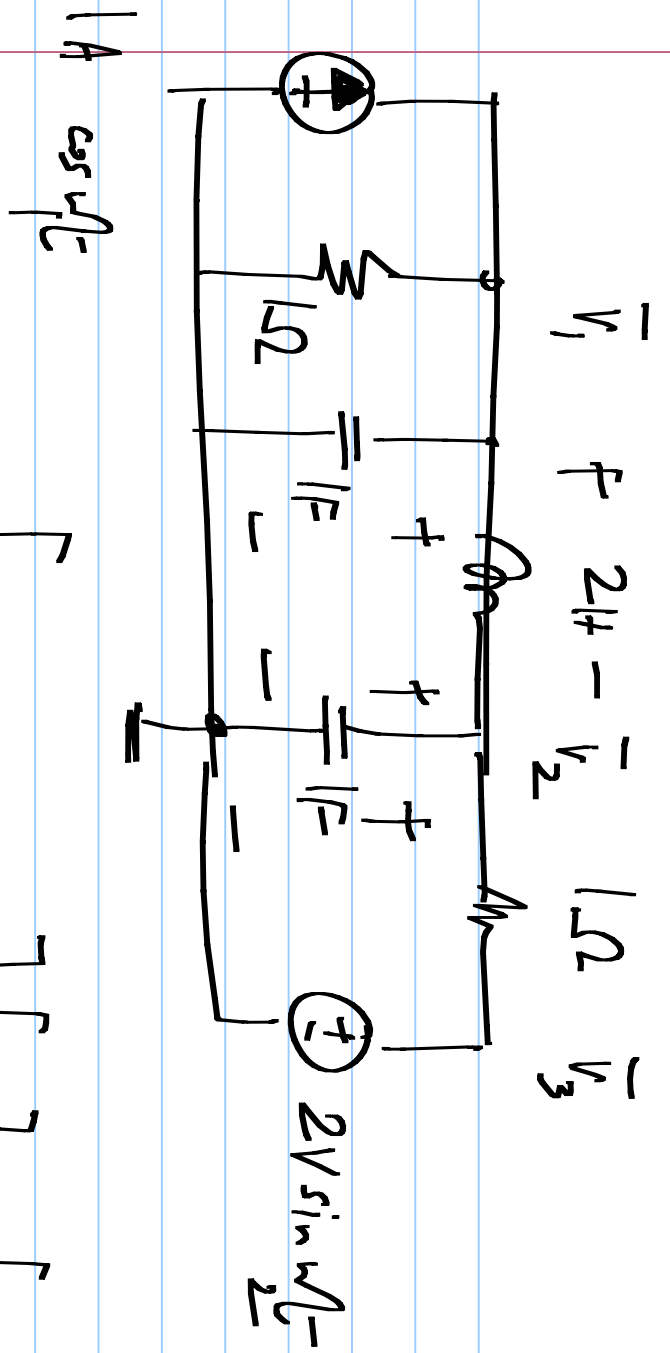

#1  $\text{Re}[V \cdot \exp(j\omega t)]$

#2  $\text{Re}[V \exp(j\omega t)]$


$$[Y] [V] = [I]$$

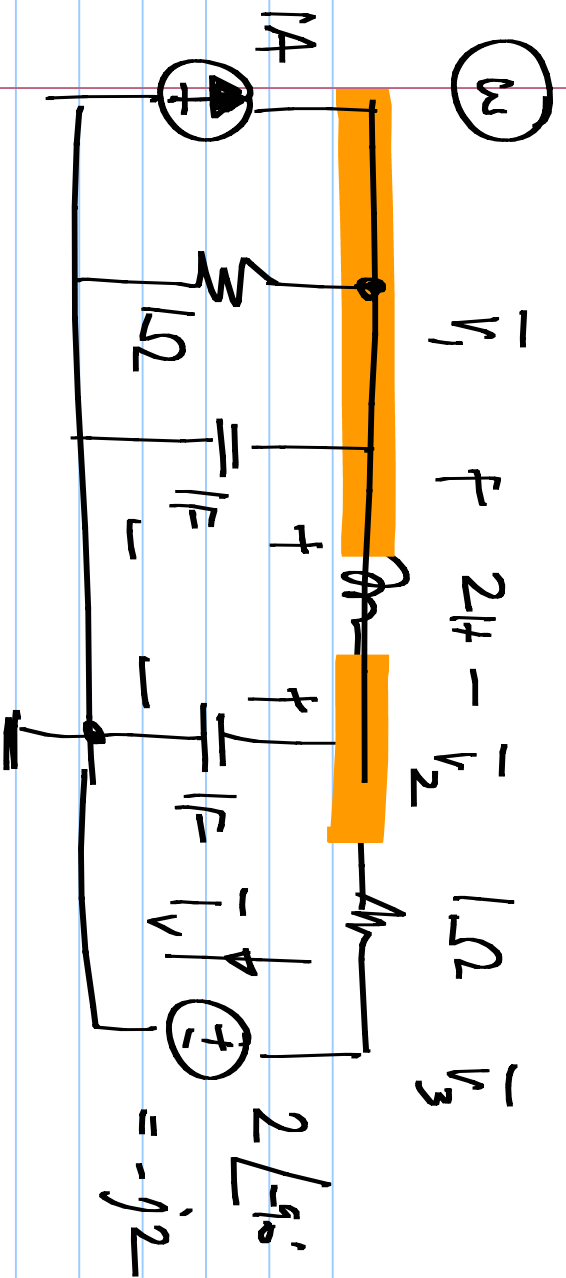

$$\begin{bmatrix}
 1 + j\omega + \frac{1}{j2\omega} & -\frac{1}{j2\omega} & 0 & 0 \\
 -\frac{1}{j2\omega} & 1 + j\omega + \frac{1}{j2\omega} & -1 & 0 \\
 0 & -1 & 1 & 1 \\
 0 & 0 & 1 & 0
 \end{bmatrix}
 \begin{bmatrix}
 \bar{V}_1 \\
 \bar{V}_2 \\
 \bar{V}_3 \\
 \bar{V}_4
 \end{bmatrix}
 =
 \begin{bmatrix}
 1 \\
 0 \\
 0 \\
 -j2
 \end{bmatrix}$$

$$i = 10^{-3} \text{ A} \quad 1 \text{ mA} \cos(10^3 t) : v_c = \int i = C \frac{dv}{dt}$$

Solution for  $t > 0$

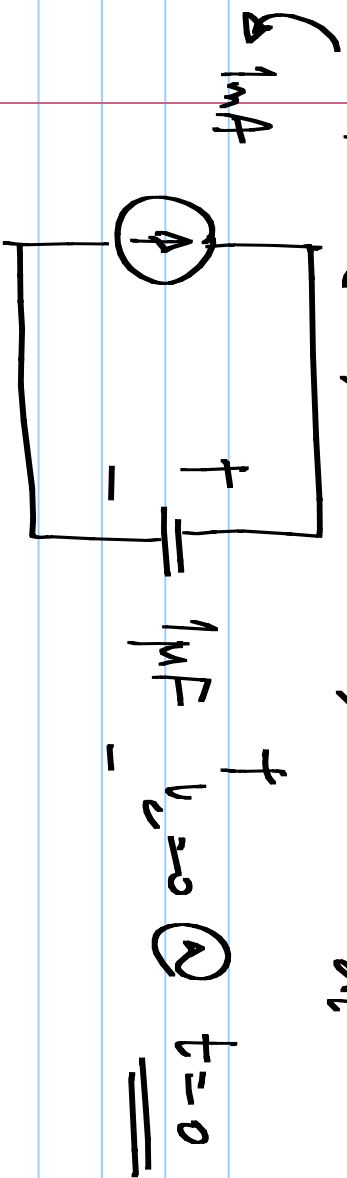

$$\frac{1}{\mu\text{F}} = -j \cdot 10^3 \Omega$$

$$1 \text{ mA} \sin(10^3 t) : v_c = [1 - \cos(10^3 t)] \text{ V}$$

$$1 \text{ mA} \cos(10^3 t) \quad \sin(10^3 t)$$

$$1 \text{ mA} \angle 0 \times (-j/10^3 \Omega) = -j \text{ V}$$

$$- \cos(10^3 t) \text{ V}$$

$$1 \text{ mA} \sin(10^3 t)$$

$$-j 1 \text{ mA} \times (-j/10^3 \Omega) = -1 \text{ V}$$