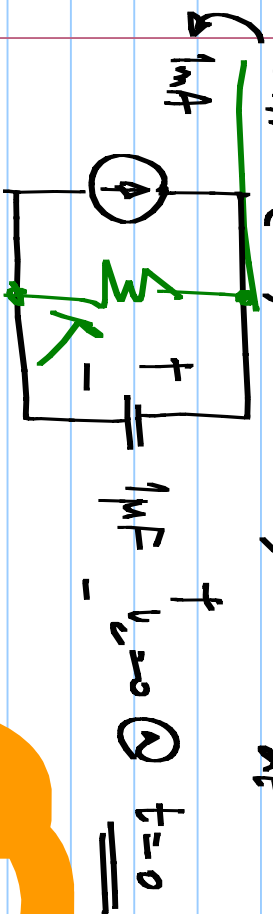


EECE1010: Lecture 31

$i = 10^{-3} \text{mA} \cos(10^3 t)$: $V_c = \sin(10^3 t) \text{V}$ $i = C \frac{dV}{dt}$

Solution for $t > 0$

$$\frac{1}{j\omega C} = -j \cdot 10^3 \Omega$$



$1 \text{mA} \sin(10^3 t)$: $V_c = [1 - \cos(10^3 t)] \text{V}$

$1 \text{mA} \cos(10^3 t)$ $\sin(10^3 t)$

$1 \text{mA} \angle 0 \times (-j10^3 \Omega) = -j \text{V}$


$1 \text{mA} \sin(10^3 t)$ $[1 - \cos(10^3 t)] \text{V}$

$-j1 \text{mA} \times (-j10^3 \Omega) = -1 \text{V}$

$- \cos(10^3 t) \text{V}$


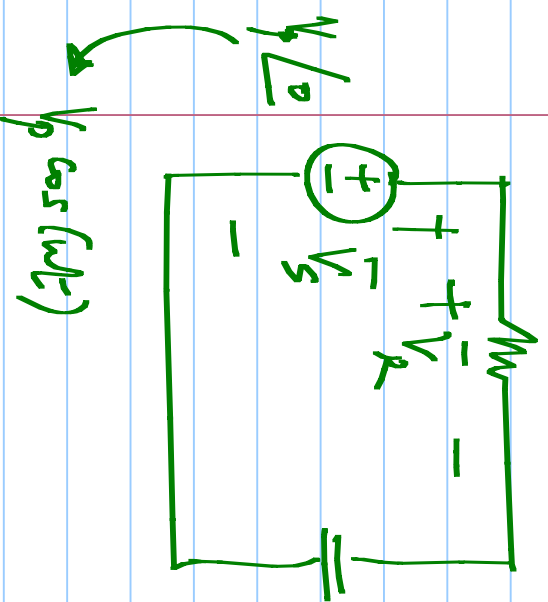
$$\underline{V}_S = \underline{V}_R + \underline{V}_C$$




$$\underline{V}_R = \frac{R}{R + 1/j\omega C} \cdot V_p = \frac{j\omega C R}{1 + j\omega C R} \cdot V_p$$

$$\underline{V}_C = \frac{1/j\omega C}{R + 1/j\omega C} \cdot V_p = \frac{1}{1 + j\omega C R} \cdot V_p$$

any given frequency:

$$\omega = 0$$

$\Delta \ln []$

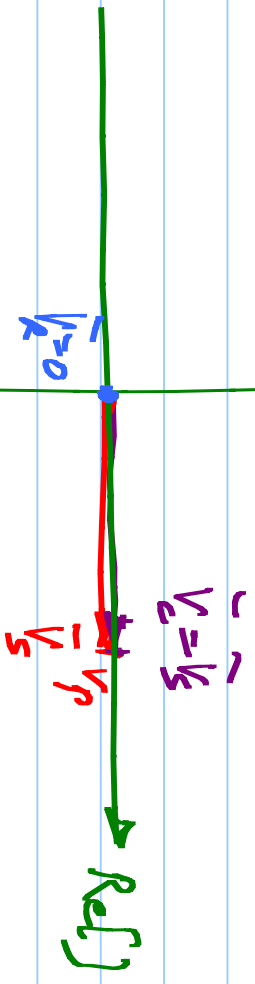


$$\frac{j}{1+j} \quad \begin{matrix} \pi/2 \\ \pi/4 \end{matrix}$$

$$\bar{V}_R = \frac{R}{R + 1/j\omega C} \cdot V_p = \frac{j\omega CR}{1 + j\omega CR} \cdot V_p$$

$$\frac{1}{1+j} \quad \begin{matrix} 0 \\ \pi/4 \end{matrix}$$

$$\bar{V}_C = \frac{1/j\omega C}{R + 1/j\omega C} \cdot V_p = \frac{1}{1 + j\omega CR} \cdot V_p$$

Ⓜ any given frequency: $\omega = 1/RC$

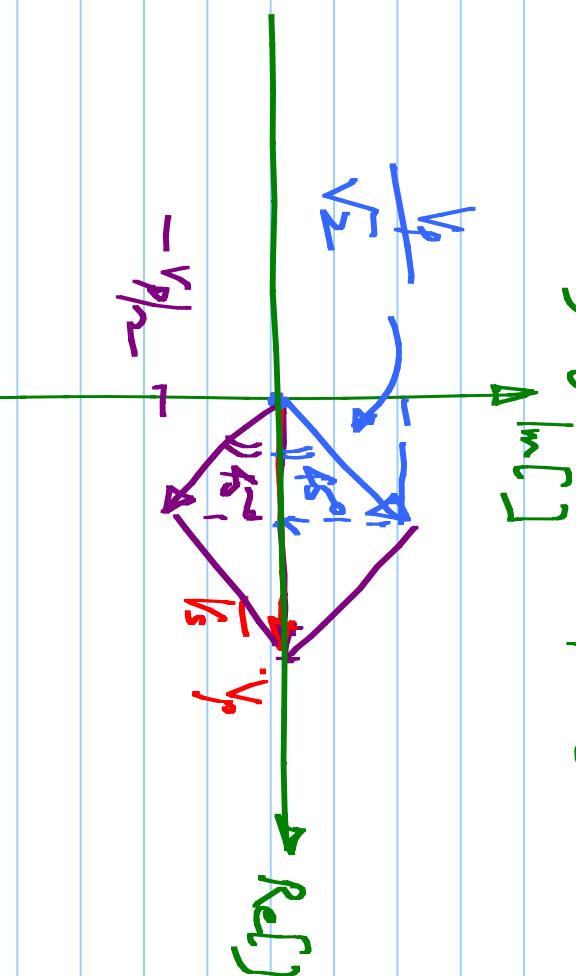

$$\frac{j\omega C}{1+j\omega C}$$


$$\bar{V}_R = \frac{R}{R + 1/j\omega C} \cdot V_p = \frac{j\omega RC}{1 + j\omega RC} \cdot V_p$$

$$\omega \ll 1/RC$$

$$\bar{V}_C = \frac{1/j\omega C}{R + 1/j\omega C} \cdot V_p = \frac{1}{1 + j\omega RC} \cdot V_p$$


⊙ any given frequency:

$$\omega = 0$$

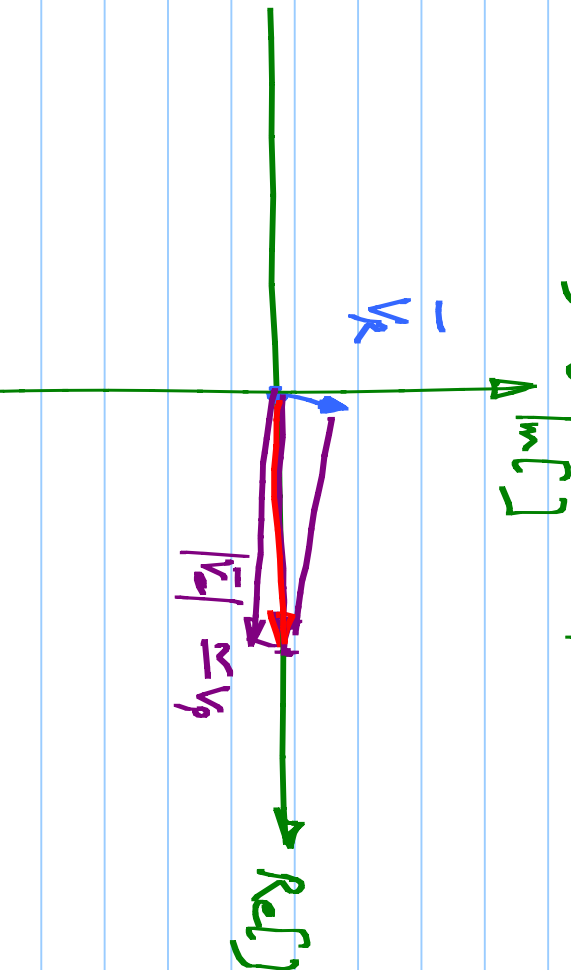

$$\bar{I}_C = j\omega C \cdot \bar{V}_R$$


$$\bar{I}_C = \bar{V}_R + 90^\circ$$

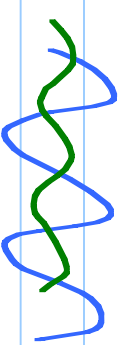


$$\bar{V}_R = \frac{R}{R + 1/j\omega C} \cdot V_p = \frac{j\omega RC}{1 + j\omega RC} \cdot V_p \quad \omega \rightarrow 1/RC$$

$$\bar{V}_C = \frac{1/j\omega C}{R + 1/j\omega C} \cdot V_p = \frac{1}{1 + j\omega RC} \cdot V_p$$


⊙ any given frequency: $\omega = 0$

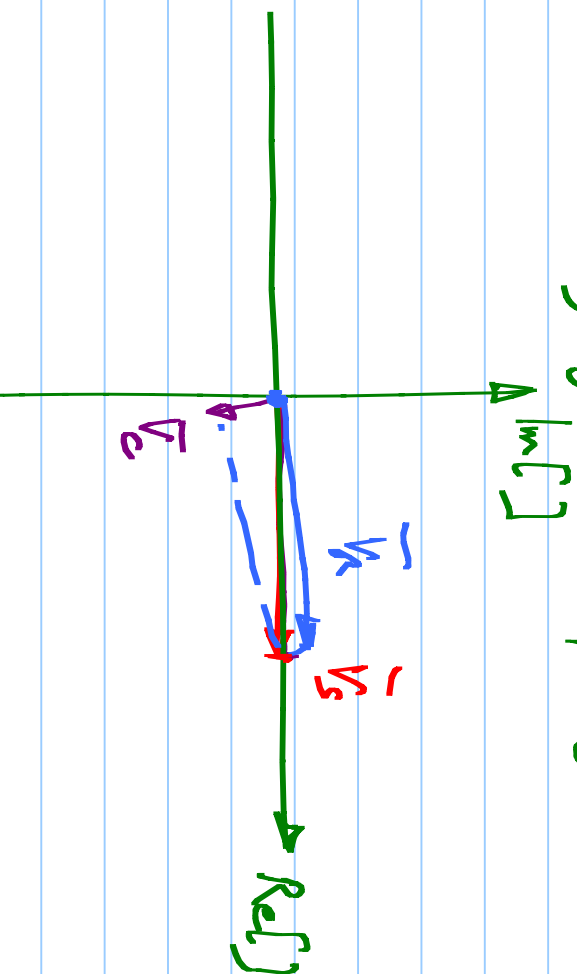

Magnitude & phase versus frequency:

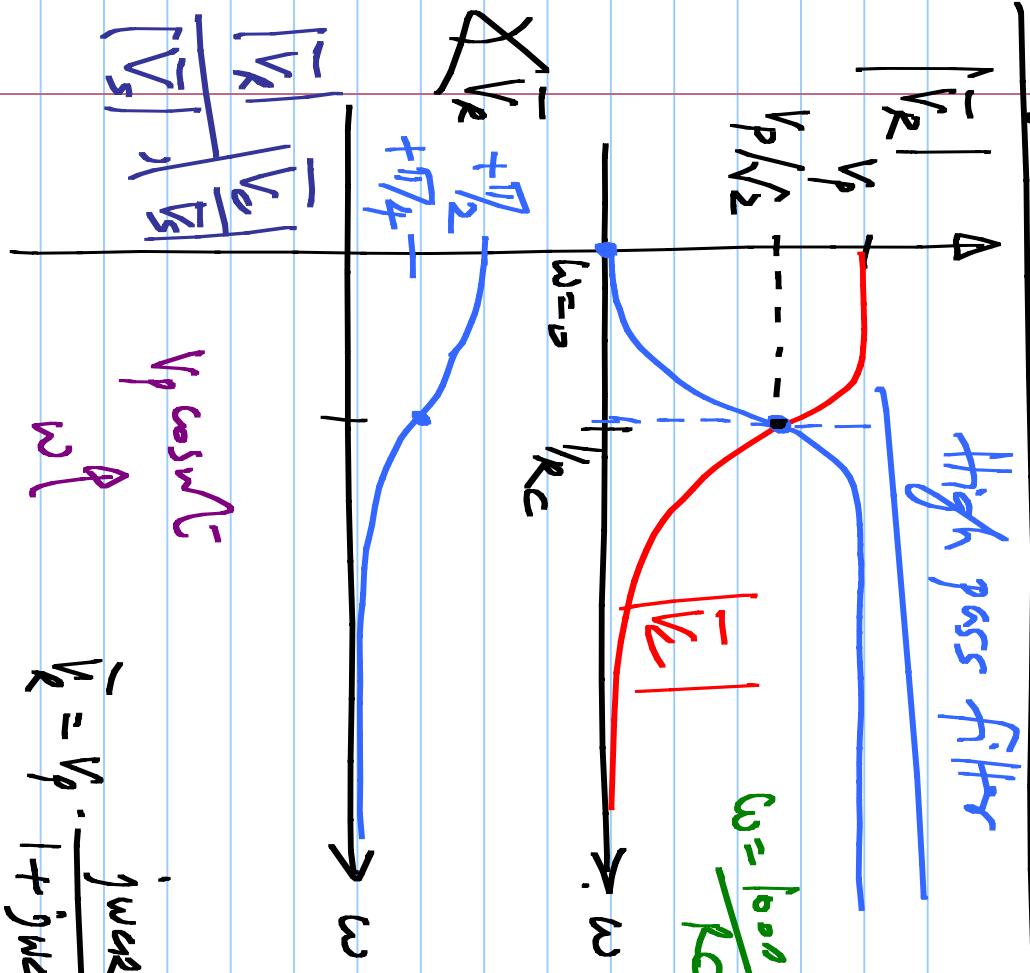

$|V_c|$: low pass filter

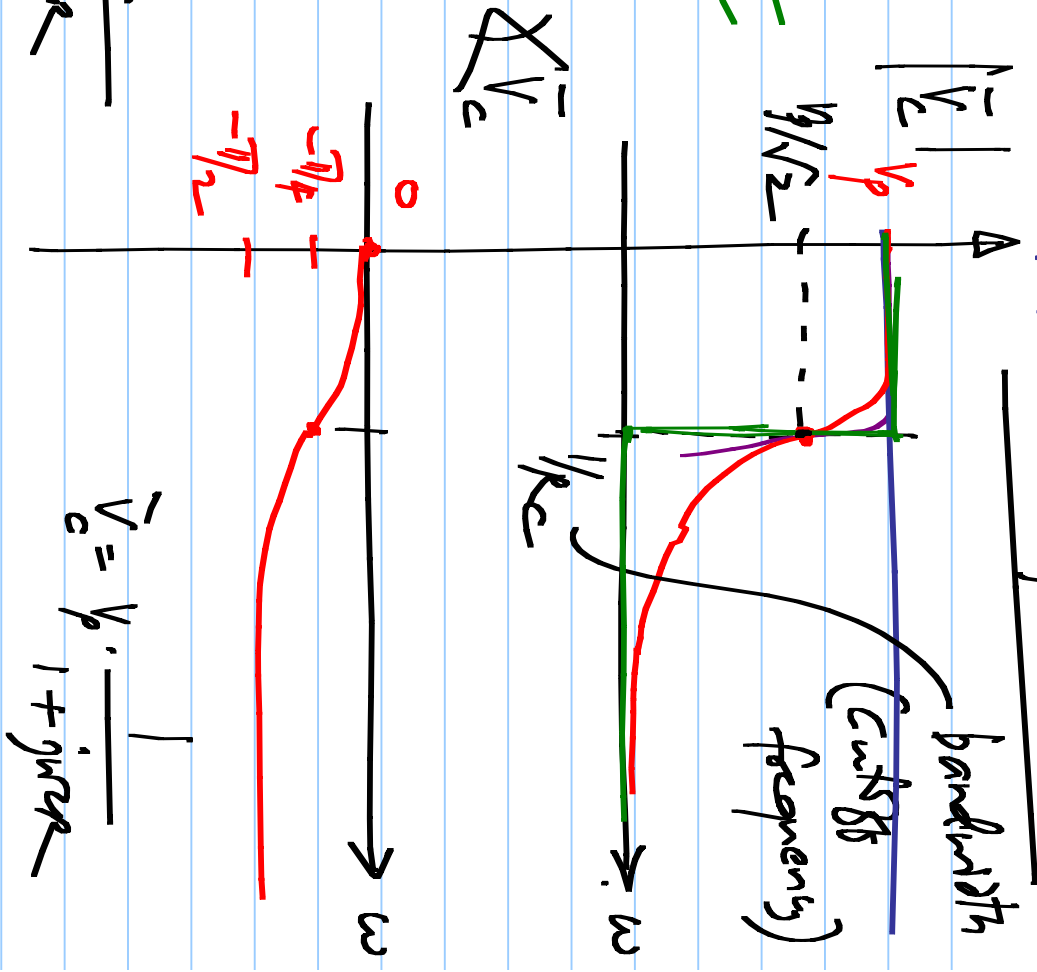

$$|\bar{V}_c| = V_p \cdot \frac{1}{\sqrt{1 + (\omega R C)^2}} \quad \sqrt{1 + (\omega R C)^2}$$

