




EC1010: Lecture 32

$V_R, V_C, V_R/V_S, V_C/V_S$

(Linear scale)

V_R/V_S

V_C/V_S

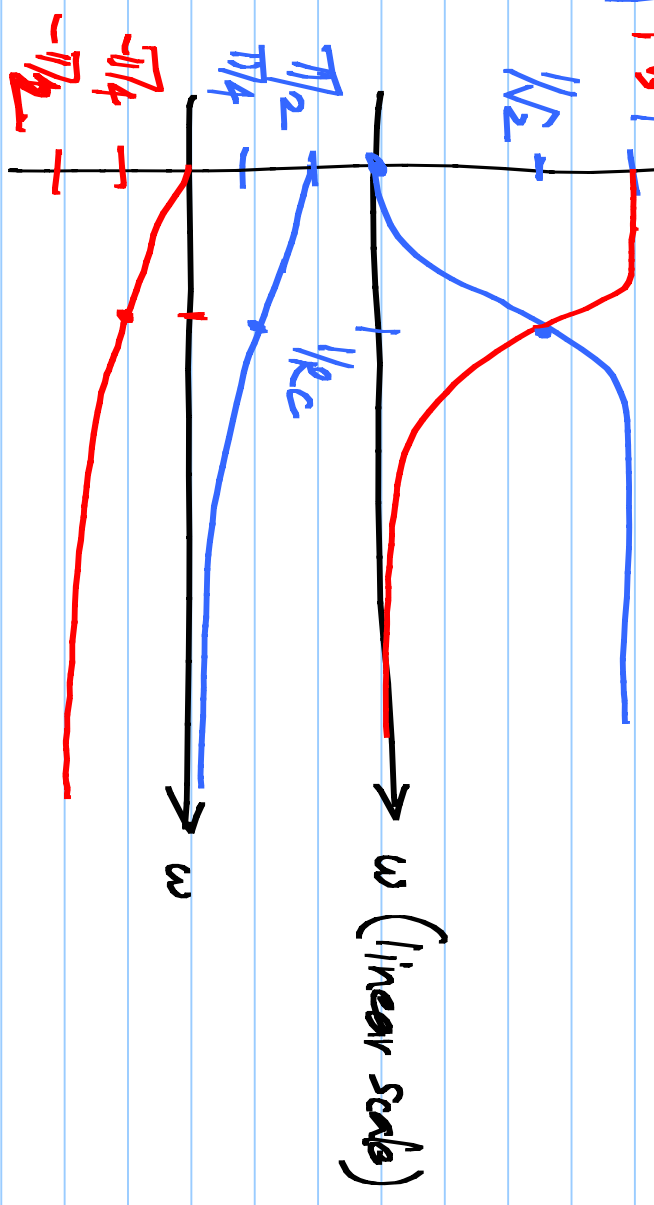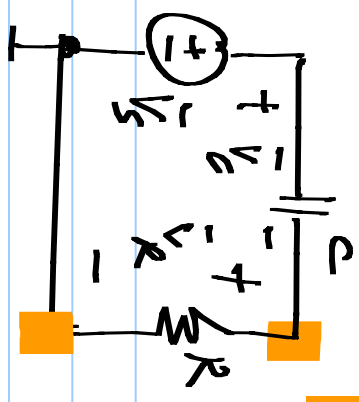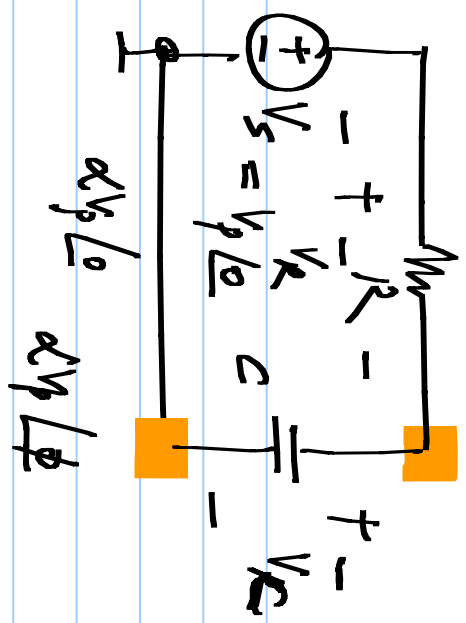

Plots of log magnitude and phase versus $\log \cdot \omega$


$$\frac{V_o}{V_s} = \frac{1}{1 + j\omega RC} \quad \log \left| \frac{V_o}{V_s} \right| = \log \left[\frac{1}{\sqrt{1 + (\omega RC)^2}} \right]$$


$$\approx 0 \quad \omega \ll 1/RC$$

$$\left| \frac{V_o}{V_s} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad -\log(\omega RC) \quad \omega \gg 1/RC$$
$$= -\log \omega + \log(1/RC)$$

$$\approx 1 \quad \omega \ll 1/RC \quad \text{dB: (decibel):} \quad -3.01 \text{ dB} \quad \omega = 1/RC$$

$$\approx \frac{1}{\omega RC} \quad \omega \gg 1/RC \quad 20 \log_{10} \left| \frac{V_o}{V_s} \right| \approx 0 \quad \omega \ll 1/RC$$
$$-20 \log(\omega RC) \quad \omega \gg 1/RC$$

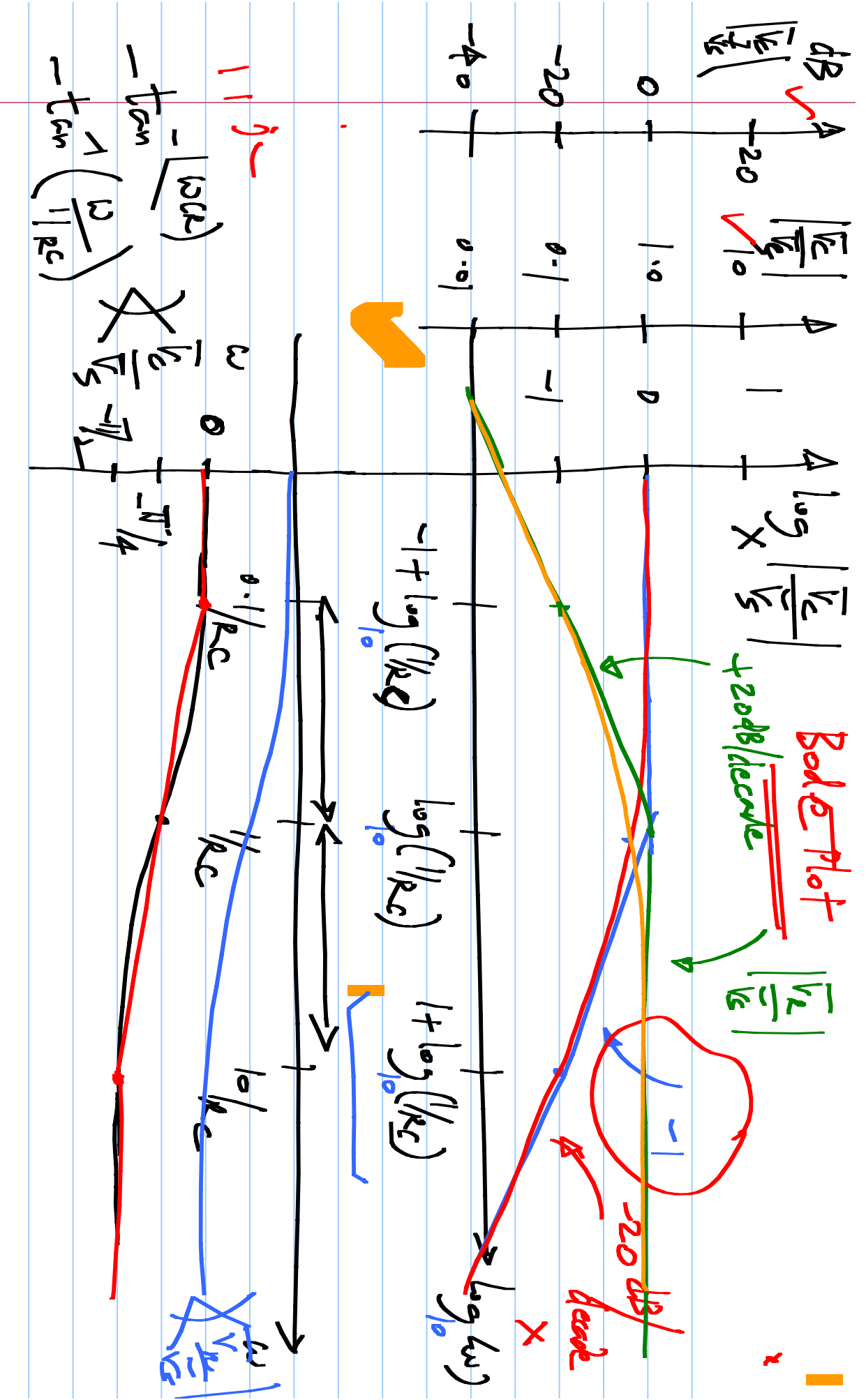

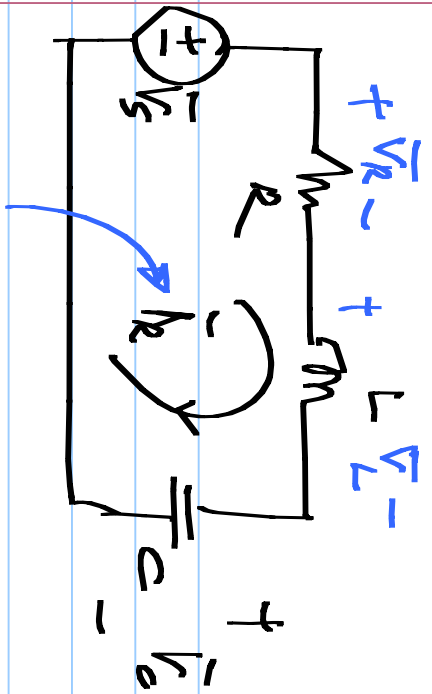

$$\frac{V_o}{V_s} = \frac{1/j\omega C}{1/j\omega C + j\omega L + R}$$



$$\approx \left(\frac{1}{-j\omega^2 LC} \right) \omega \gg \frac{1}{\sqrt{LC}}$$