


EE1010: Lecture 39

3 phase systems:


* Source: balanced.

* Load: { star, delta }



{ balanced, unbalanced }
 { 3, 4 wire }

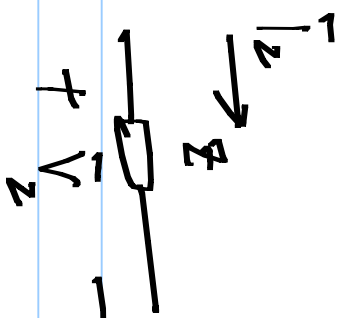

3 wire


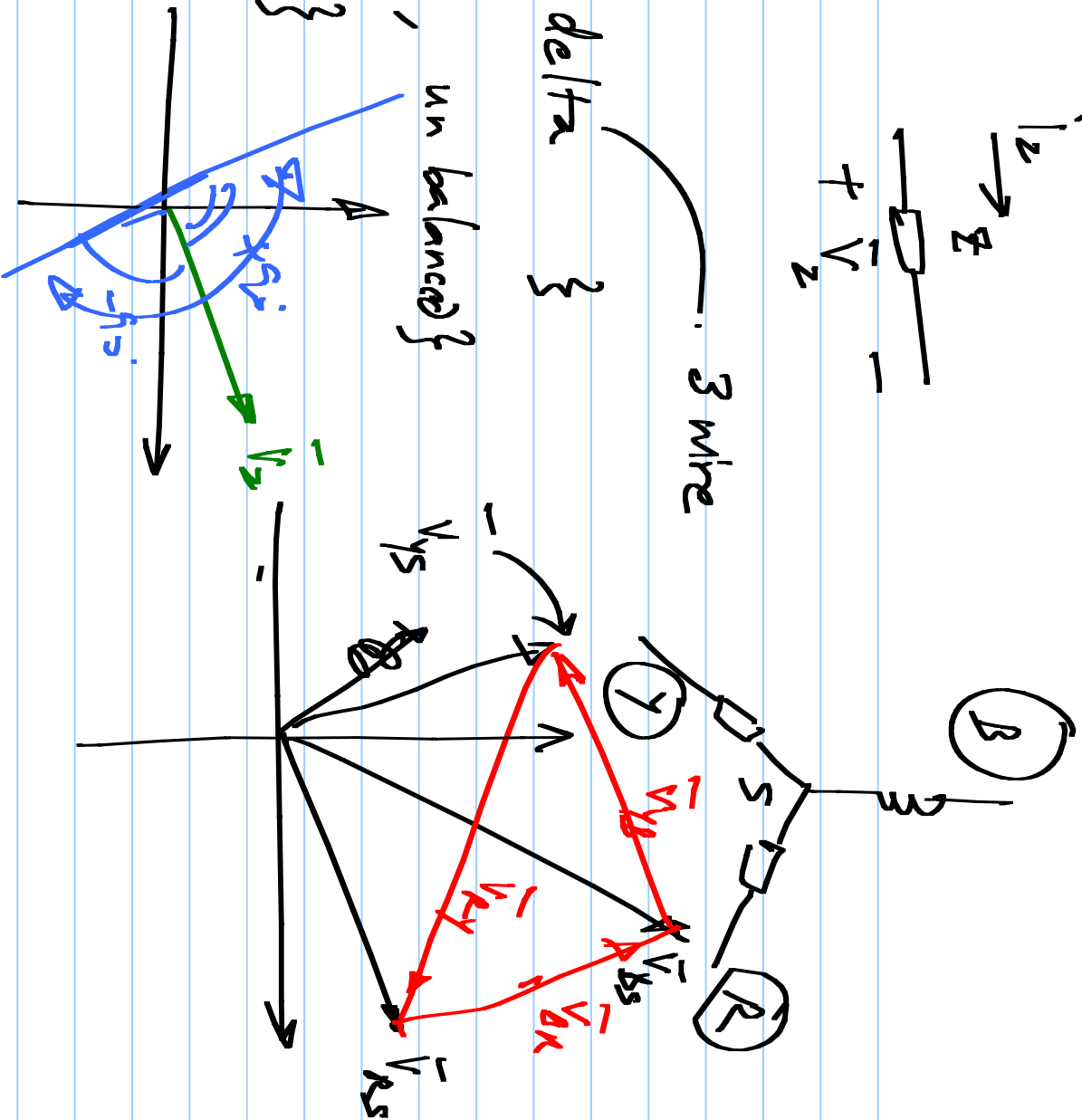



Un bal. load

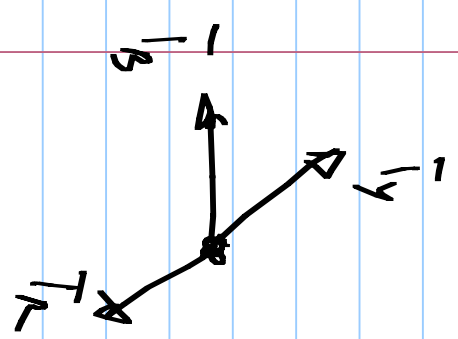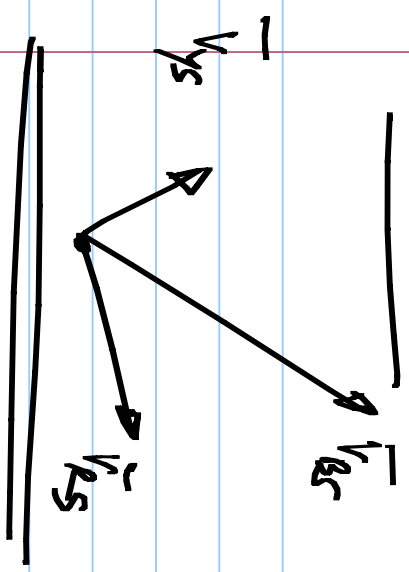

$$\sum \left(\frac{V_1 + V_2}{2} \right) \left(\frac{V_1 - V_2}{2} \right)$$

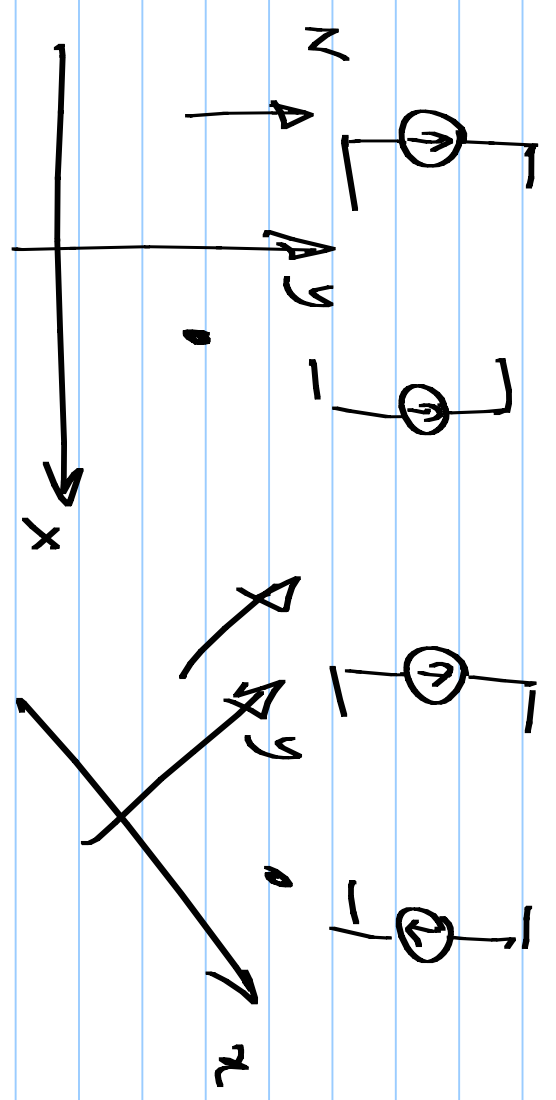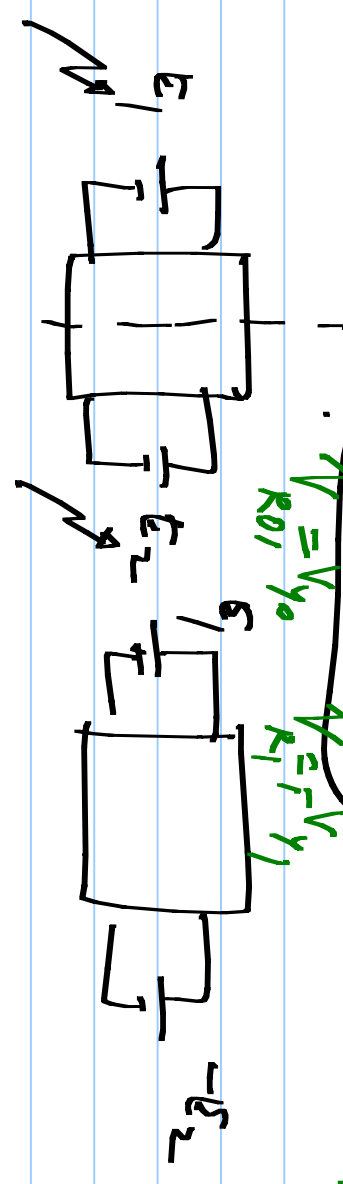$V = k_0 + V_{R_1}$
 $v = x y_0 + v_{y_1}$



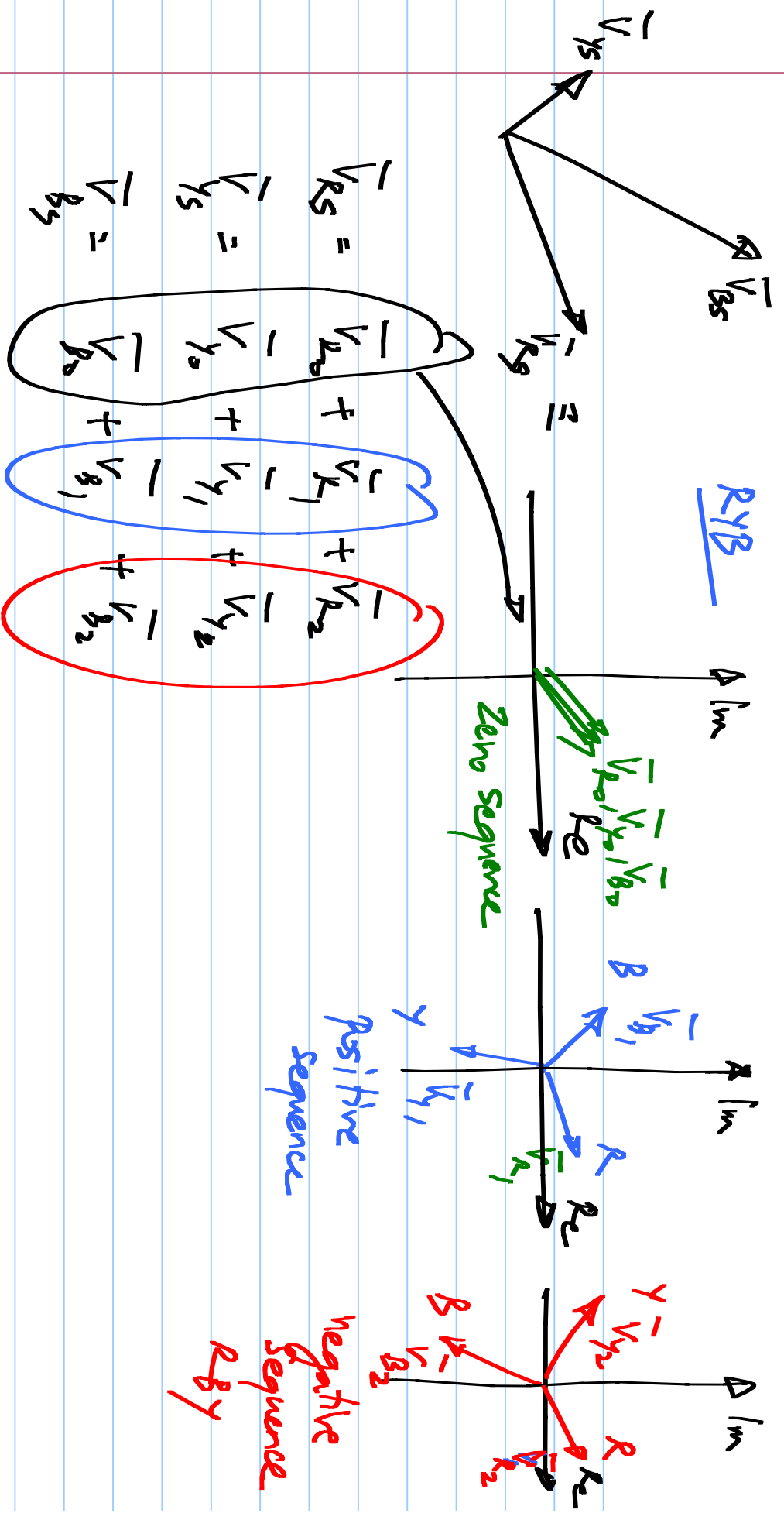

R Y B

Zero sequence

positive sequence

negative sequence
RBY

$$\bar{V}_y = \bar{V}_{y_0} + \bar{V}_{y_1} + \bar{V}_{y_2}$$

$$\alpha = \exp(j\frac{2\pi}{3})$$

$$\alpha^2 = \exp(-j\frac{2\pi}{3}) = \exp(-j\frac{4\pi}{3})$$

$$= \bar{V}_R + \exp(-j\frac{2\pi}{3})\bar{V}_{R_1} + \exp(-j\frac{4\pi}{3})\bar{V}_{R_2} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix}$$

$$\alpha^2 = \alpha^*$$

$$1 + \alpha + \alpha^2 = 0$$

$$= \bar{V}_{R_0} + \alpha^2 \bar{V}_{R_1} + \alpha \bar{V}_{R_2}$$

$$\begin{bmatrix} \bar{V}_R \\ \bar{V}_y \\ \bar{V}_B \end{bmatrix} =$$

$$\begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix}$$

$$\begin{bmatrix} \bar{V}_R \\ \bar{V}_{R_1} \\ \bar{V}_{R_2} \end{bmatrix}$$

$$= [A]$$

$$[A] = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix}$$

$$[A]^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix}$$

Positive seq: $\bar{V}_1 = \bar{V}_2 \cdot \exp(-j2\pi/3)$; $\bar{V}_B = \bar{V}_1 \exp(-j4\pi/3)$

$$\bar{V} = [A] \cdot \bar{V}_s$$

$$\bar{V}_s = [A]^{-1} \bar{V}$$

$$\begin{bmatrix} \bar{V}_A \\ \bar{V}_B \\ \bar{V}_C \end{bmatrix}$$

$$\begin{bmatrix} \bar{V}_R \\ \bar{V}_Y \\ \bar{V}_B \end{bmatrix}$$

