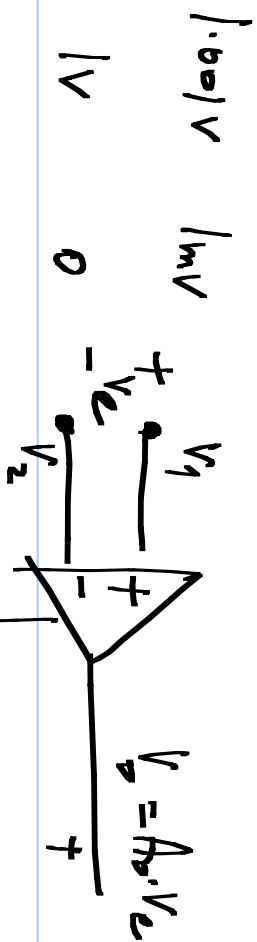


EECD10: Lecture 40



$$\vec{V} = [A]^{-1} \vec{V} \quad \text{unbalanced}$$

0, +ve & -ve seq.

$$V = [A] \vec{V}_s$$

$$V_b = A_{vd} \cdot V_c + A_{cm} \left(\frac{V_1 + V_2}{2} \right)$$

$$V_b = \alpha_1 V_1 + \alpha_2 V_2$$

$$\alpha_2 = -\alpha_1$$


$$\begin{bmatrix} I_R \\ I_Y \\ I_B \end{bmatrix}$$

* Motor: -ve seq. current \Rightarrow negative torque

* 4-wire load: Zero seq current \Rightarrow neutral wire current

$$\underline{V} = [Z] \cdot \underline{I}$$
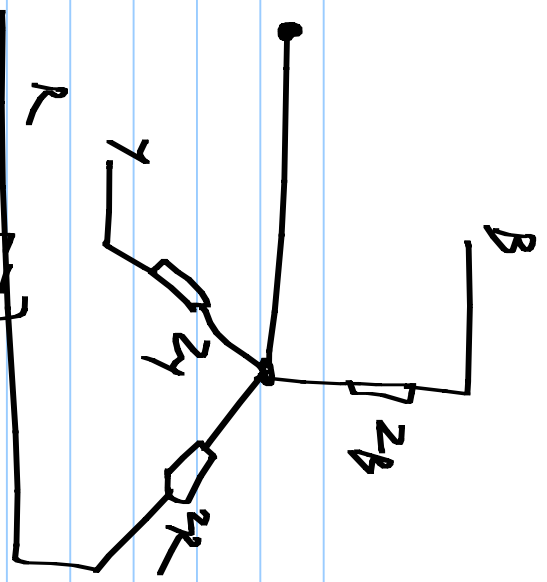
$$\begin{bmatrix} z_R & 0 & 0 \\ 0 & z_Y & 0 \\ 0 & 0 & z_B \end{bmatrix}$$




$$[A] \underline{V}_s = [Z][A] \underline{I}_s$$

$$\underline{V}_s = \{ [A]^{-1} [Z] [A] \} \underline{I}_s$$





$$\underline{I}_s = [A]^{-1}$$

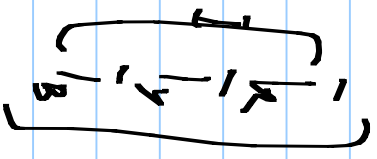

$$\frac{1}{3} \quad \frac{1}{3} \quad \frac{1}{3}$$

$$230\text{V}_{\text{rms}} \rightarrow 400\text{V line-line} \quad 230\sqrt{3} = 398\text{V}$$

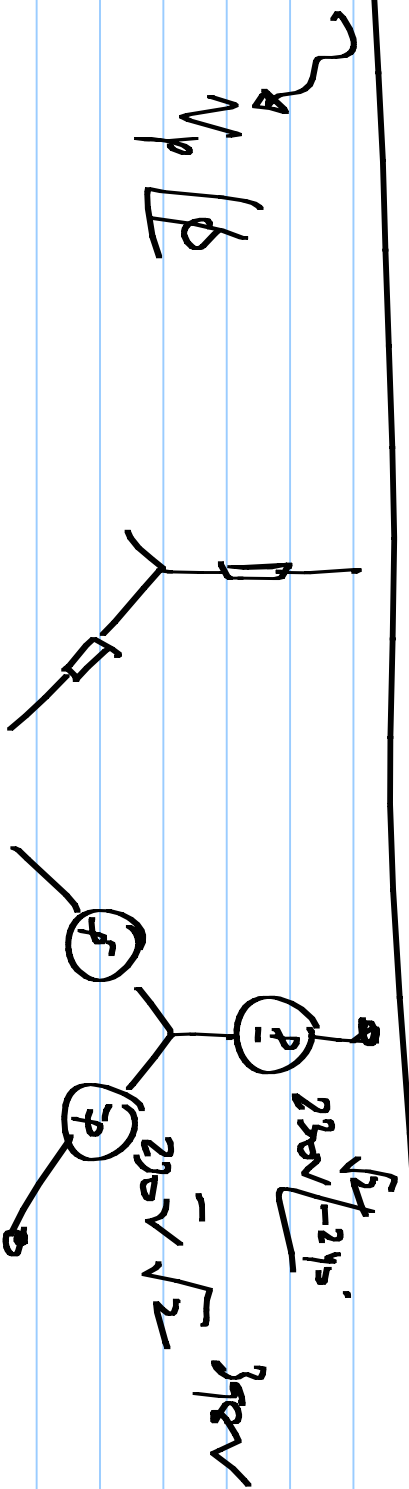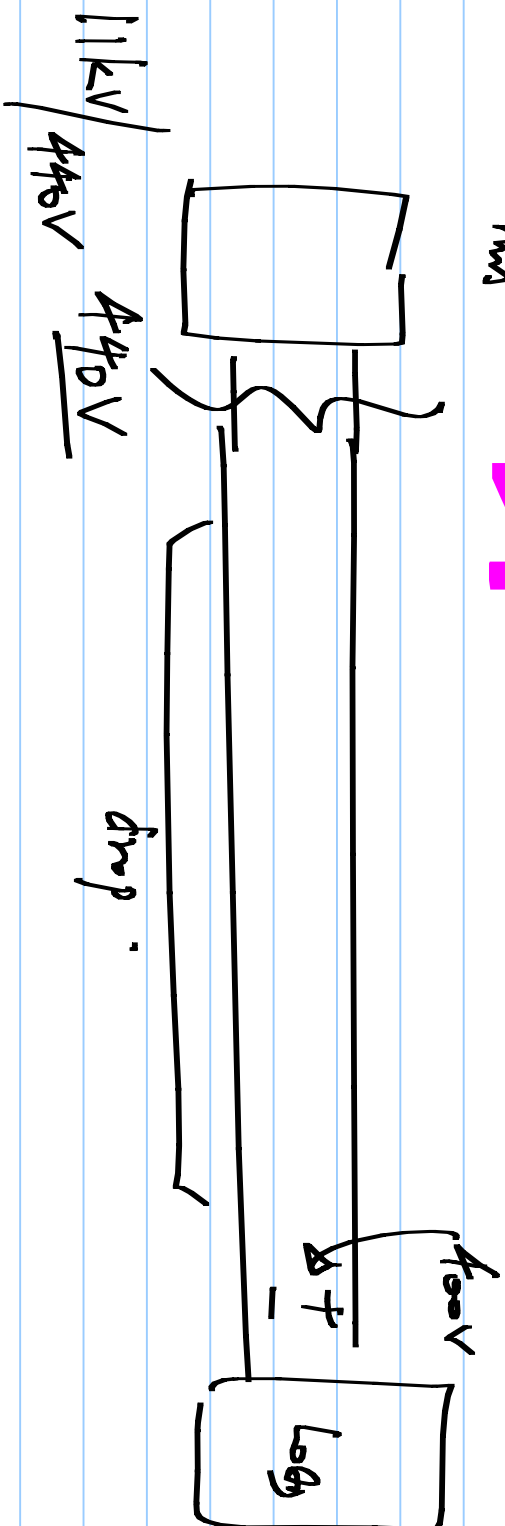
$$230\text{V}_{\text{rms}} \rightarrow 400\text{V}$$



AC power + measurement

$$i_p \cos(\omega t + \phi)$$

$$p(t) = \frac{V_p I_p}{2} \cos \phi$$

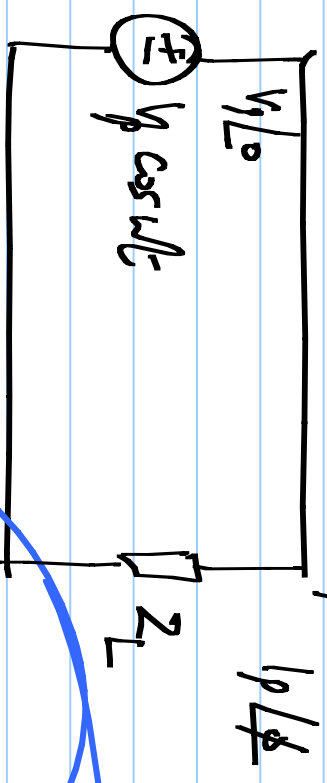

$$+ \frac{V_p I_p}{2} \cos(2\omega t + \phi)$$

$$\bar{p} = \frac{V_p I_p}{2} \cos \phi = \frac{V_p I_p}{2} \cos \phi - j \frac{V_p I_p}{2} \sin \phi$$


Apparent power $P_{av} = \text{Re}[\bar{p}]$

reactive power $- \left(\frac{V_p I_p}{2} \right) \sin(2\omega t) \sin \phi$

$$PF = \frac{\text{Re}[\bar{p}]}{|\bar{p}|}$$

$$|\bar{p}|$$

3 phase balanced case:

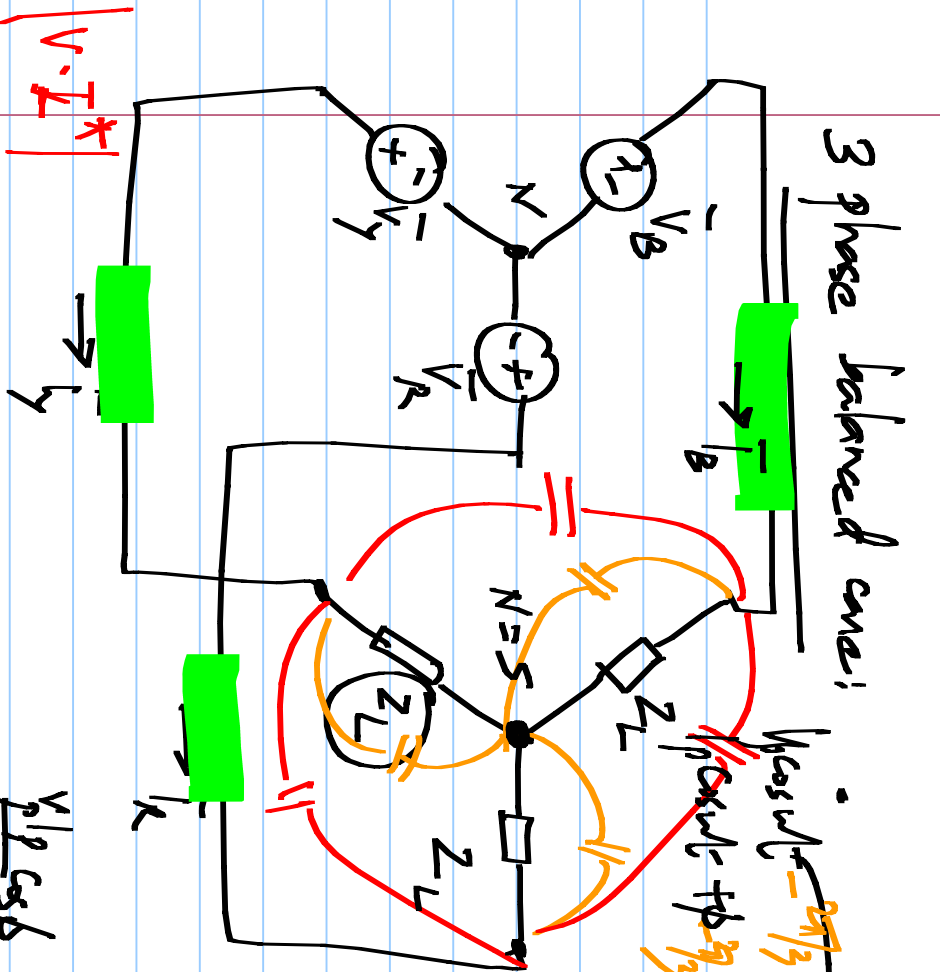

$$P_{av} = \frac{3}{2} V_p I_p \cos \phi$$

$$PF = \frac{P}{|P|_{\text{per phase}}}$$


$$P = \frac{V_p I_p}{2} \cos \phi + \frac{V_p I_p}{2} \cos \left(2\omega t + \frac{4\pi}{3} \right) \cos \phi - \frac{V_p I_p}{2} \sin \left(2\omega t - \frac{4\pi}{3} \right) \sin \phi$$

$$P = \frac{V_p I_p}{2} \cos \phi + \frac{V_p I_p}{2} \cos \left(2\omega t - \frac{4\pi}{3} \right) \cos \phi - \frac{V_p I_p}{2} \sin \left(2\omega t - \frac{4\pi}{3} \right) \sin \phi$$


$$P(t) = \frac{V_p I_p}{2} \cos \phi + \frac{V_p I_p}{2} \cos(2\omega t) \cos \phi - \frac{V_p I_p}{2} \sin(2\omega t)$$

$$\bar{V}_R = V_p \quad \bar{I} = I_p \quad \phi$$

Wattmeter,

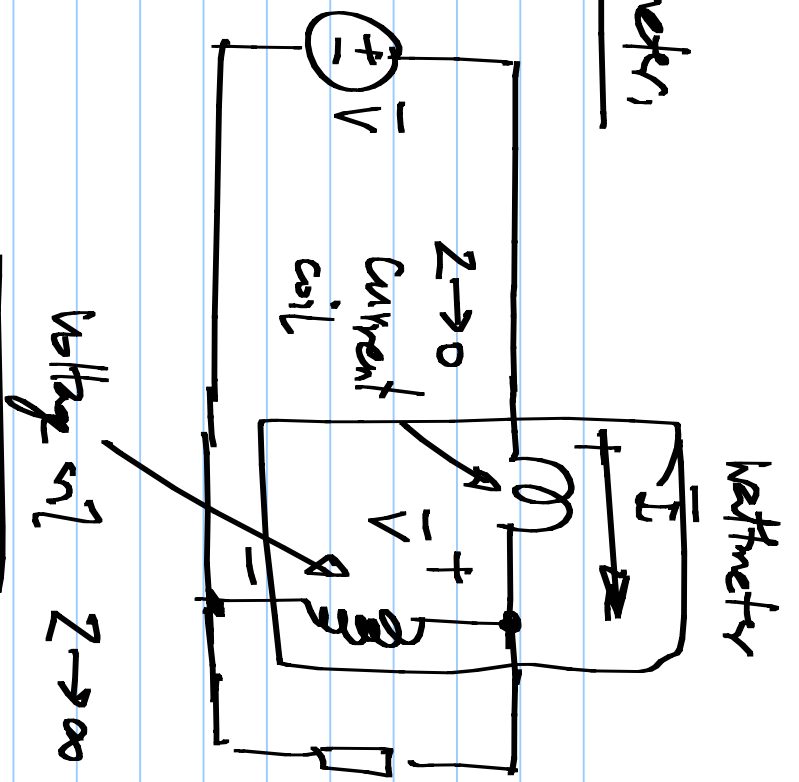
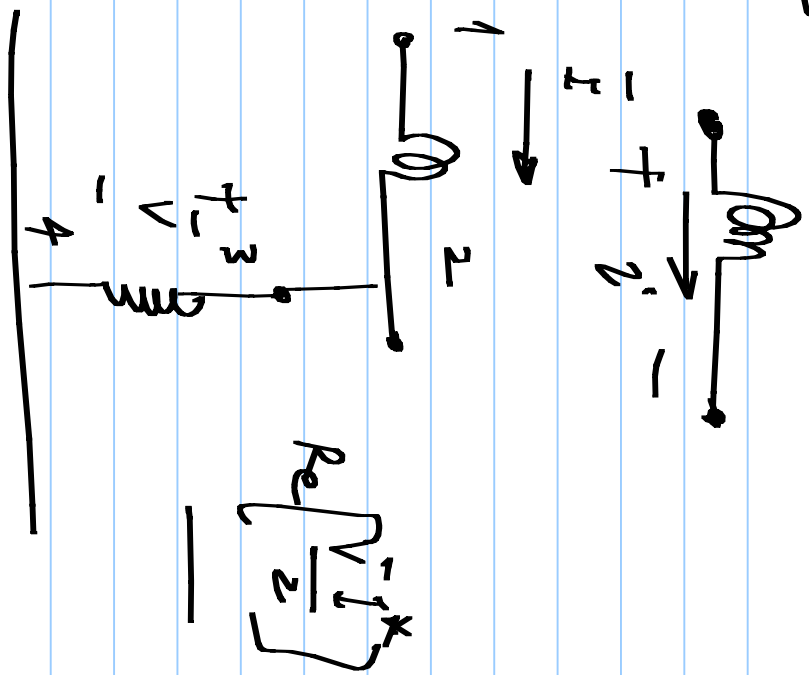
$$\text{Re} \left[\frac{V I^*}{2} \right]$$



$$\text{Re} \left[\frac{V I^*}{2} \right]$$

3 wire, 3 phase: R

P₁

Two wattmeter

method for


measuring 3 phase

power

Y


P₂

B

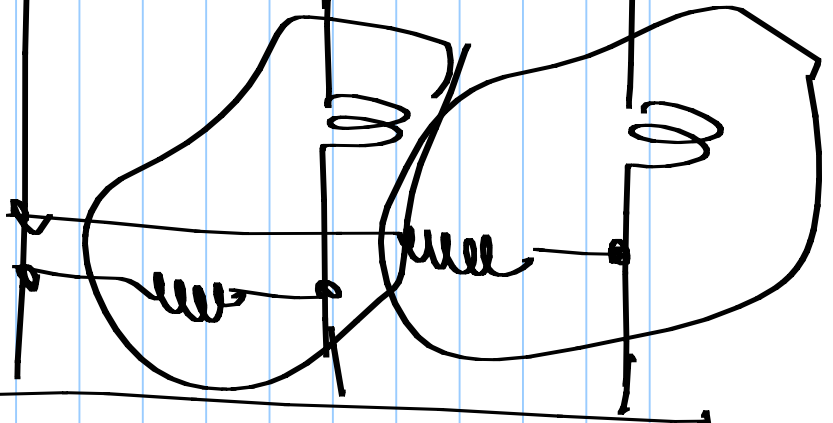

P₁ + P₂: TOTAL power




3 ph.
3 wire
(4)

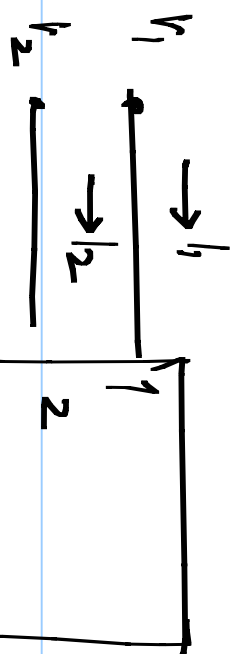

$$v_1 + v_2 + \dots + v_N$$

x

0

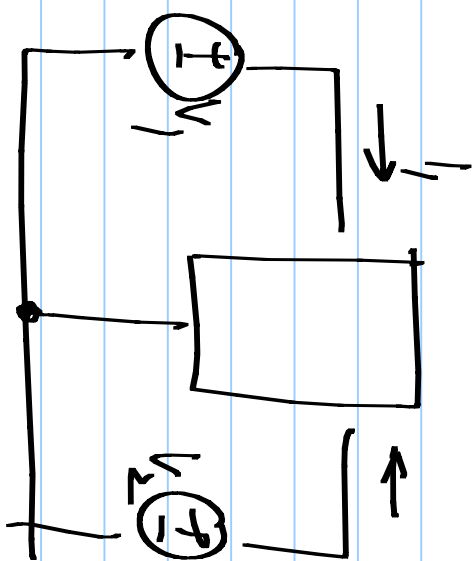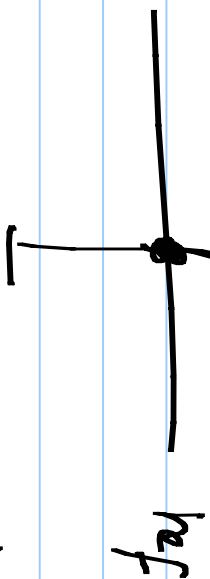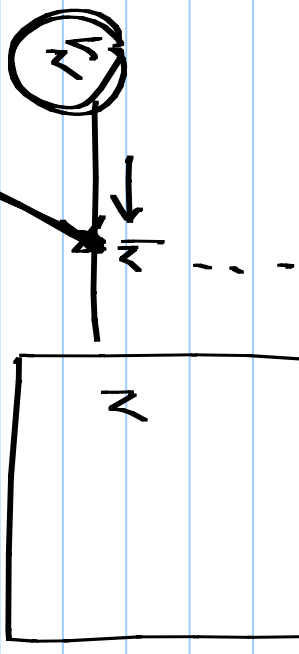

$$(v_1 - v_N) i_1 + (v_2 - v_N) i_2 - \dots$$