
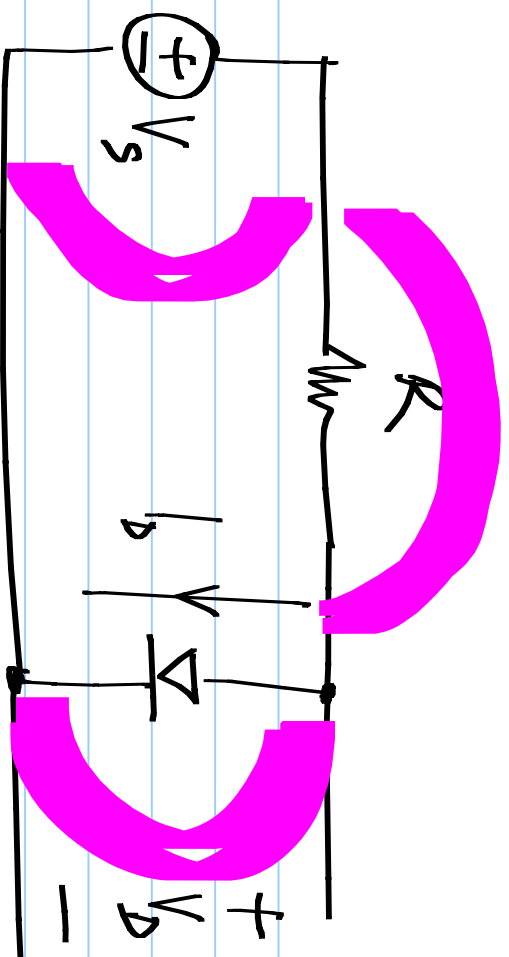


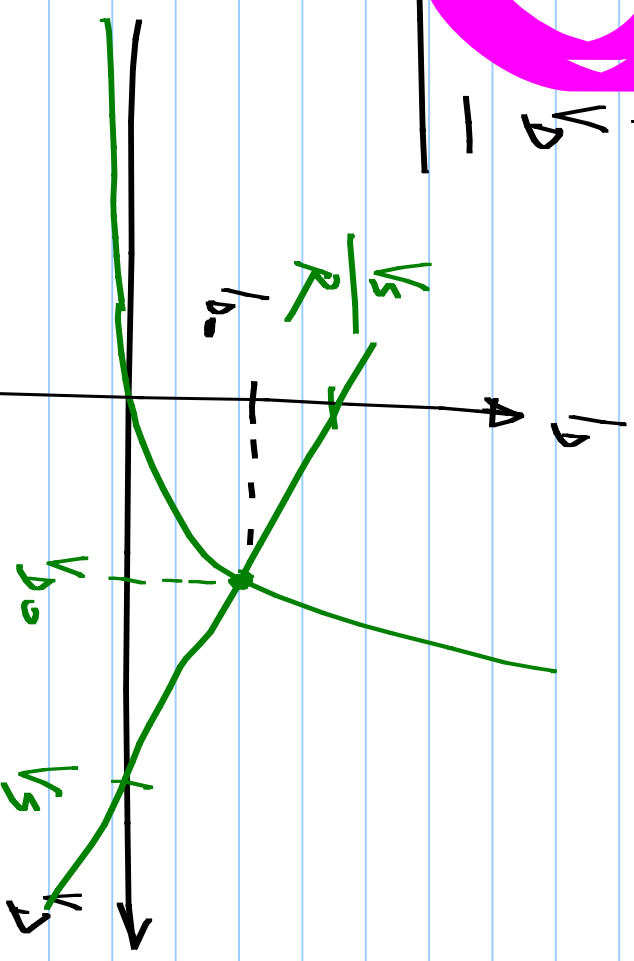

$V_s = 3V$ operating point

$$V = V_d + I_d \cdot R$$

$$I_d = I_s \left[\exp\left(\frac{V_d}{V_T}\right) - 1 \right]$$



V_{d0}, I_{d0} : operating point of the diode

V_S changes to $3.5V$

$$V_S = V_{S0} + \Delta V_S$$

$$V_D = V_{D0} + \Delta V_D$$

$$V_{S0} = I_{S0} R + V_{D0}$$

$$I_D = \underbrace{I_{D0}}_{\text{op. point}} + \underbrace{\Delta I_D}_{\text{increment}}$$

$$I_{D0} = I_S \left[\exp \left(\frac{V_{D0}}{V_T} \right) - 1 \right]$$

op. point increment

$$V_{S0} + \Delta V_S = (I_{D0} + \Delta I_D) R + V_{D0} + \Delta V_D$$

$$I_{D0} + \Delta I_D = I_S \left[\exp \left(\frac{V_{D0} + \Delta V_D}{V_T} \right) - 1 \right]$$

higher order term

$$I_S \left[\exp \left(\frac{V_{D0}}{V_T} \right) - 1 + \frac{\Delta V_D}{V_T} \exp \left(\frac{V_{D0}}{V_T} \right) + \dots \right]$$

$$V_S = I_D R + V_D \quad \Delta I_D \cdot R_D$$

①

$$\Delta V_S = \Delta I_D \cdot R + \Delta V_D$$

$$\Delta I_D = I_S \left[\frac{1}{V_T} \exp\left(\frac{V_{D0}}{V_T}\right) \cdot \Delta V_D + \text{higher order terms} \right]$$

~~terms~~
≪ first order


②

$$\Delta I_D = \left[\frac{I_S}{V_T} \cdot \exp\left(\frac{V_{D0}}{V_T}\right) \cdot \Delta V_D \right] \cdot \Delta V_D$$


term

Linear equation in $\Delta V_D, \Delta I_D$ — easy to solve
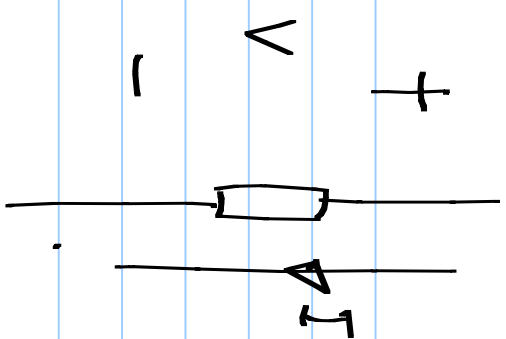
$$\Delta I_j = \left[\frac{I_s}{V_T} \exp\left(\frac{V_{D0}}{V_T}\right) \right] \Delta V_D$$



$$I = f(V)$$

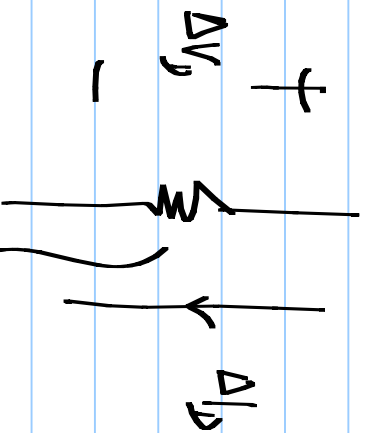

$$\gamma = \frac{V_T}{I_s \exp\left(\frac{V_{D0}}{V_T}\right)}$$

$$I = f(V)$$

$$I = I_0 + \Delta I$$


$$V = V_0 + \Delta V$$

$$I_0 = f(V_0)$$

$$I_0 + \Delta I = f(V_0 + \Delta V)$$

$$= \cancel{f(V_0)} + f'(V_0) \cdot \Delta V$$

$$V = V_0$$

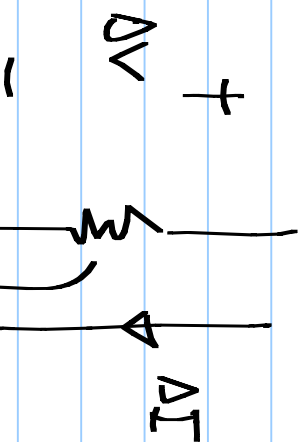

$$\Delta I = f'(V_0) \cdot \Delta V$$

$$r = \frac{f'(V_0)}{f'(V_0)}$$

$$V = I R$$


$$V_o = I_o R$$

$$V_o + \Delta V = (I_o + \Delta I) R$$



$$\Delta V = \Delta I \cdot R$$

$$\Delta V_s = \Delta I_D (R + r_d)$$

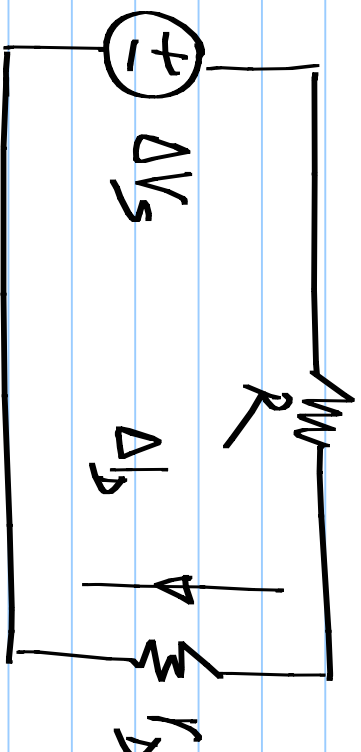


incremental eq.

Analysis of nonlinear circuits.


- * Evaluate operating pt. — set of nonlinear equations
- * Obtain the equivalent circuit @ operating point
- * Calculate increments from the incremental equivalent ckt.

"
increments are small" $\rightarrow$ higher order terms

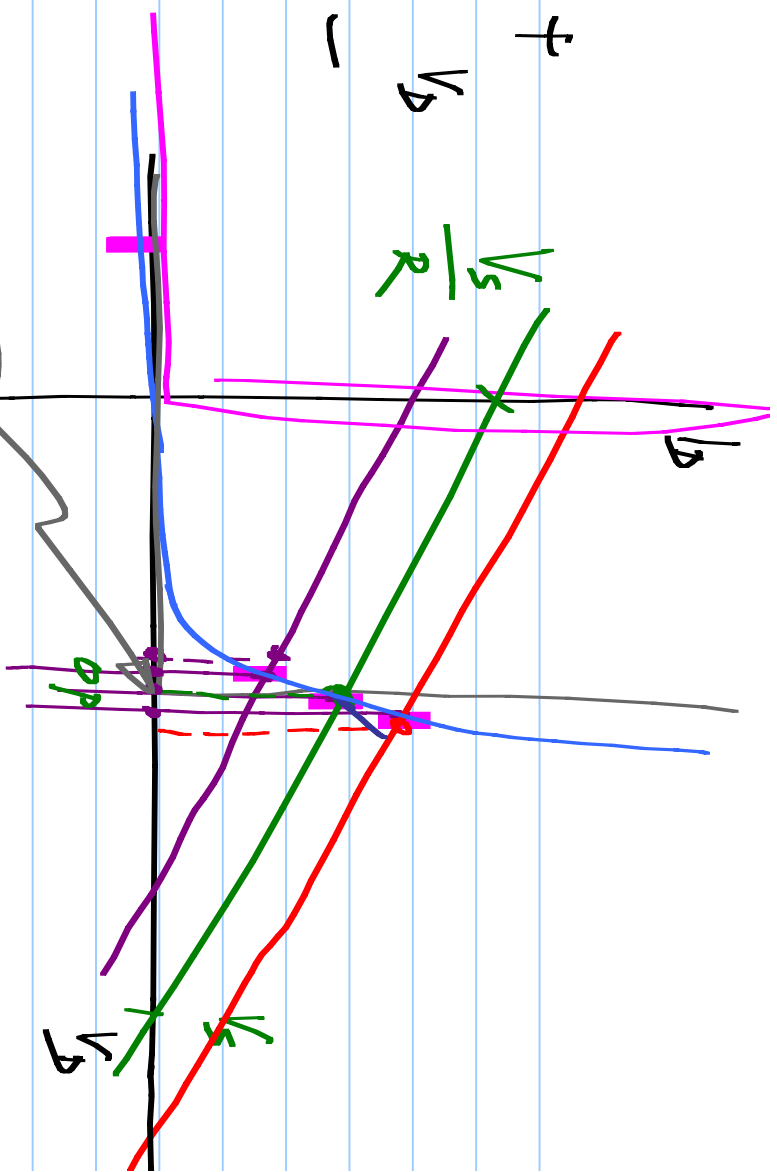Small signal incremental equivalent negligible.



$$= f(x) + f'(x) \cdot \Delta x$$

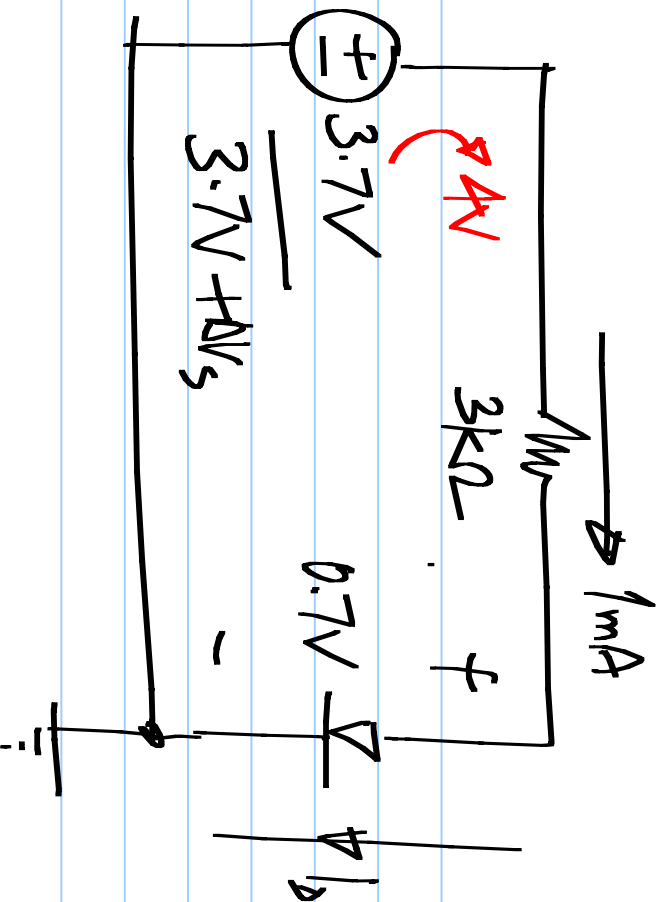

$$I_s = \frac{I_f}{\underbrace{I_s \exp\left(\frac{V_0}{V_t}\right)}} = \frac{I_f}{\underbrace{\left[\exp\left(\frac{V_0}{V_t}\right) \right] \times \cancel{-1}}}$$

$I_s = I_s$

