

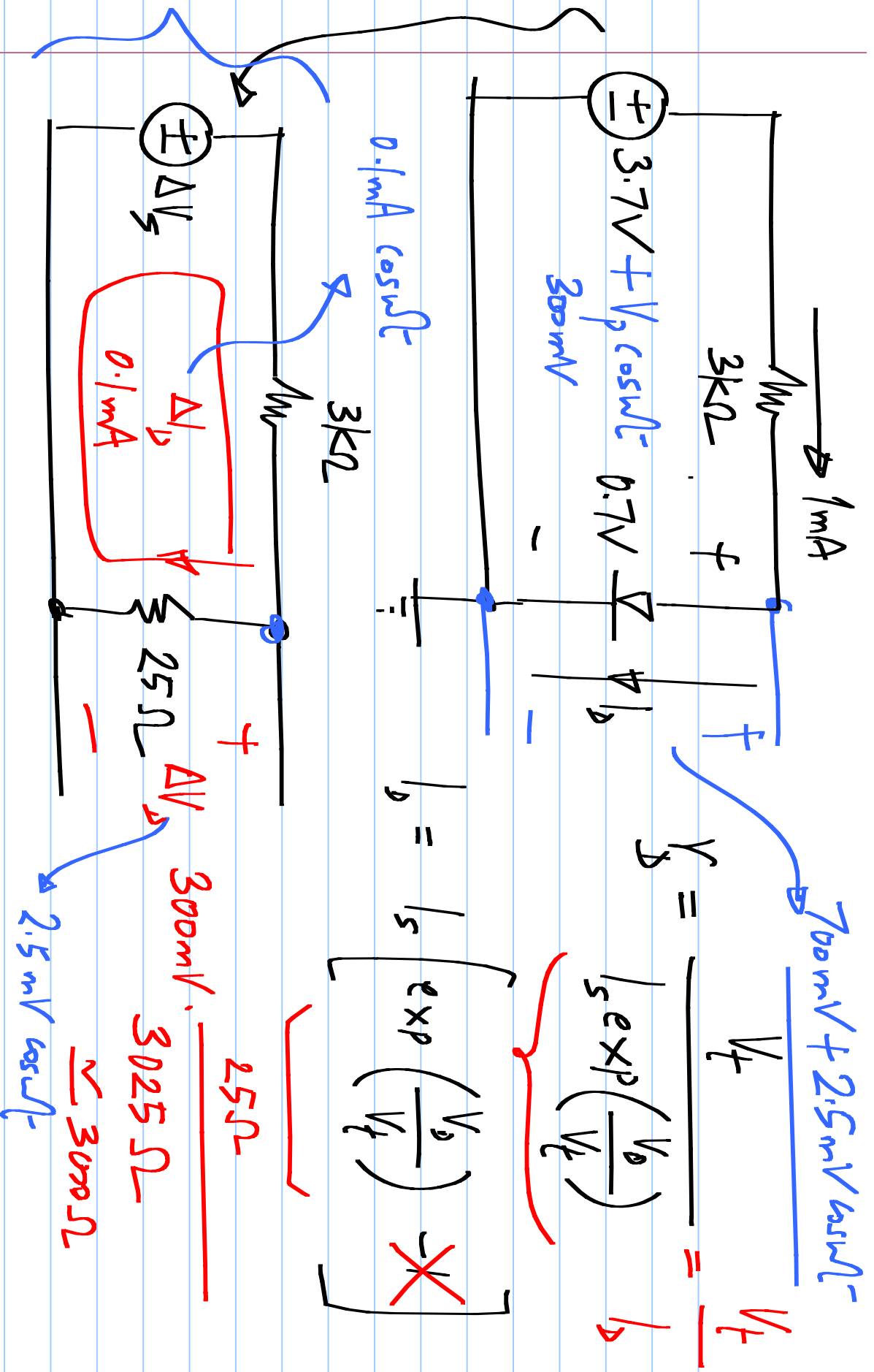
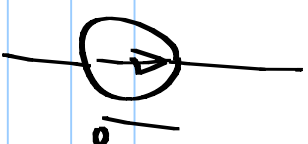
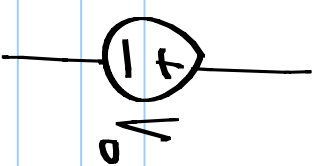


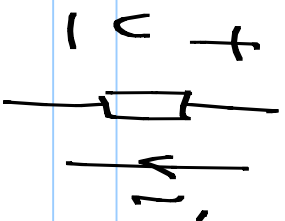

Element

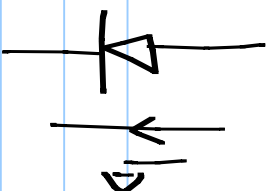



$$I = f(V)$$

incr.

eq. circuit



$$V_D = \frac{V_t}{I_D}$$

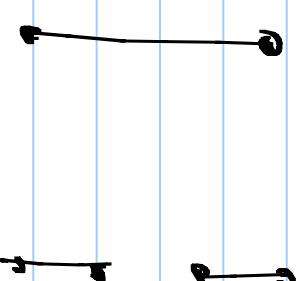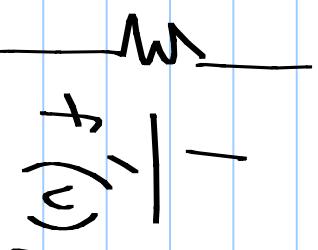



op.

Operating pt. $\equiv$ bias point

Short open
ckt.

Diode model




$$V = 0.7V$$

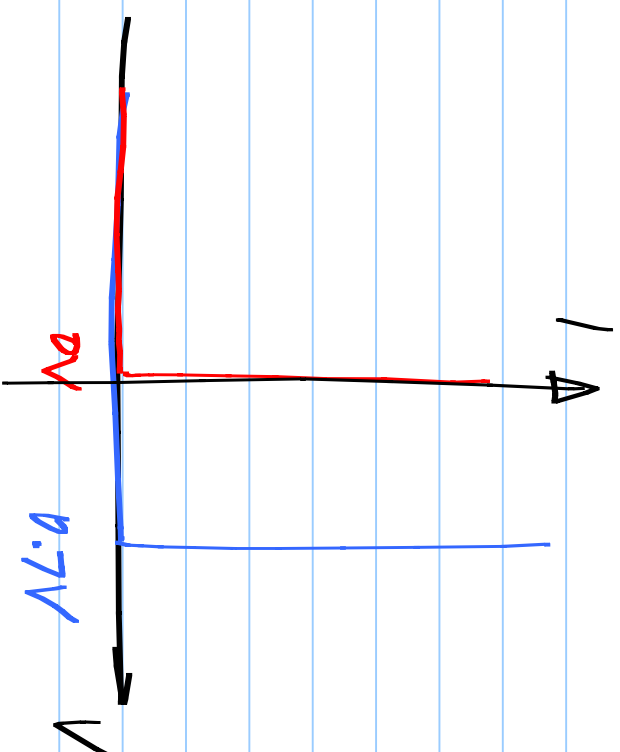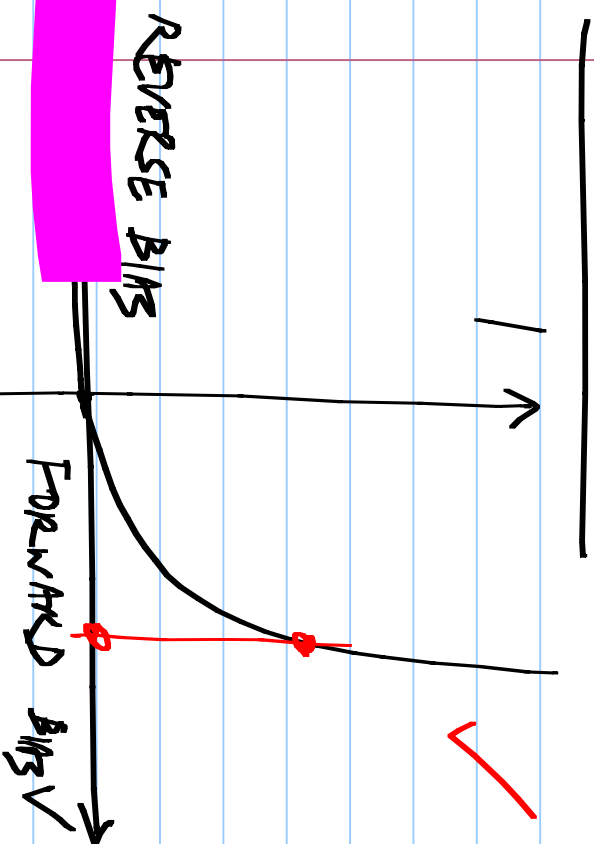

$$\approx I_s \exp\left(\frac{V}{V_T}\right)$$





$$\exp\left(\frac{V}{V_T}\right) \gg 1$$
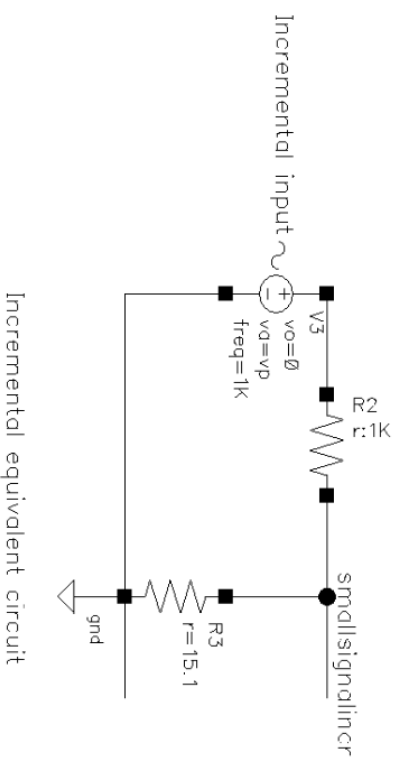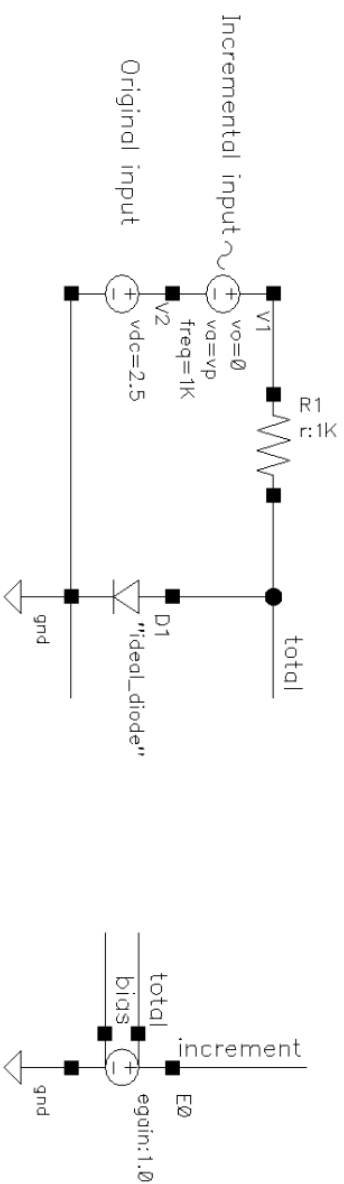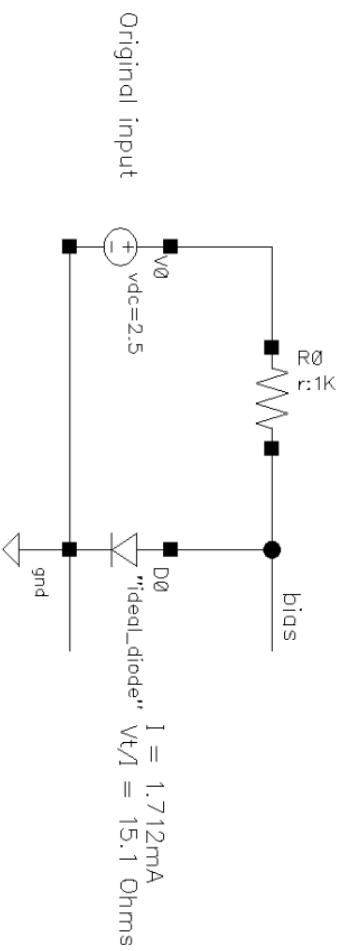
$$I = I_s \left[\exp\left(\frac{V}{V_T}\right) - 1 \right]$$



300mV increment in the input source


Transient Response

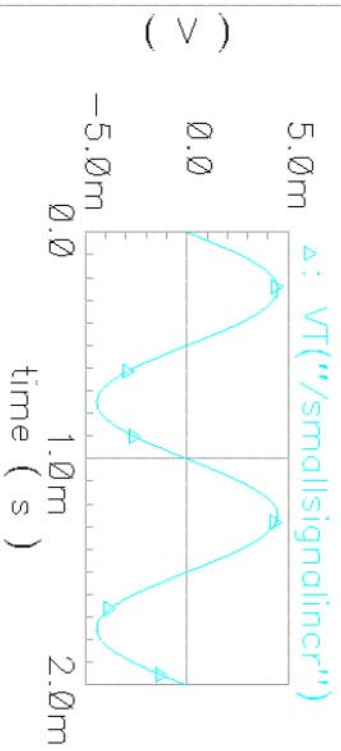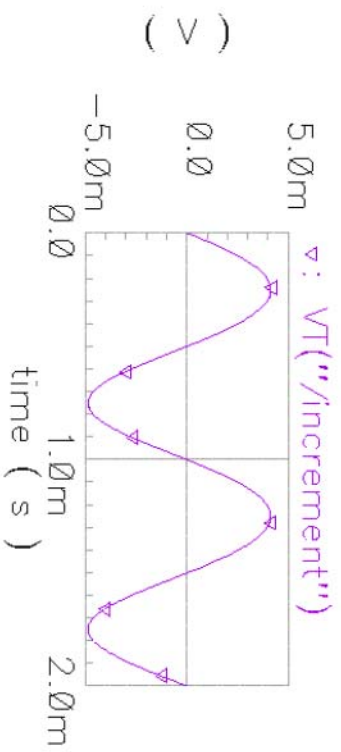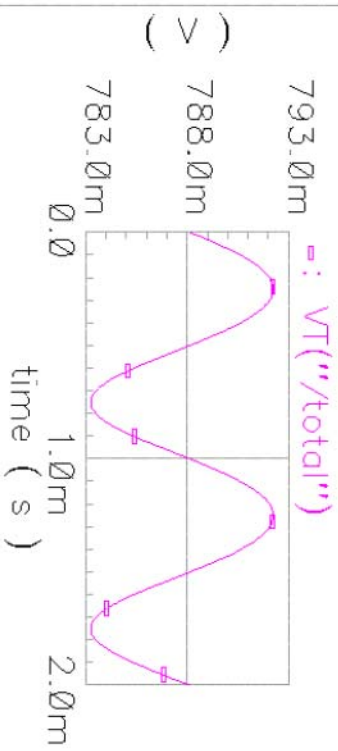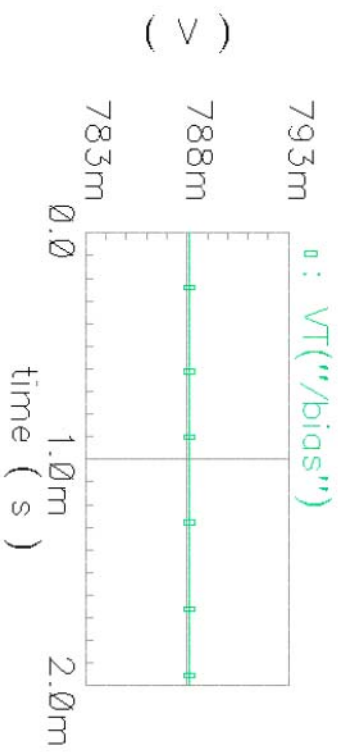

Transient Response

1


0 : vp="10m";
□ : vp="10m";

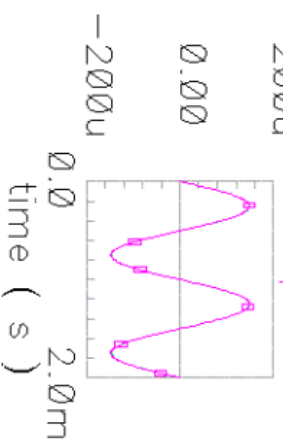

(>)

2


0 : vp="31.62"
□ : vp="31.62"

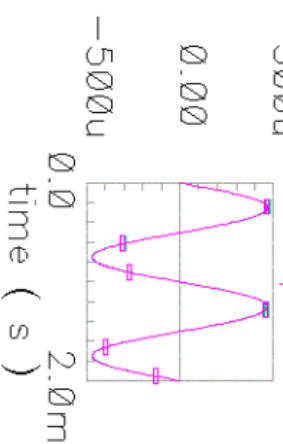

(>)

3


△ : vp="100m"
△ : vp="100m"

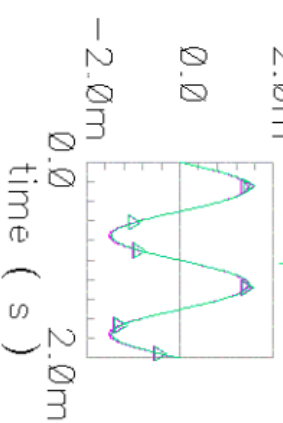

(>)

4


▽ : vp="316.2"
▽ : vp="316.2"

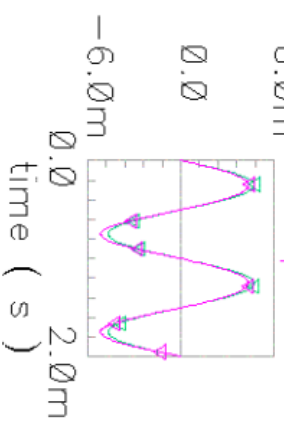

(>)

5

□ : vp="1";VT
□ : vp="1";VT

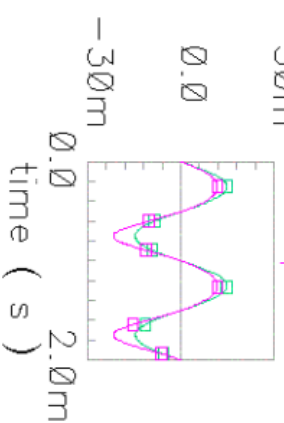


(>)


Transient Response

6


0 : vp="2.5";
□ : vp="2.5";

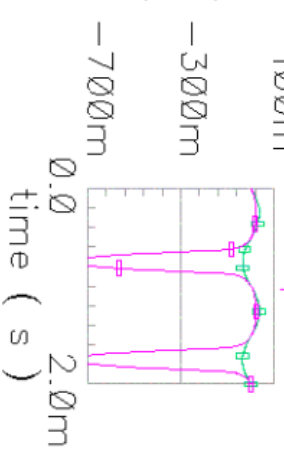


(>)

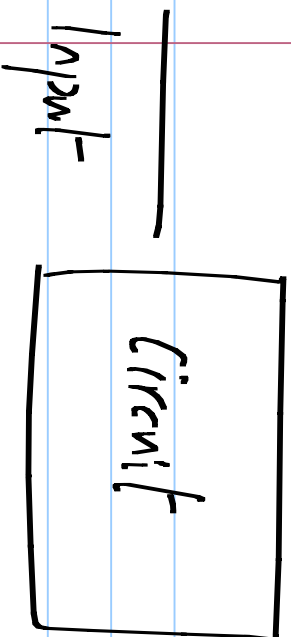

Operating point

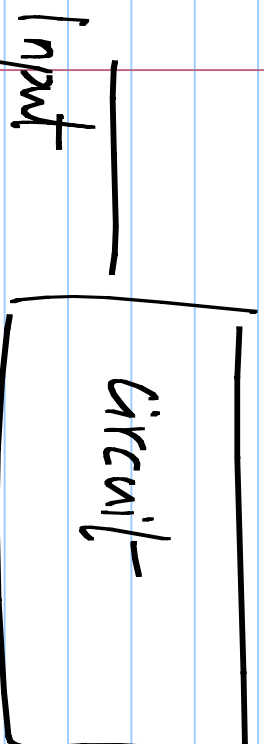

$\equiv$

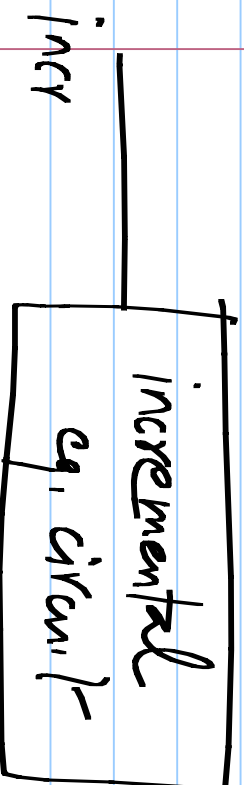

$\oplus$


$\rightarrow$

}


equal if
small signal

assumption

is valid

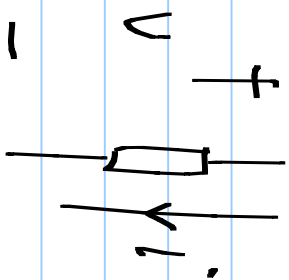

$$i' = f(v)$$

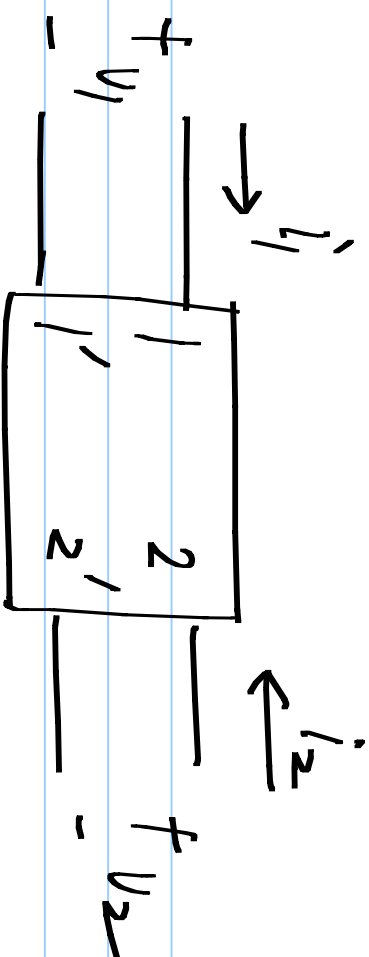

$$i_1' = y_{11} v_1 + y_{12} v_2$$

$$i_2' = y_{21} v_1 + y_{22} v_2$$

$$i_1' = f_1(v_1, v_2)$$

$$i_2' = f_2(v_1, v_2)$$

$$I_1 = f_1(V_1, V_2) \rightarrow \cancel{I_1} + \Delta I_1 = f_1(V_1 + \Delta V_1, V_2 + \Delta V_2)$$

$$I_2 = f_2(V_1, V_2) \rightarrow \cancel{I_2} + \Delta I_2 = f_2(V_1 + \Delta V_1, V_2 + \Delta V_2)$$

$$\cancel{f_1(V_1, V_2)} + \frac{\partial f_1}{\partial V_1} \Big|_{op} \cdot \Delta V_1 + \frac{\partial f_1}{\partial V_2} \Big|_{op} \cdot \Delta V_2 + \text{higher order terms}$$


$$\cancel{f_2(V_1, V_2)} + \frac{\partial f_2}{\partial V_1} \Big|_{op} \cdot \Delta V_1 + \frac{\partial f_2}{\partial V_2} \Big|_{op} \cdot \Delta V_2 + \text{higher order terms}$$

$$\Delta f_1 = \left\{ \frac{\partial f_1}{\partial v_1} \right|_{op} \cdot \Delta v_1 + \frac{\partial f_1}{\partial v_2} \bigg|_{\Delta v_2} \bigg\}$$

Incremental
y-parameters
of the
nonlinear
2. port

$$\Delta f_2 = \frac{\partial f_2}{\partial v_1} \bigg|_{op} \cdot \Delta v_1 + \frac{\partial f_2}{\partial v_2} \bigg|_{op} \cdot \Delta v_2$$

$$y_1 = \frac{\partial f_1}{\partial v_1} \bigg|_{op} \cdot y_{12} = \frac{\partial f_1}{\partial v_2} \bigg|_{op} \cdot y_{21} = \frac{\partial f_2}{\partial v_1} \bigg|_{op} \cdot y_{22} = \frac{\partial f_2}{\partial v_2} \bigg|_{op}$$

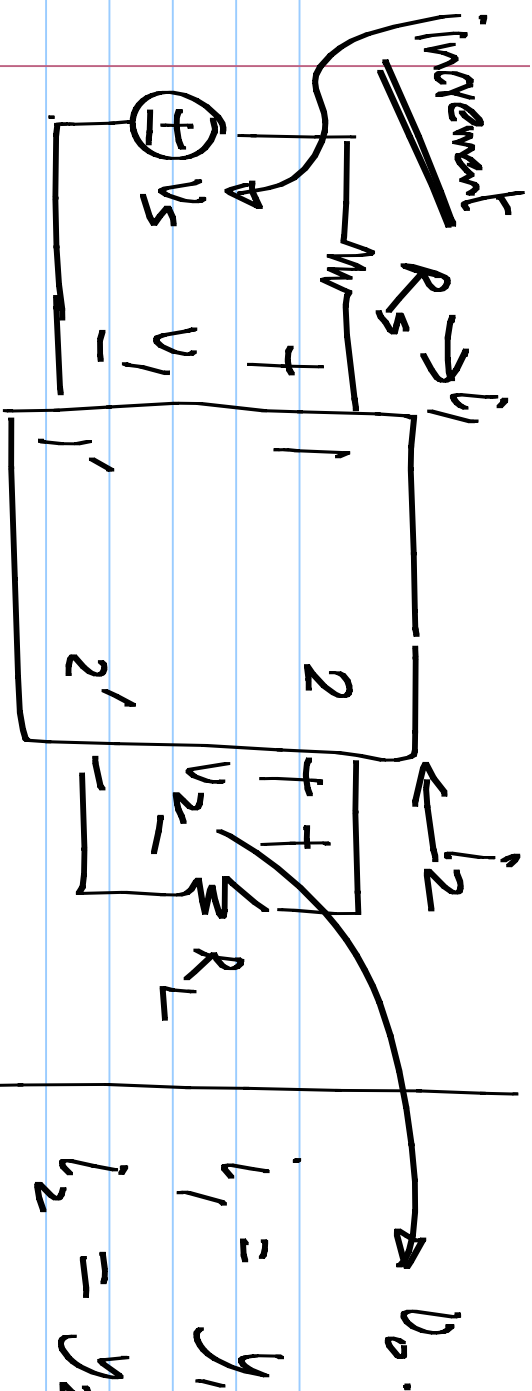

$$i_1 = y_{11} v_1 + y_{12} v_2$$

$$i_2 = y_{21} v_1 + y_{22} v_2$$

inv. y

parameters

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$v_s = i_1 R_s + v_1$$

$$v_2 = -i_2 R_L$$