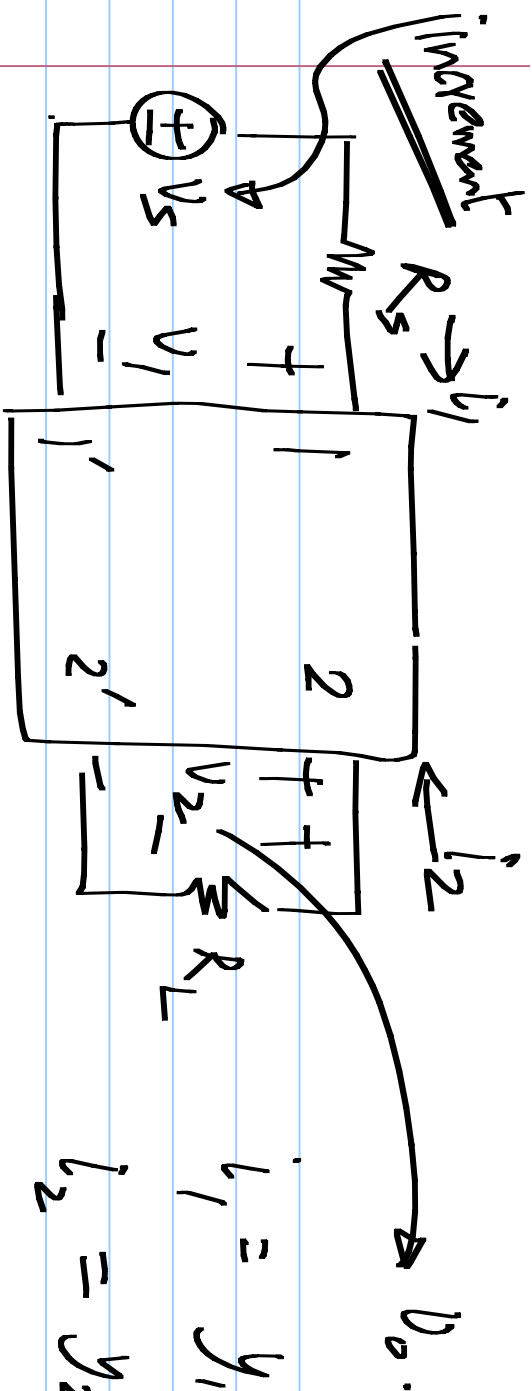




$$i_1' = y_{11} v_1 + y_{12} v_2$$

$$i_2 = y_{21} v_1 + y_{22} v_2$$

inv. y parameters

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$v_s = i_1' R_s + v_1$$

$$v_2 = -i_2 R_L$$

$$\frac{v_2}{v_s} = \frac{-y_{21} R_L}{(1 + y_{22} R_L)(1 + y_{11} R_s) - y_{12} y_{21} R_L R_s}$$

$$\frac{v_2}{v_s} = \frac{-y_{21} R_L}{(1 + y_{22} R_L)(1 + y_{11} R_s) - y_{12} y_{21} R_L R_s}$$

$$\frac{V_2}{V_S} = \frac{-Y_{21} R_L}{(1 + Y_{11} R_S)(1 + Y_{22} R_L) - Y_{12} Y_{21} R_L R_S}$$

For high gain:



$$Y_{11} = 0$$

$$Y_{22} = 0$$




Y_{21} : large

$$Y_{12} = 0$$

To avoid instability

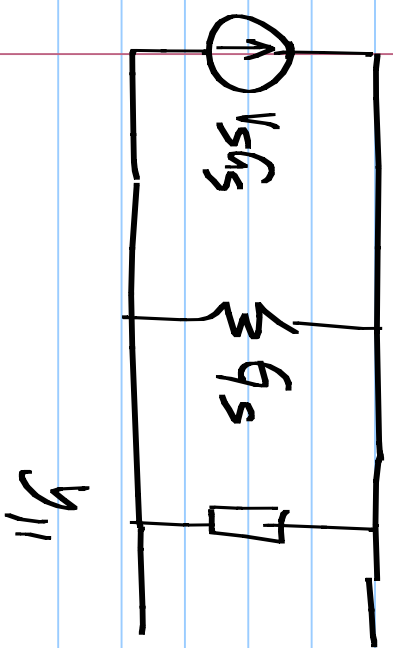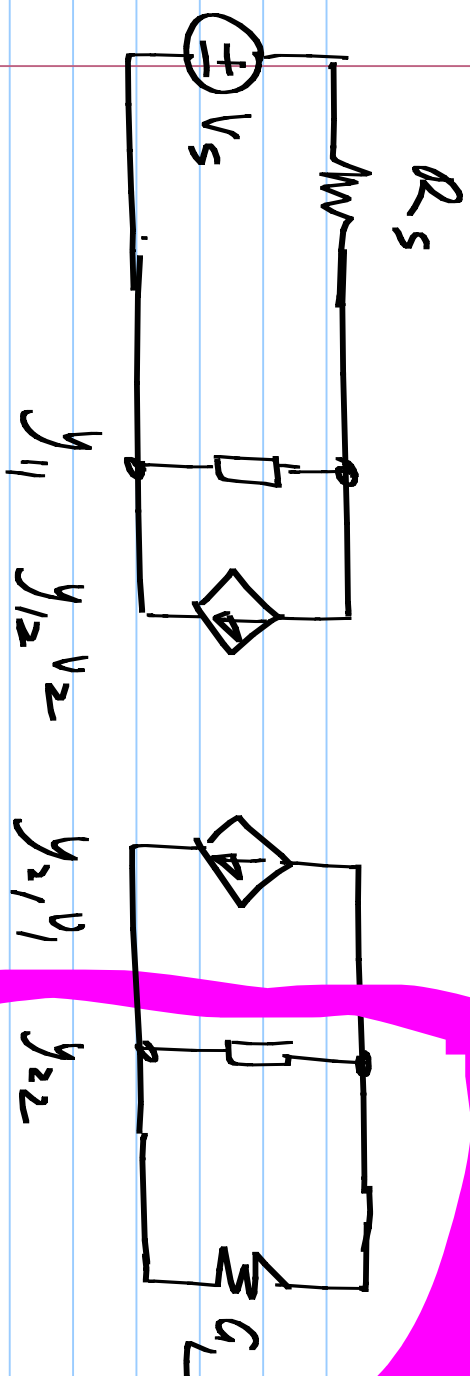

I_1 : constant

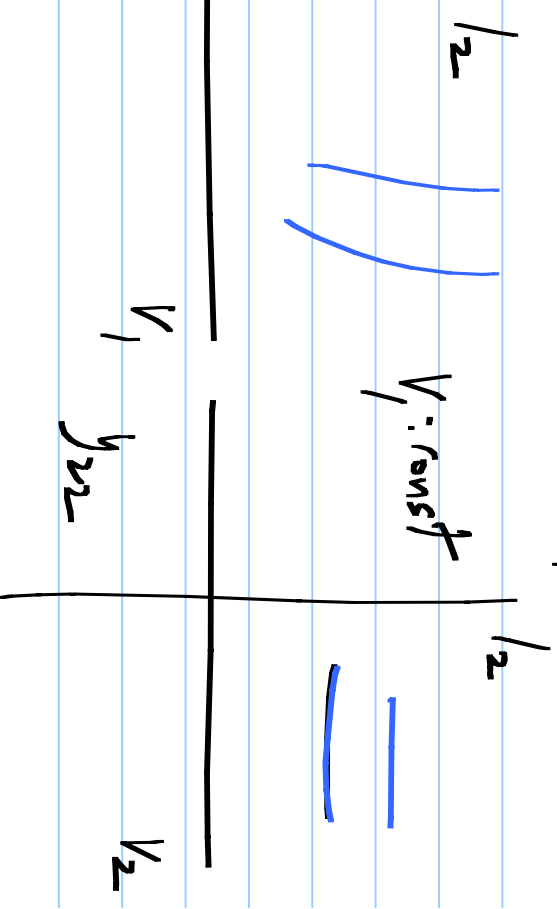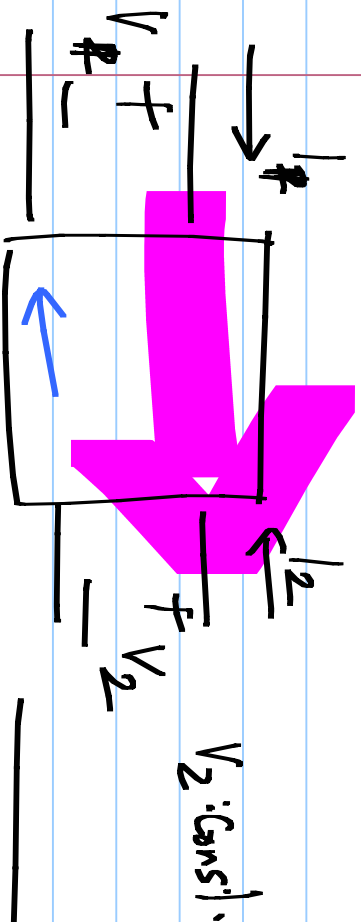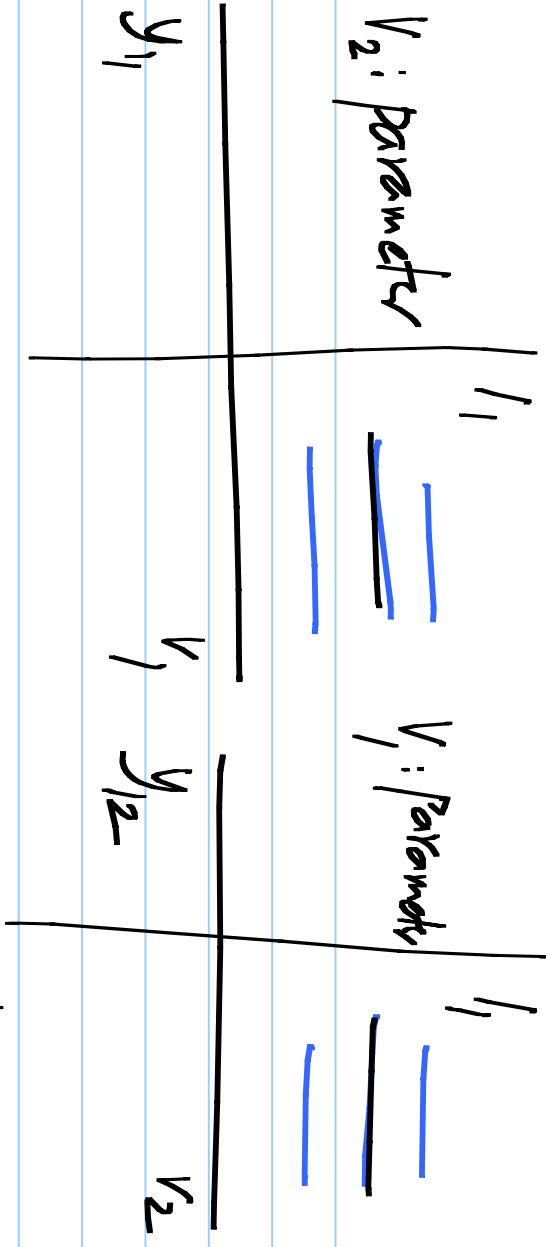

$$I_1 = f_1(V_1, V_2)$$


$$I_2 = f_2(V_1, V_2)$$

MOS (Metal - Oxide - Semiconductor) transistor

* 3 terminal device

* Ports: G-S, D-S

* $I_n = 0$ (dc)

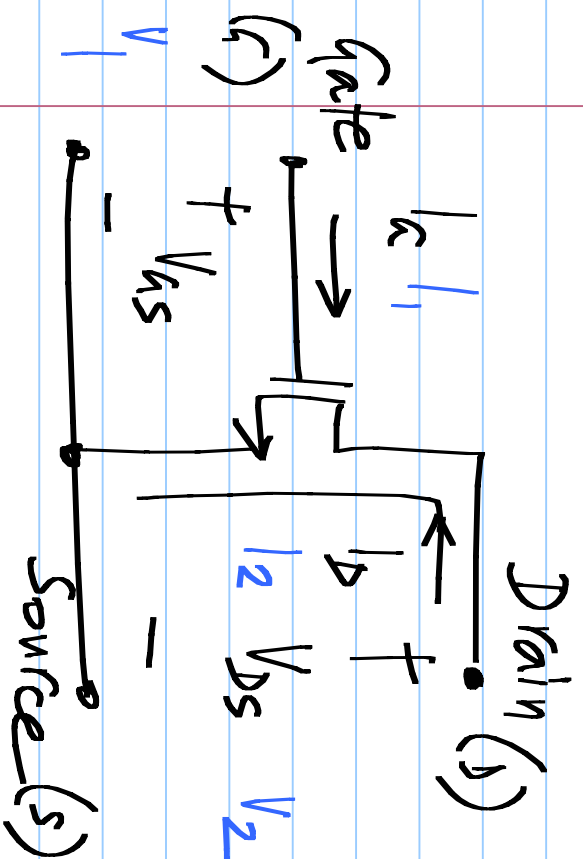

nMOS transistor

$$I_D = 0$$

$$V_{GS} < V_T \quad \left[\begin{array}{l} \text{Threshold} \\ \text{voltage} \end{array} \right]$$

$$= \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$V_{GS} > V_T$$

$$V_{DS} < V_{GS} - V_T$$

$$= \frac{\mu C_{ox}}{2} \frac{W}{L} \left[(V_{GS} - V_T)^2 \right]$$


$$V_{GS} > V_T$$

$$V_{DS} > V_{GS} - V_T$$

$$\left[V_{DS} \geq 0 \right]$$

$$| = |_y = 0$$

I_D

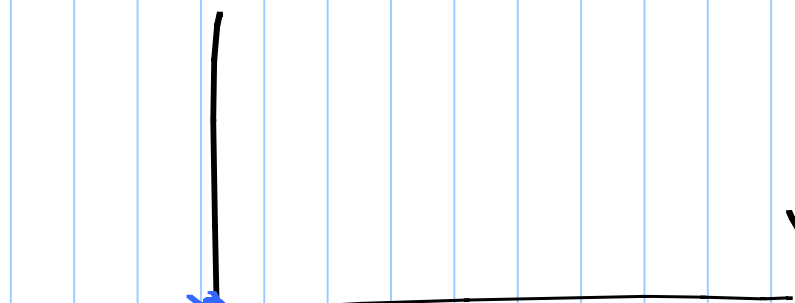

$$V_{GS} = V_{GS3}$$

$$V_{GS} = V_{GS2}$$

$$V_{GS} = V_{GS1}$$

V_{DS}