

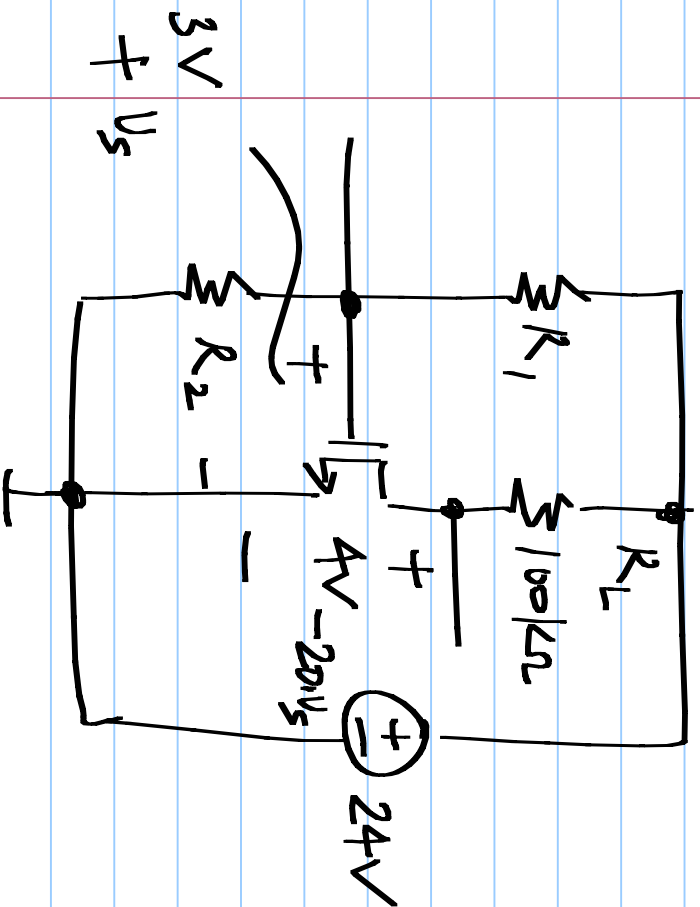


$$V_{a5} = 3V, \quad V_{b5} = 4V$$

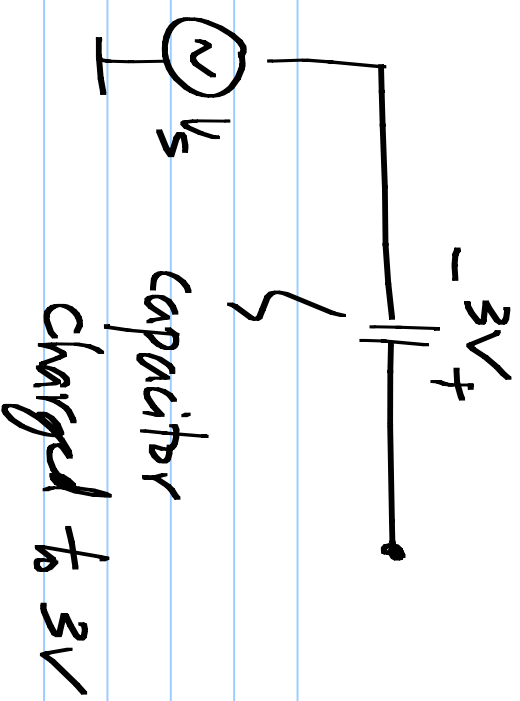

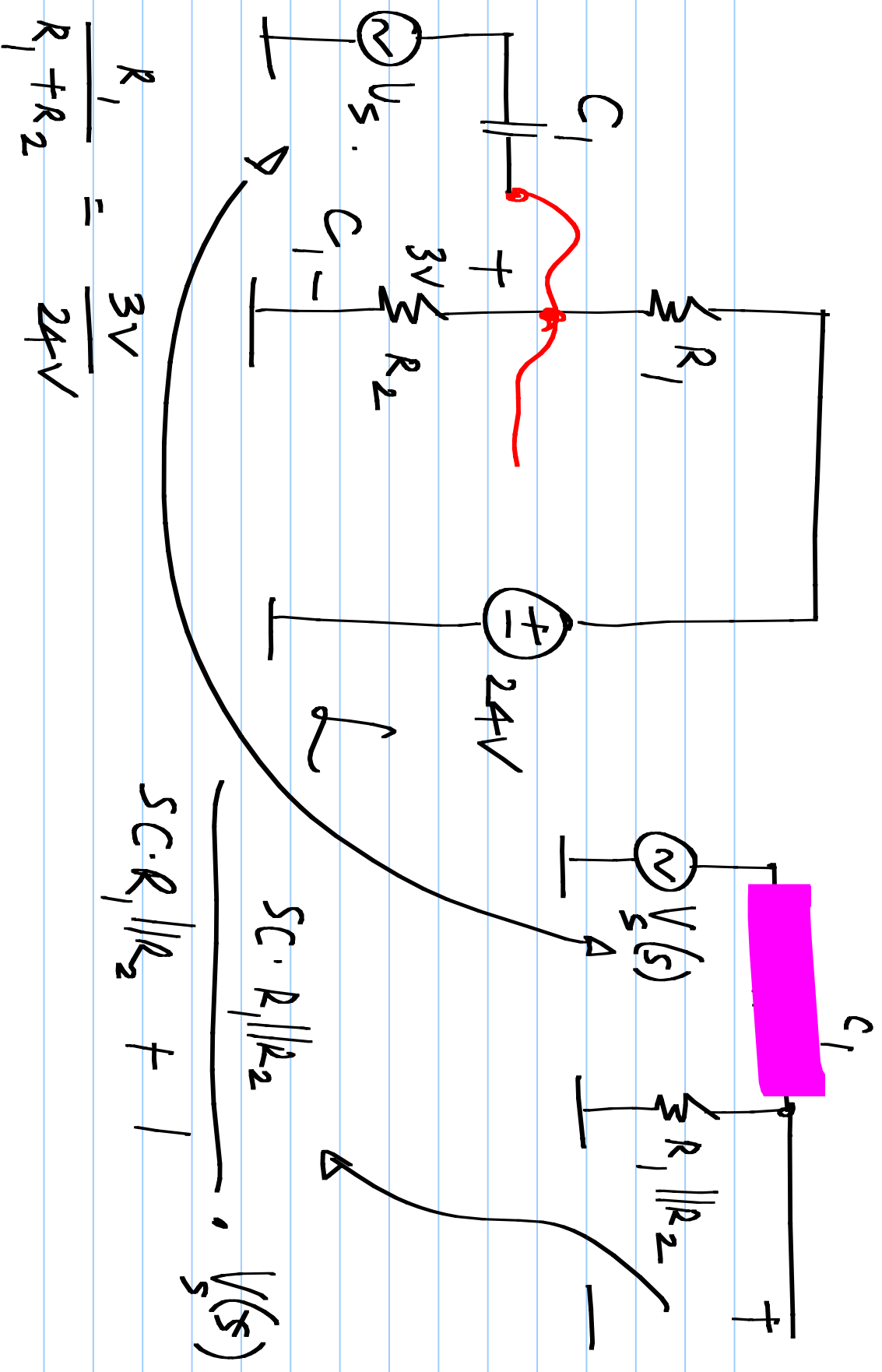
$$\frac{R_2}{R_1 + R_2} = \frac{3V}{24V}$$




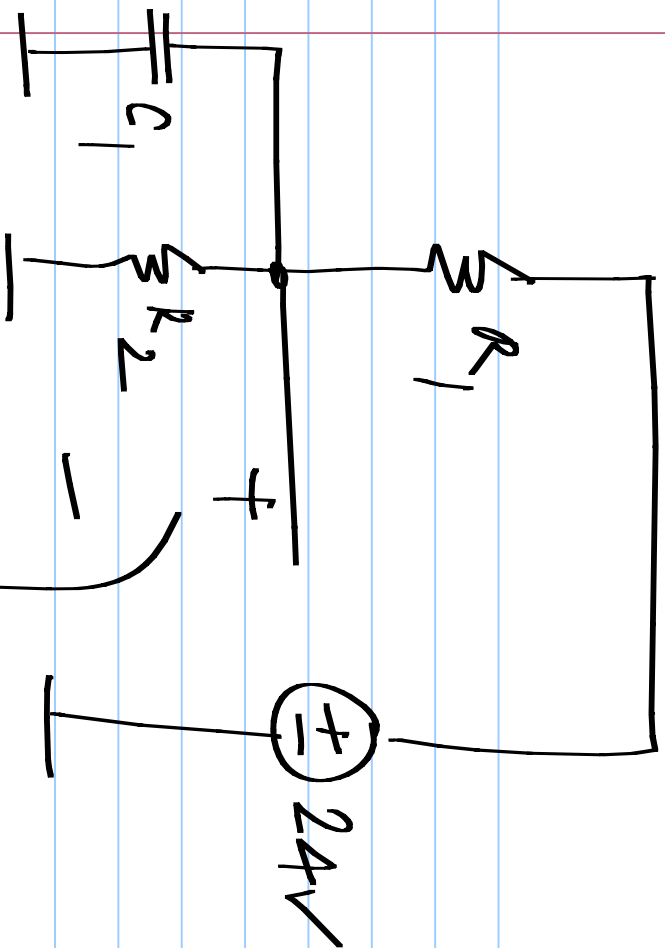
$$\frac{\exp(st)}{s} \rightarrow \boxed{H(s)} \rightarrow H(s) \exp(st)$$



$$\frac{24V \cdot \frac{1}{sC_1} \parallel R_2}{\frac{1}{sC_1} \parallel R_2 + R_1} = 24V \frac{R_2}{R_2 + R_1}$$

Voltage across $R_2 =$ 3V +
{Laplace domain} due to

24V source


$$V_s(s) \cdot \frac{sc(R_1 || R_2)}{1 + sc(R_1 || R_2)}$$

$$V_{R_2} \approx 3V + v_s(t)$$

u_s : 1 kHz sinusoid

$$s = j \cdot 2\pi \cdot 10^3 \text{ rad/s}$$

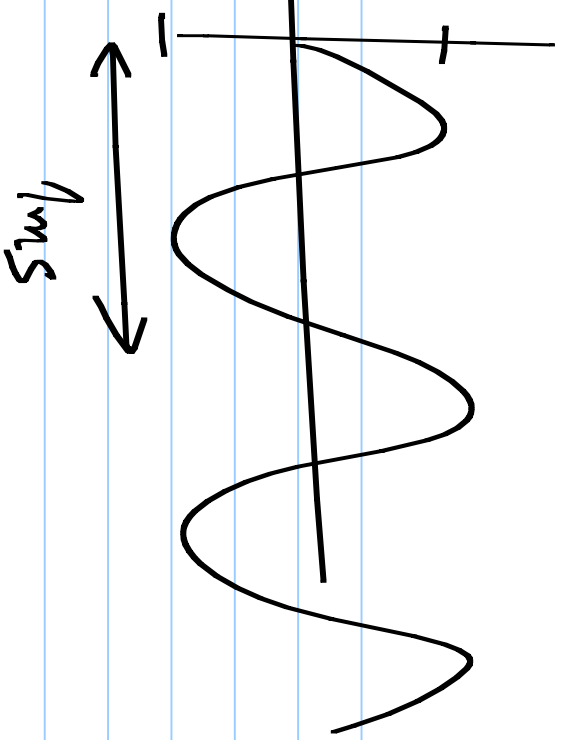
$$\exp(st) \xrightarrow{H(s)} \exp(st) H(s)$$



$$s = \sigma + j\omega$$

$$\exp(\sigma t + j\omega t)$$

$$\exp(\sigma t) \exp(j\omega t)$$

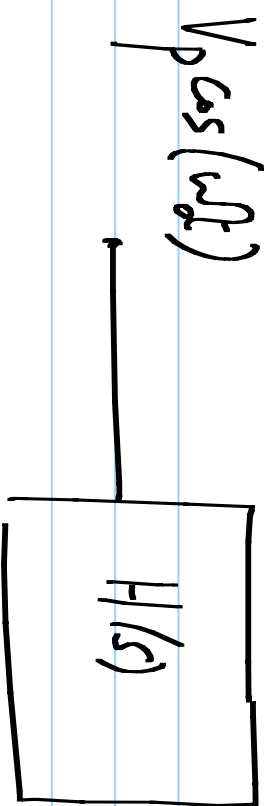

$$\frac{1}{\rho} |H(j\omega)| \cdot \cos(\omega t + \angle H(j\omega))$$

$$V_{R_2}(j\omega) = 3V + \frac{j\omega C_1(R_1 \parallel R_2)}{1 + j\omega C_1(R_1 \parallel R_2)}$$

$$\omega C_1(R_1 \parallel R_2) \gg 1 \quad R_1 \parallel R_2 \gg \frac{1}{\omega C_1}$$

$$C_1 \gg \frac{1}{\omega(R_1 \parallel R_2)}$$

$$\frac{\omega C_1(R_1 \parallel R_2)}{\sqrt{1 + \omega^2 C_1^2 (R_1 \parallel R_2)^2}}$$