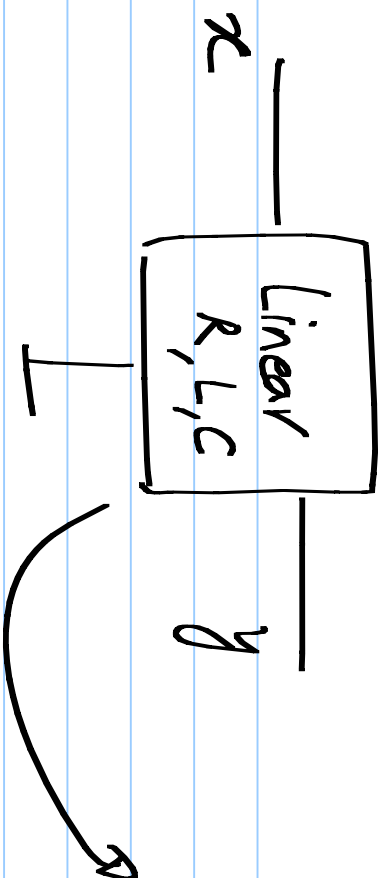




$$\sum_{k=0}^N a_k \frac{d^k y}{dt^k} = \sum_{k=0}^M b_k \frac{d^k x}{dt^k}$$

$$\sum_{k=0}^N a_k \frac{d^k y}{dt^k} = 0$$

$$\sum c_k \exp(p_k t)$$

LTI system : Linear diff. equation w/ constant
(R, L, C) coefficients

$$\sum_{k=0}^N a_k \frac{dy}{dt}^k = \sum_{k=0}^N b_k \frac{dx}{dt}^k$$

Stable
amplifiers
go to
zero

$$y(t) = \left\{ \begin{array}{l} \text{Steady state} \\ \text{particular} \\ \text{solution} \end{array} \right\} + \left\{ \begin{array}{l} \text{transient} \\ + \\ \text{homogeneous solution} \end{array} \right\}$$

forced response + ~~Natural response~~

$$= \text{Zero input response} + \text{Zero state response}$$


$$y(t) = \left\{ \begin{array}{l} \text{Steady state} \\ \text{particular solution} \end{array} \right\} + \left\{ \begin{array}{l} \text{transient} \\ \text{homogeneous solution} \end{array} \right\}$$


if $x(t) = e^{st}$ forced response + ~~natural response~~

$s = j\omega$

$$\text{Forced response} = \underbrace{H(s)} \cdot e^{st}$$


Transfer function

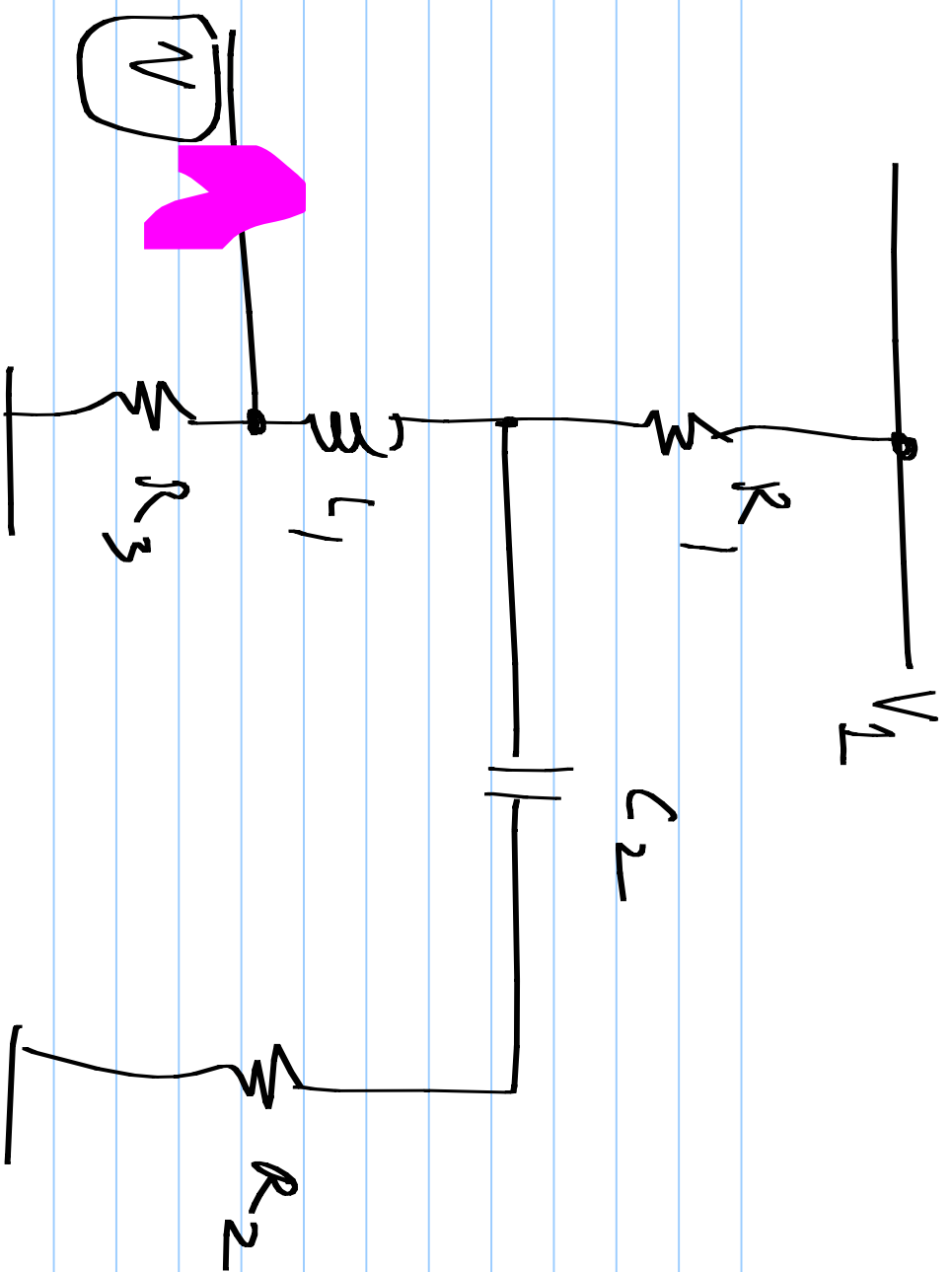

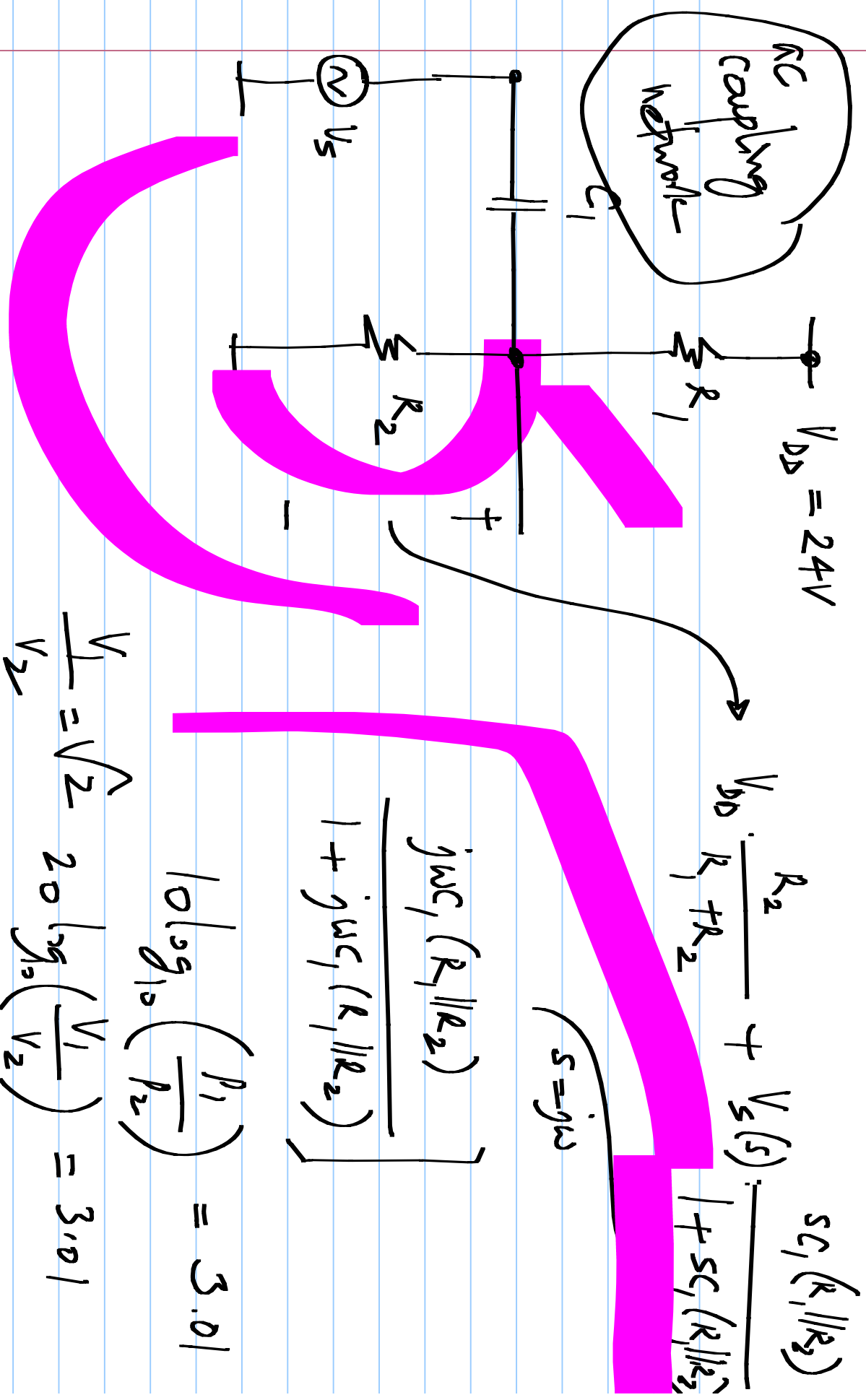

$$H(j\omega) = \frac{j\omega C_1(R_1 || R_2)}{1 + j\omega C_1(R_1 || R_2)}$$

$$\frac{j1}{1+j1}$$

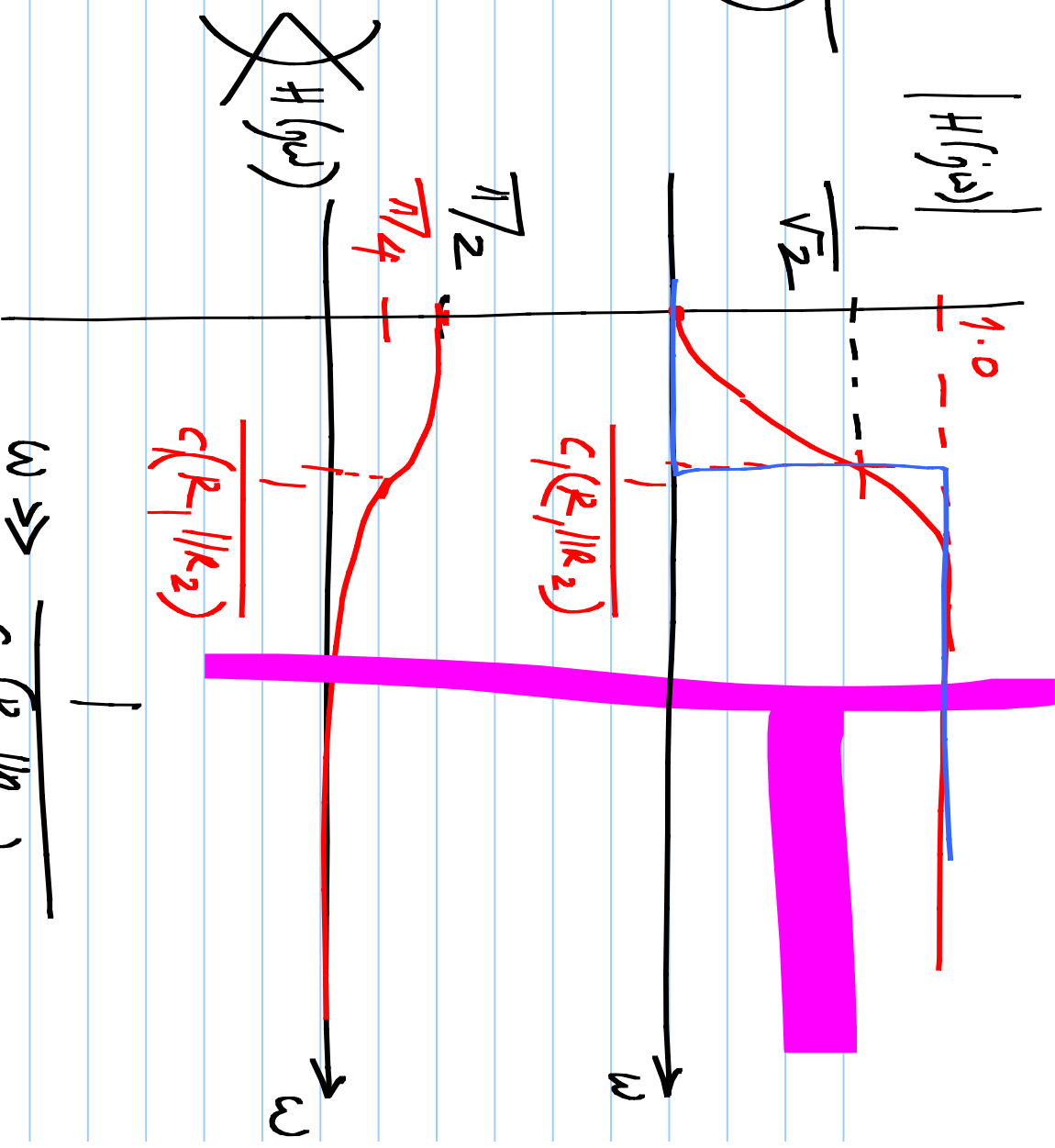

$$\frac{V_{AS}(j\omega)}{V_S(j\omega)}$$

$$\omega \gg \frac{1}{C_1(R_1 || R_2)}$$