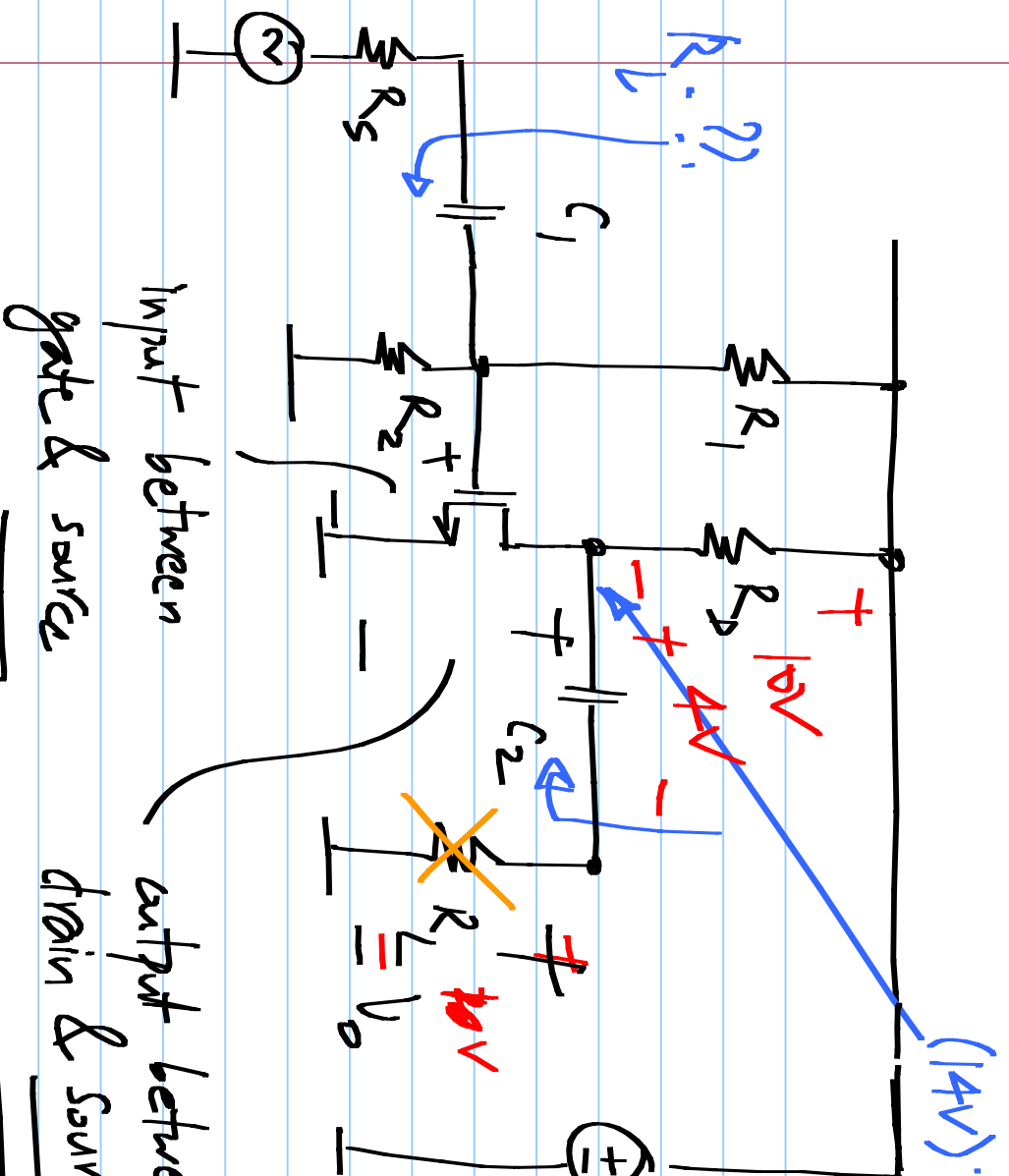




COMMON SOURCE AMPLIFIER

$$-\frac{I_{DQ}}{g_m} < V_S < \frac{V_{DD} - V_{DSQ} + V_T}{1 + g_m(R_D || R_L)}$$

$$-1V < V_S < \frac{2}{11}V$$

$$-20V < V_D < +10V$$

Common source amplifier;

$$\left[\begin{array}{ll} \text{Gain:} & -g_m (R_D \parallel R_L) \\ \text{Small signal } R_i: & R_1 \parallel R_2 \end{array} \right] \quad \left\{ R_1 \parallel R_2 \gg R_S \right\}$$

$$\left[\begin{array}{ll} R_o: & R_D \\ -\frac{V_{DS}}{g_m} & < V_S < \frac{V_{DSQ} - V_{th} + V_T}{1 + g_m (R_D \parallel R_L)} \end{array} \right]$$

Triode region: (linear)


$$V_{GS} > V_T \quad ; \quad V_{DS} < V_{GS} - V_T$$

$$I_D = \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$V_{DS} \ll V_{GS} - V_T$$

$$\approx \underbrace{\mu C_{ox} \frac{W}{L} (V_{GS} - V_T)}_{\text{Conductance}} V_{DS}$$
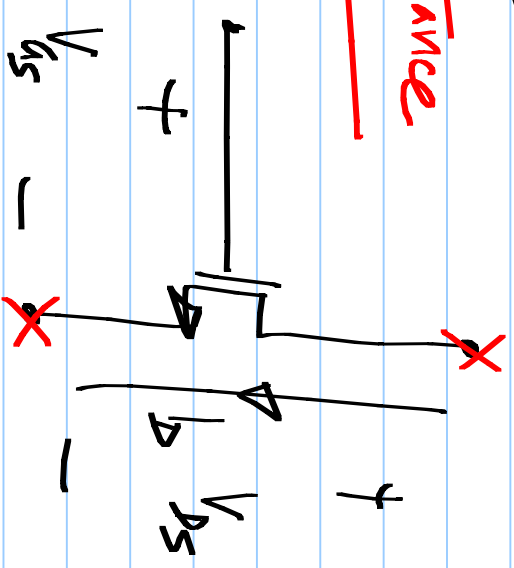
$$R_{DS} = \frac{V_{DS}}{I_D} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_T)}$$




Saturation region:

$$\lambda = 0.05 \text{ V}^{-1}$$

$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$
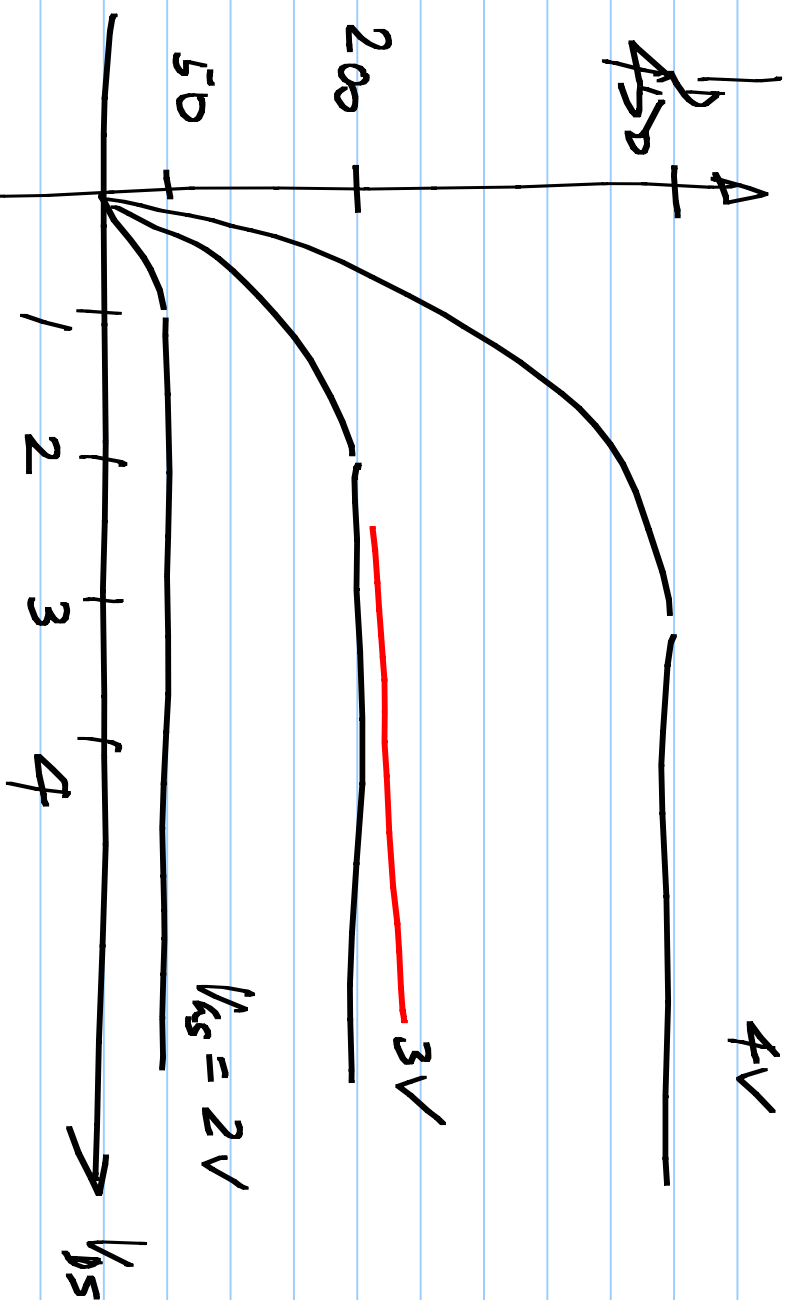
$$\left[\begin{array}{l} V_{GS} > V_T \\ V_{DS} > V_{GS} - V_T \end{array} \right]$$



gds

$$g_{22} = \frac{\partial I_D}{\partial V_{DS}} = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 \cdot \lambda = \lambda I_D$$

$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \quad \boxed{V_{DS} = \frac{1}{\lambda I_D}}$$

$$\approx \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 \quad \left. \vphantom{\frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2} \right\} \text{for op. point calculations}$$

$$r_{ds} = \frac{1}{0.05 \text{ V}^{-1} \cdot 200 \mu\text{A}} = 100 \text{ k}\Omega \quad \lambda = 0.05 \text{ V}^{-1}$$