
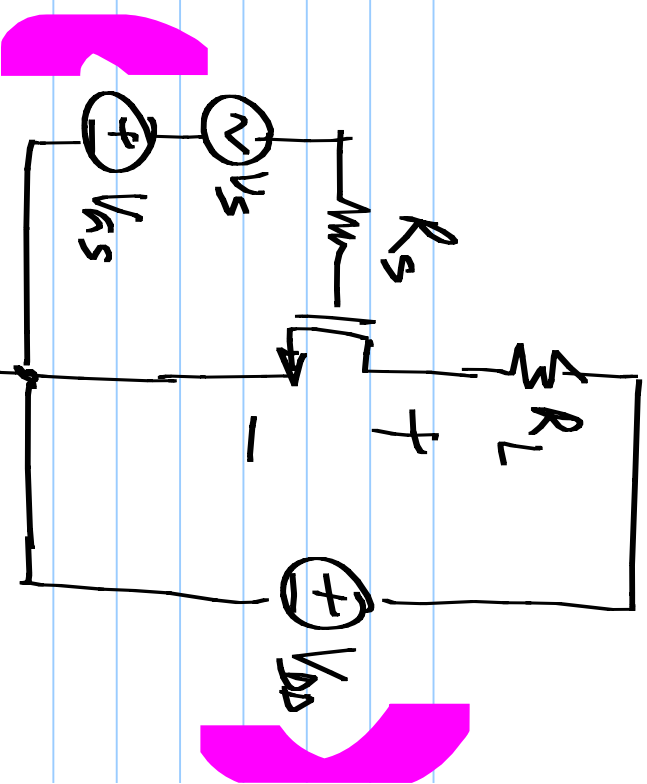
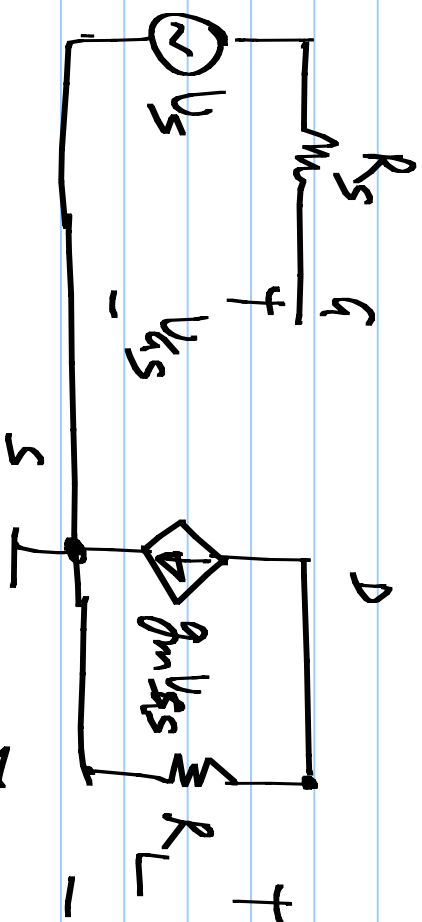


Amplifier:


$$V_o = k \cdot V_s$$

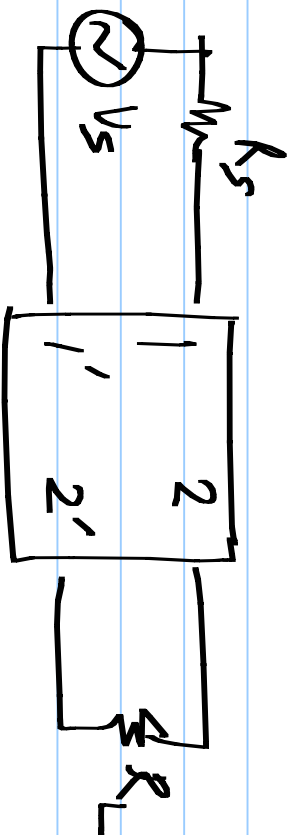

Small signal eq.

$$\frac{1}{\omega C} \ll (R_1 \parallel R_2)$$


low V

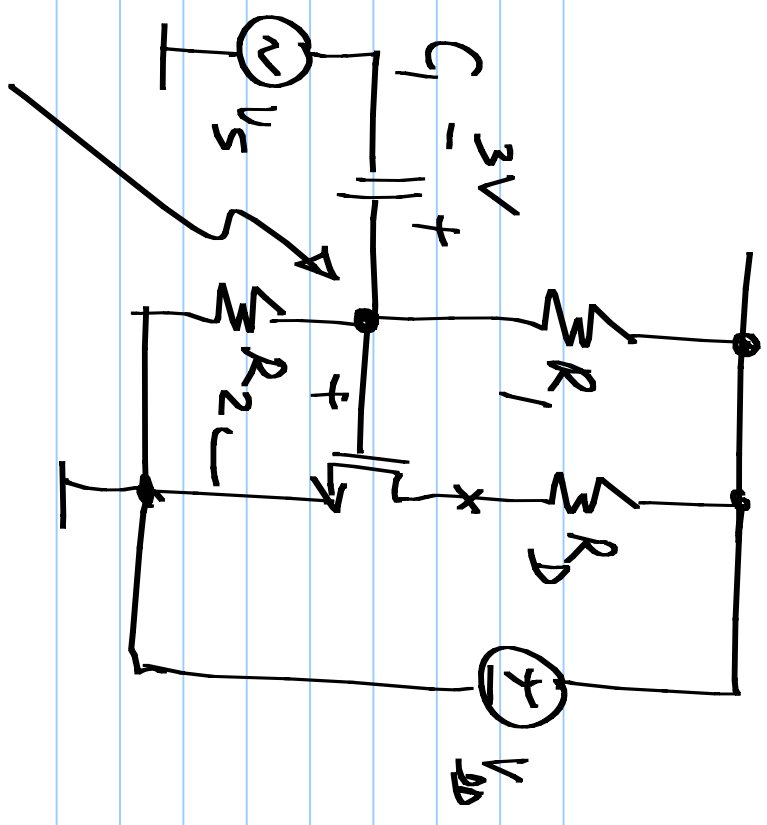

3V


$$V_x = \alpha V_1 + \beta V_2$$
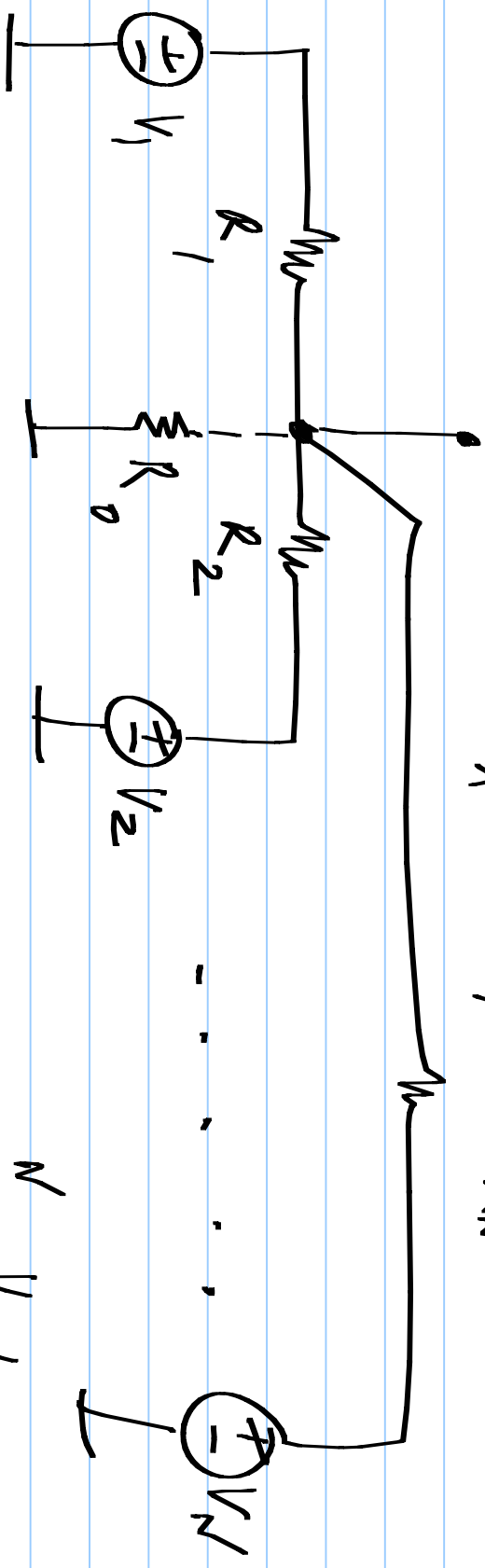
$$V_x = \alpha V_1 + \beta V_2 + \dots + \beta V_N$$



$$V_x = \frac{\sum_{k=1}^N V_k / R_k}{\sum_{k=1}^N 1/R_k + 1/R_0}$$

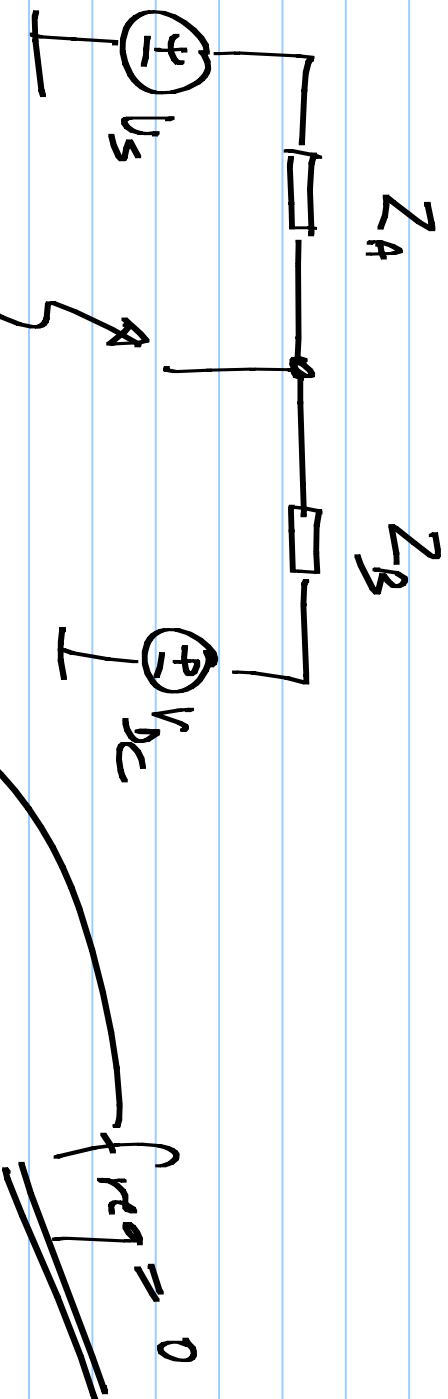Across q-s of the mos transistor: $V_s + V_{dc}$



$$V_s(s) \left[\frac{Z_B}{Z_A + Z_B} \right] + \left[V_{dc} \right] \left[\frac{Z_A}{Z_A + Z_B} \right]$$

$\text{freq} \neq 0$ points to the first term.

$\text{freq} = 0$ points to the second term.

$$Z_B \rightarrow 0$$

② $s \rightarrow 0$

✓ $|Z_A| \gg |Z_B|$ (a) dc. so that $V_{oc} \cdot \frac{Z_A}{Z_A + Z_B}$
 $(s=0)$



$|Z_B| \gg |Z_A|$


(a) the freq. ω_0 is so that V_{oc}


$V_s(s) \cdot \frac{Z_B}{Z_A + Z_B} \approx V_s(s)$

① Capacitor Resistor / Inductor $\frac{Z_A}{C} \frac{Z_B}{R}$

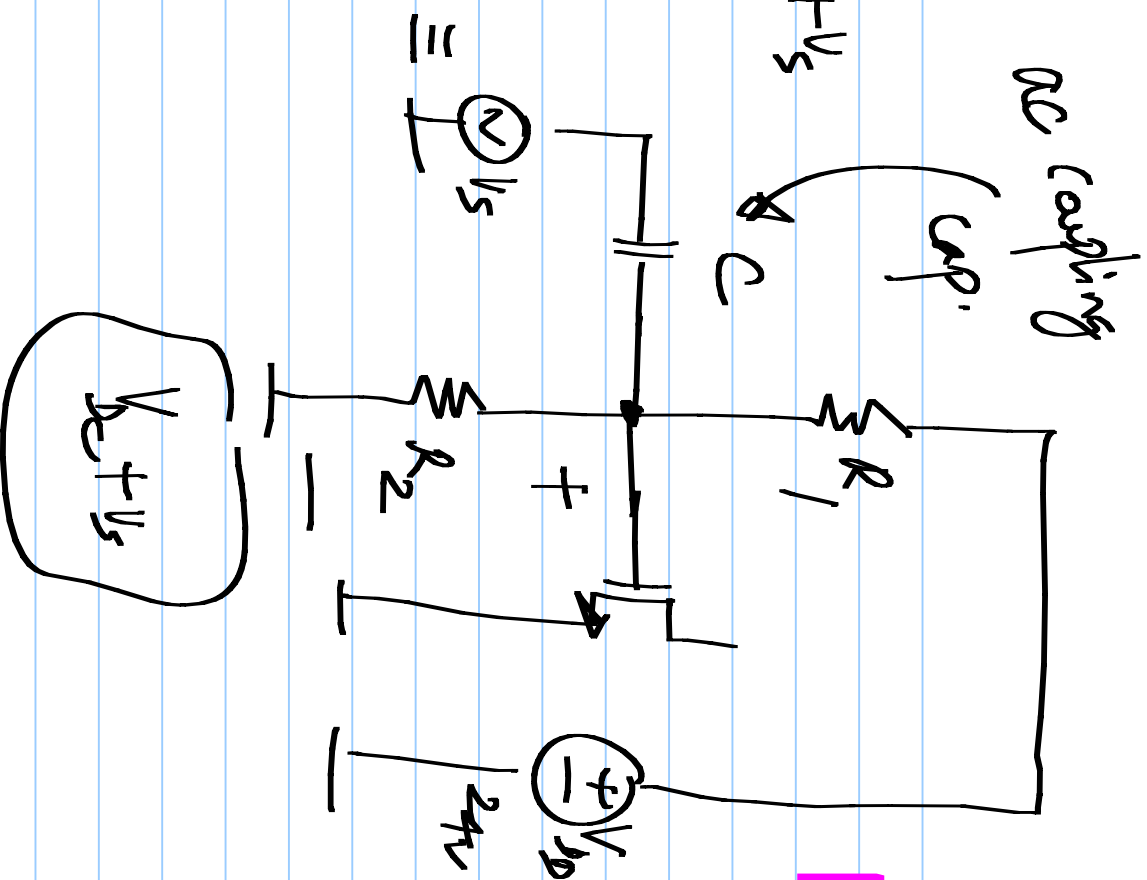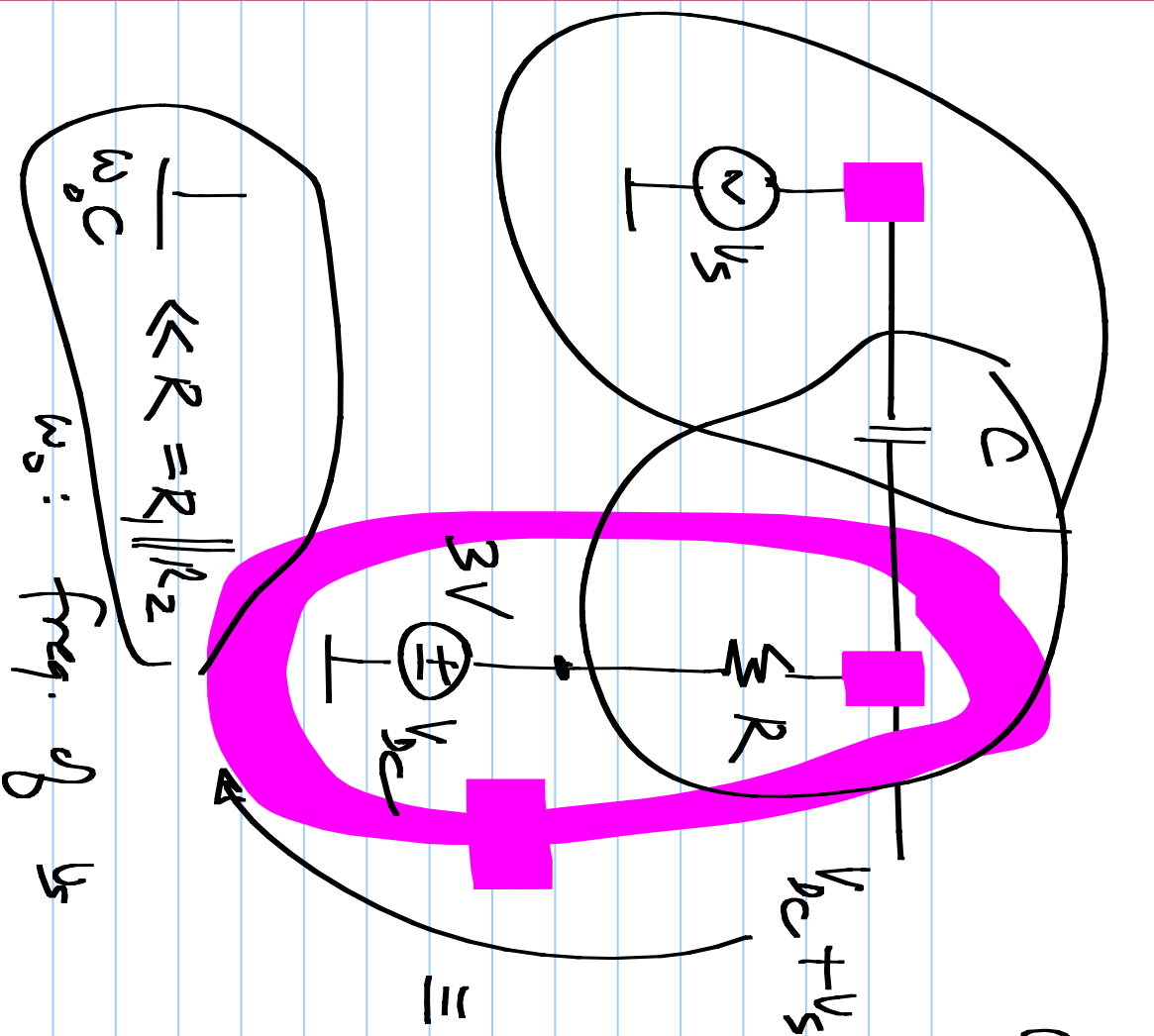② Cap/resistor Inductor $R \gg \frac{1}{\omega C}$



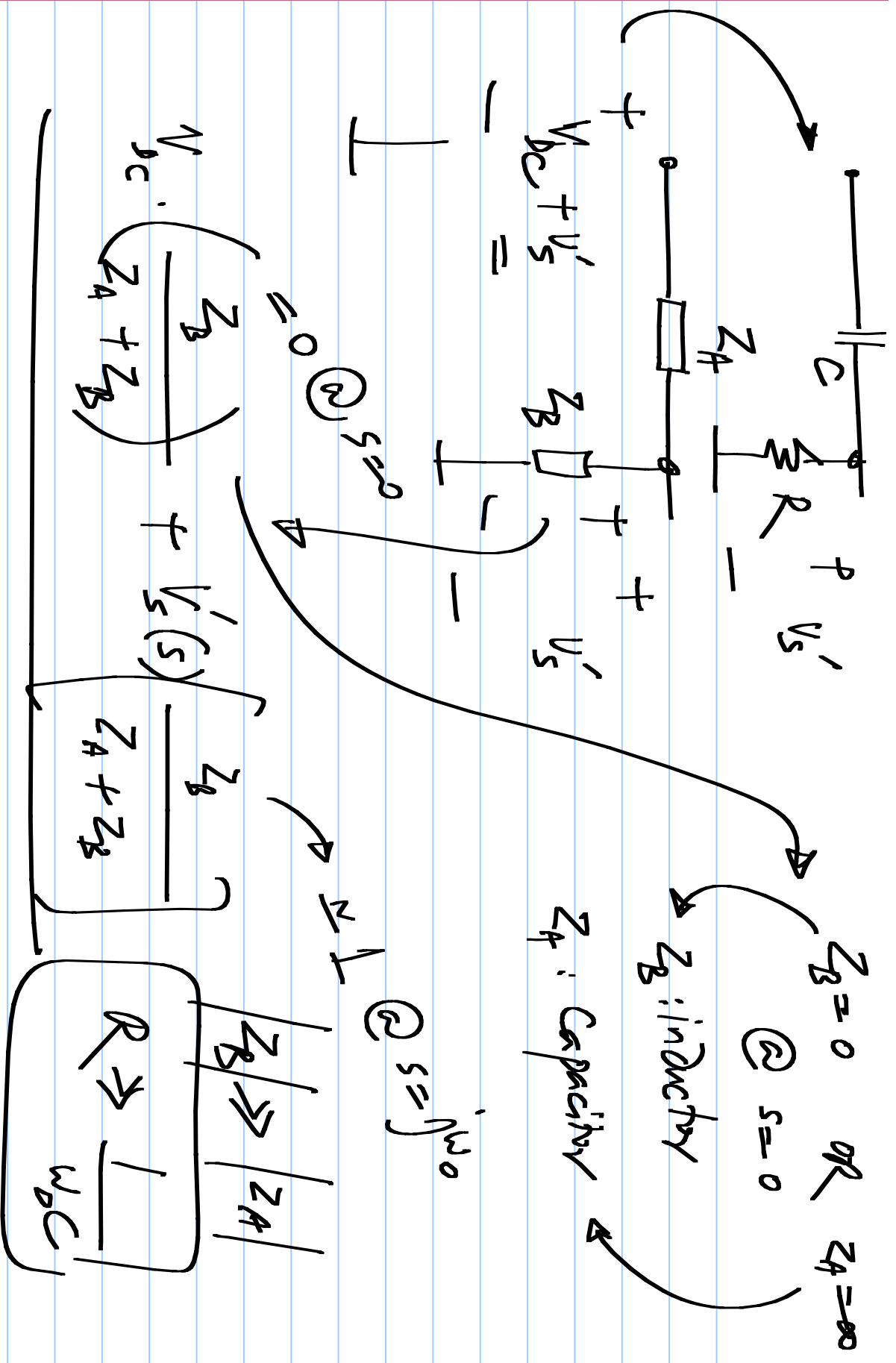


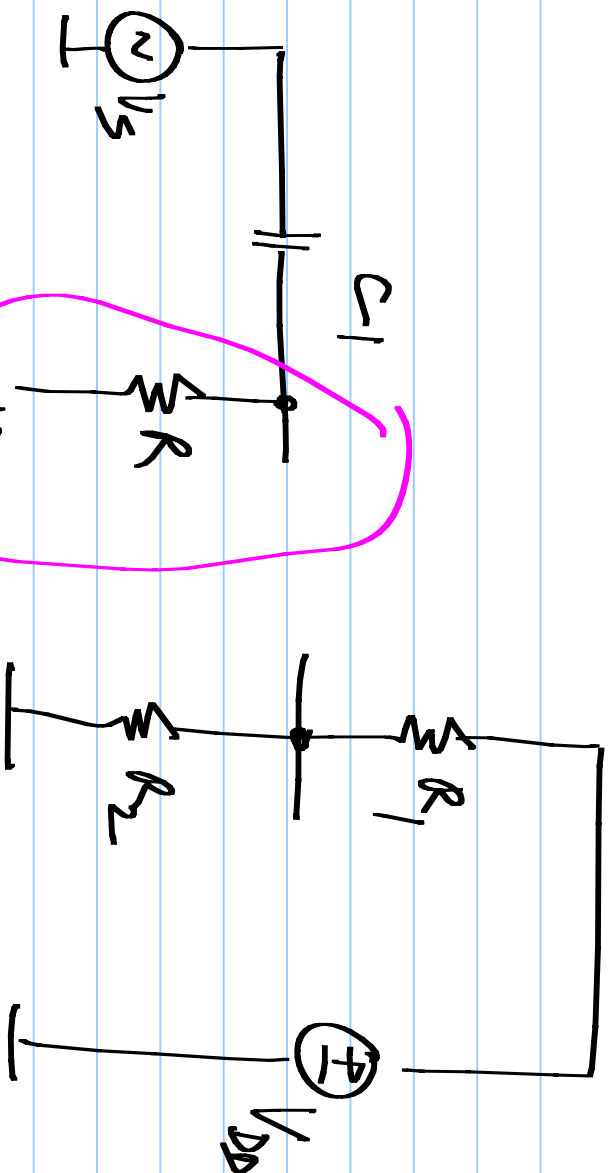

Combine V_s, V_{DC}

$$\frac{1}{\omega_b C_1} \ll R$$

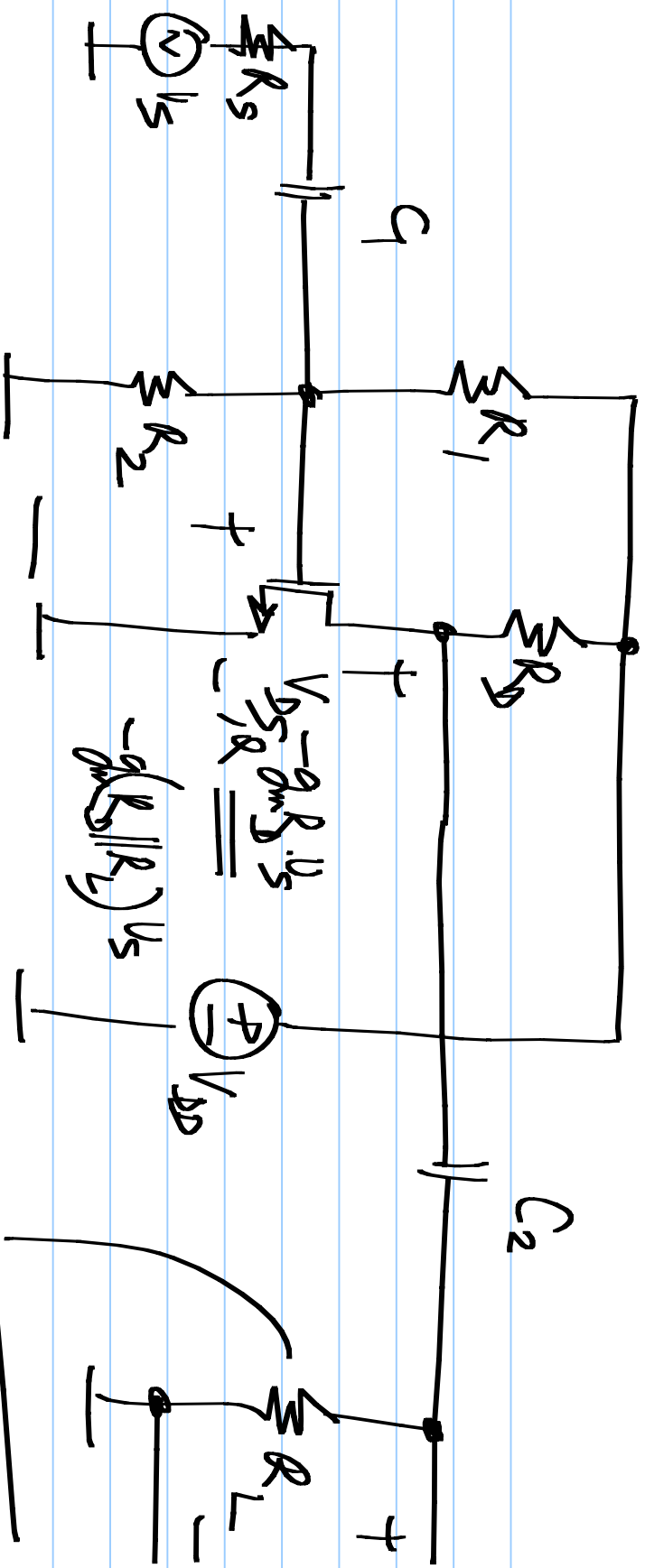
$$\equiv \frac{V_{DD} \cdot \frac{R_2}{R_1 + R_2}}{R_1 \parallel R_2}$$



$$(R_1 \parallel R_2) \gg R_s$$

$$\underline{\underline{-g_m (R_D \parallel R_L) V_s}}$$

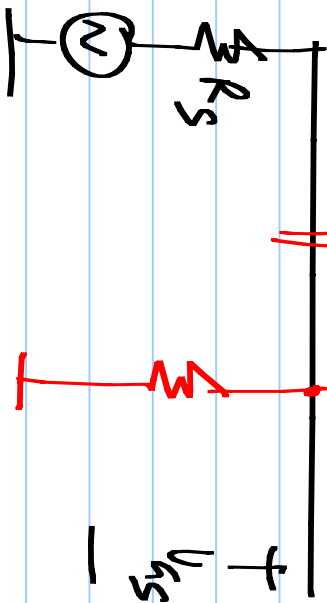
$$\checkmark \left[\frac{1}{\omega C_1} \ll R_S + (R_1 \parallel R_2) \right]$$



$$(R_1 \parallel R_2)$$

$$R_1 \parallel R_2 \gg R_S$$

$$\frac{1}{\omega C_2} \ll R_D + R_L$$

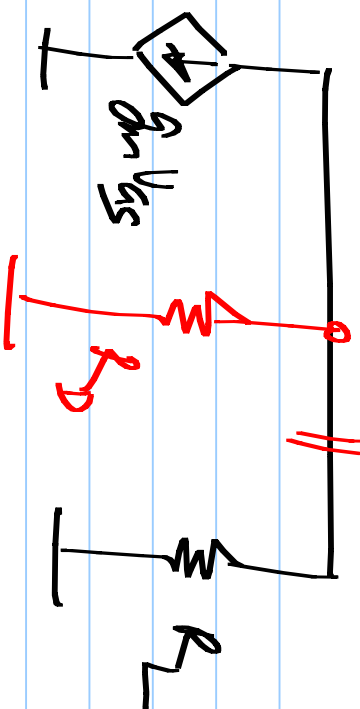

$$R_D \gg R_L$$