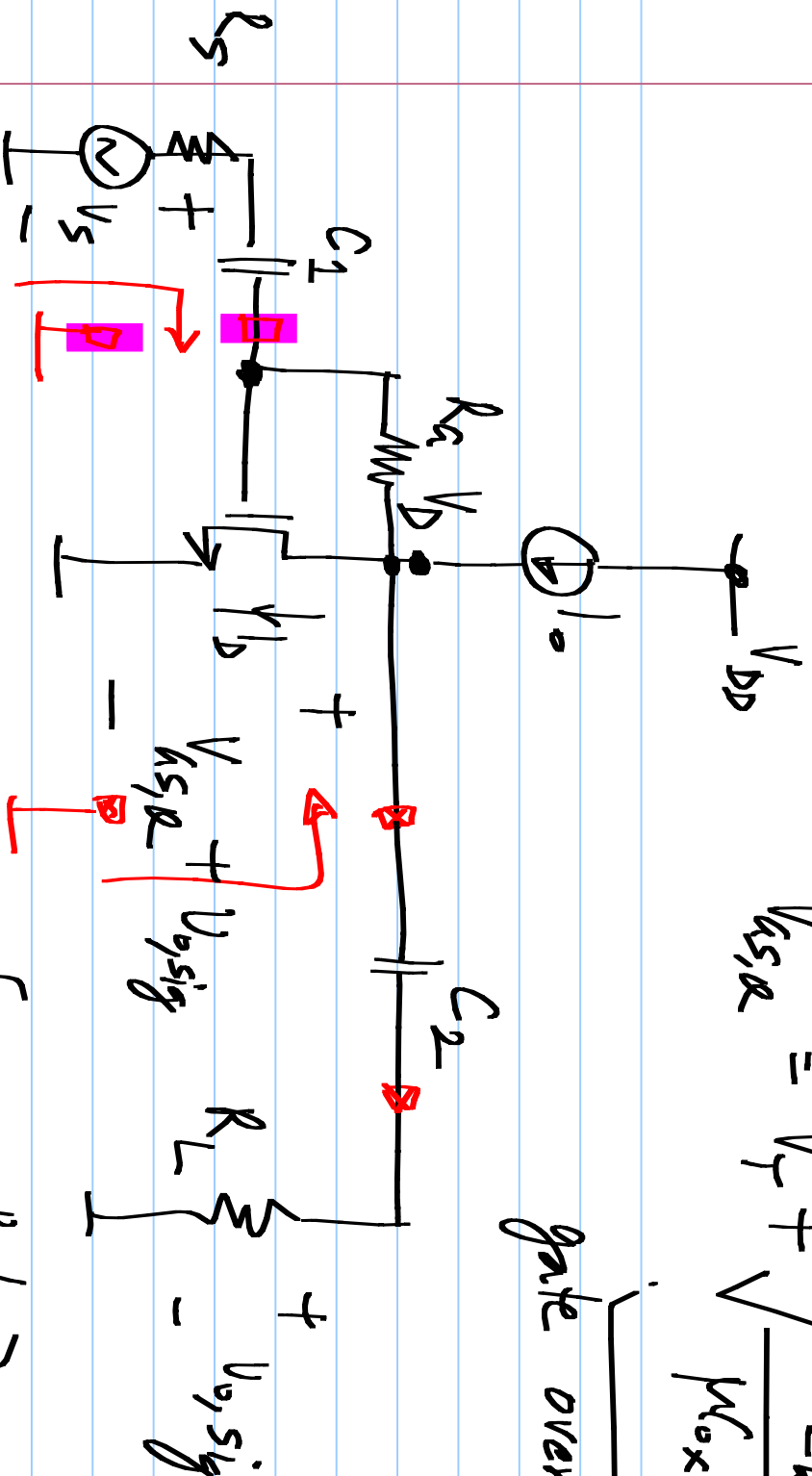


$$V_{GS,R} = V_T + \sqrt{\frac{2I_D}{\mu_{ox} W/L}}$$


gate overdrive



$$\frac{v_o}{v_s} = - \left[\frac{g_m R_L - R_L / R_a}{1 + R_L / R_a} \right] \approx -g_m R_L \quad \text{if } R_a \gg R_L$$

v_D (at dc)



$+ v_s$ (at v_{sig})

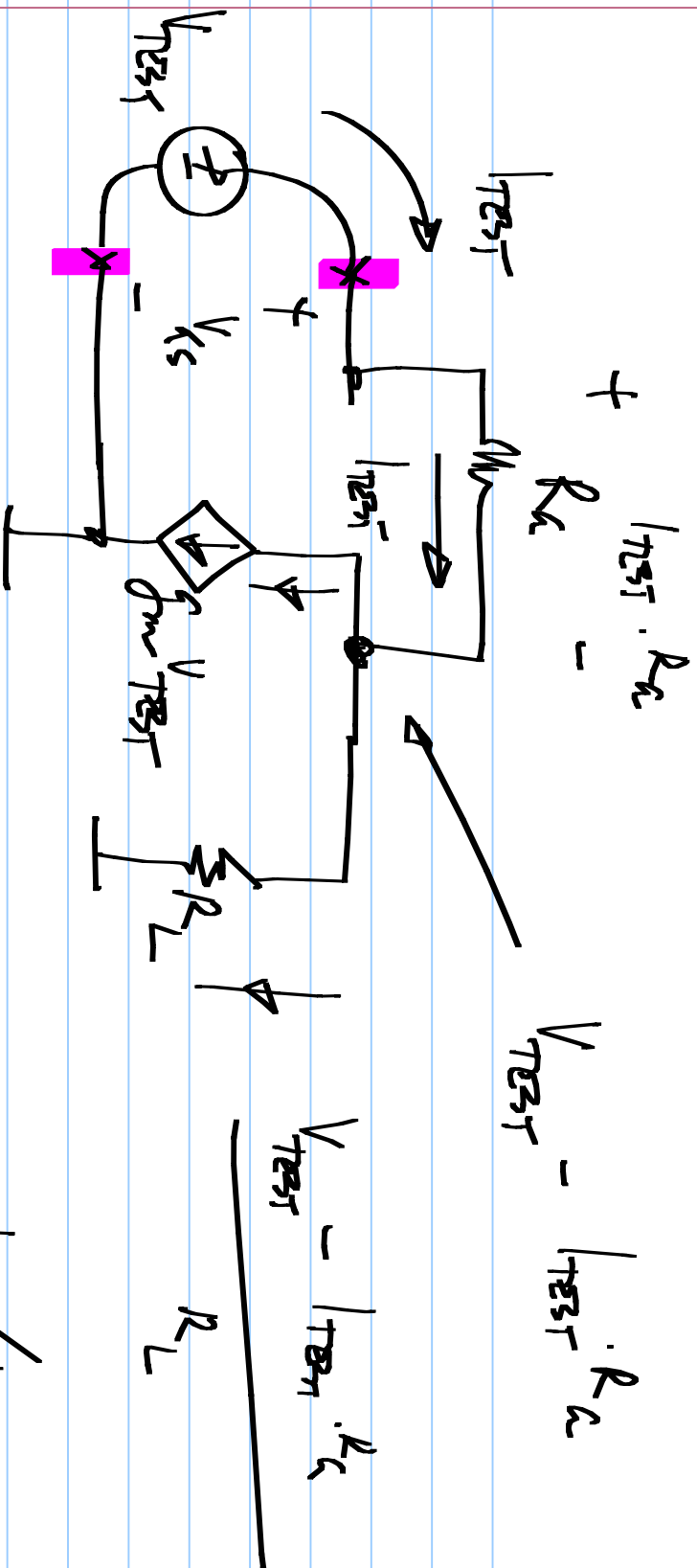


$$\left(1 + \frac{R_a}{R_L}\right) I_{test} = \left(\frac{1}{R_L} + g_m\right) V_{test} + \frac{V_{test} - I_{test} \cdot R_a}{R_L}$$


$$\frac{V_{test}}{I_{test}} = \frac{1 + R_a/R_L}{[g_m + 1/R_L]} \approx \frac{R_a}{g_m R_L + 1}$$
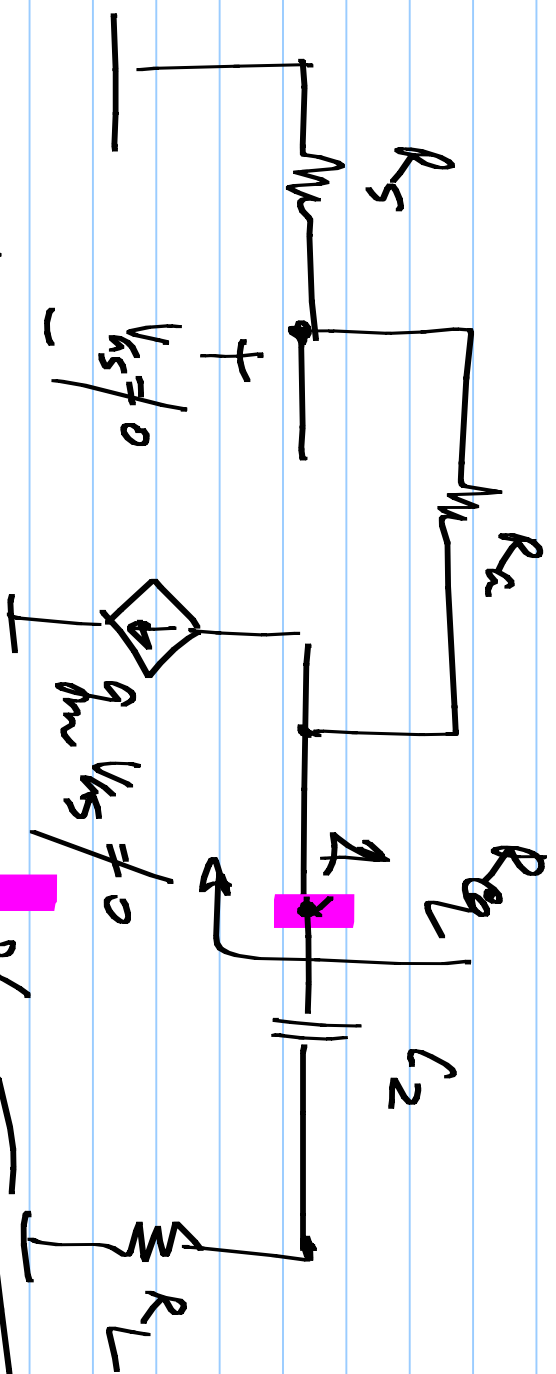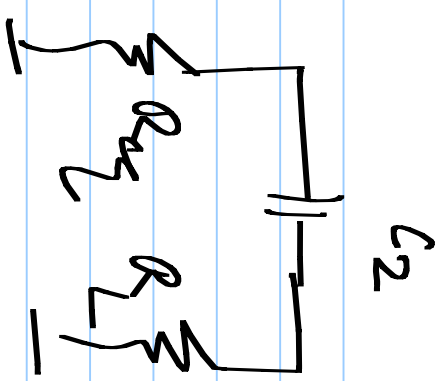
$$\frac{1}{\omega C_1} \ll R_s + \frac{1 + R_s/R_L}{g_m + 1/R_L}$$




$$\frac{1}{\omega C_2} \ll R + R_{eq}$$

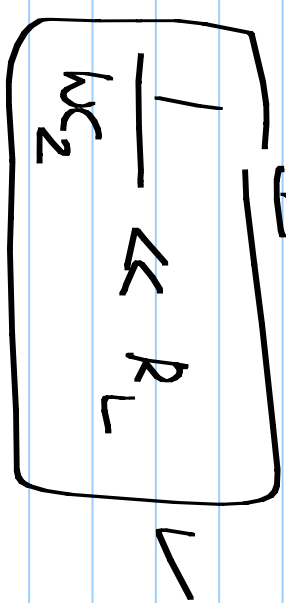

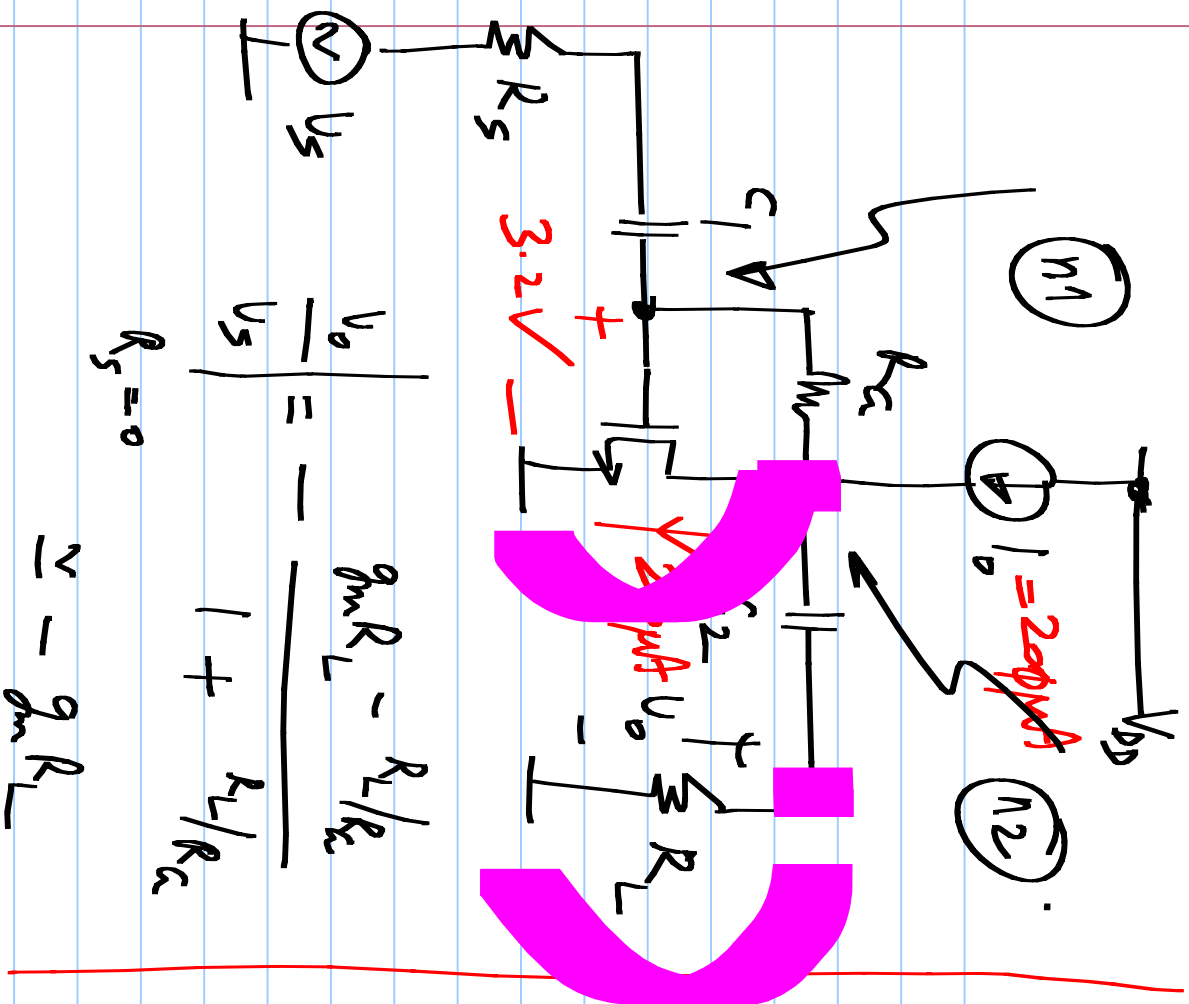

$$\left. \frac{v_o}{v_s} \right|_{R_S=0} = - \frac{g_m R_L - R_L / R_D}{1 + R_L / R_D}$$

$$\approx -g_m R_L$$

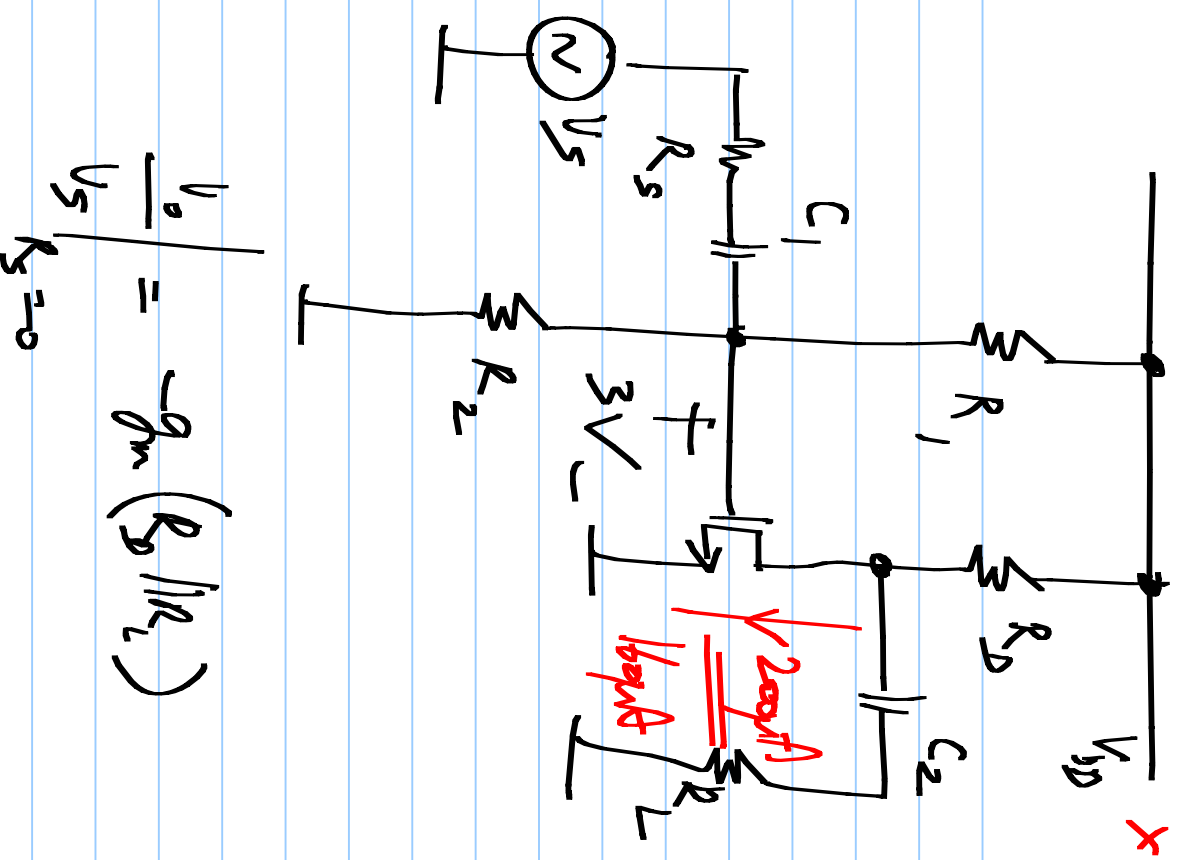

$$\left. \frac{v_o}{v_s} \right|_{R_S=0} = -g_m (R_D \parallel R_L)$$

Quiescent

Increment:-

$$V_{GS} = V_T + \sqrt{\frac{2I_D}{\mu_{ox} W/L}} + V_S$$

$$V_{DS} = V_T + \sqrt{\frac{2I_D}{\mu_{ox} W/L}} + (-g_m R_L V_S)$$

$$I_D = I_D + g_m V_S$$

$$\frac{1}{g_m} < V_S < \left[\frac{V_T}{1 + g_m R_L} \right]_{\text{total}} \quad \left[\begin{array}{l} V_{DS} > V_{GS} - V_T \\ I_D > 0 \end{array} \right]$$

* Calculate $\frac{V_o}{V_s}$, constraints on C_1, C_2

$\{ R_{in}, R_{out} \}$

with $R_s \neq 0$
