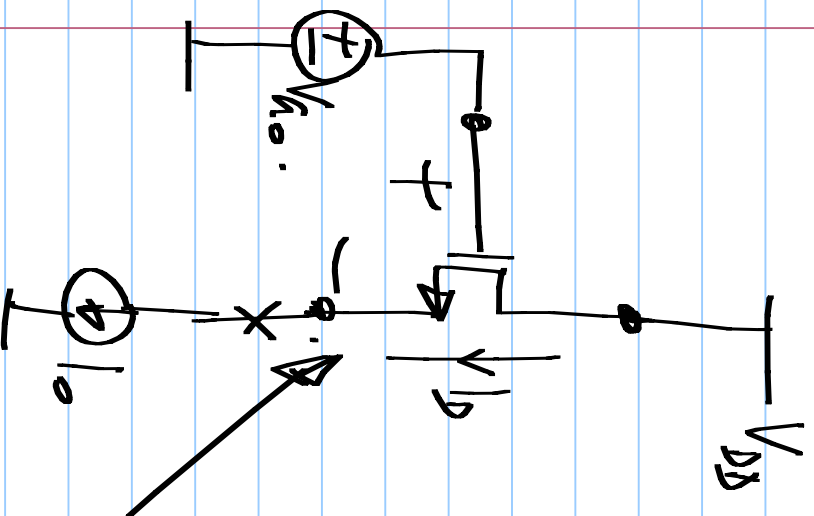



Sense I_D @ drain; feedback to the gate ✓
Source I_D @ source; feedback to the source

$\left\{ \begin{array}{l} I_D < I_o : V_S \text{ must decrease} \\ \end{array} \right.$
 $(V_{GS} = V_{GS0} - V_S \text{ must } \uparrow)$



If $I_D < I_o$, V_S will decrease

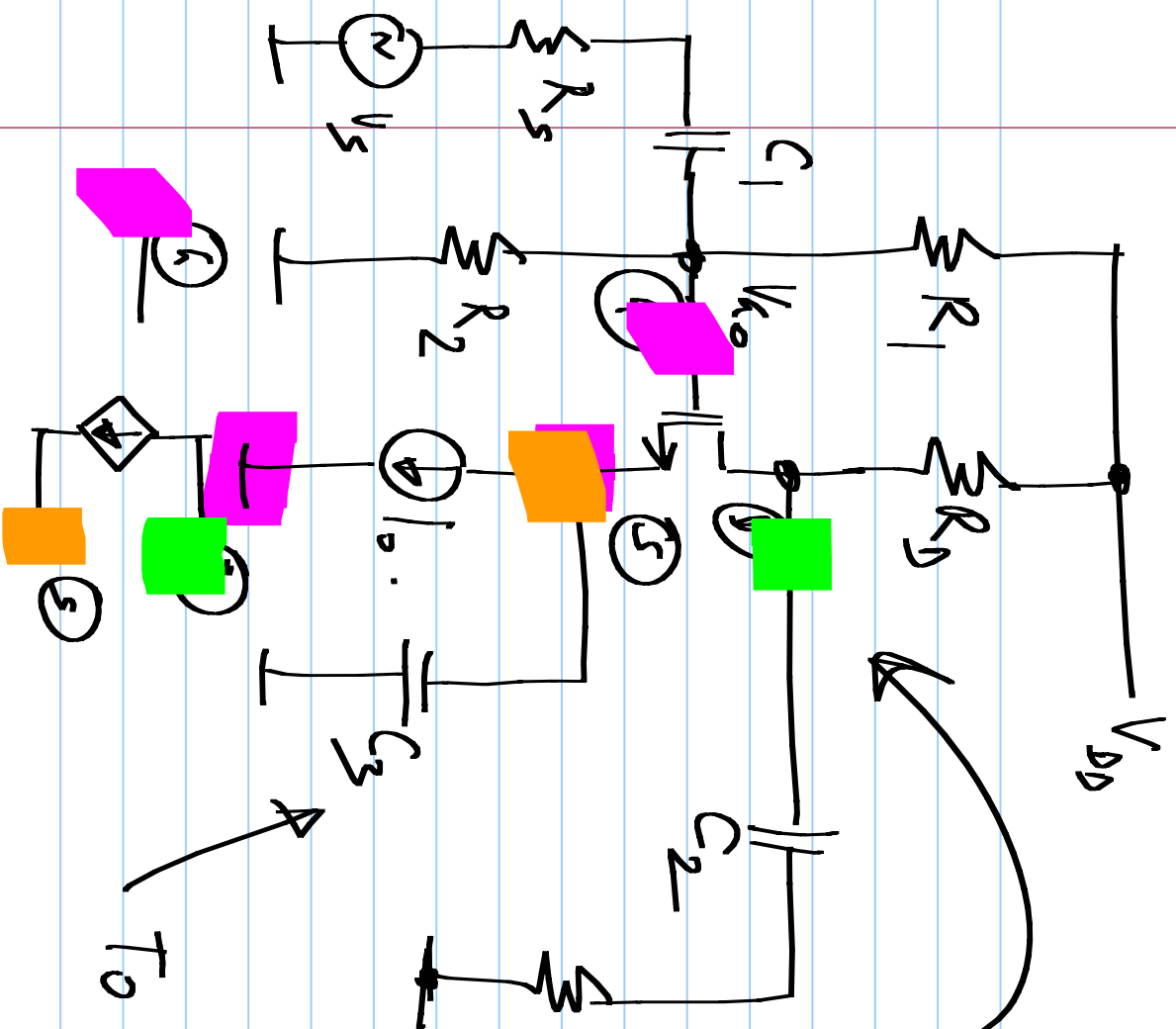
$$V_{GS} - V_T = \sqrt{\frac{2I_D}{\mu C_{ox} W/L}}$$




To ground the source of the MOS

$$\left[\frac{1}{\omega C_1} \ll R_1 \parallel R_2 + R_S \right]$$


$$\frac{1}{\omega C_2} \ll R_D + R_L$$

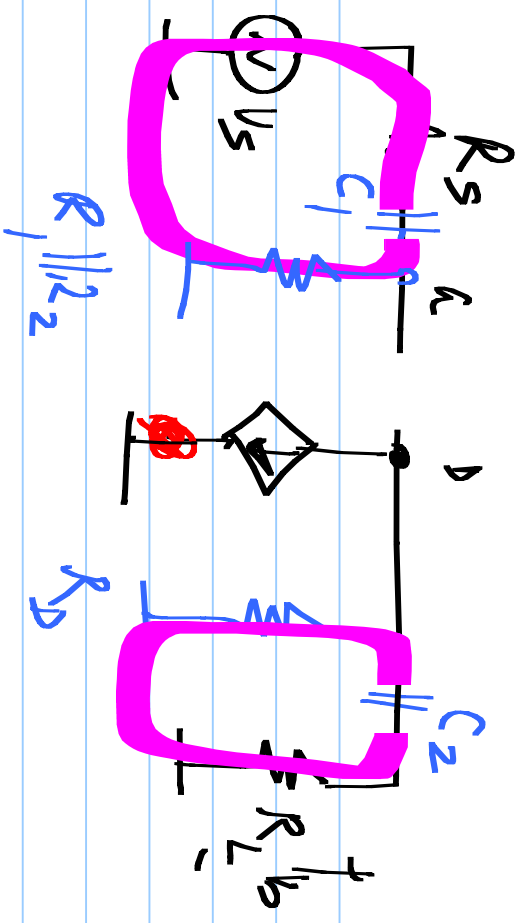

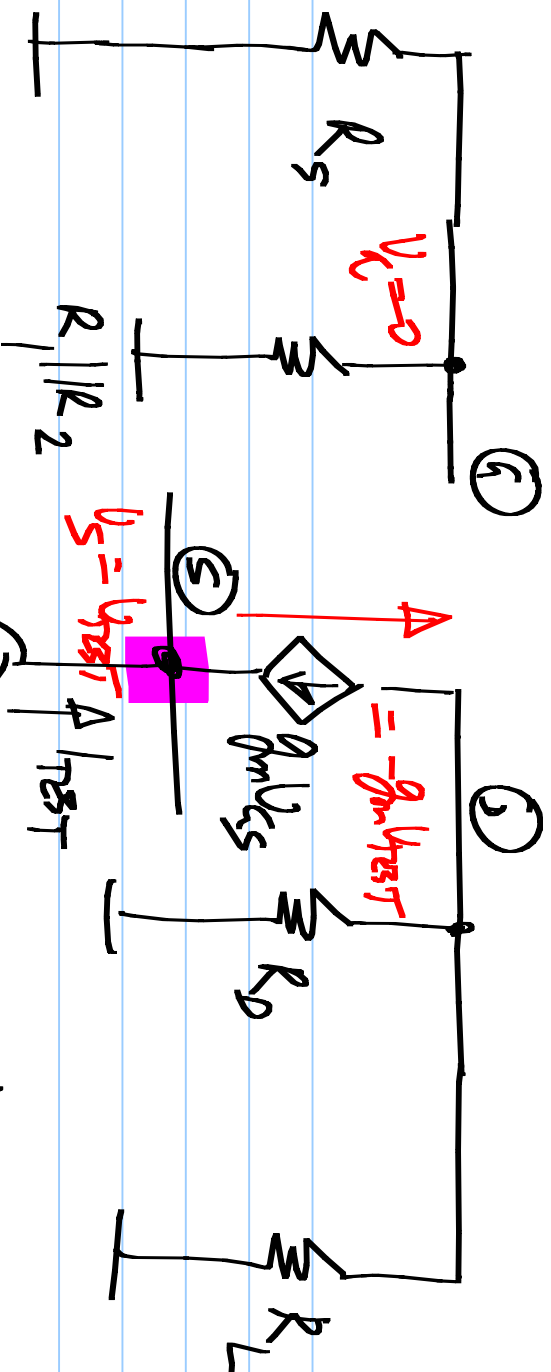



$$V_{DS} = -V_{DS} \quad \frac{1}{g_m}$$
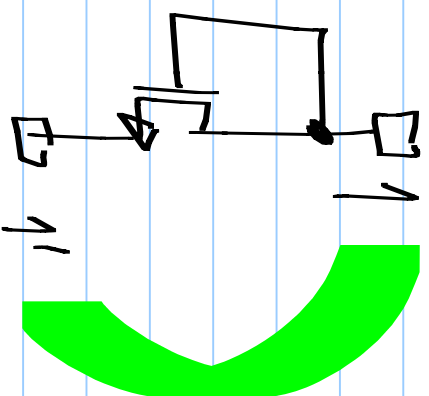
$$\frac{V_{DS}}{V_{DS}} = \frac{g_m \cdot V_{DS}}{g_m}$$



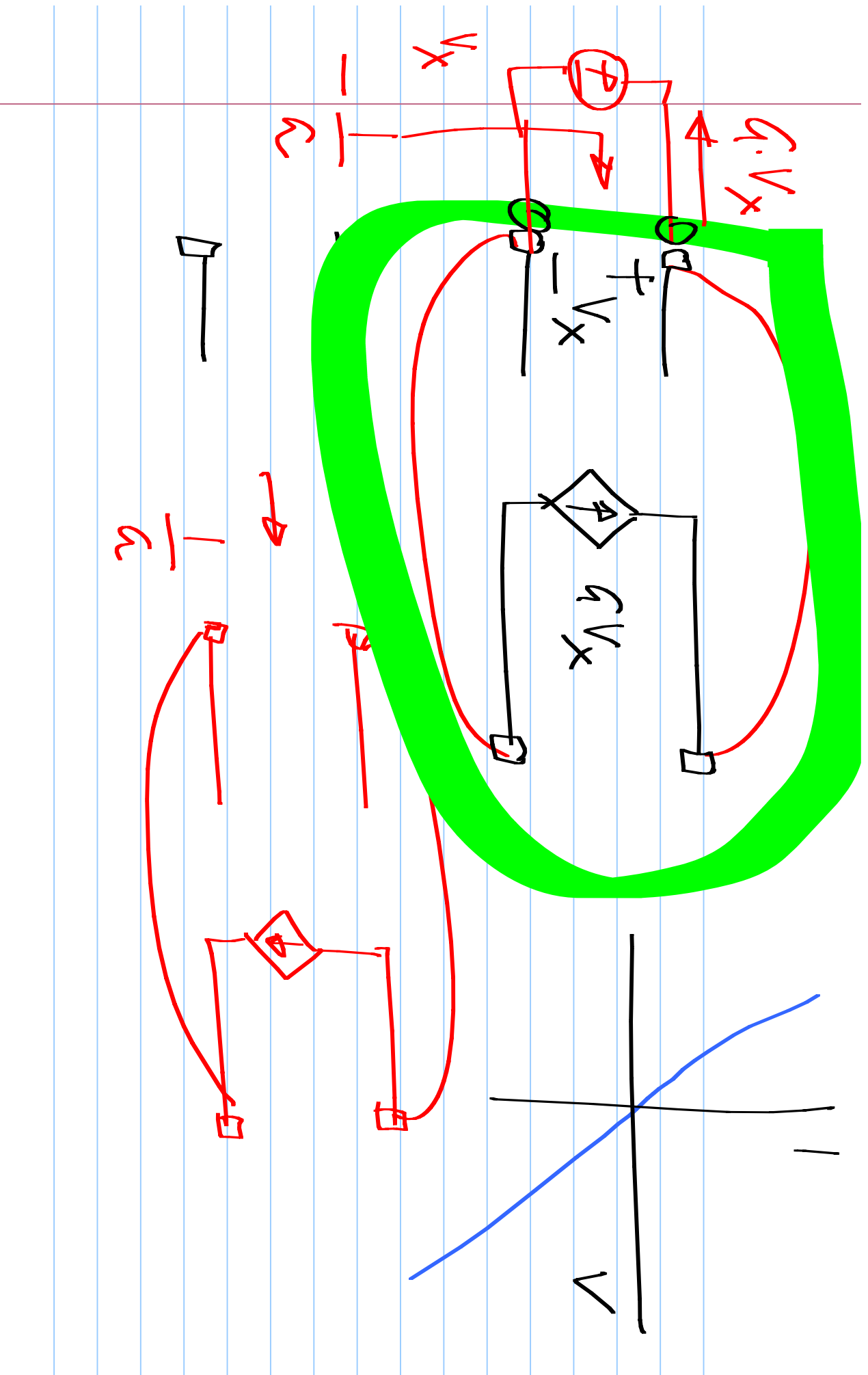
$$\frac{1}{\omega C_3} \ll \frac{1}{g_m} = \left(\frac{1}{g_m} \right)$$



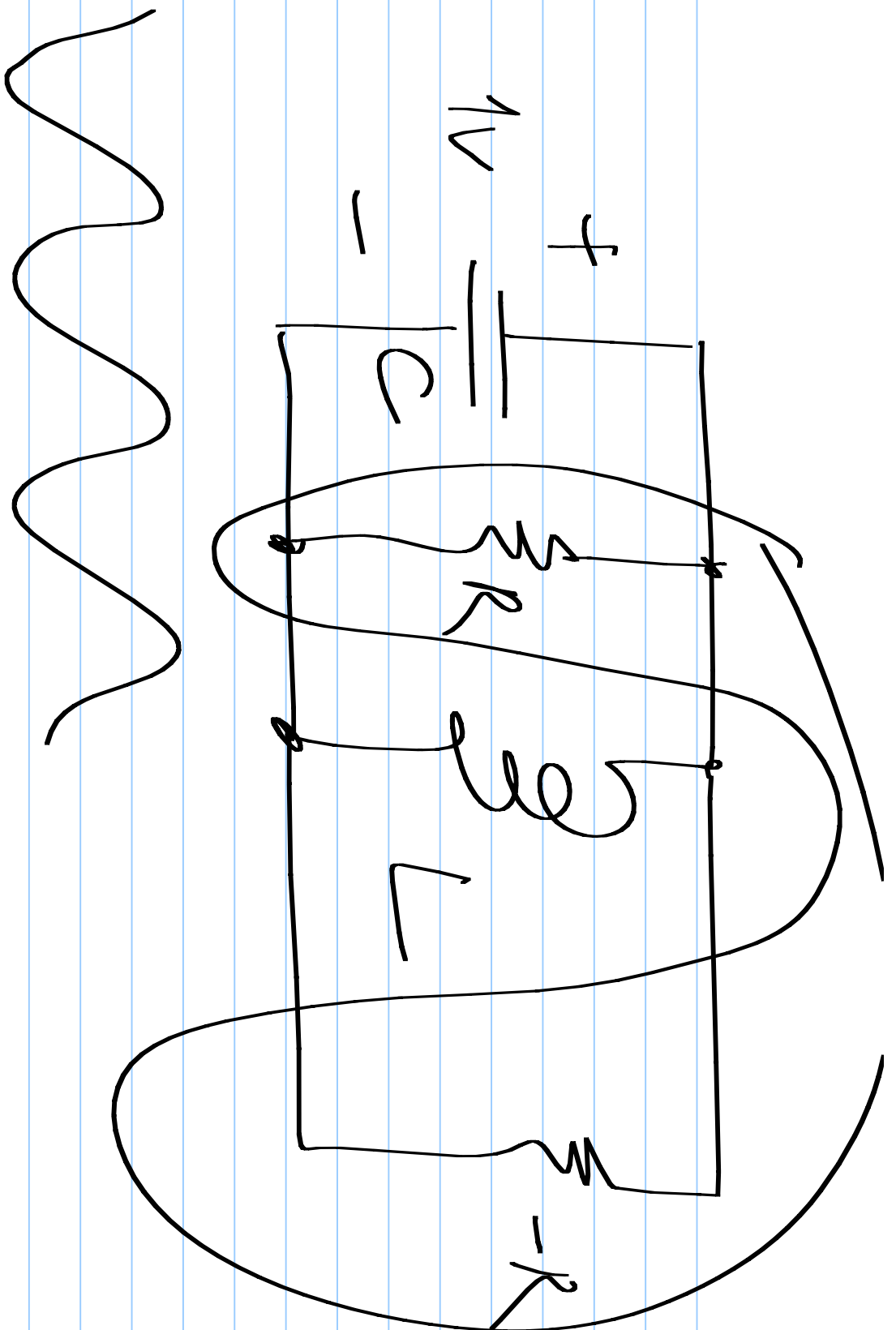

10⁶ rad/s

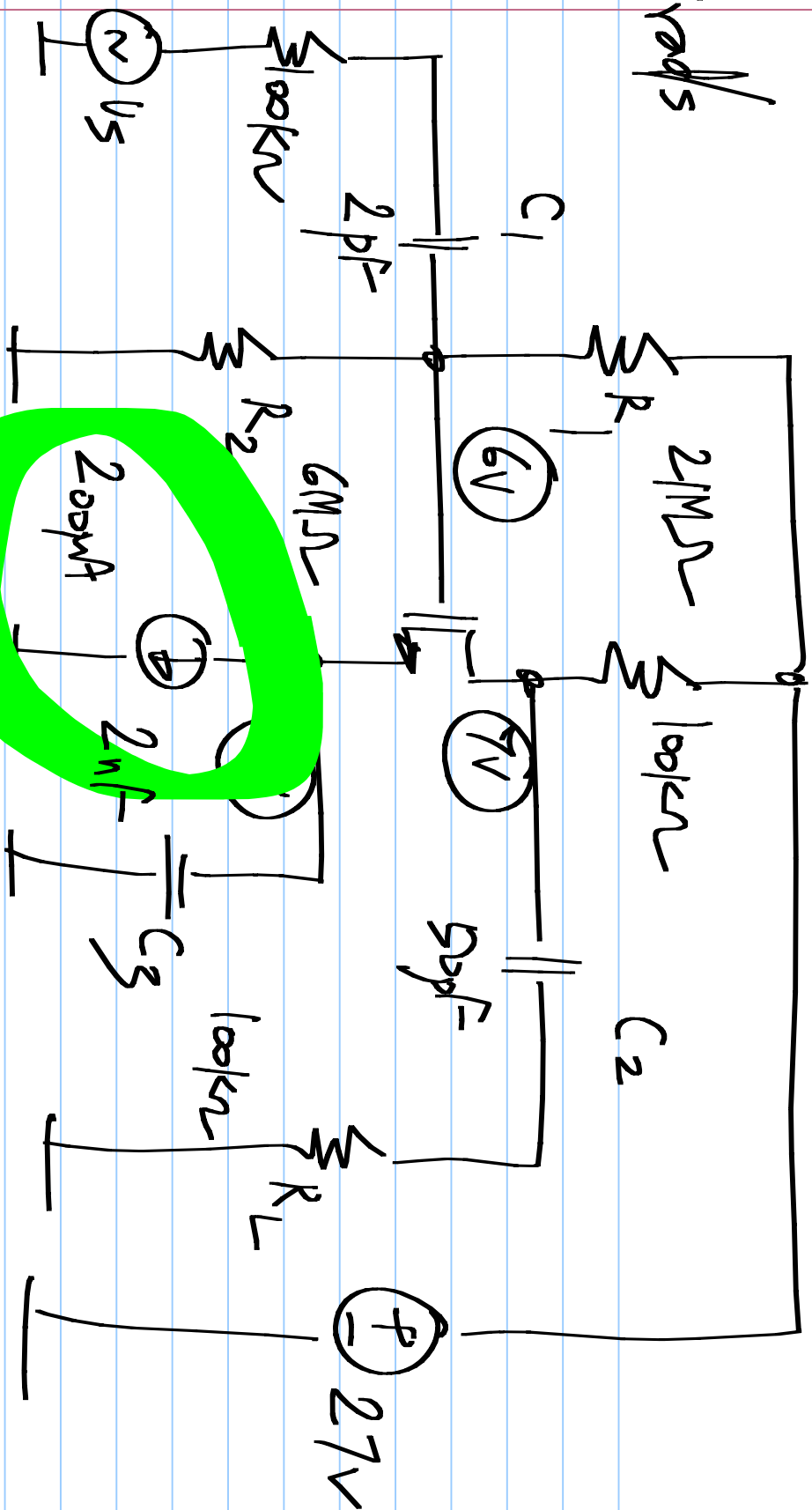

$$C_1 \gg 0.2/pF$$

$$C_2 \gg 5pF$$

$$C_3 \gg 200pF$$

