
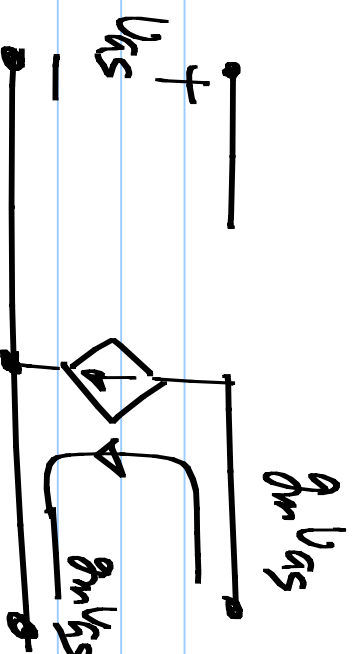


VCS: $V_o = v_i$

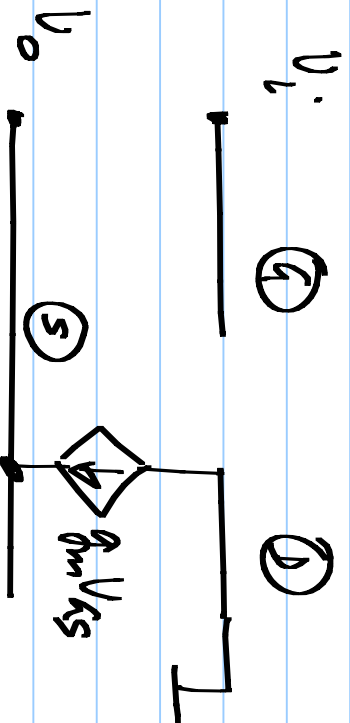


If $v_i > v_o$: current flows into the source node - increases v_o

$v_i < v_o$: " out of the source node
— reduces v_o

VCVS:

$$v_o = v_i$$

Common drain amplifier

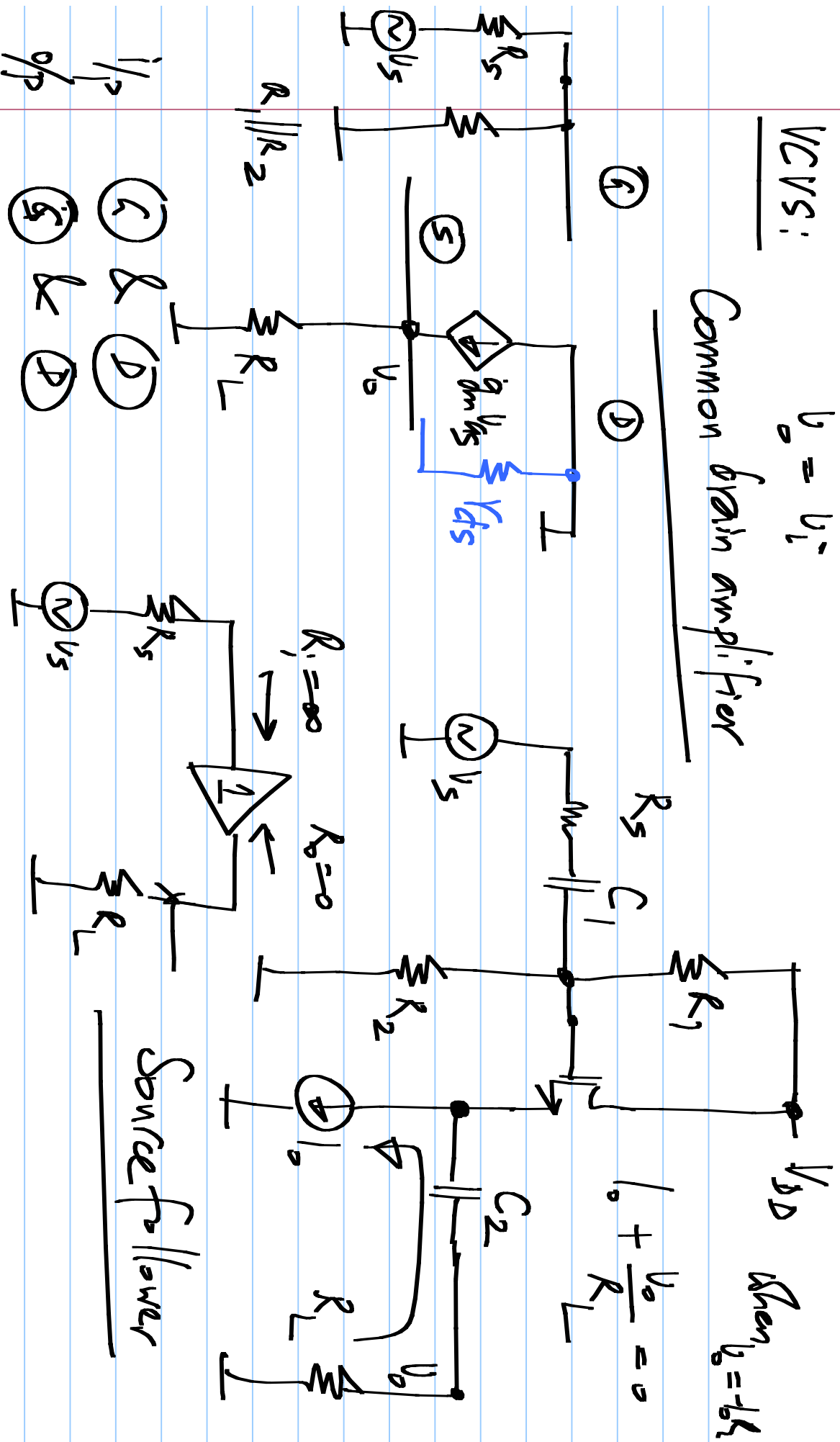

$$\frac{V_o}{V_s} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_s} \cdot \underbrace{\frac{g_m R_L}{1 + g_m R_L}}$$

$$g_m R_L \gg 1$$

$$V_{\text{out}} > V_{\text{gate}} - V_T$$

$$V_{DD} > V_{DD} \cdot \frac{R_2}{R_1 + R_2} + V_S - V_T$$

$$\{R_1 \| R_2 \gg R_S\}$$

$$-I_{DQ_L} \cdot \left(\frac{g_{mL} R_L + 1}{g_{mL} R_L} \right) < V_S < V_{DD} \cdot \frac{R_1}{R_1 + R_2} + V_T$$


cut off:

$$V_O > -I_{DQ_L} R_L$$

$$V_S > -I_{DQ_L} \cdot \left(\frac{g_{mL} R_L + 1}{g_{mL} R_L} \right)$$

VCCS: $i_o = \frac{v_s}{R} = v_s \cdot g$

$v_s = i_o R$

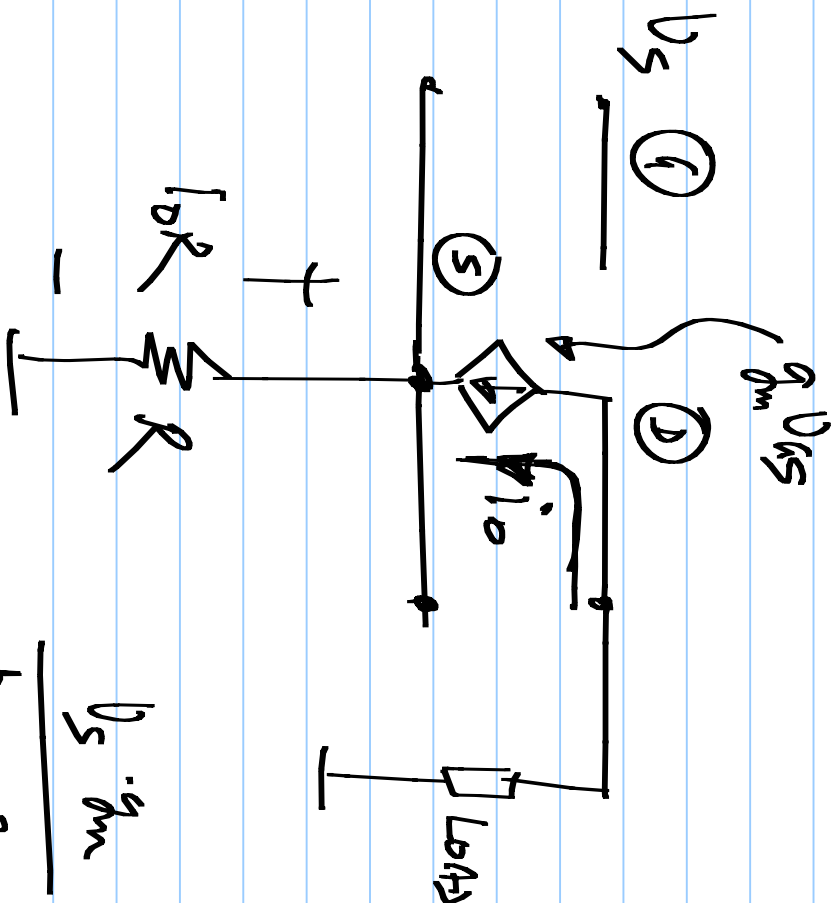

If $v_s > i_o R$

increase $i_o \rightarrow$ increase v_s
 $v_s < i_o R$


reduce i_o

$\Rightarrow$ reduce v_s

$$\frac{v_s \cdot g_m}{1 + g_m R} = \frac{v_s}{R + 1/g_m}$$

1
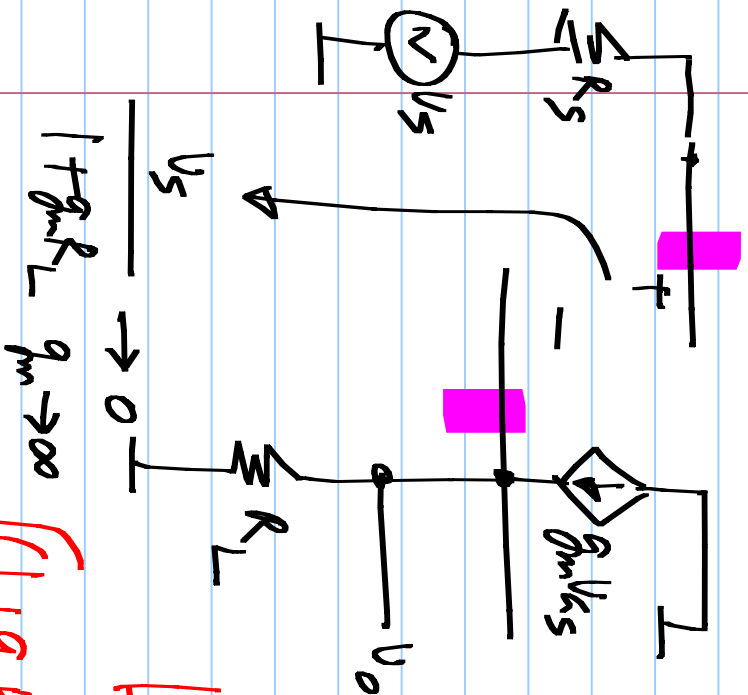
$$\frac{V_o}{V_S} = \frac{g_m R_L}{1 + g_m R_L} \approx 1$$



$$I_{\text{BQ}}(g_{\text{m}K} + I)$$

WCS:

$$\frac{v_0}{v_s} = \frac{q_m}{1 + q_m^2} \approx \frac{1}{R} \quad q_m \rightarrow \infty$$

