

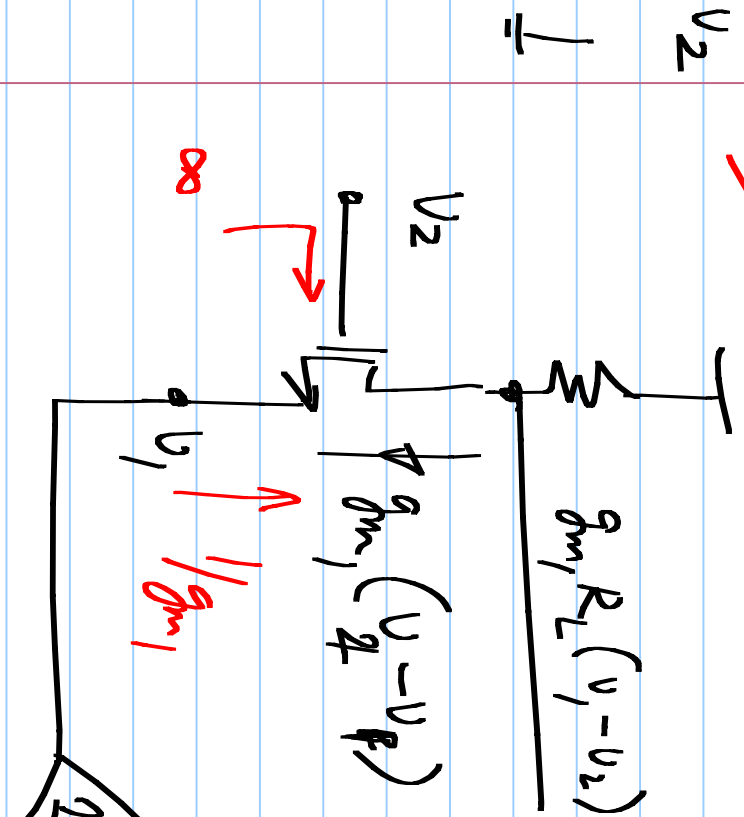
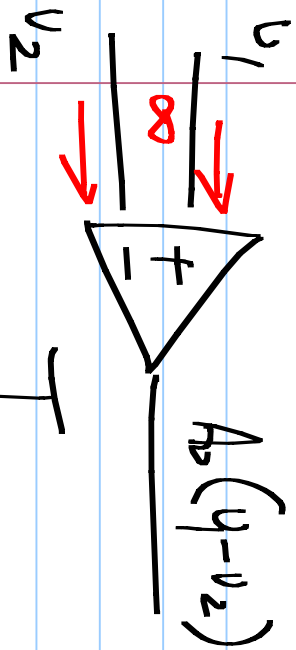


OPAMP:

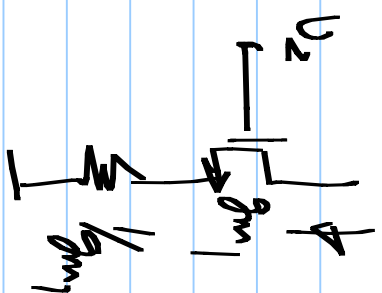


$$v_o = \frac{g_{m1}R_L(v_1 - v_2)}{2}$$

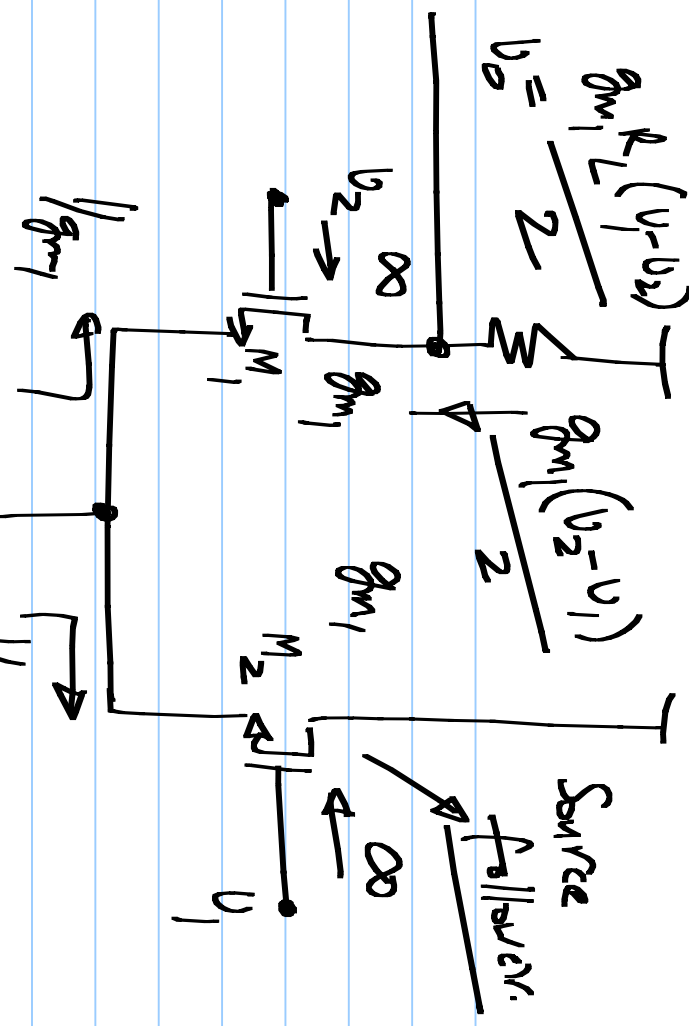


$$\frac{g_m}{1 + g_m R} = \frac{g_m}{2}$$


Differential pair

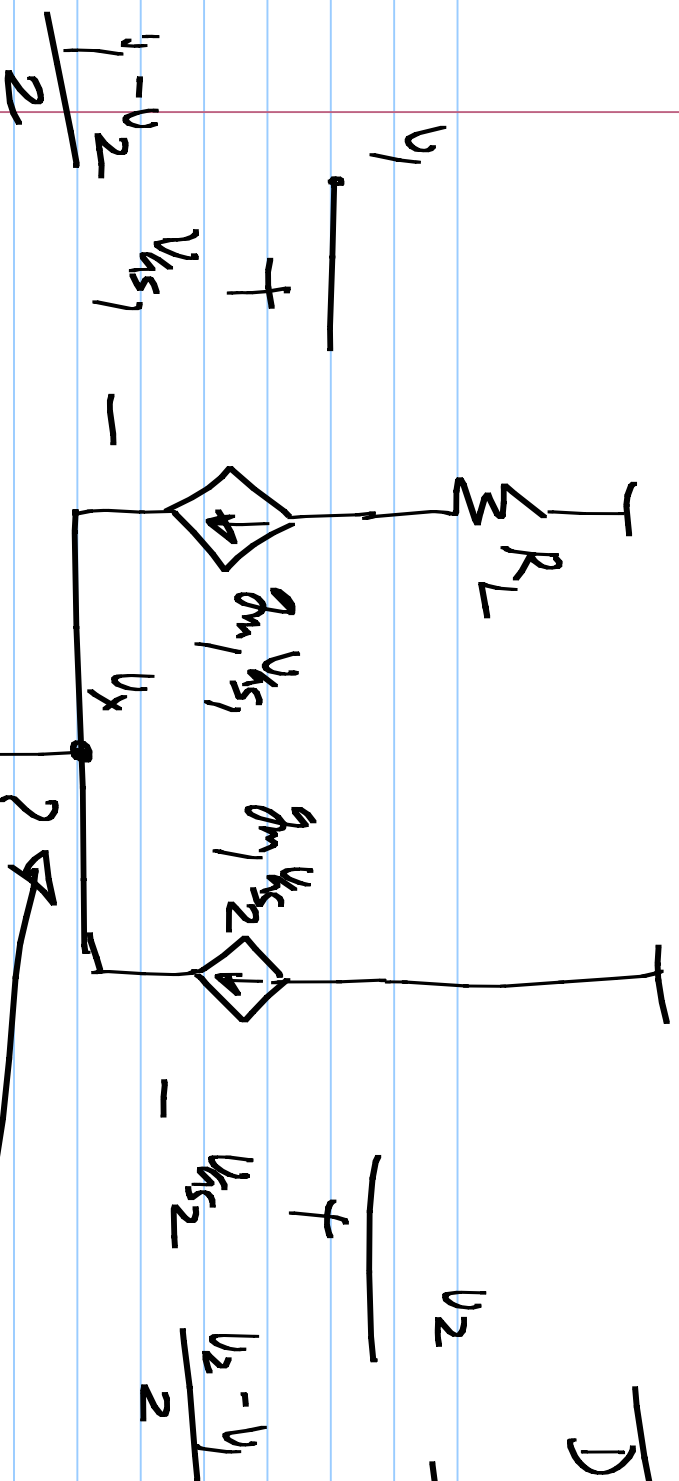

$$g_m(v_1 - v_x) + g_m(v_2 - v_x) = 0$$

$$v_x = \frac{v_1 + v_2}{2}$$

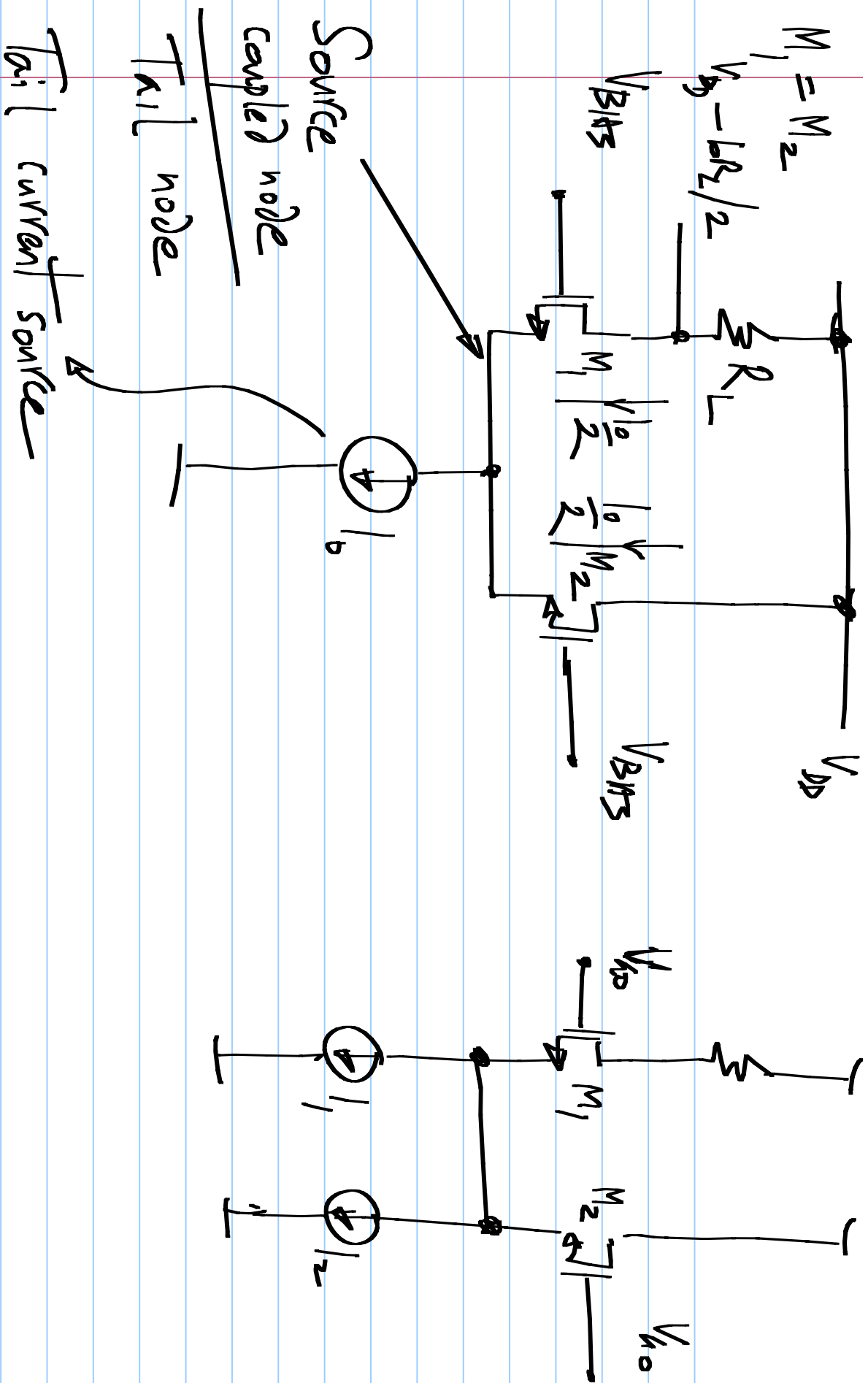

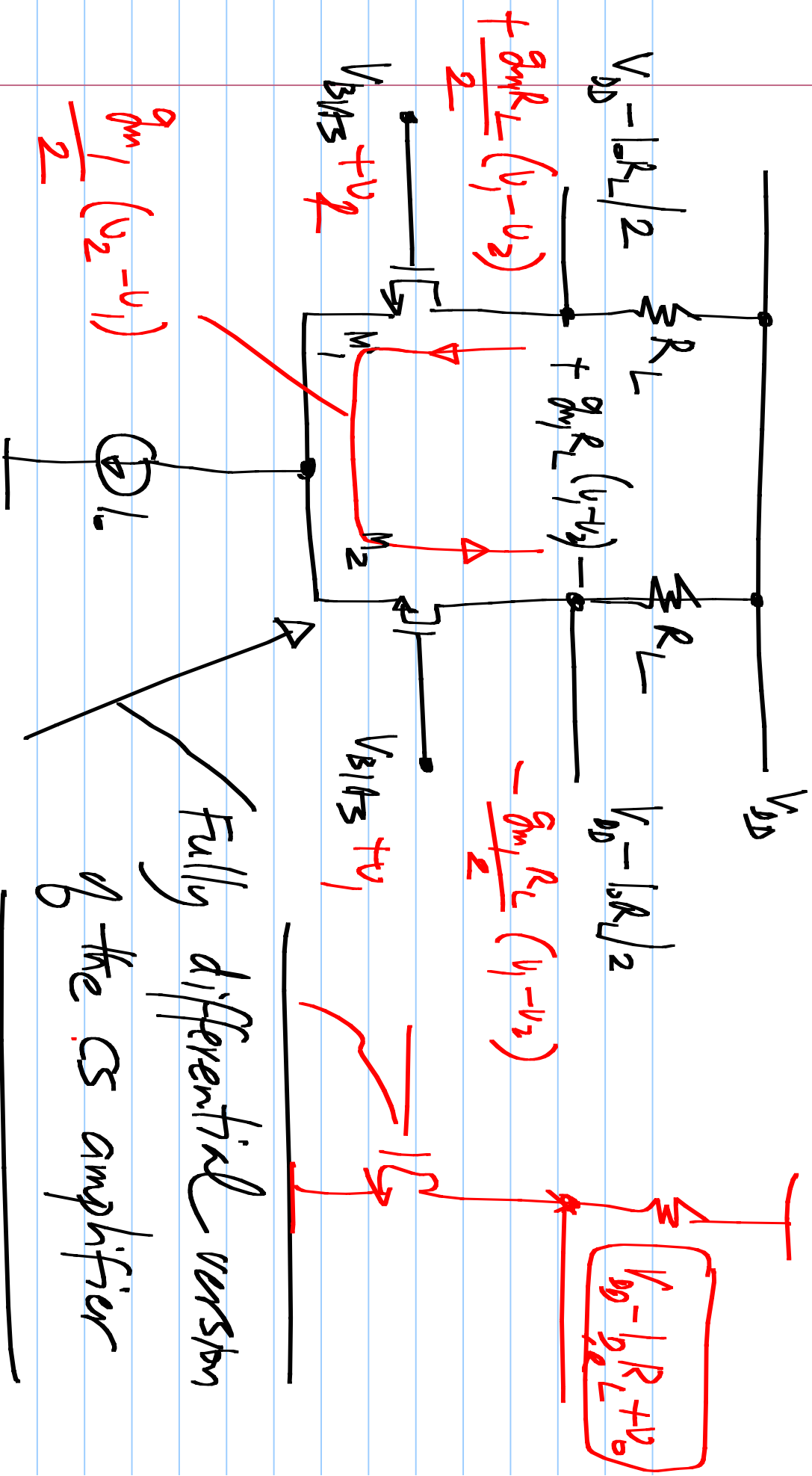

Fully differential version
of the CS amplifier

