


$$G_{m2} - sC_3 \rightarrow G_{m2} - \frac{sC_3}{1+sC_3R_3}$$

$$R_3 = \frac{1}{G_{m2}}$$

$$= \frac{[G_{m2} + sC_3(G_{m2}R_3 - 1)]}{\cancel{(1+sC_3R_3)}}$$


Bipolar junction transistor (BJT)

NPN

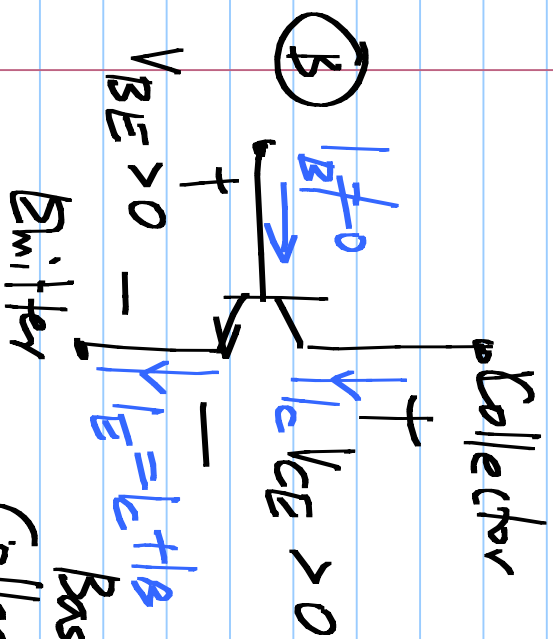


Base $\longleftrightarrow$ Gate
 Collector $\longleftrightarrow$ Drain
 Emitter $\longleftrightarrow$ Source


MOS

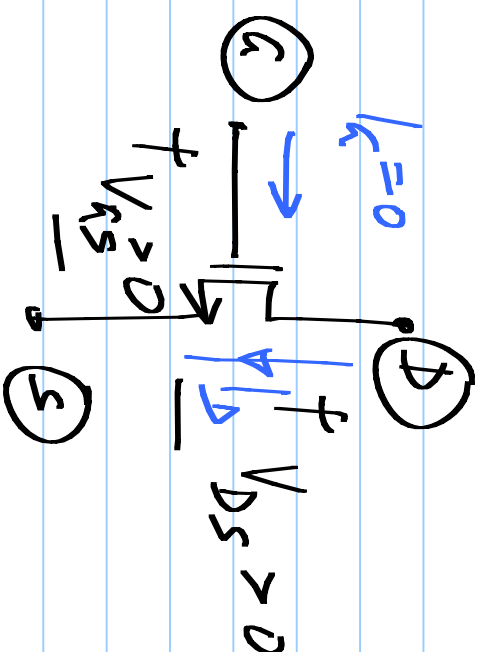

NPN

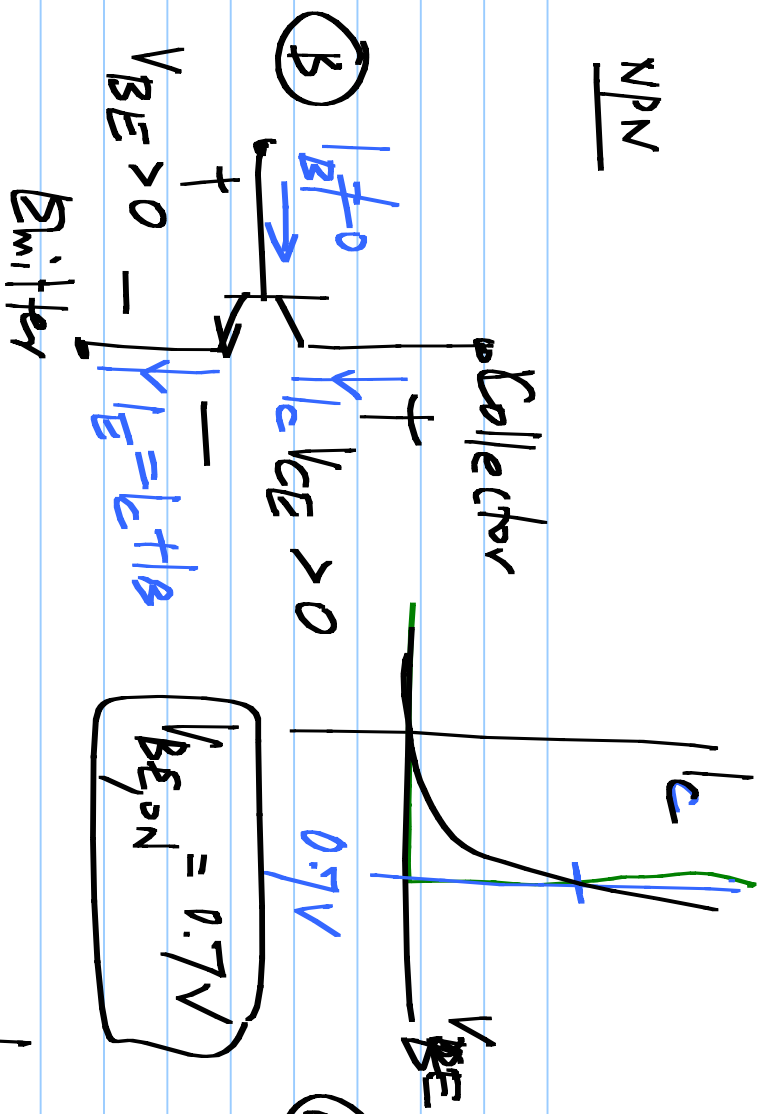

nMOS

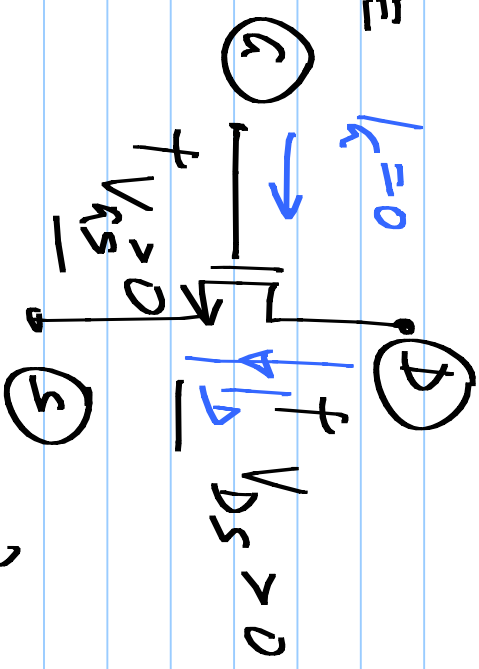

Active region

$$I_C \approx I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

$V_{CE} > V_{CE(sat)} = \underline{\underline{V_{BE(on)} = 0.7V}}$

Sat. region

$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$V_{DS} > V_{GS} - V_T$

$$I_B = \frac{I_C}{\beta} \quad \beta \gg 1 \quad \sim 100$$

[For op. points, $\beta = \infty$]





i.e. $I_B = 0$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$


→ Saturation current

$$V_T = \frac{kT}{q} \approx 25.9 \text{ mV} @ 300\text{K}$$


→ Early voltage

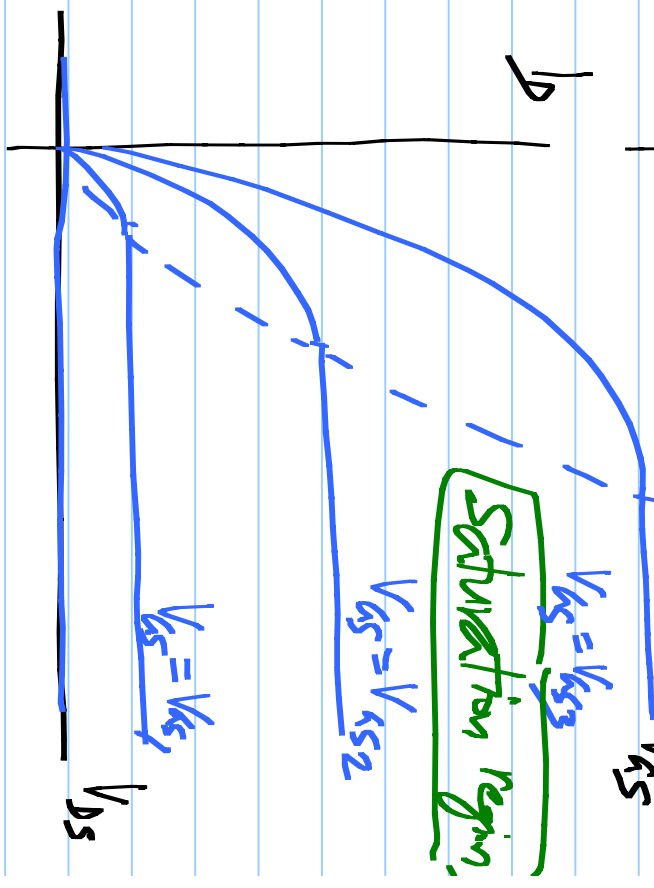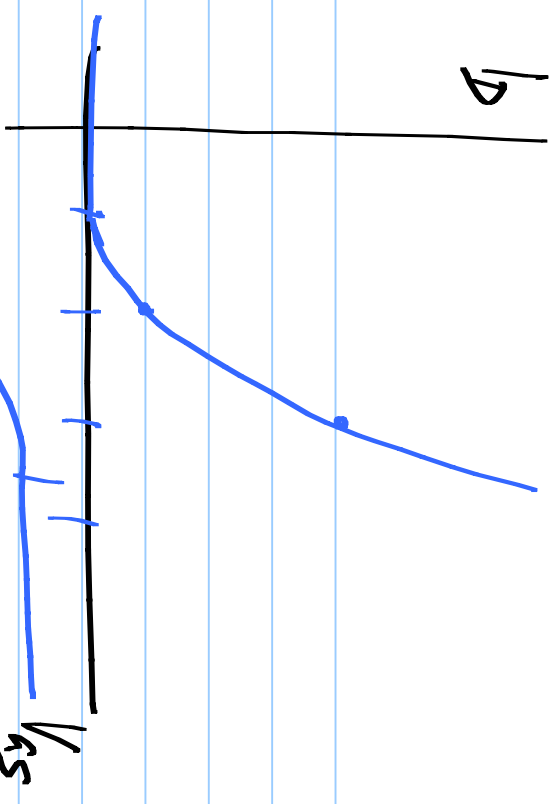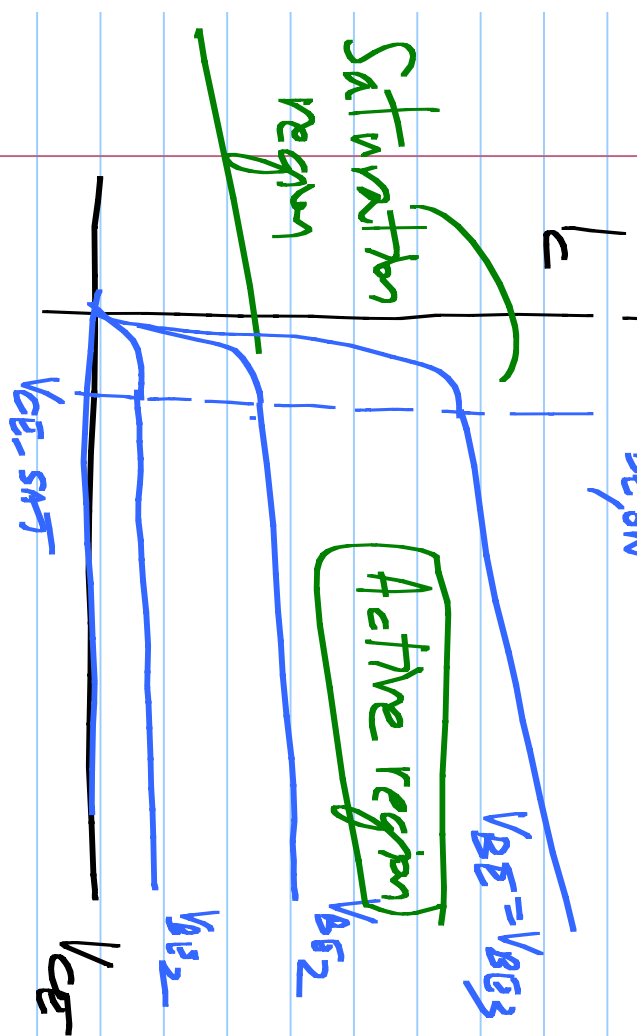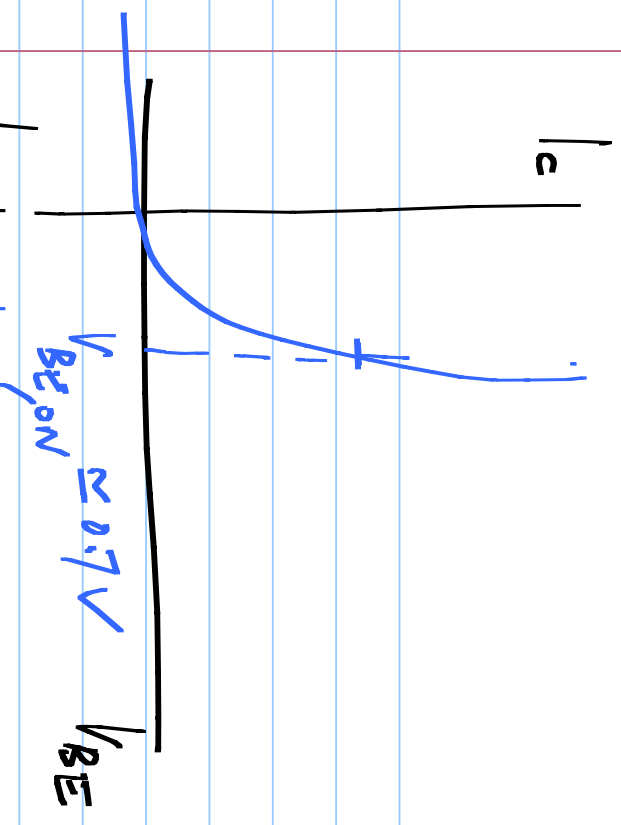

PNP

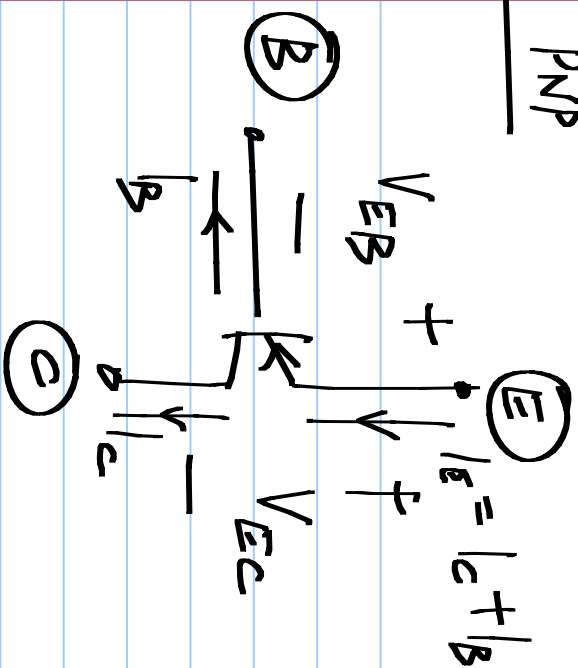

PMOS

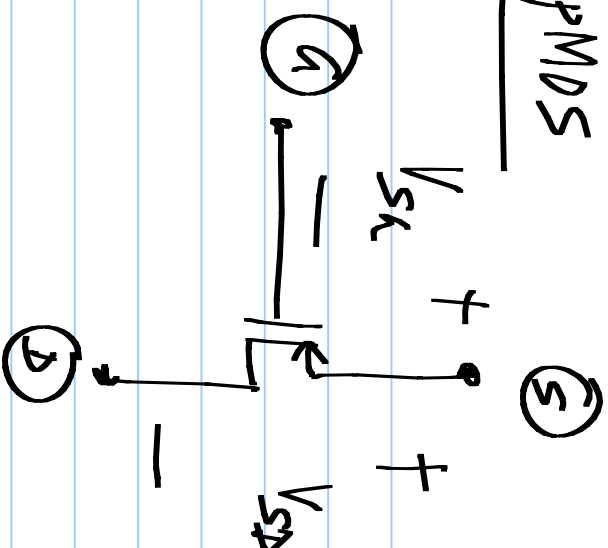


$$I_C = I_S \exp\left(-\frac{V_{EB}}{V_T}\right) \left(1 + \frac{V_{EC}}{V_A}\right)$$

$$I_B = \frac{I_C}{\beta} \quad (\text{Active region})$$


$$V_{EB, \text{on}} \approx 0.7V \quad ; \quad V_{EC} > V_{EC, \text{sat}} \approx 0.7V$$

NPN/PNP

neglected

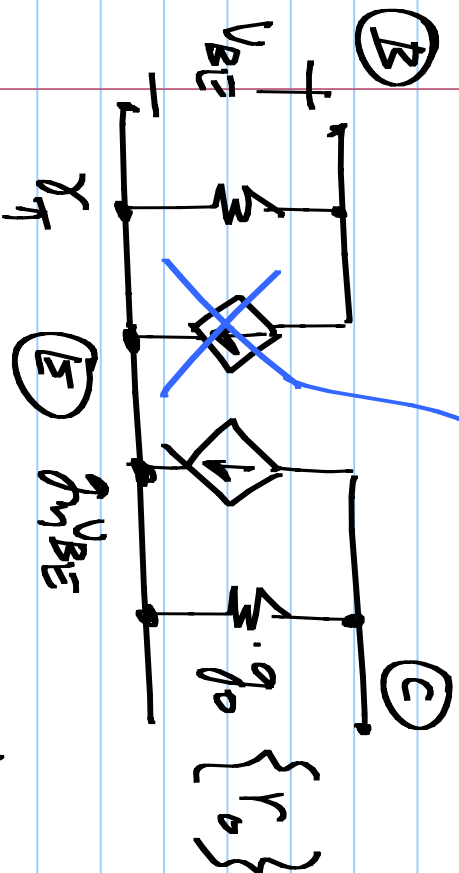

nMOS/pMOS

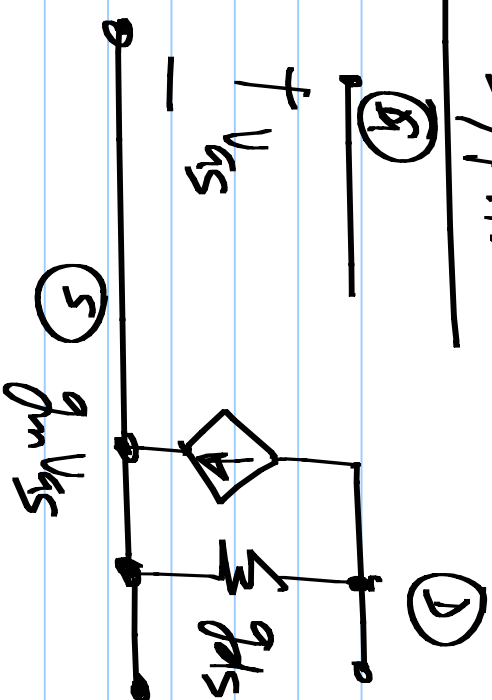

$$g_m = \frac{I_C}{V_T} \quad ; \quad g_o = \frac{I_C}{V_A} = \frac{1}{r_o}$$





$$g_m = \mu_{ox} \frac{W}{L} (V_{GS} - V_T)$$


$$= \frac{2 I_D}{V_{GS} - V_T} = \sqrt{\frac{2 \cdot \mu_{ox} \frac{W}{L} I_D}{V_{GS} - V_T}}$$

$$\frac{1}{r_{\pi}} = \frac{g_m}{\beta}$$


$$r_{\pi} = \frac{\beta}{g_m}$$

$$g_{ds} = \lambda I_D$$

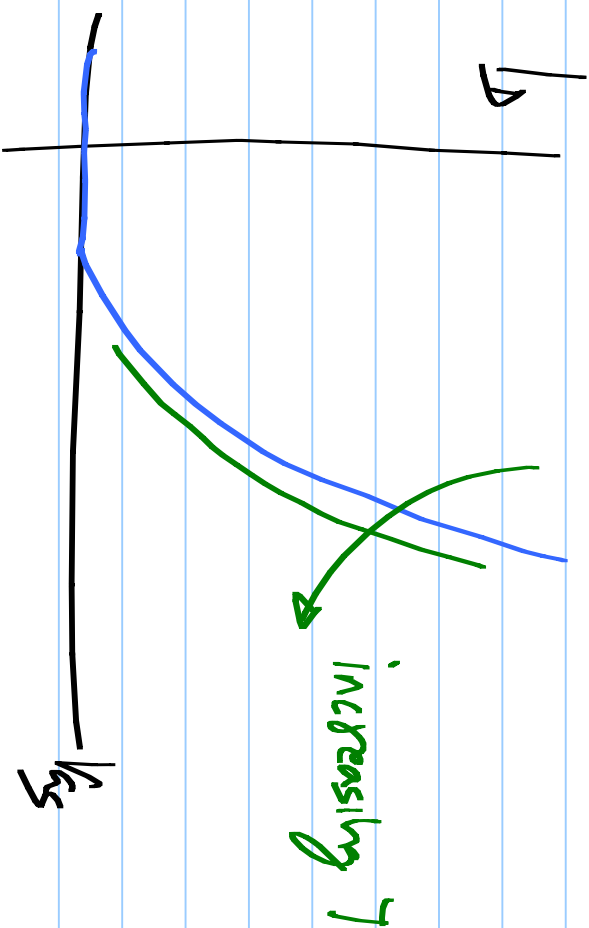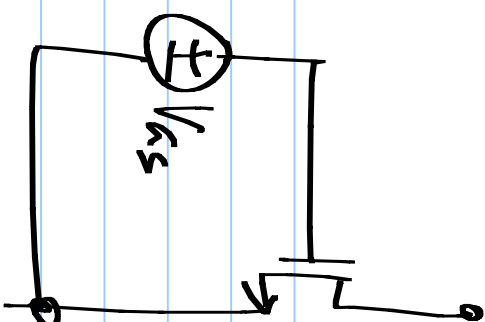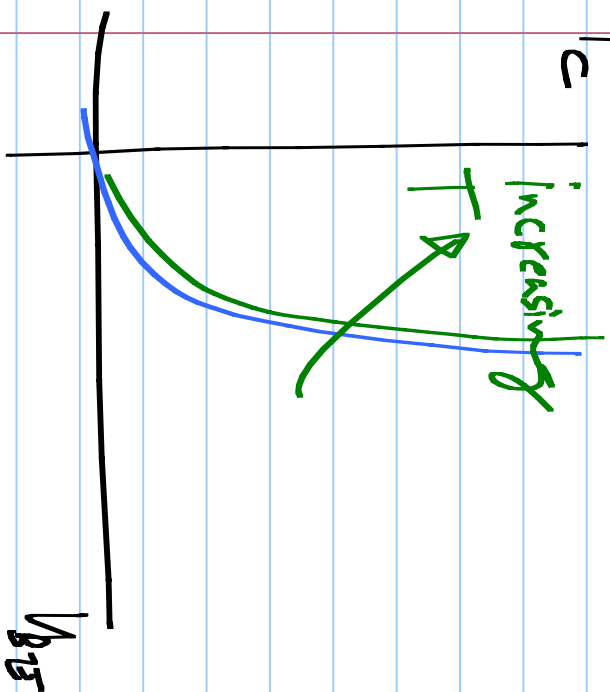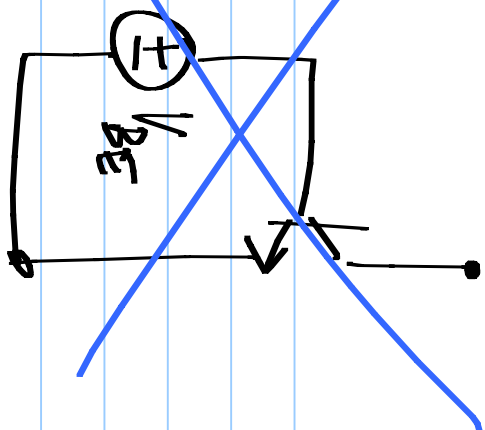

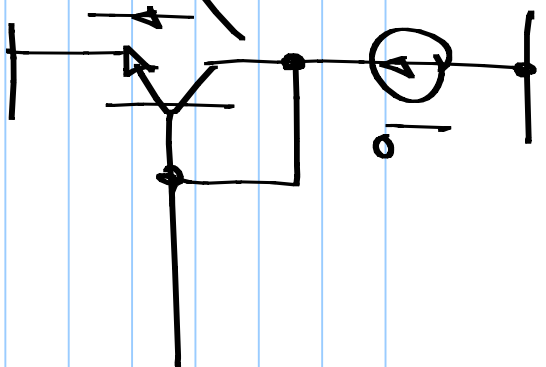

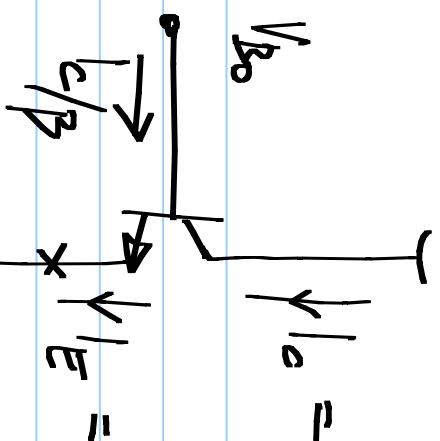BJT
biased at
a fixed
current using
-ve fb.



$$I_c = I_c + I_{c/\beta}$$


$$I_c = \frac{I_E}{(1 + 1/\beta)}$$

$$= \frac{I_0}{(1 + 1/\beta)}$$


$$I_c = \alpha \cdot I_E$$

$$I_0 = I_c + \frac{2I_c}{\beta}$$
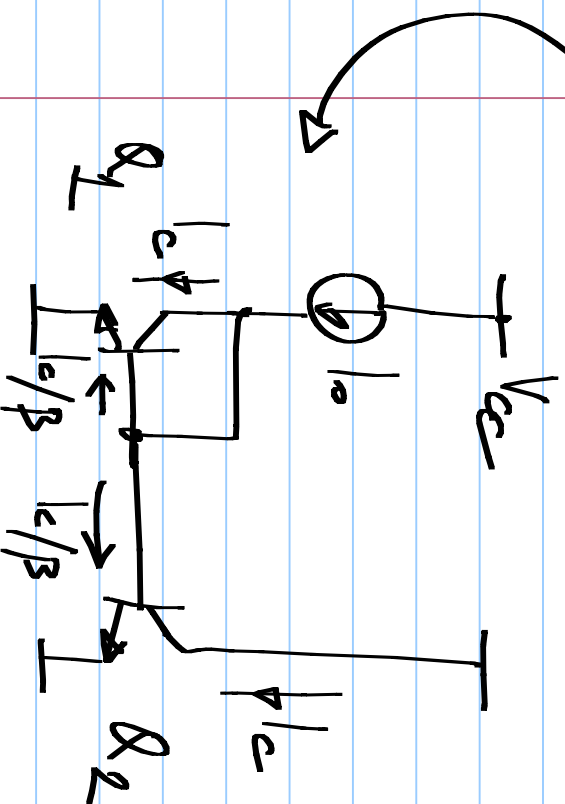
$$I_c = \frac{I_0}{(1 + \frac{2}{\beta})}$$




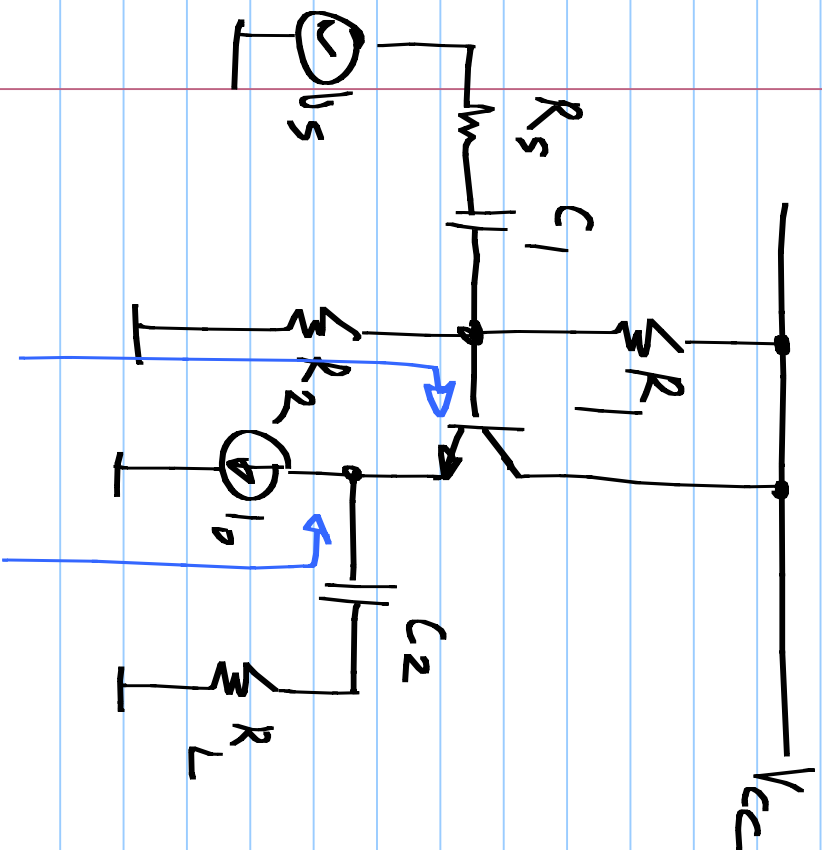Common-drain amplifier — Emitter follower (Collector)



$$R_{in} =$$



$$R_{out} =$$

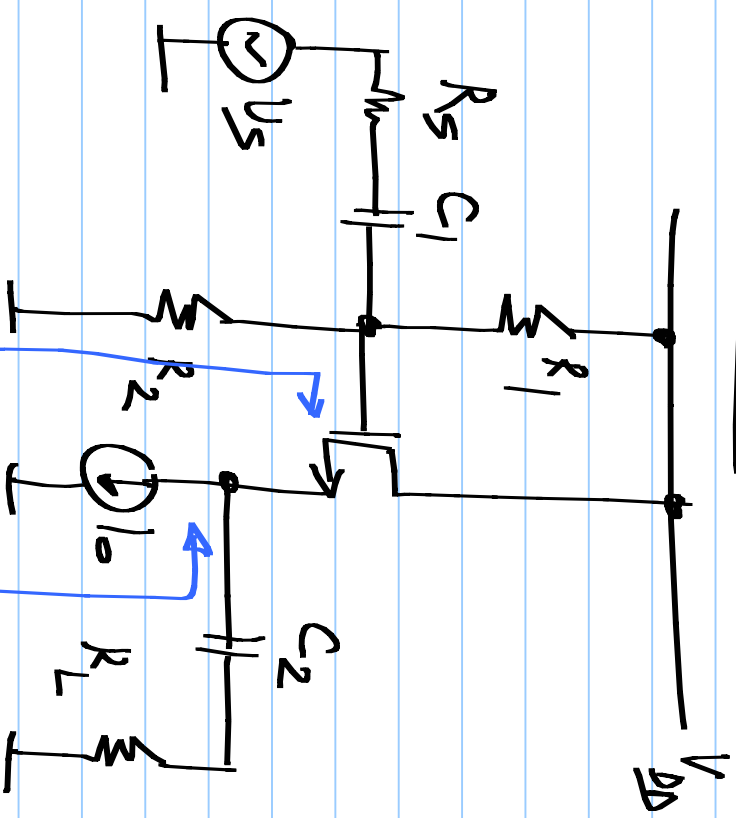

$$R_{in} = \infty$$

$$R_{out} = 1/g_m$$

$$I_B = \frac{I_o}{\beta + 1}$$

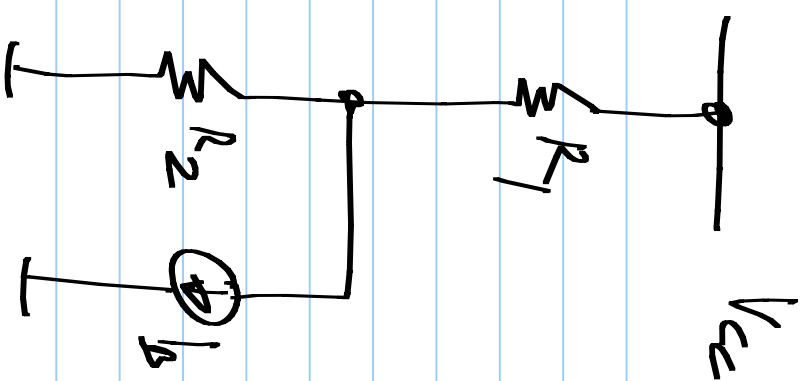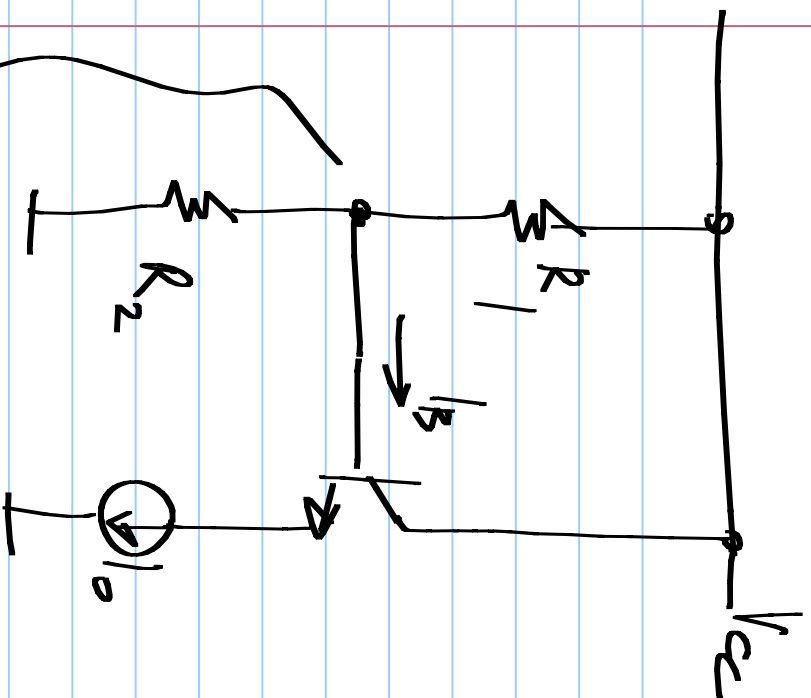

$$V_c = \frac{R_2}{R_1 + R_2} V_{cc} - \frac{I_B (R_1 || R_2)}{\beta + 1}$$

has to be small

