

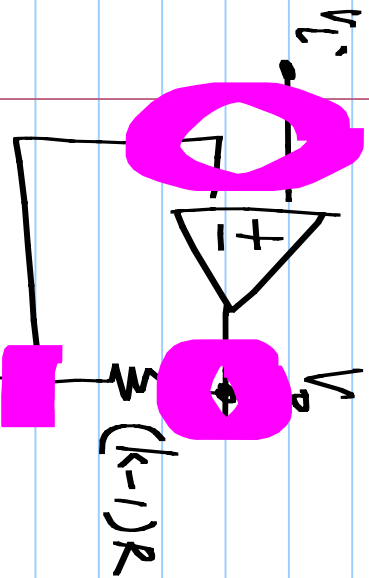


# Lecture 8

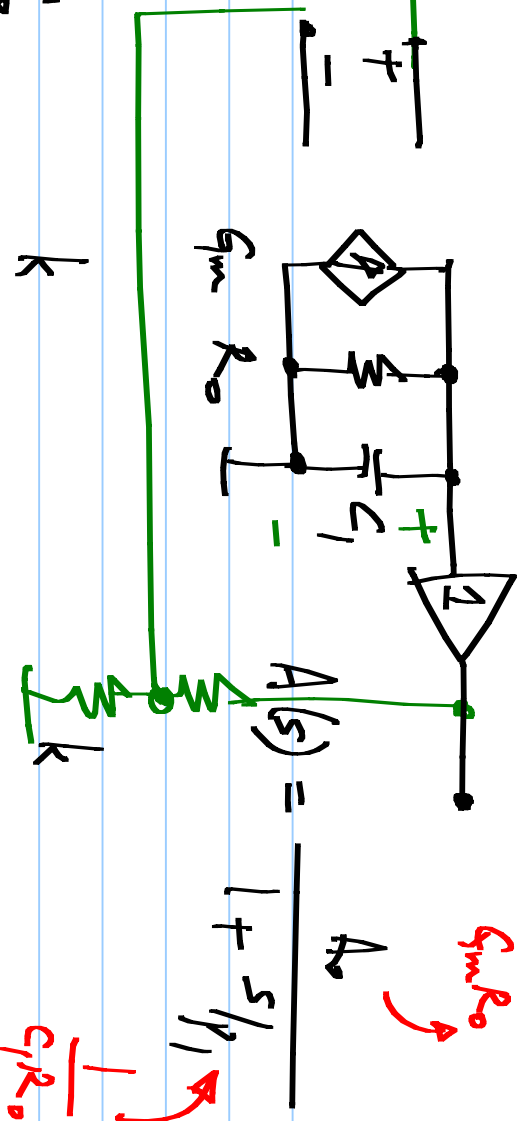
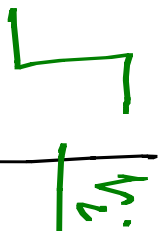
$$\left[ \frac{k}{1 + \frac{k}{A_o}} \right] \frac{1}{1 + \frac{s}{p_a}}$$



$$\frac{v_o}{v_i} = \frac{k}{1 + \frac{k}{A(s)}} = \frac{k}{1 + \frac{k}{A_o} (1 + \frac{s}{p_1})}$$



$$= \frac{k}{\left( 1 + \frac{k}{A_o} \right) + \frac{s}{\left( \frac{A_o}{k} \cdot p_1 \right)}}$$

$$= \frac{k}{1 + \frac{k}{A_o} + \frac{s}{\frac{A_o}{k} p_1 (1 + \frac{k}{A_o})}}$$


$$= \frac{k}{1 + \frac{k}{A_o} + \frac{s}{\frac{A_o}{k} p_1 (1 + \frac{k}{A_o})}}$$

Closed loop amplifier

$$P_a = P_1(A_1)$$


\* Guaranteed to be stable.


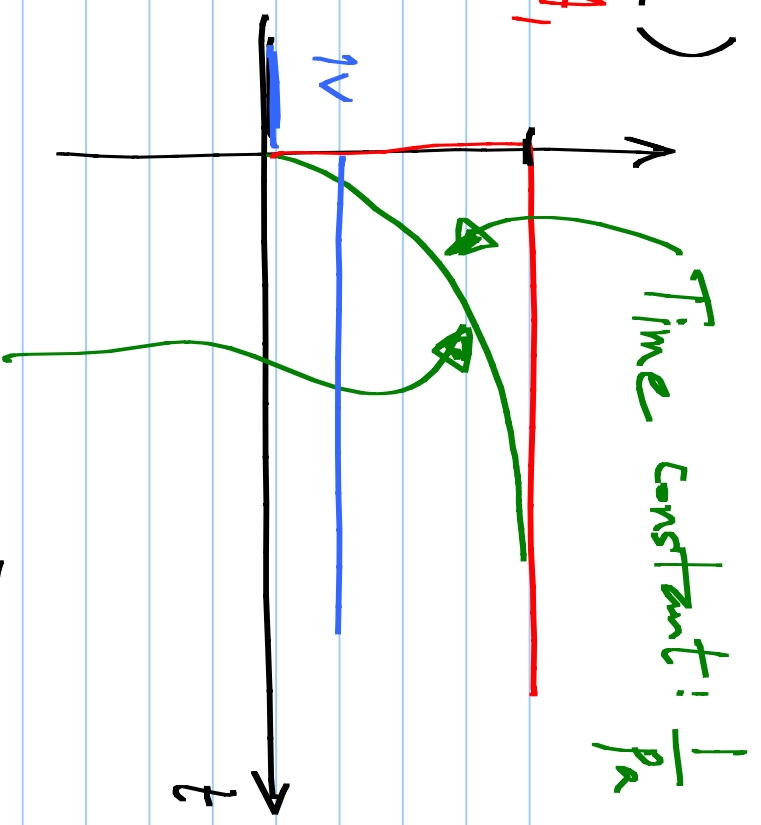
$$\frac{1}{s} \cdot \frac{A_1}{1 + s/p_a}$$



$$A_1 \left[ \frac{1}{s} - \frac{1/p_a}{s + 1/p_a} \right]$$

$$A_1 [1 - \exp(-P_a t)] v(t)$$

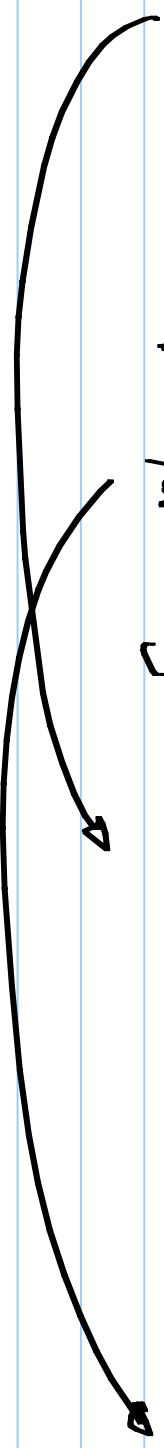

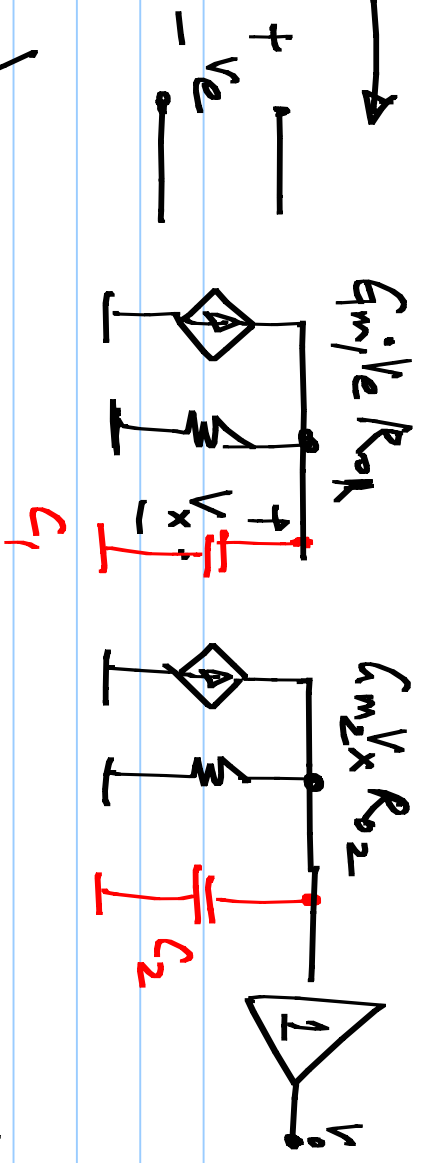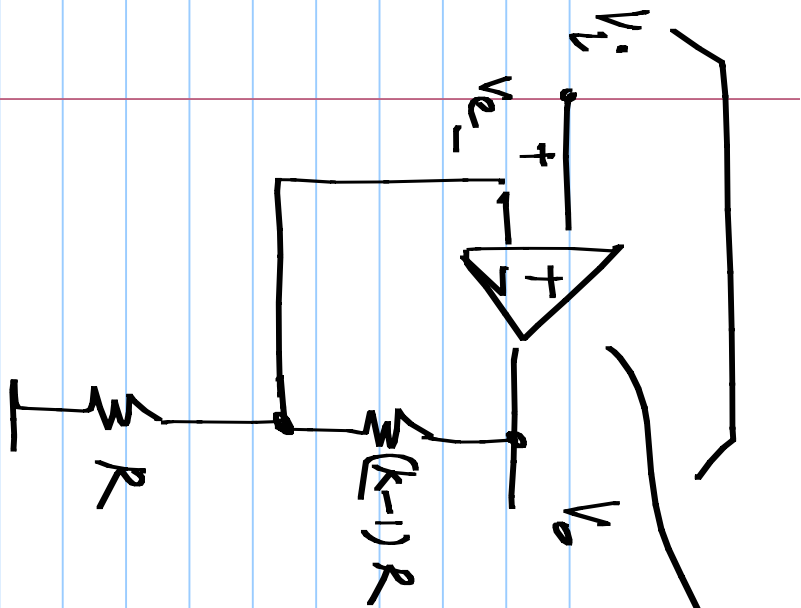

Two stage opamp:

$$\frac{V_o}{V_e} = \frac{G_{m1} G_{m2} R_{o1} R_{o2}}{(1 + s C_1 R_{o1}) (1 + s C_2 R_{o2})}$$

$A_{10}$

$$= \frac{A_{10}}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{k}{A(s)}} = \frac{k}{1 + \frac{k(1+s/p_1)(1+s/p_2)}{A_o}}$$

$$= \frac{k}{\left(1 + \frac{k}{A_o}\right) + \frac{k}{A_o} \left(\frac{1}{p_1} + \frac{1}{p_2}\right) \cdot s + \frac{s^2}{p_1 p_2} \cdot \frac{k}{A_o}}$$

$$s^2 + 2\zeta \omega_n s + \omega_n^2 \quad \left| \quad \frac{s^2}{\omega_n^2} + \frac{s}{\omega_n} + 1 \right.$$

$$\frac{V_0}{V_L} = \frac{k}{1 + \frac{k}{A_0} + s \cdot \frac{k}{A_0} \left( \frac{1}{p_1} + \frac{1}{p_2} \right) + s^2 \cdot \frac{k}{A_0} \frac{1}{p_1 p_2}}$$

$$\omega_n = \sqrt{\left( \frac{A_0}{k} + 1 \right) p_1 p_2} \quad \omega_c = \frac{p_1 + p_2}{2 \sqrt{\left( \frac{A_0}{k} + 1 \right) p_1 p_2}}$$

$$R_L = \frac{\sqrt{\frac{A_0}{k} + 1}}{\sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}}} = \frac{1}{2} \cdot \frac{1}{\sqrt{\frac{A_0}{k} + 1}} \cdot \left( \sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right)$$

