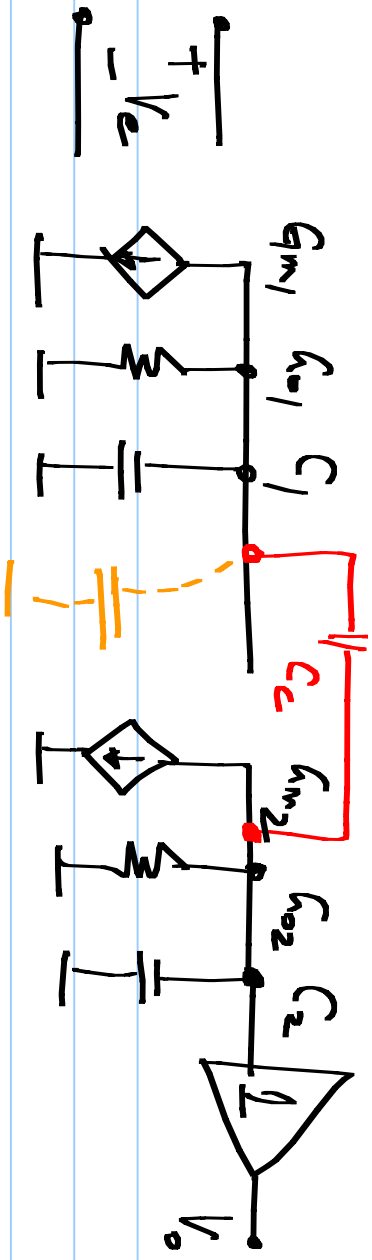


Lecture 13

$k=10$



$$V_o = \frac{V_e}{k-1} \cdot \frac{g_{m1} (g_{m2} - sC_c)}{s^2 (C_1 C_2 + C_2 C_1) + s [g_{m2} C_2 + g_{o1} (C_2 + C_c) + g_{o2} (C_1 + C_2)] + g_{o1} g_{o2}}$$

$$As^2 + bs + c = 0 \quad \left\{ \begin{array}{l} s_1 = -\frac{c}{b} \\ s_2 = -\frac{b}{a} \end{array} \right.$$

Without C_c

$$s_1 = -\frac{g_{m1}}{C_1} \quad s_2 = -\frac{g_{m2}}{C_2}$$

output of the 1st stage
output of the 2nd stage

With C_c

$$s_1 = -\frac{g_{m1} g_{m2}}{g_{m2} C_c + g_{m1} (C_2 + C_c) + g_{m2} (C_1 + C_c)}$$

$$s_2 = -\frac{g_{m1}}{C_1}$$

$$C_1 + \left(\frac{g_{m2}}{g_{m2}} + 1 + \frac{g_{m1}}{g_{m2}} \right) (C_c + \frac{g_{m1}}{g_{m2}})$$




Miller multiplied C_c

$$s_2 \approx -\frac{g_{m2} C_c + g_{m1} (C_2 + C_c) + g_{m2} (C_1 + C_c)}{C_1 C_c + C_c C_2 + C_2 C_1}$$

$$= -\frac{g_{m2} + g_{m1} \frac{C_2 + C_c}{C_1 + C_c} + g_{m1} \frac{C_2 + C_c}{g_{m2}}}{C_2 + \frac{C_1 C_c}{C_1 + C_c}}$$

$$C_2 + \frac{C_1 C_c}{C_1 + C_c}$$




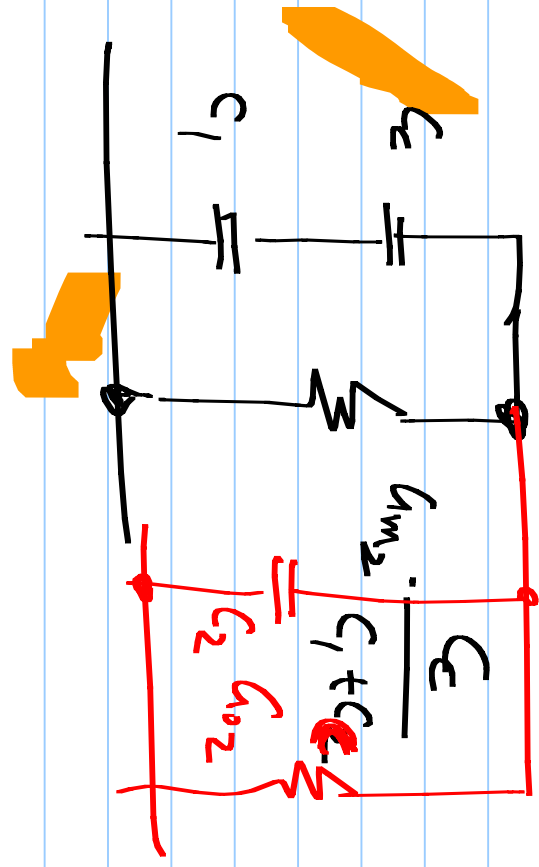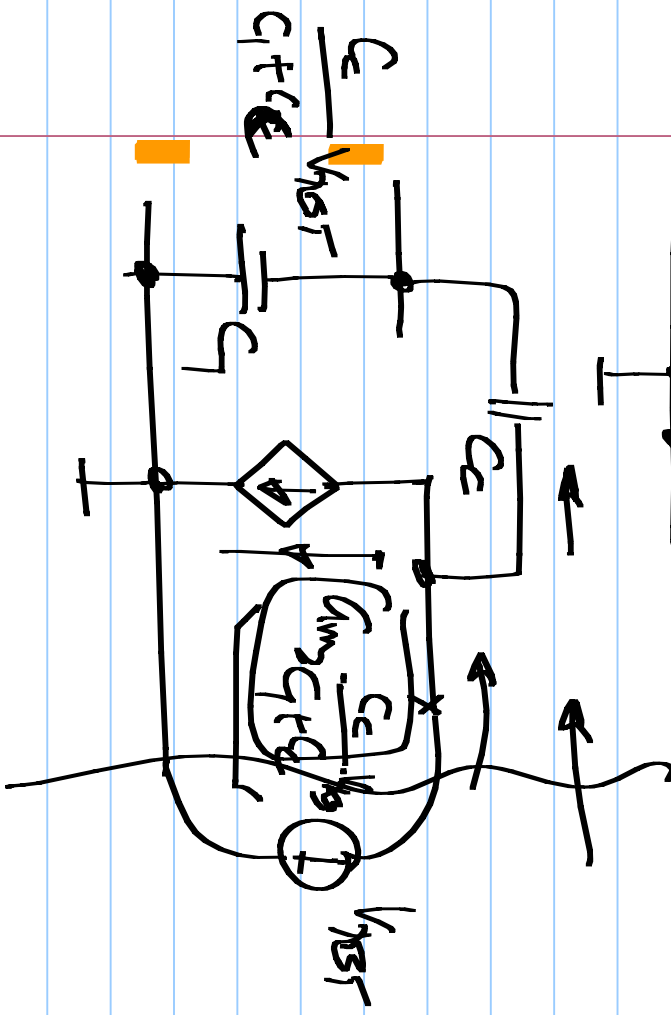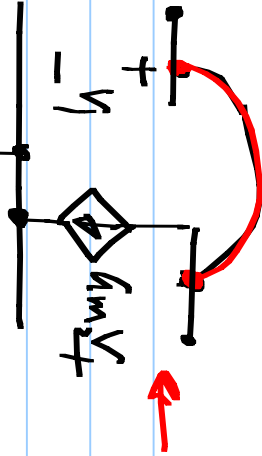

$$W_{u,loop} < p_2 \left(= -s_2 \right) \approx \frac{G_m2 \cdot \frac{C_c}{C_1 + C_c}}{C_2 + \frac{C_1 C_c}{C_1 + C_c}} \approx \frac{G_m2}{C_1 + C_2}$$

$C_c \gg C_1$

$$|A_{dc,loop} \cdot s_1| = \frac{1}{K} \cdot \frac{G_{m1} G_{m2}}{G_{o1} G_{o2}} \cdot \frac{G_{o1} G_{o2}}{G_{m2} C_c + G_{o1} (C_2 + C_c) + G_{o2} (C_1 + C_c)}$$

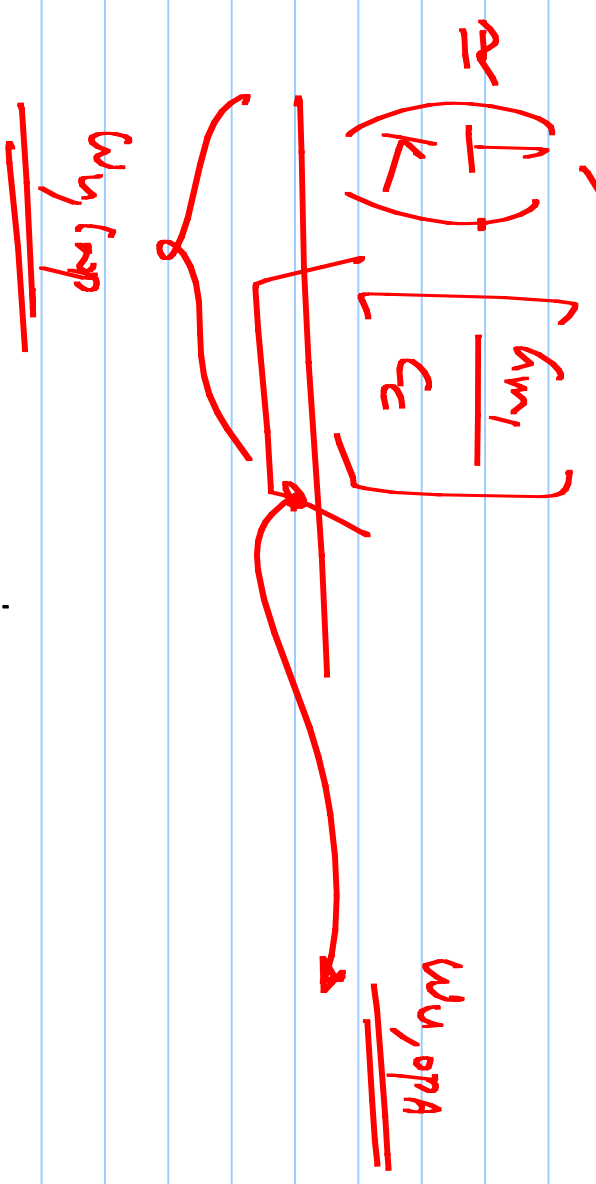

$$L(s) = \frac{A_0}{K} \frac{[1 - s/z_1]}{(1 + s/p_1)(1 + s/p_2)}$$

2.5 Mod/ls
227 Mod/ls

$$\angle L = -\frac{\pi}{2} - \tan^{-1}\left(\frac{1}{K} \cdot \frac{g_{m1}}{g_{m2}}\right) - \tan^{-1}\left(\frac{\omega_{loop}}{p_2}\right) = -104^\circ$$

$s = j\omega_{loop}$

$$-\tan^{-1}\left(\frac{\omega_{loop}}{z_1}\right)$$

$$Z = \frac{g_{m2}}{C_c}$$

$$\omega_{loop} = \frac{1}{K} \cdot \frac{g_{m1}}{C_c}$$

$$C_c = \frac{1}{100} \cdot \frac{11 \mu F}{4} \cdot 4$$



$$p_2 \approx \left[\frac{g_{m2}}{C_1 + C_c} \right] \left\{ C_c \gg C_1 \right\} = 0.4 \mu F$$

