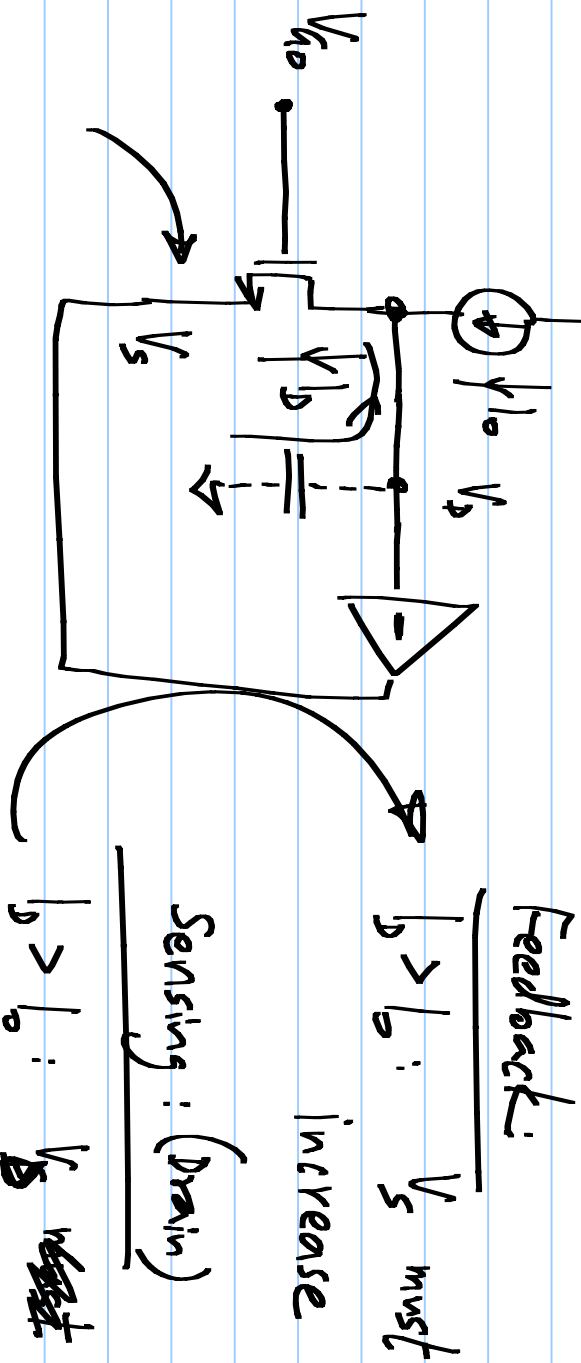


Lecture 20

Biasing @ I_D :

Sensing @ drain, FB to source




Feedback:

$I_D > I_{D0}$: V_s must increase


Sensing: (Drain)

$I_D > I_{D0}$: V_s must decrease

$V_{dc} + V_{ac}$ op-point

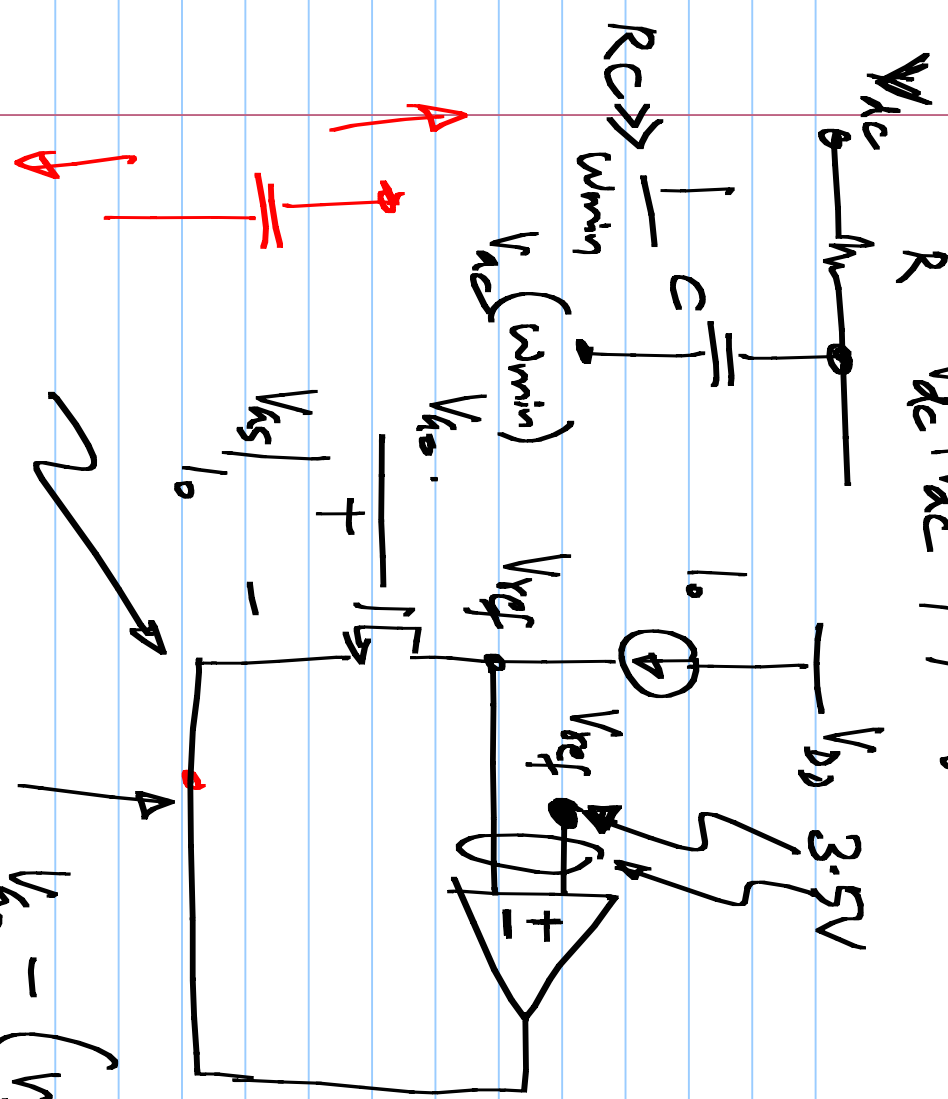


signals (ac)

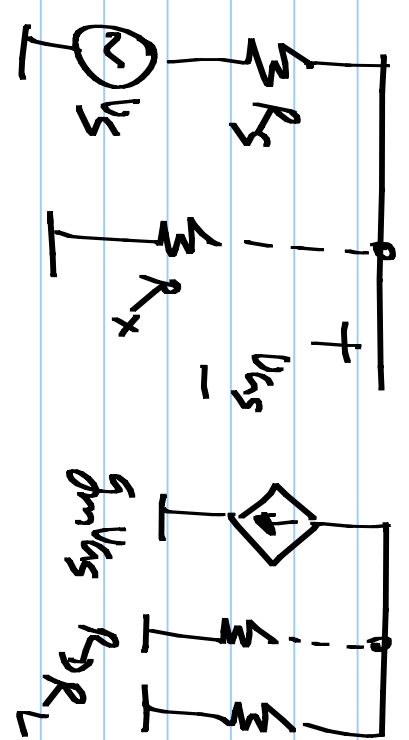

$$V_o = (V_T + \sqrt{\frac{2I_o}{\mu_n C_{ox} W/L}})$$

Sensing @ source, feedback to the gate

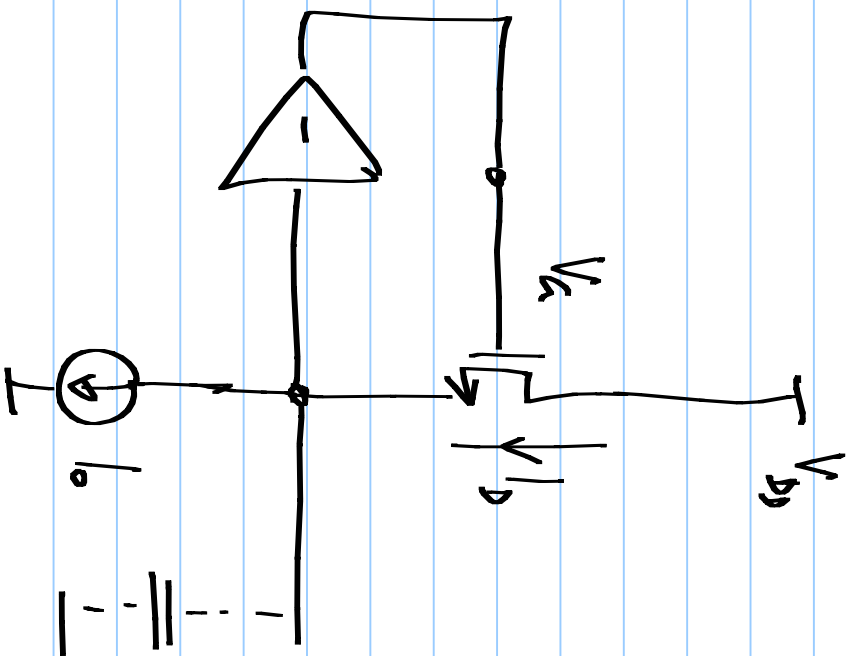


Feedback:


$I_d > I_o$: V_a must decrease

Sensing


$I_d > I_o$: V_s increases

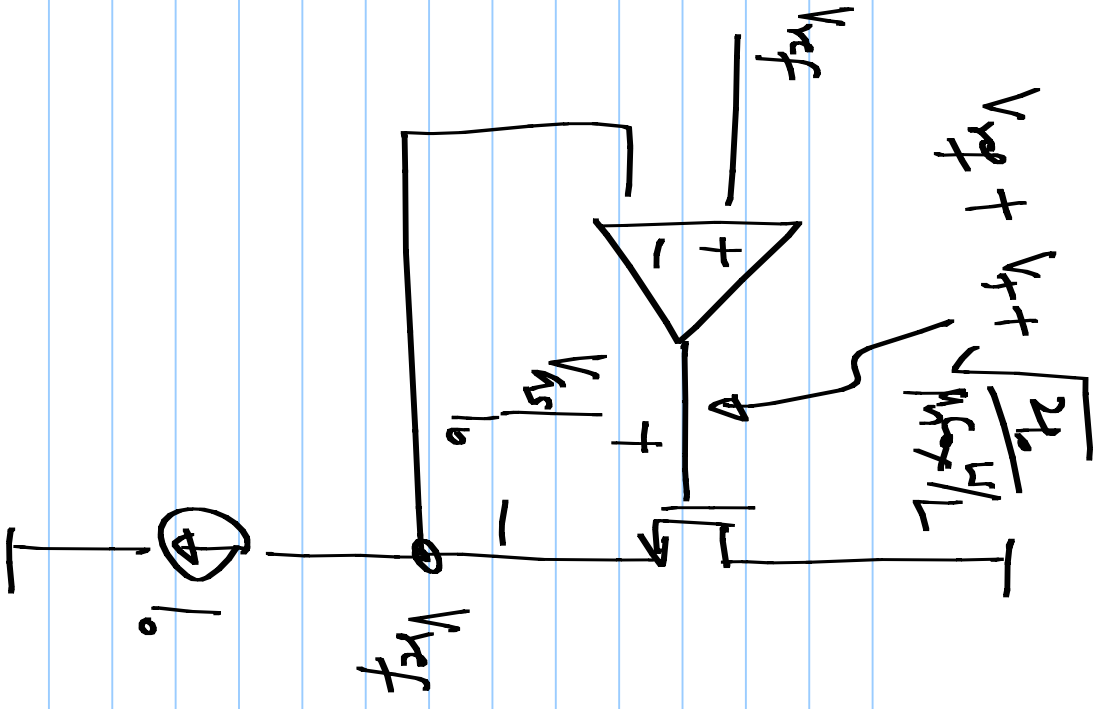



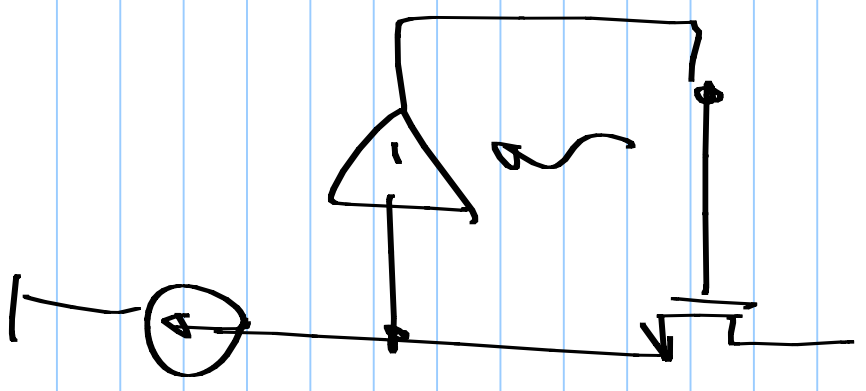
$$V_{ref} + V_{ref} + \sqrt{\frac{2I_0}{\mu_n C_{ox} W/L}}$$




Controlled source :

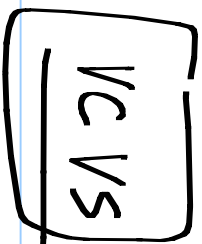

(Realized using negative feedback)

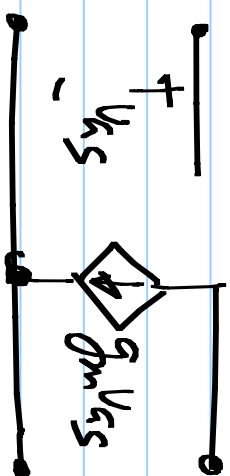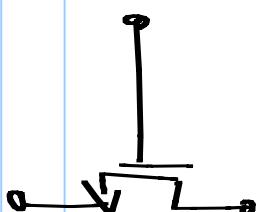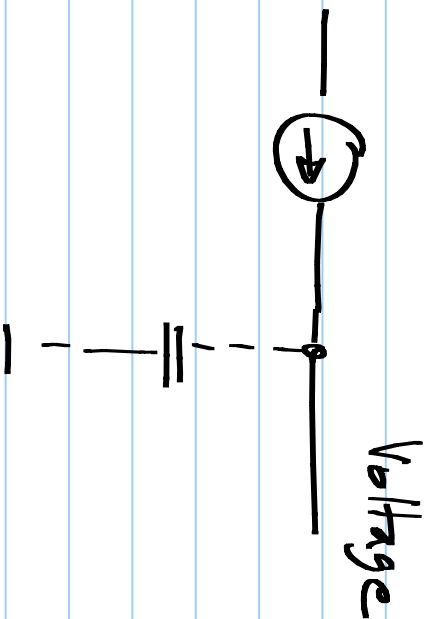

Voltage controlled voltage source

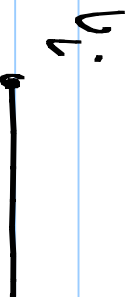

Sense v_o
control v_o



$$v_o = k \cdot v_i$$

$$v_o = v_i \quad k=1$$

$$v_i - v_o > 0$$


$$v_o < v_i$$

* ~~larger~~ current must be pushed into the o/p node


$\Rightarrow v_{rs}$ must increase

Current source increase the voltage (2)

increase i_{push}

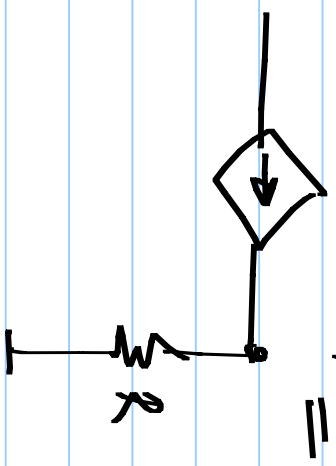

VCVS

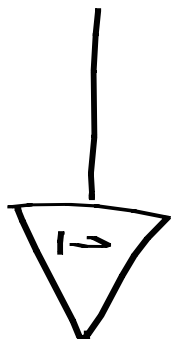

⑤


$$V_o = V_i$$

$$\underbrace{(V_o - V_i)}_{= 0} = 0$$

$$V_i \approx V_o > 0$$

Make $V_{gs} = (V_i - V_s)$

to have the right sense of feedback

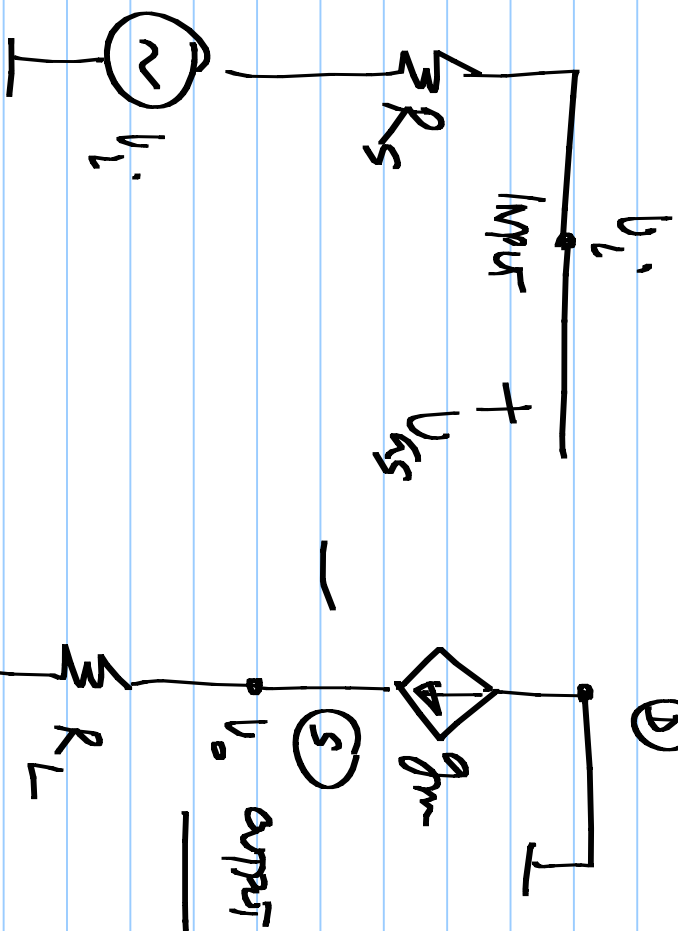

$$\frac{V_o}{V_i} =$$

$$\frac{g_m R_L}{1 + g_m R_L}$$

$$\approx 1$$

$$g_m \gg \frac{1}{R_L}$$