

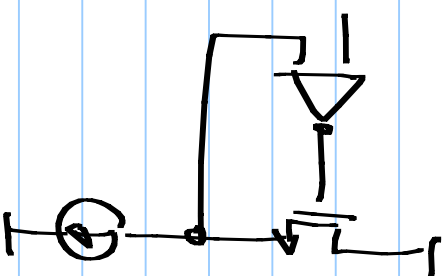
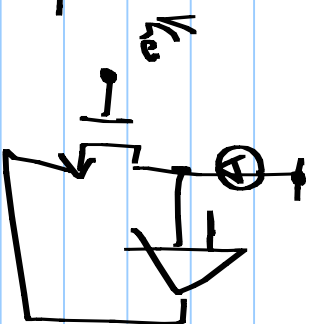
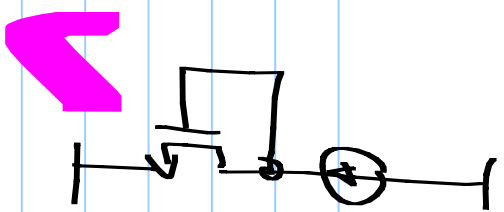



CCVS using a transistor.

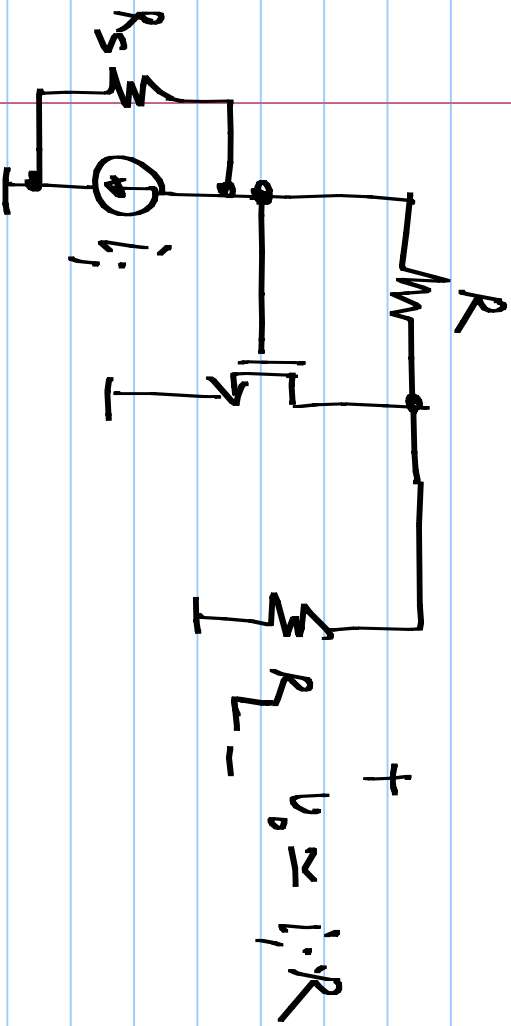

!!

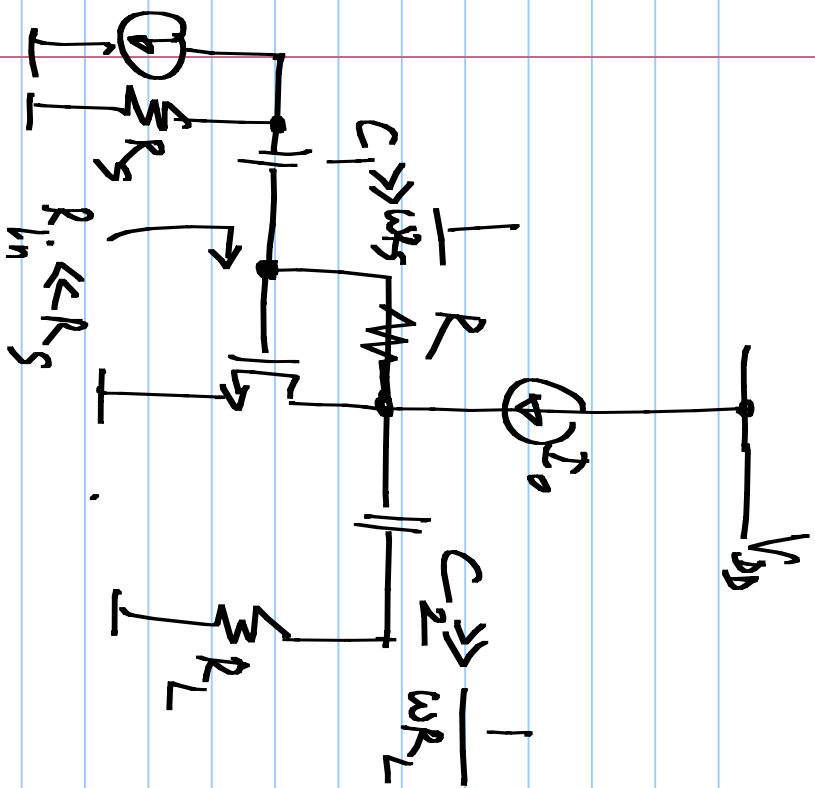


CCVS

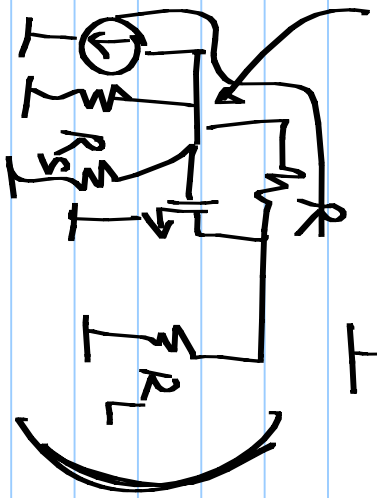

$$\frac{V_o}{I_0} = R$$





$$C_2 \gg \frac{1}{\omega R_L}$$

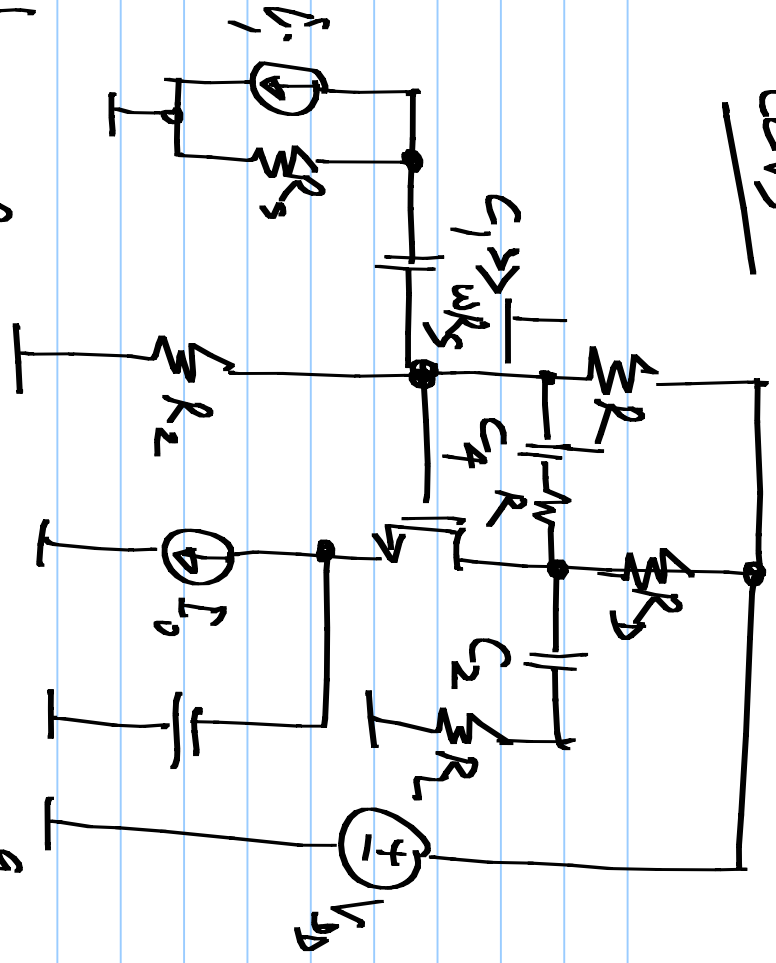



CCVS



CCVS using an opamp

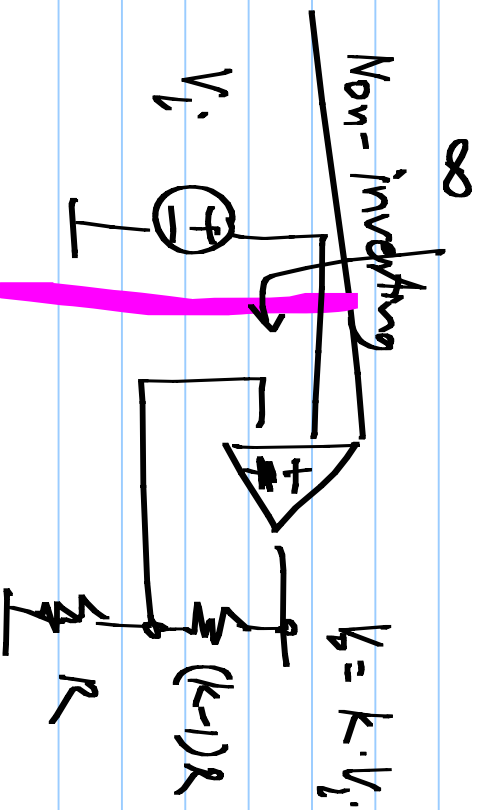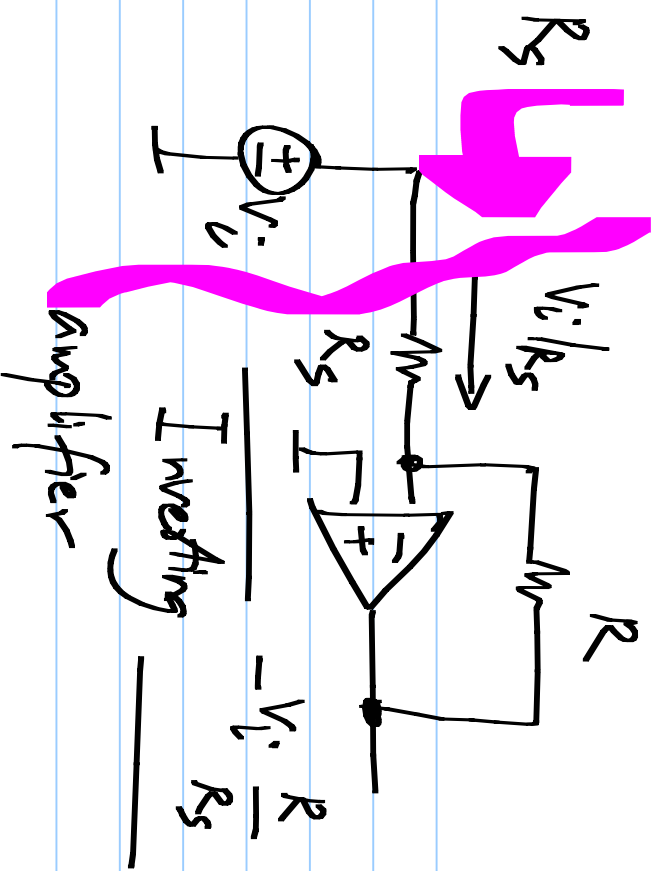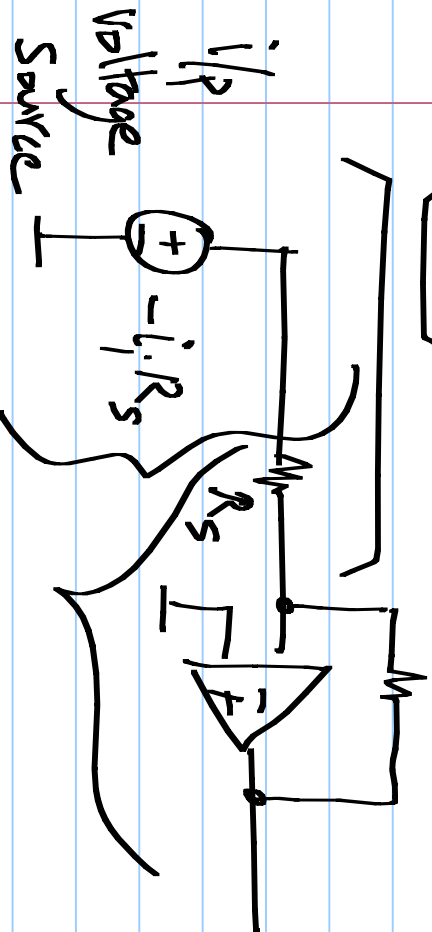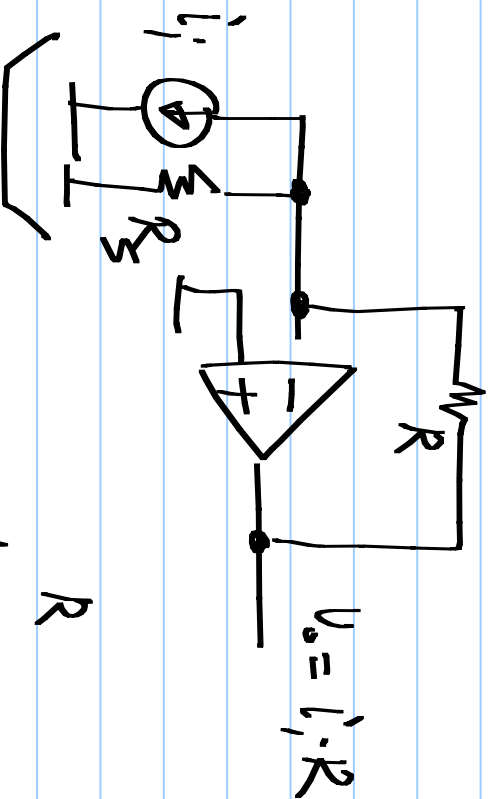


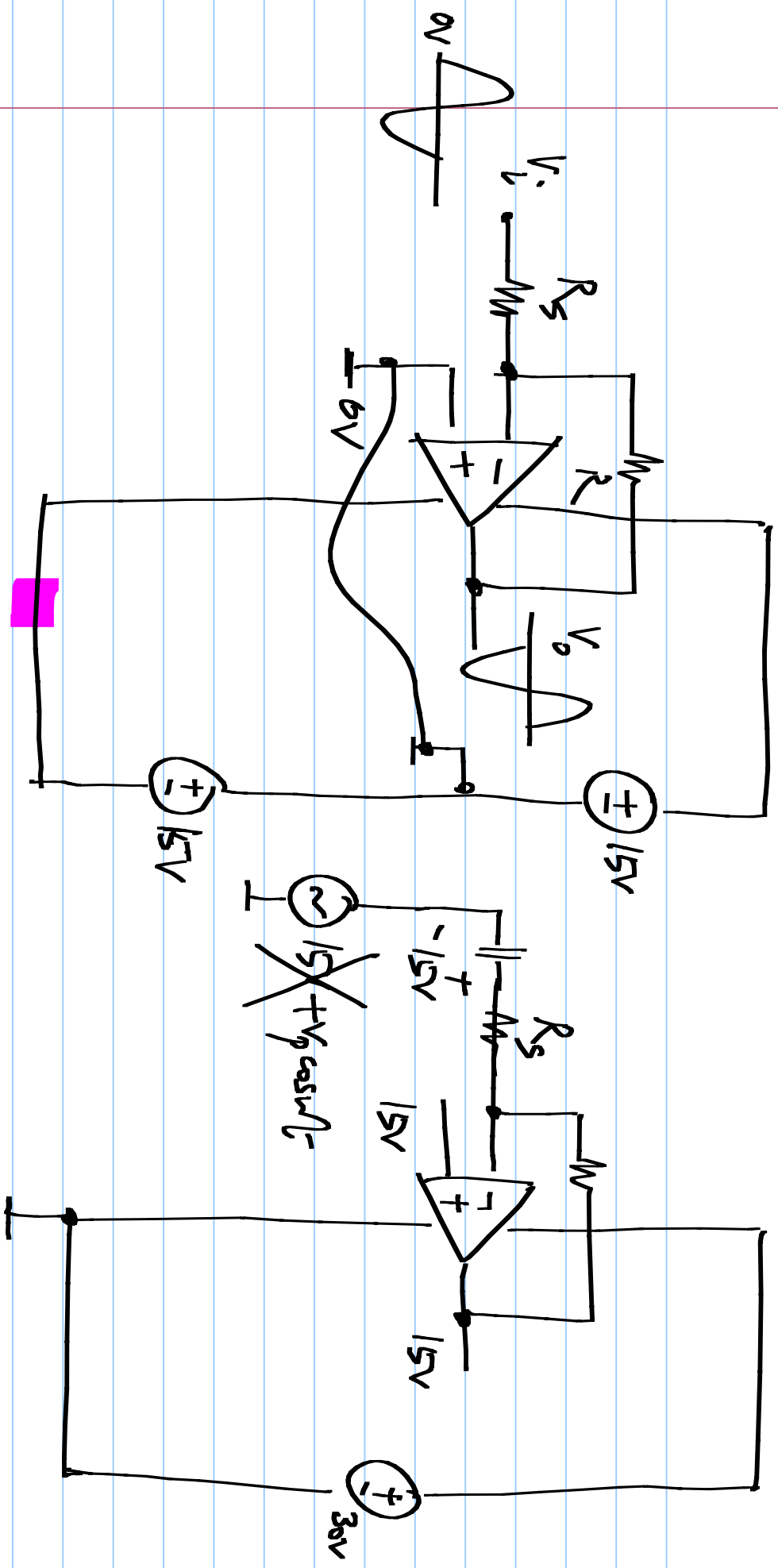


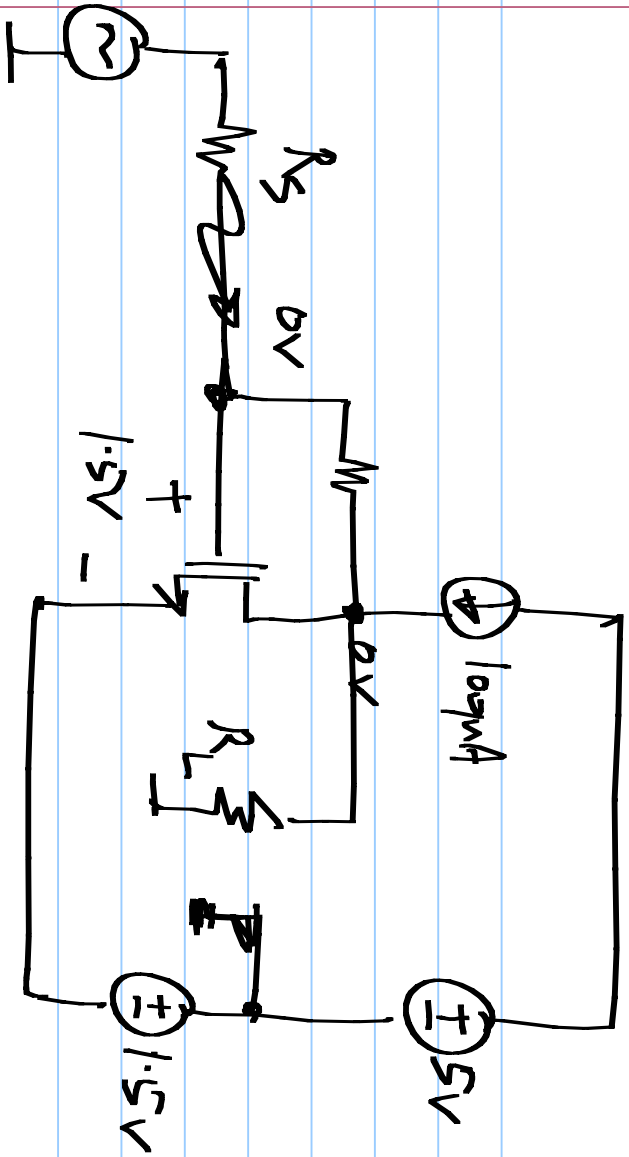


R. very large

$g_p \approx -g_m R_L V_i$

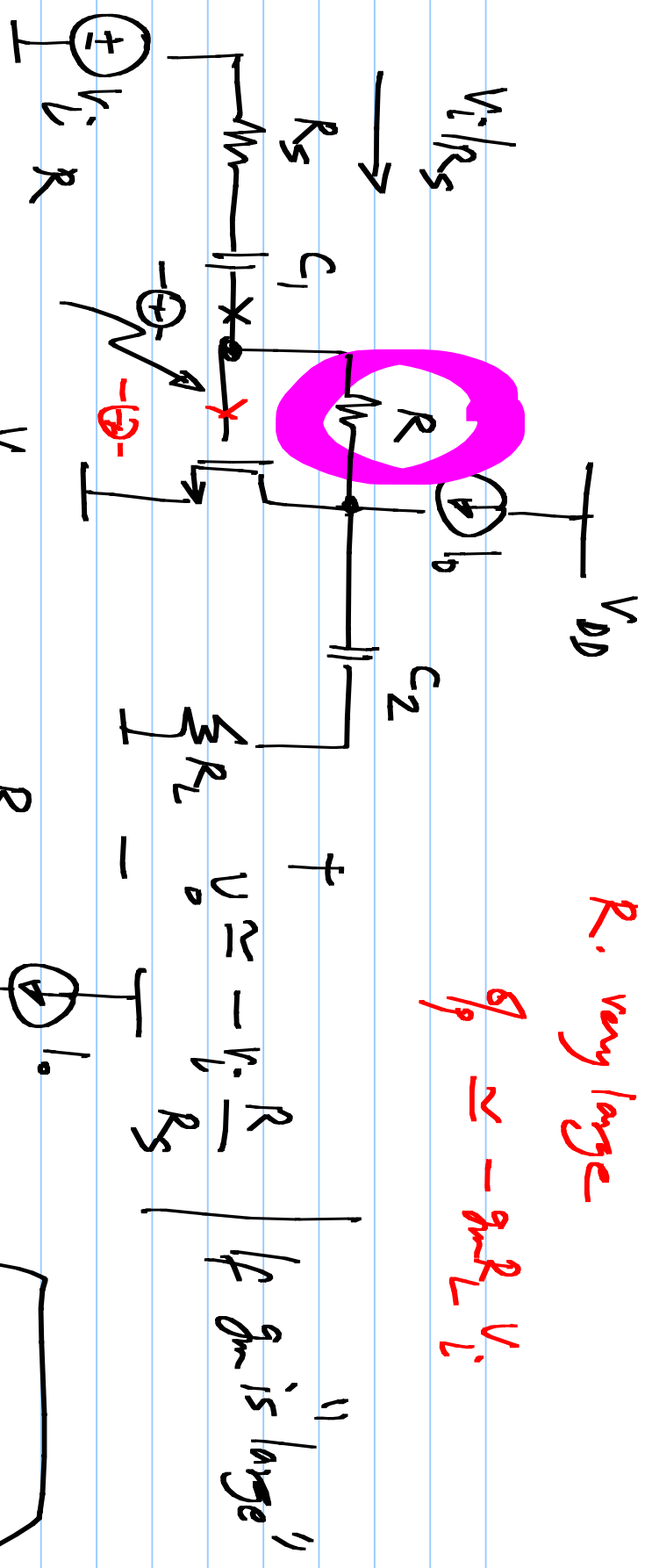


"If g_m is large"

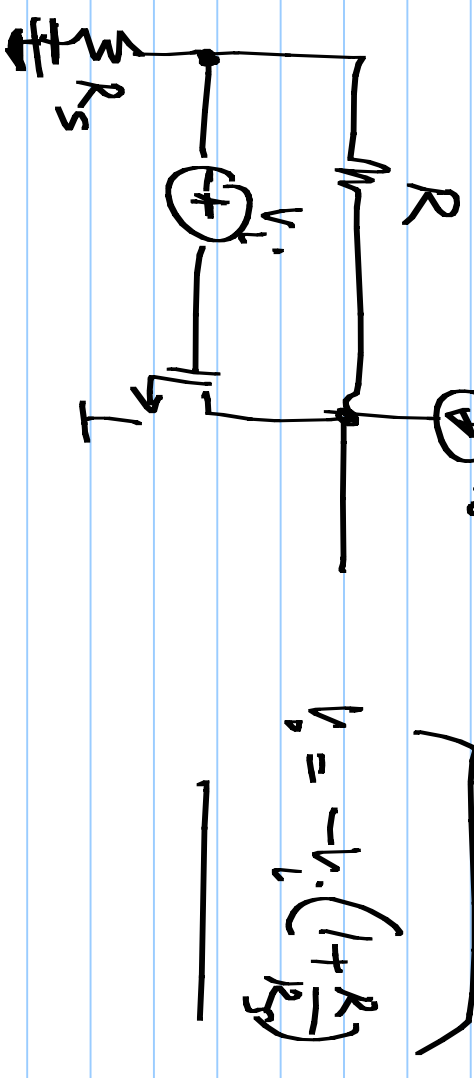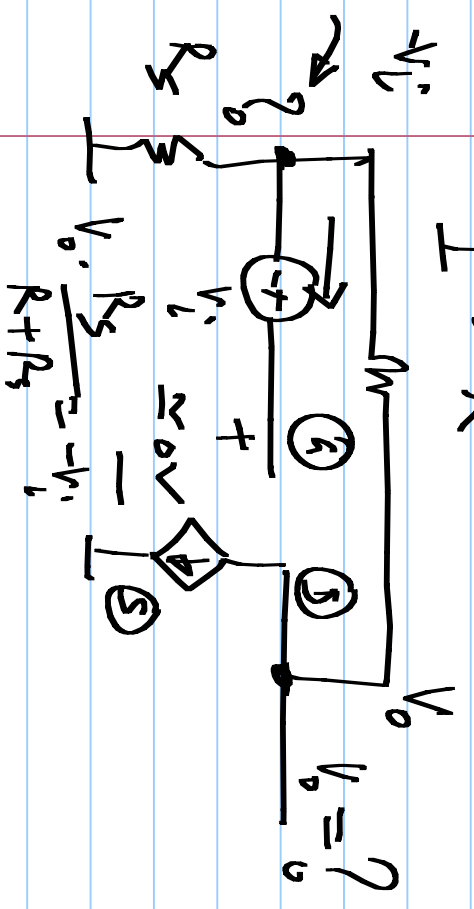

$V_o = -V_i \cdot \left(1 + \frac{R}{R_S}\right)$

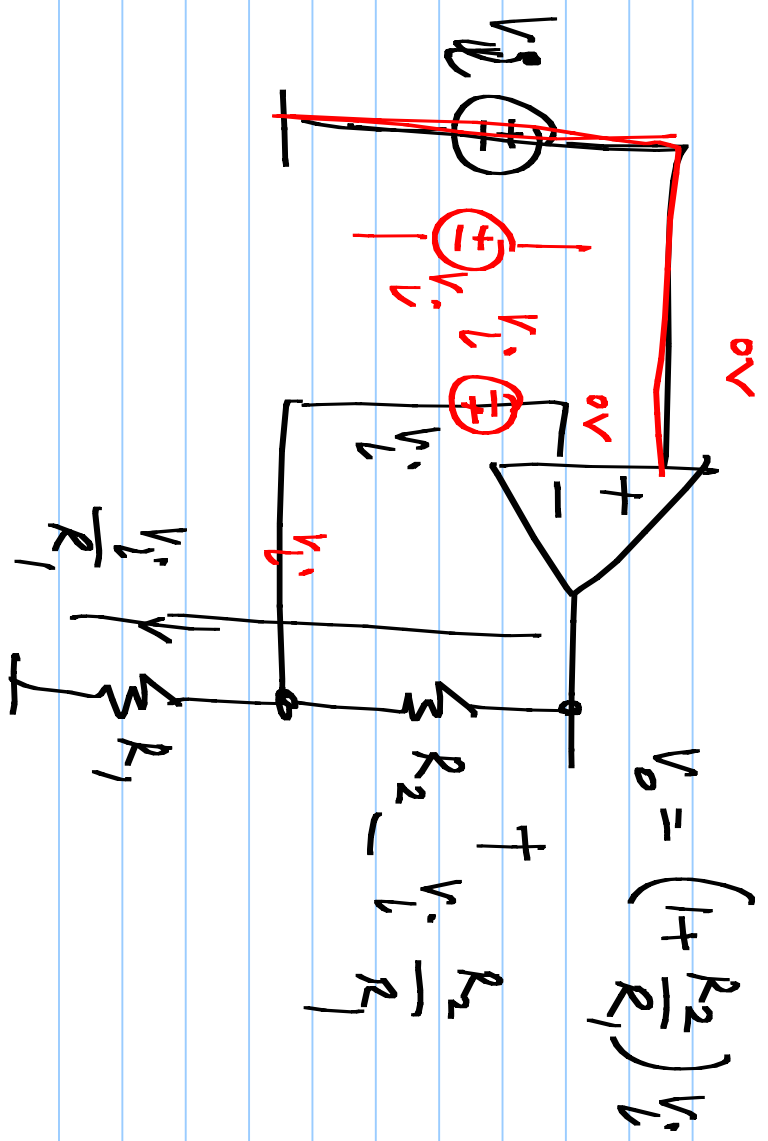$V_o \cdot \frac{R_S}{R+R_S} \approx -V_i$



$$v_o = \left(1 + \frac{R_2}{R_1}\right) v_i$$

-

—

