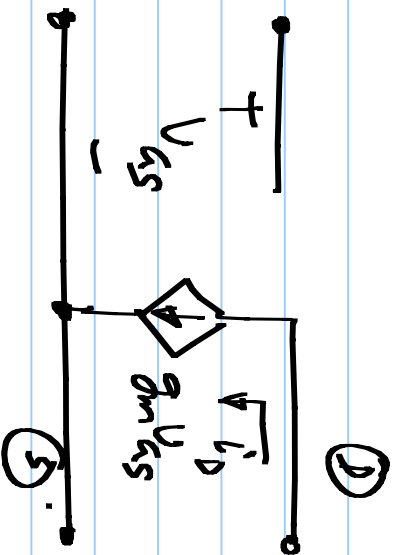


Lecture 24 : CCCS using a transistor



$$I_o = k \cdot I_i \quad k=1$$

$I_o = I_i$ current

$i_o = i_i$ buffer





If $i_o > i_i$ $R_L = 0$

$i_o > i_i$ must decrease $R_o = \infty$

V_{gs} must decrease



$i_o < i_i$


V_{gs} must increase

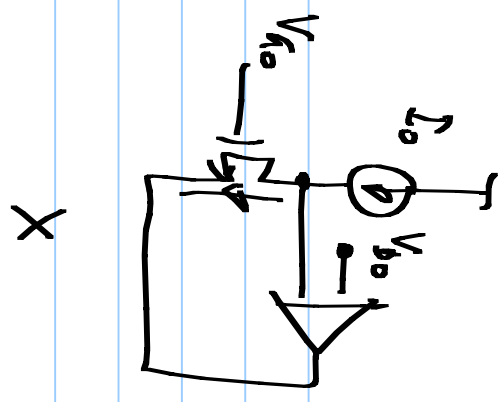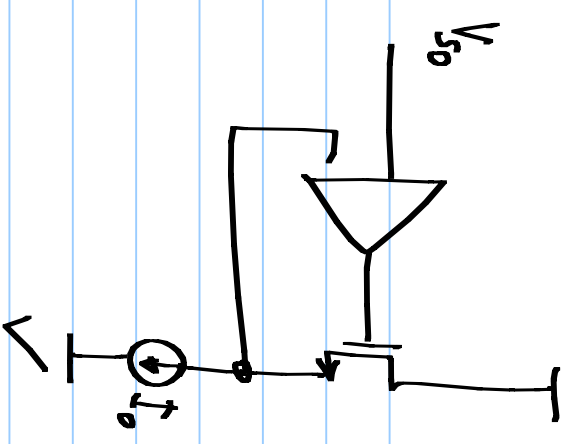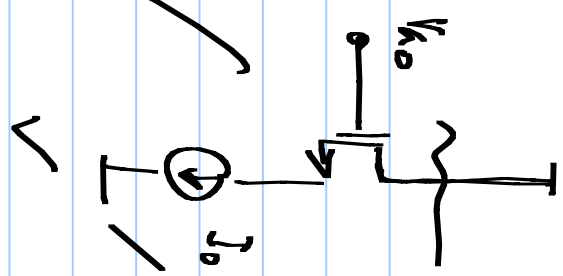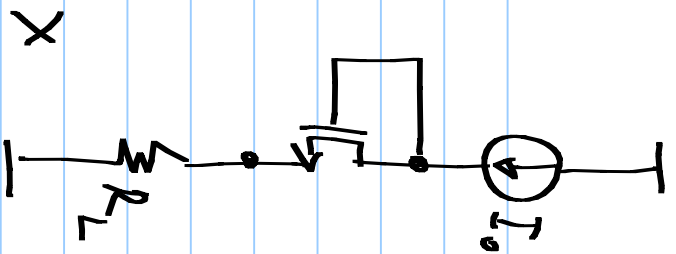


Compare I_o & I_s at the source terminal

Feedback to the source

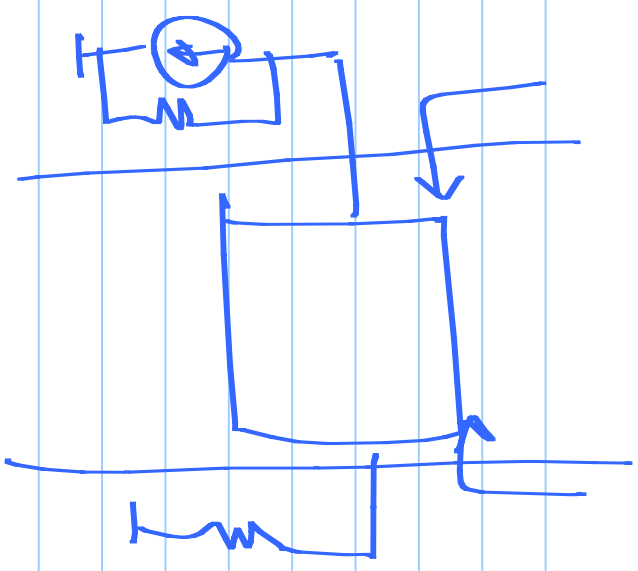
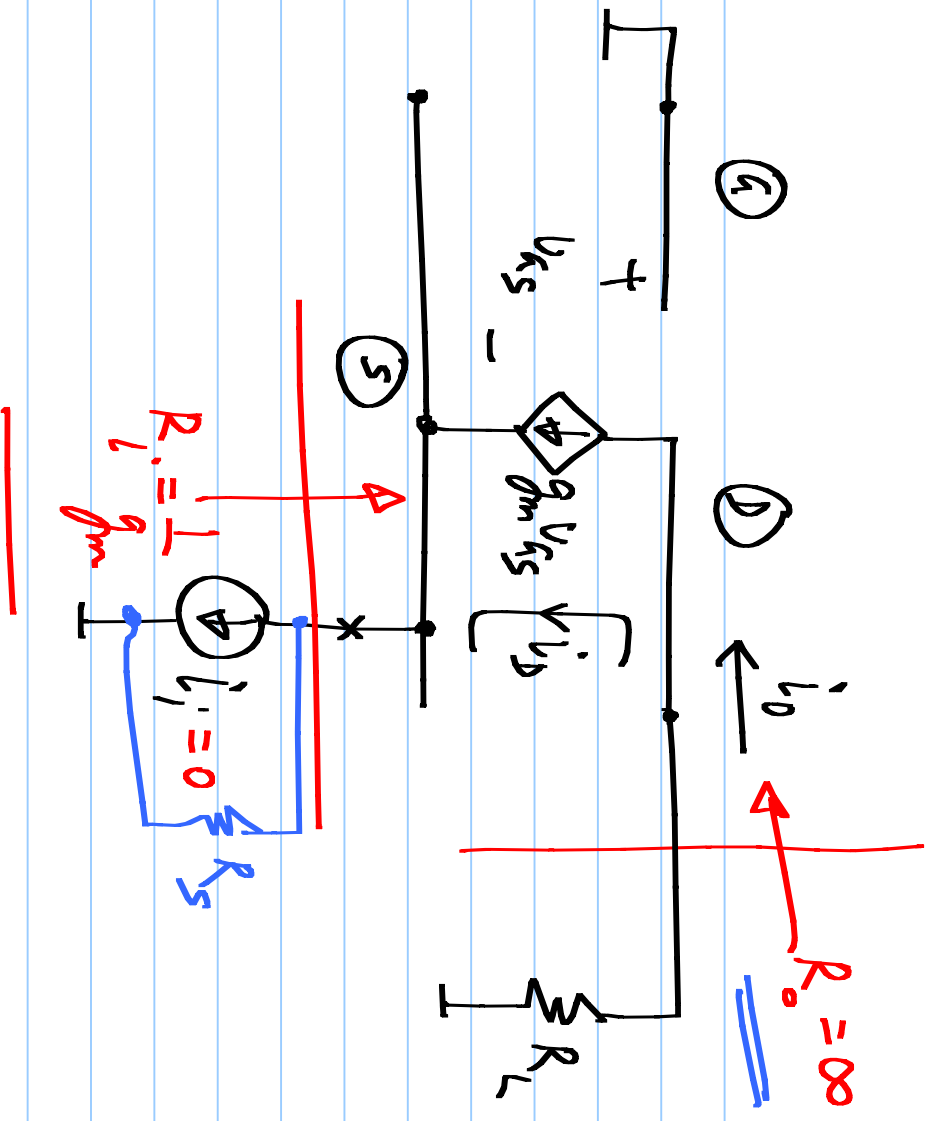


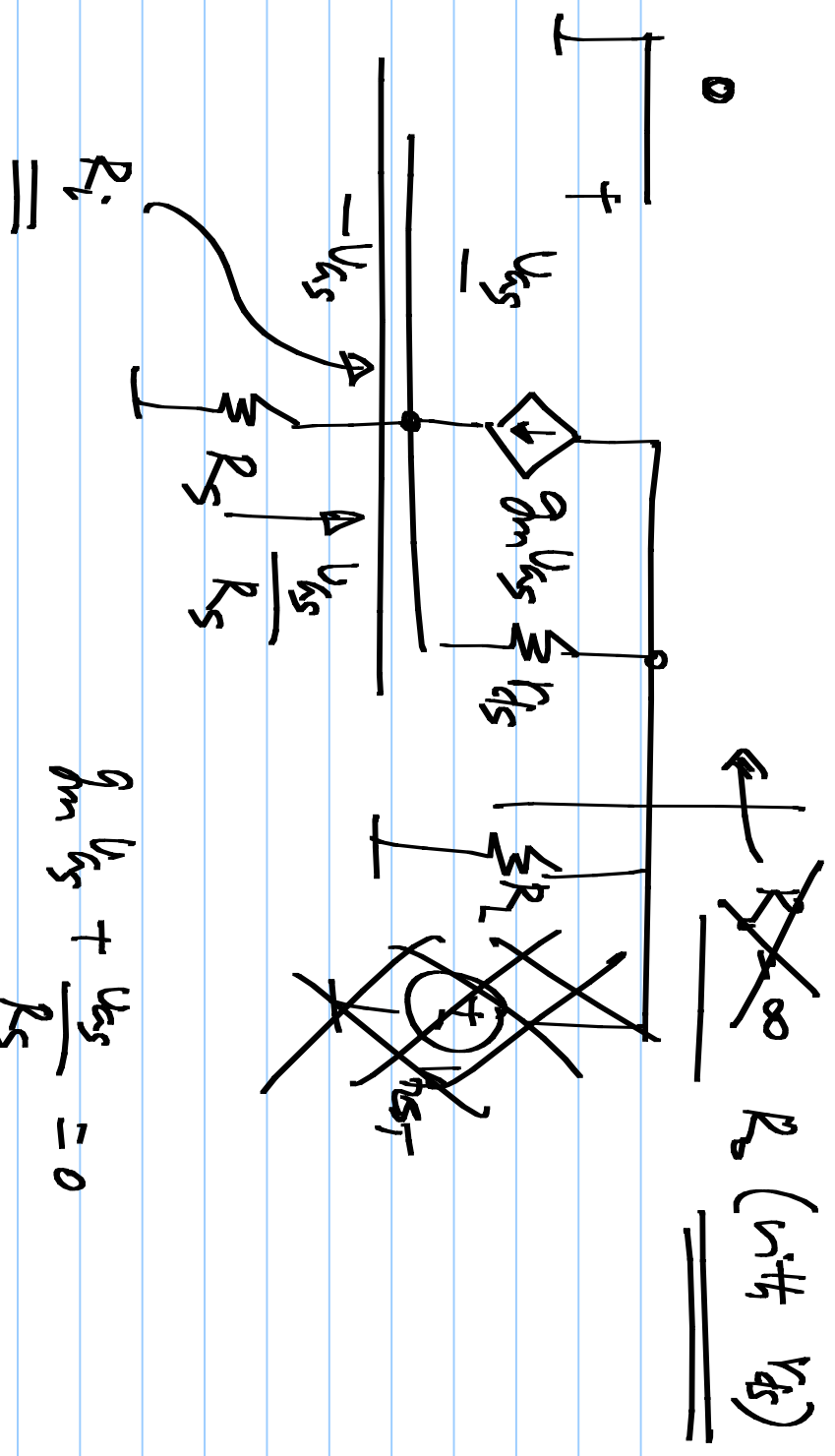
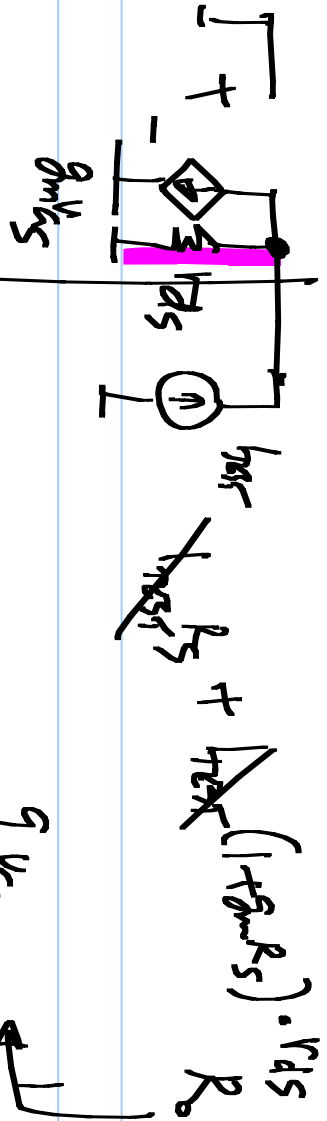
$$R_L = \frac{r_{ds} + R_L}{1 + g_m r_{ds}}$$




$$R_o = \frac{r_{ds}}{1 + g_m R_s}$$

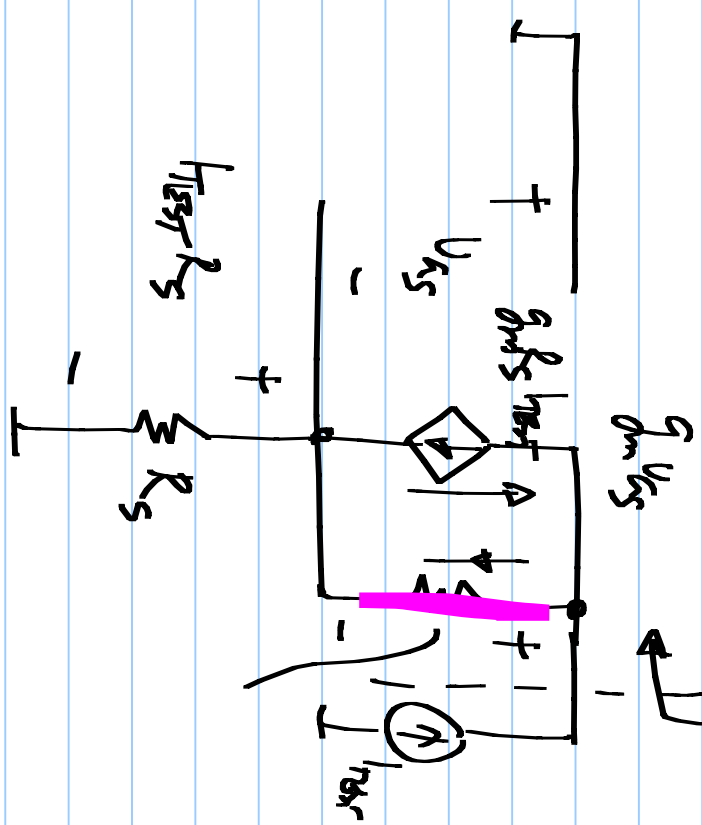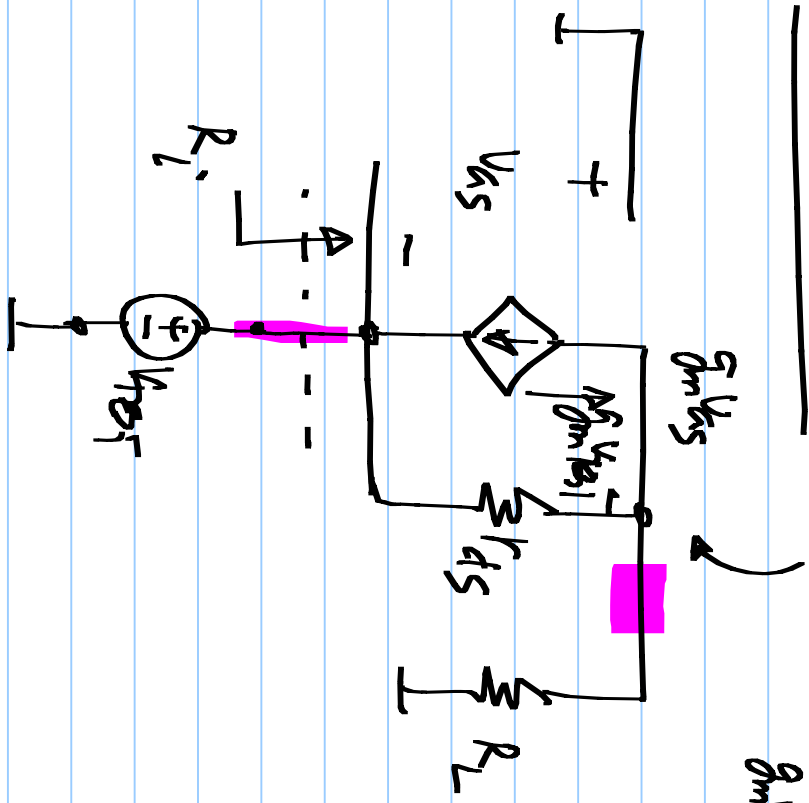

$$R_{out} = R_s + r_{ds} + g_m r_{ds} R_s$$

$$r_{ds} + R_s + g_m R_s r_{ds} \quad \left[\frac{i_o}{i_i} = \frac{g_m}{g_m + g_s} = \frac{g_m R_s}{g_m R_s + 1} \approx 1 \quad \text{if } g_m R_s \gg 1 \right]$$

$$\left. \frac{i_o}{i_i} \right|_{v_i \text{ w/rds}} = ? \quad \left[\frac{v_o}{v_i} = \frac{g_m R_L}{1 + g_m R_L} \right]$$

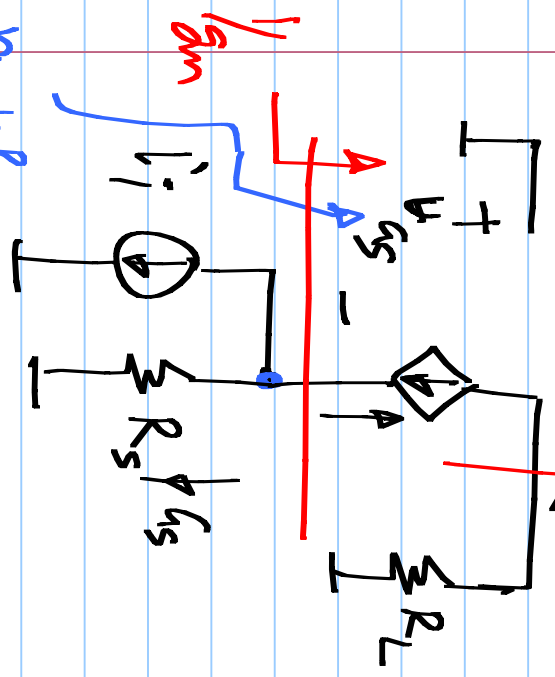

input: source & ground (gate)
 o/p: drain & source (gate)

$$\frac{r_{ds} + R_L}{1 + g_m r_{ds}}$$

COMMON GATE AMP.