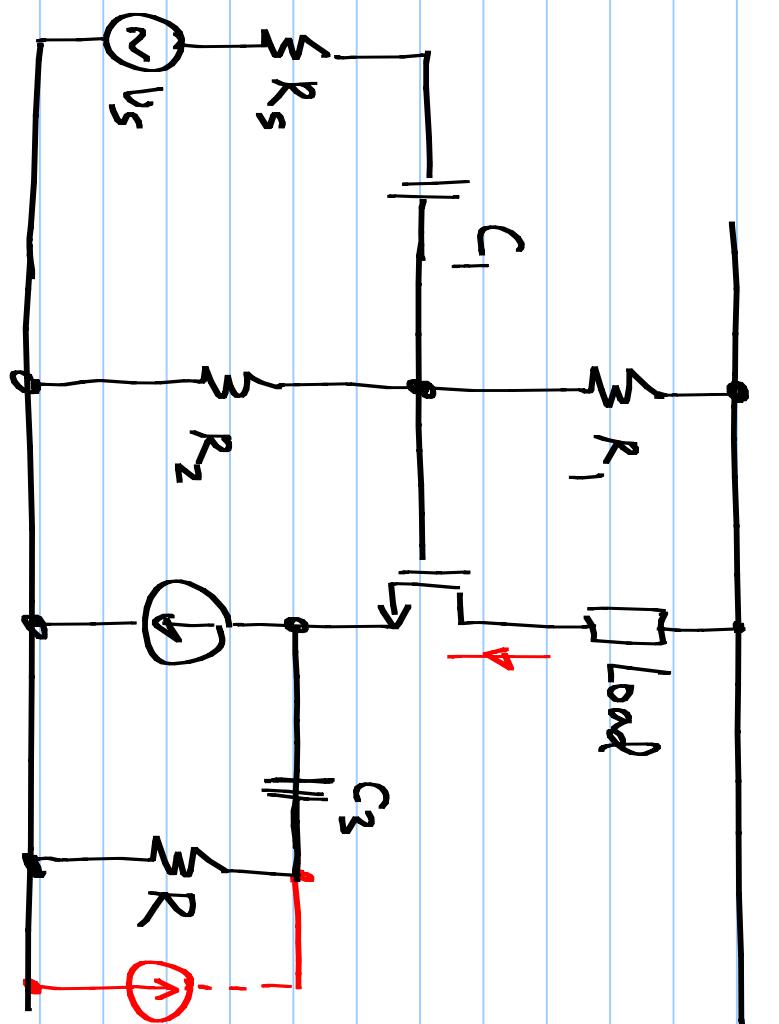


Lecture 26





Transistor
CCVS
 $k=1$



opamp:
 $VCVS$
 $CCVS$


$CCCS$
 $k=1$

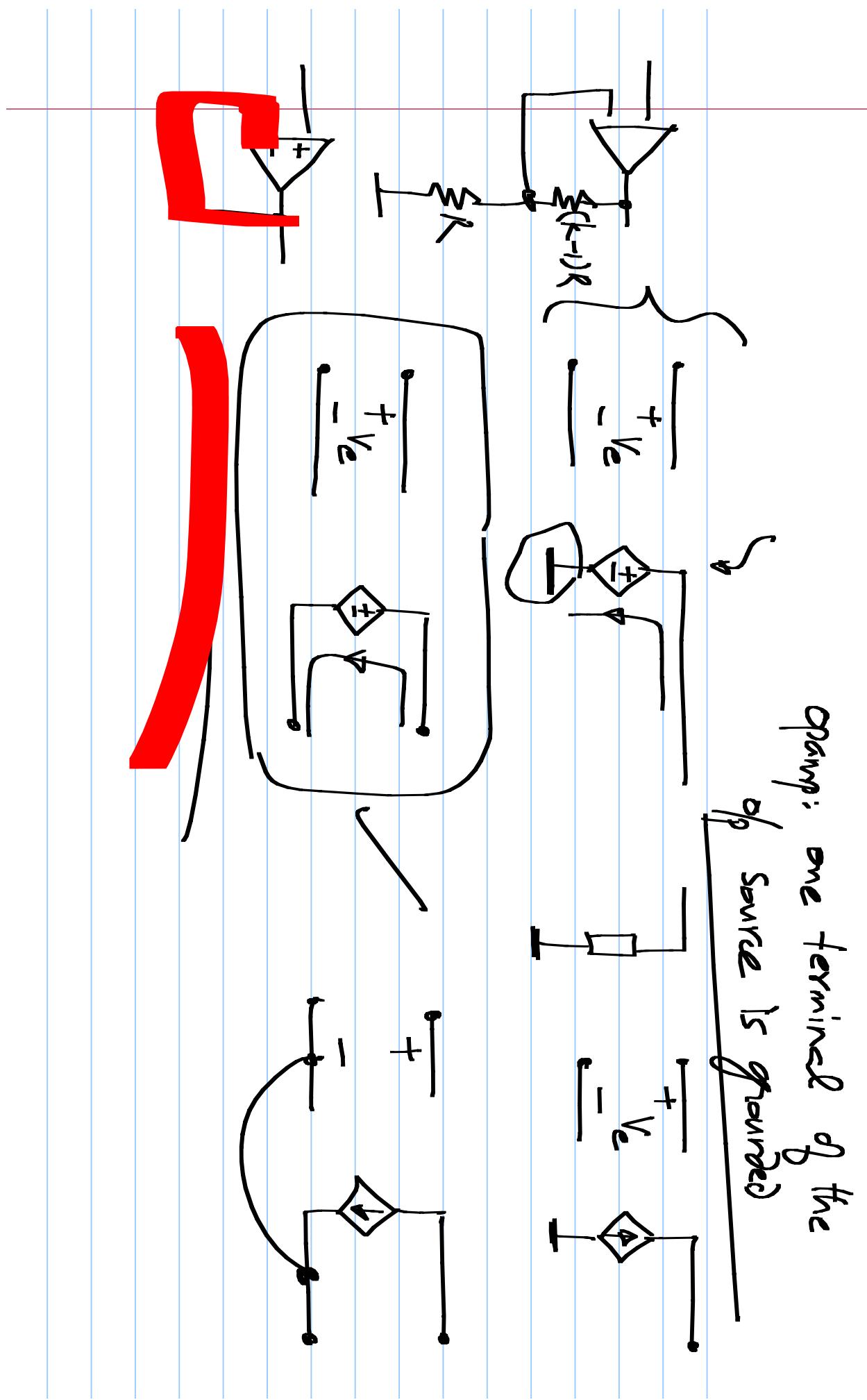opamp: one terminal of the
source is grounded



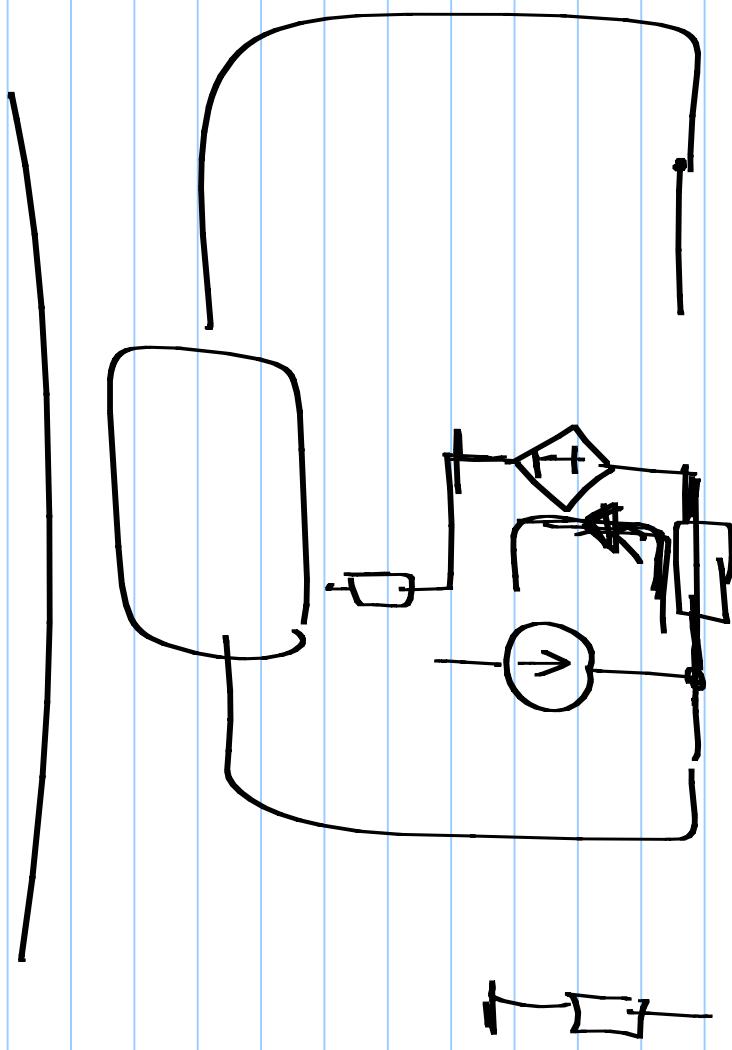


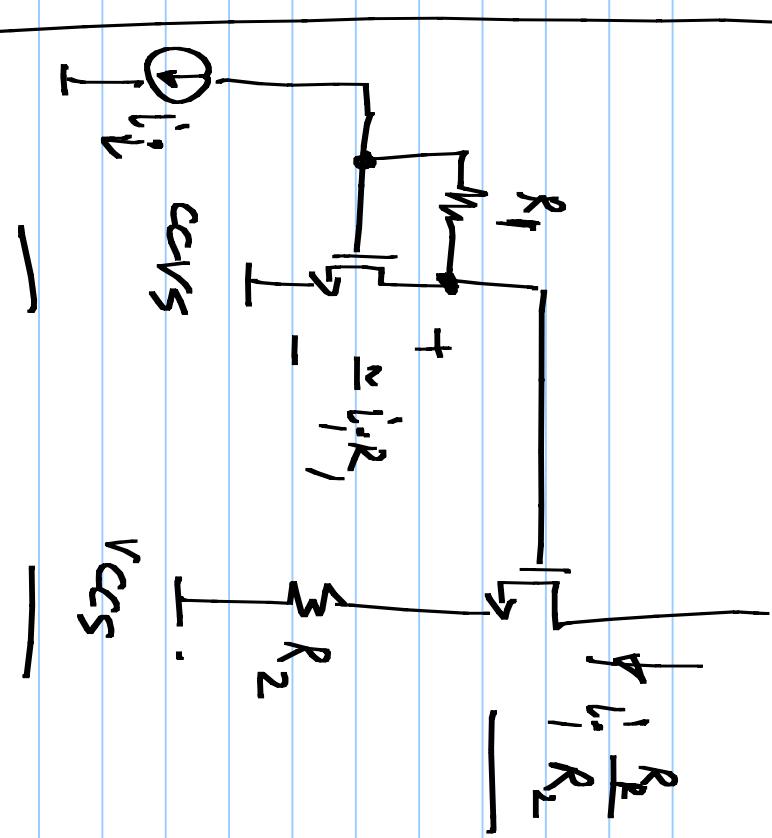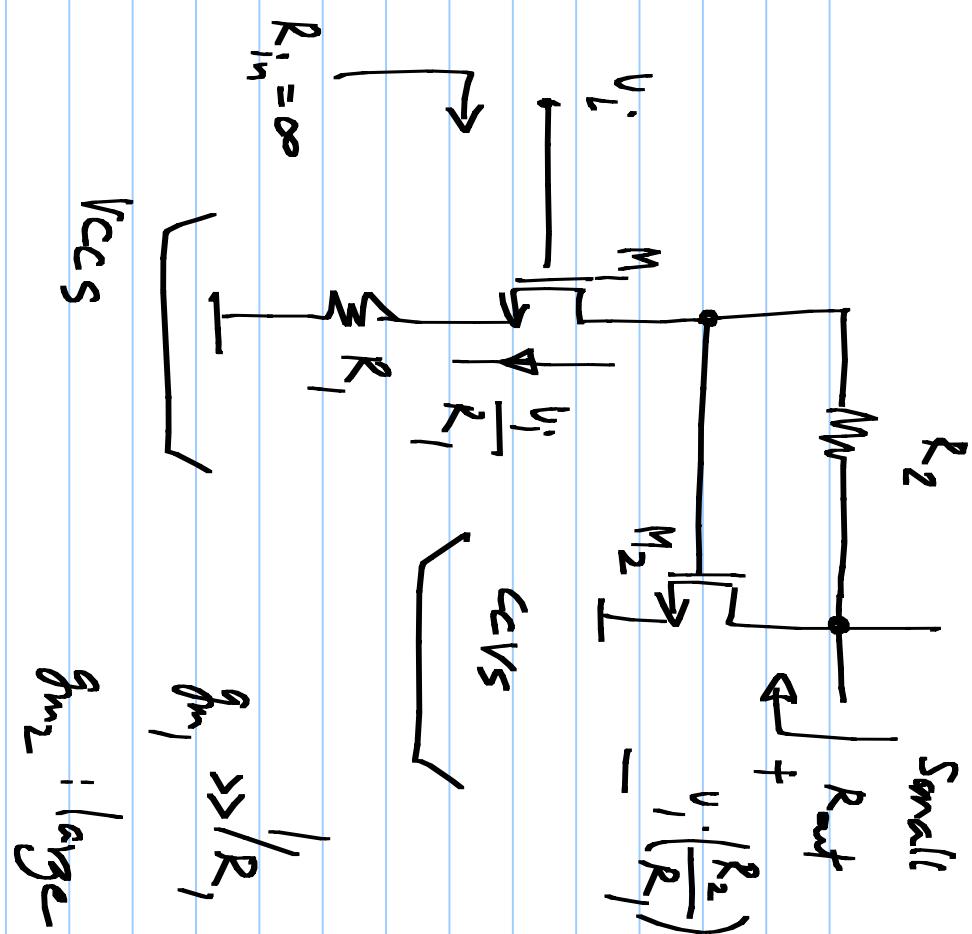

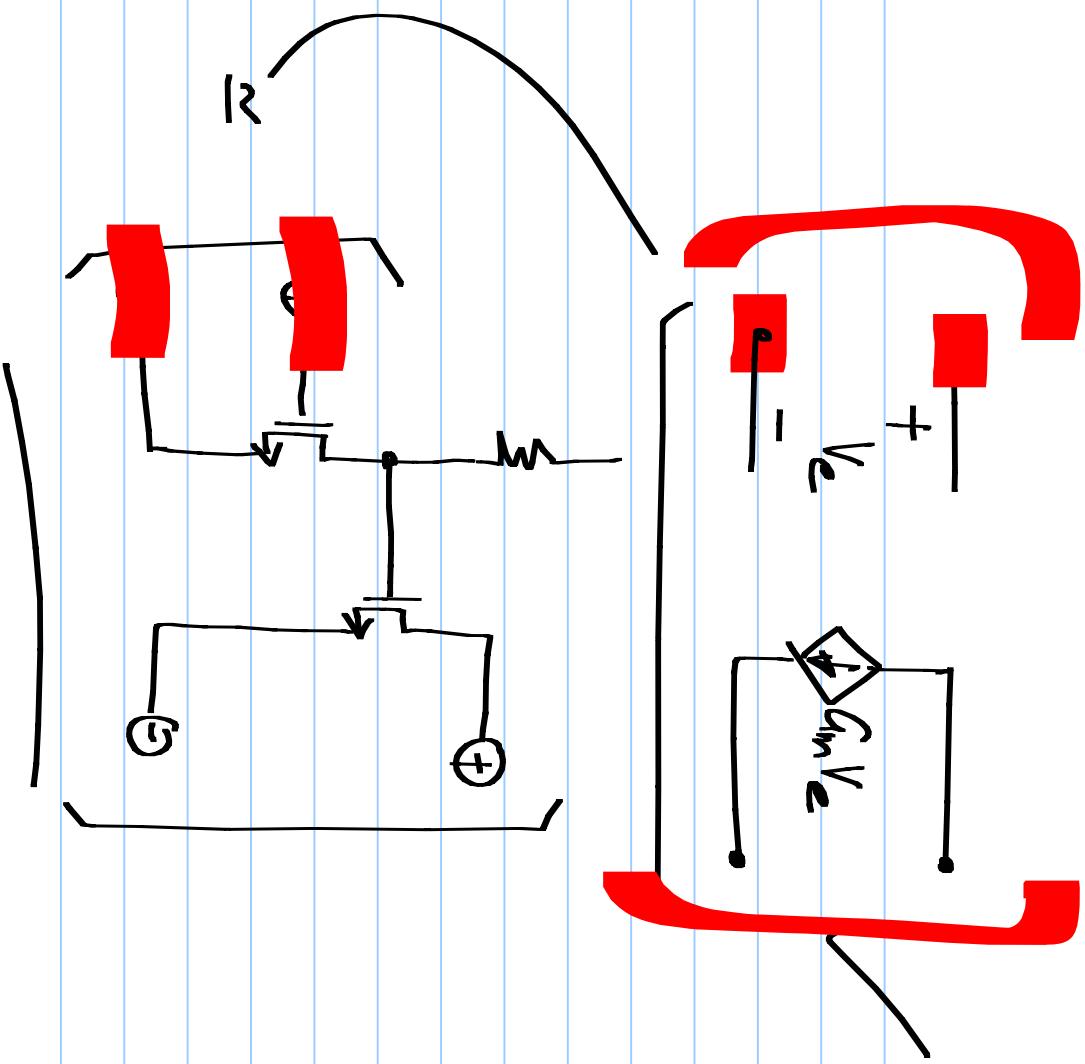

pMOS transistor

b: Source to drain

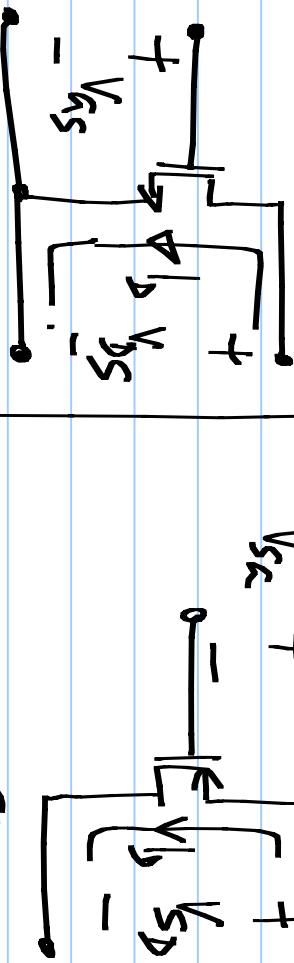

(1)

$$V_{S_a} \geq 0, V_G \geq 0, V_{D_p} > 0$$

$$V_{G_k} < V_{T_p}$$

$$V_{G_k} > V_{T_p}$$

$$V_{G_k} > 0$$


$$V_{D_p} > 0$$

$$V_{G_k} > 0$$

$$I_D = 0$$

$$\frac{V_{G_k}}{V_{T_p}} \leq \left[\frac{(V_{S_a} - V_{T_p})V_{S_d} - \frac{V_D}{2}}{V_{S_d}} \right]$$

$$V_{G_k} > 0$$

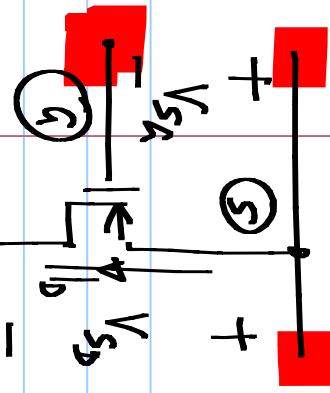

$$I_D = 0 \quad \text{for } V_{DS} < V_{TP}$$

Triode / $\frac{\mu_p C_{ox}}{L} \left[(V_{SD} - V_T)^2 - \frac{V_{SD}^2}{2} \right]$


Linear

$$(Saturation) \quad \frac{\mu_p C_{ox}}{2} \frac{W}{L} (V_{SD} - V_T)^2$$


$$\begin{aligned} V_{SD} &> V_T \\ V_{SD} &> V_{SD} - V_T \end{aligned}$$

$$\frac{\mu_p C_{ox}}{2} \frac{W}{L} (V_{SD} - V_T)^2 (1 + \frac{1}{\beta} V_{SD})$$

$$V_{SD}, V_{DS}$$

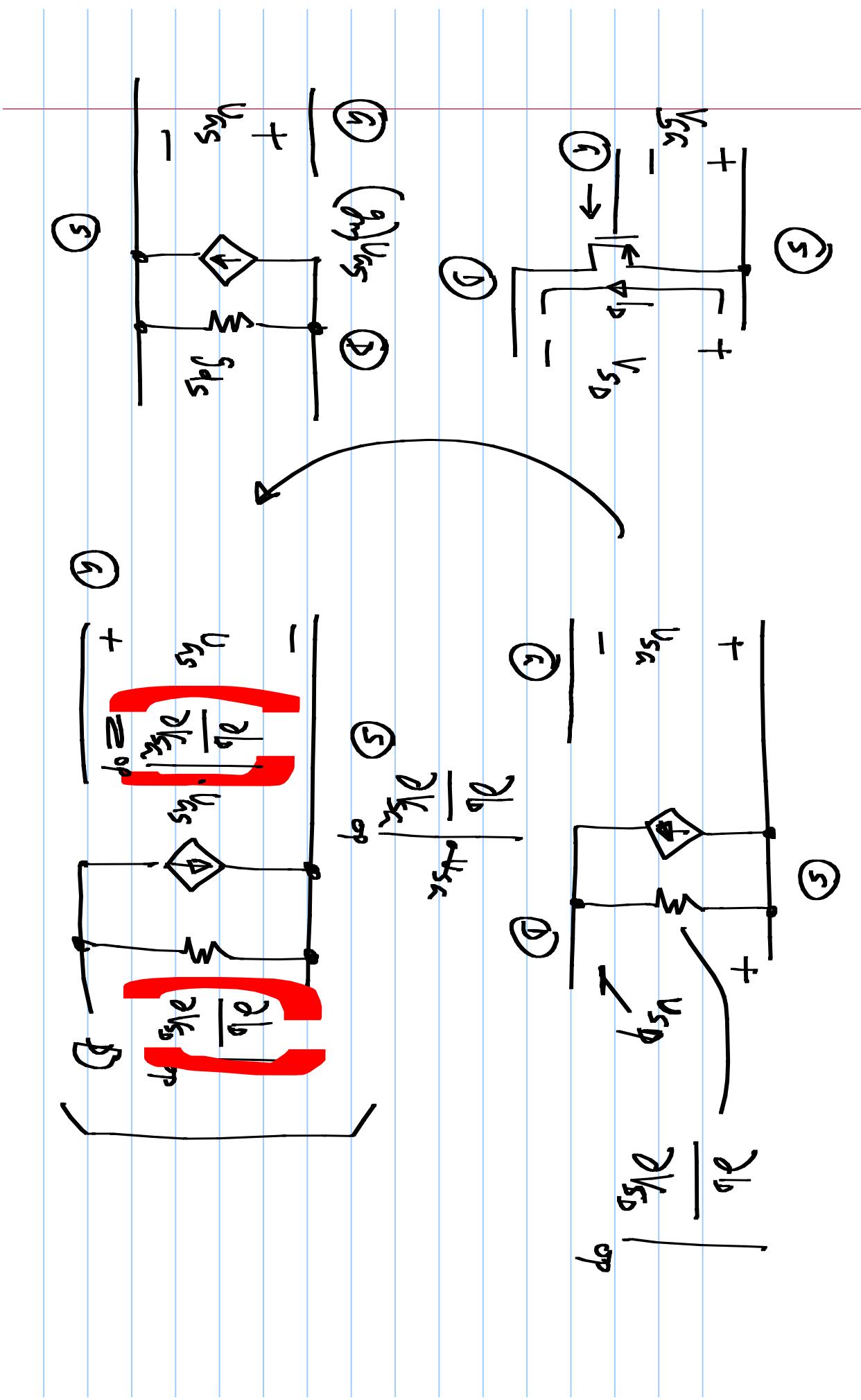

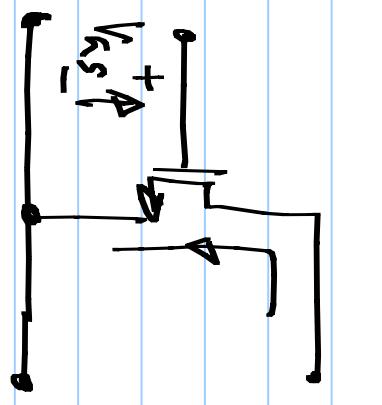NMOS: +ve increment V_{GS} $\Rightarrow V_S$ increases



↳ (going into the drain) increases
+ve incremental current into the drain

PMOS: +ve increment V_{GS} $\Rightarrow V_S$ decreases



↳ (coming out of the drain) decreases
+ve incremental current into the drain