



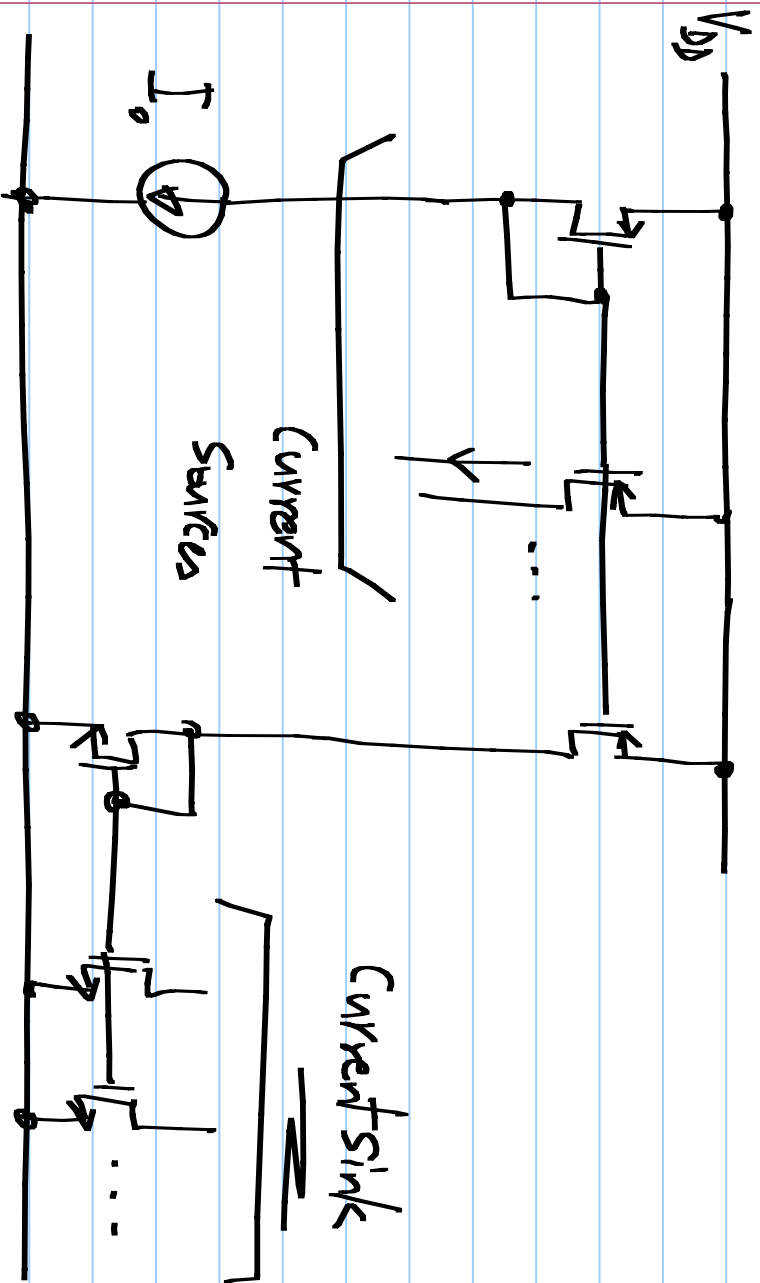
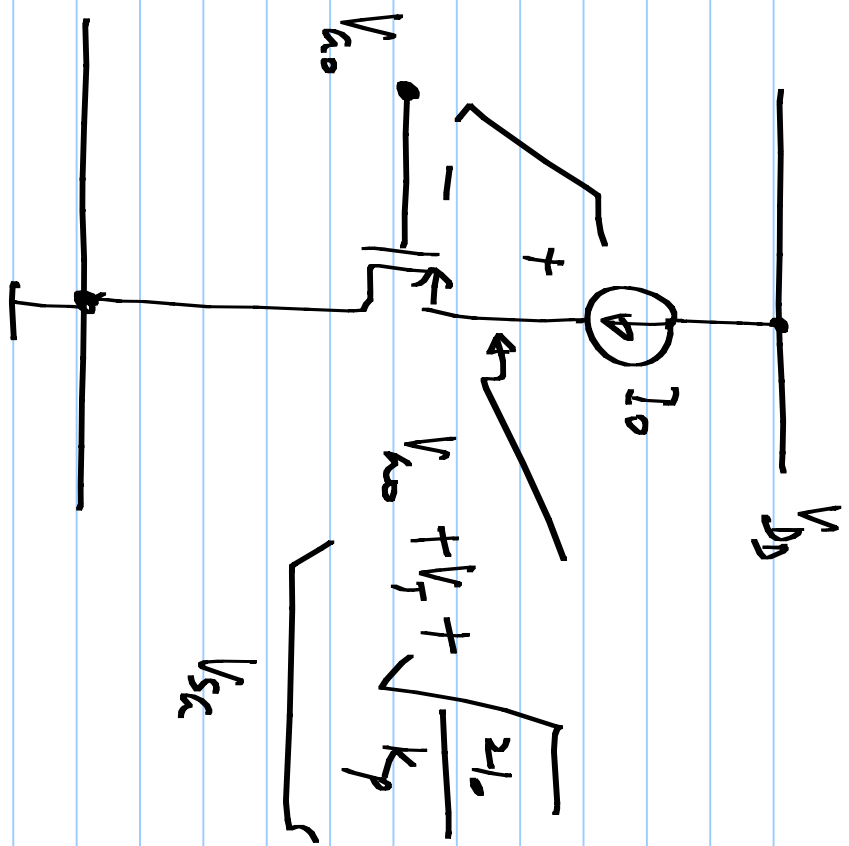
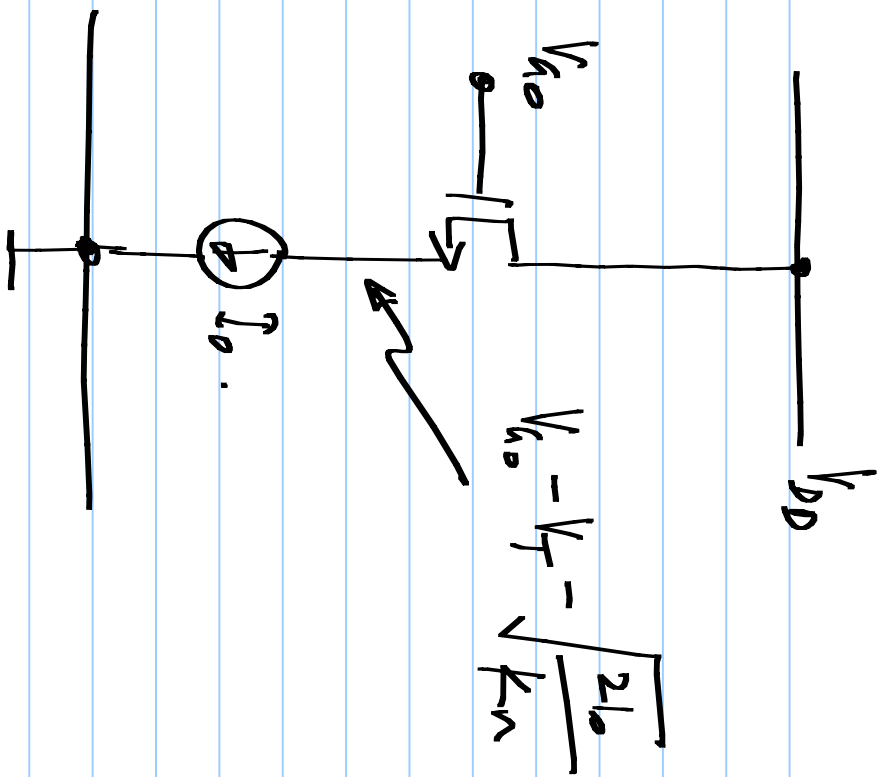


# Lecture 28


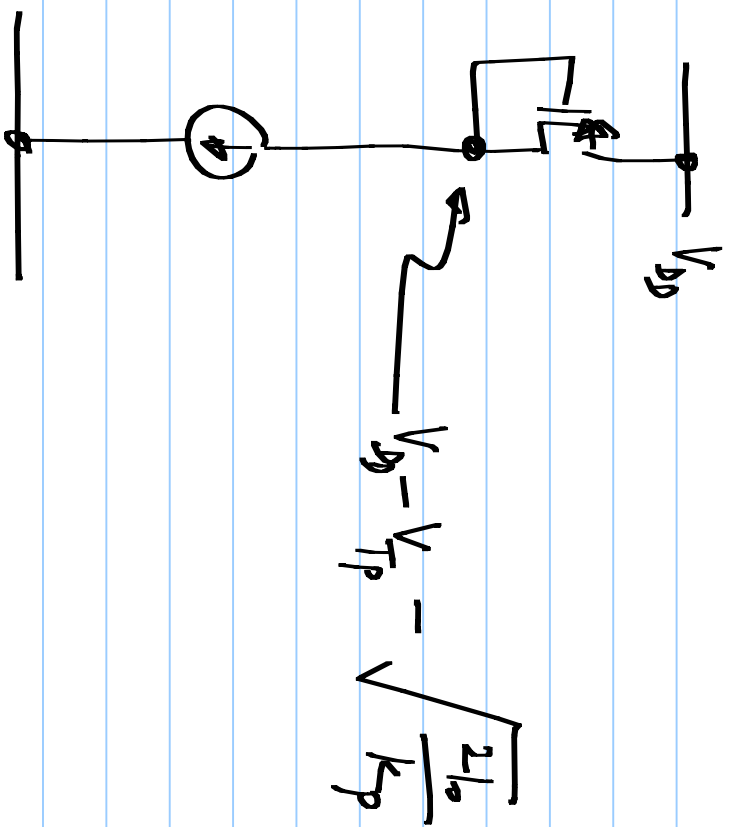


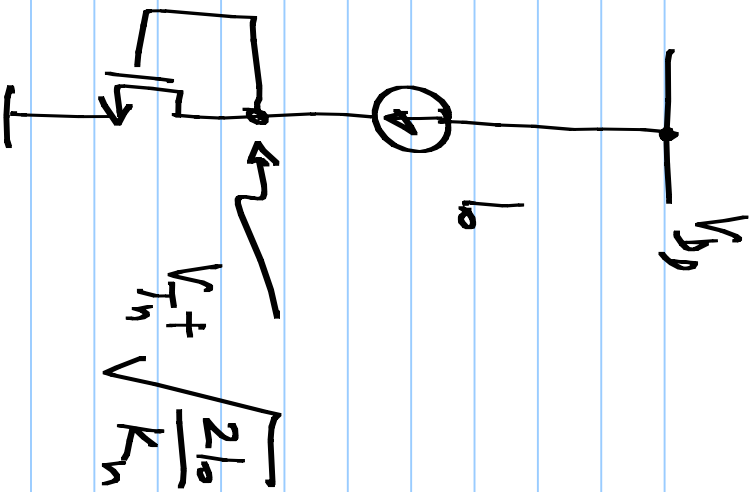

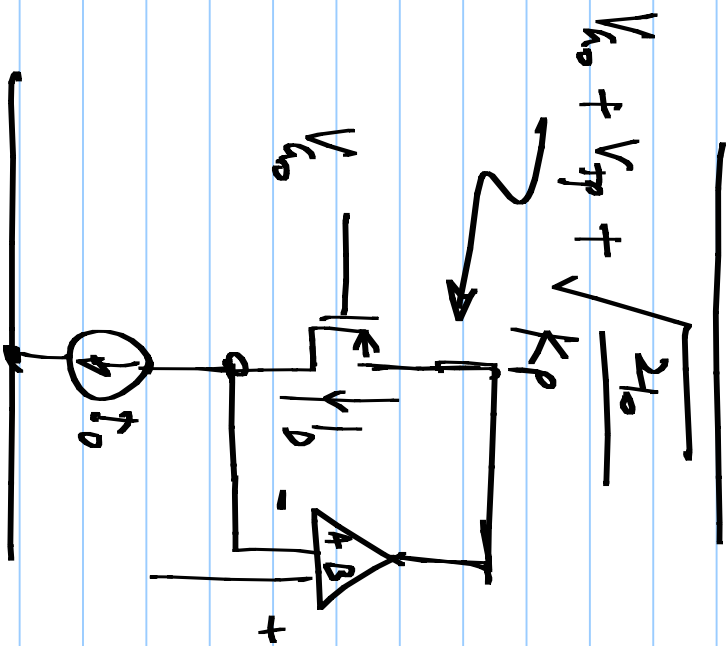


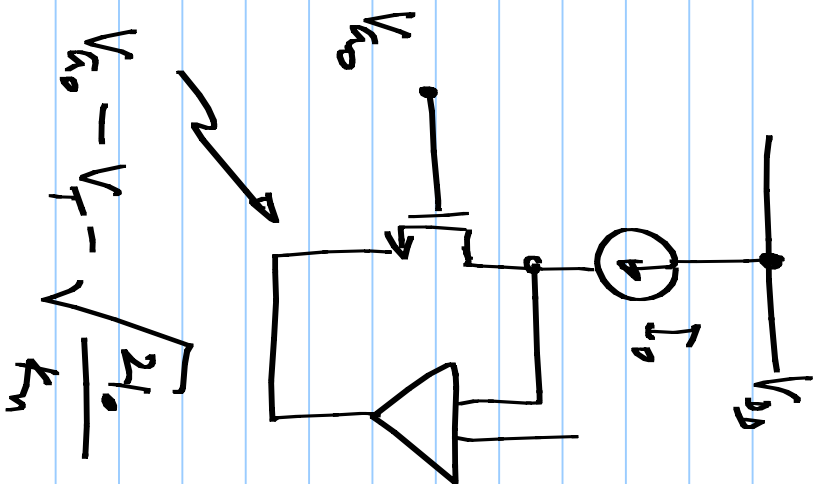

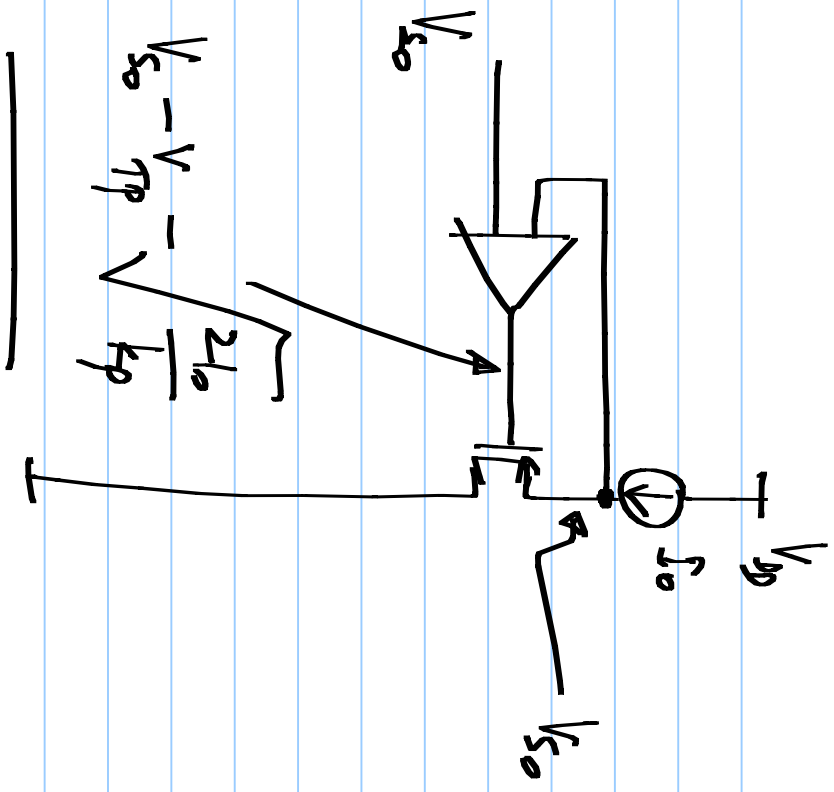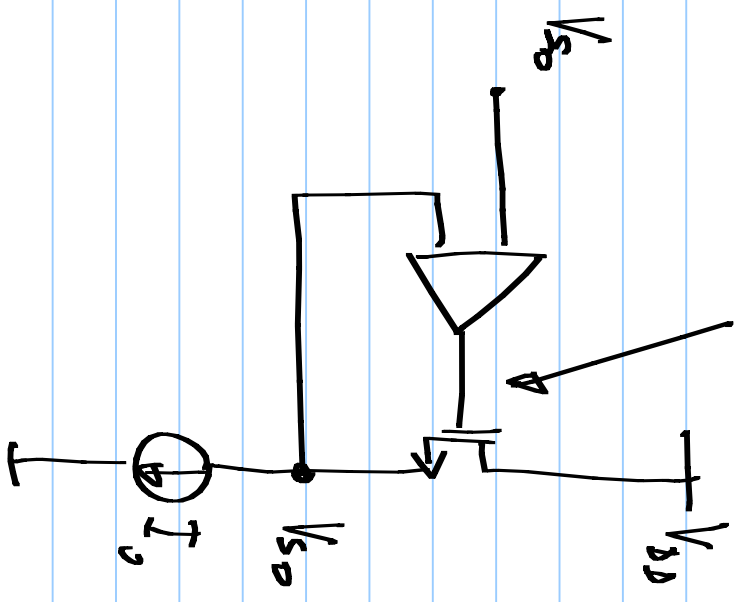
$$V_{S0} + V_{Tn} + \sqrt{\frac{2I_0}{k_n}}$$



$$V_{S0} - V_{Tp} - \sqrt{\frac{2I_0}{k_p}}$$

# Common source amplifier

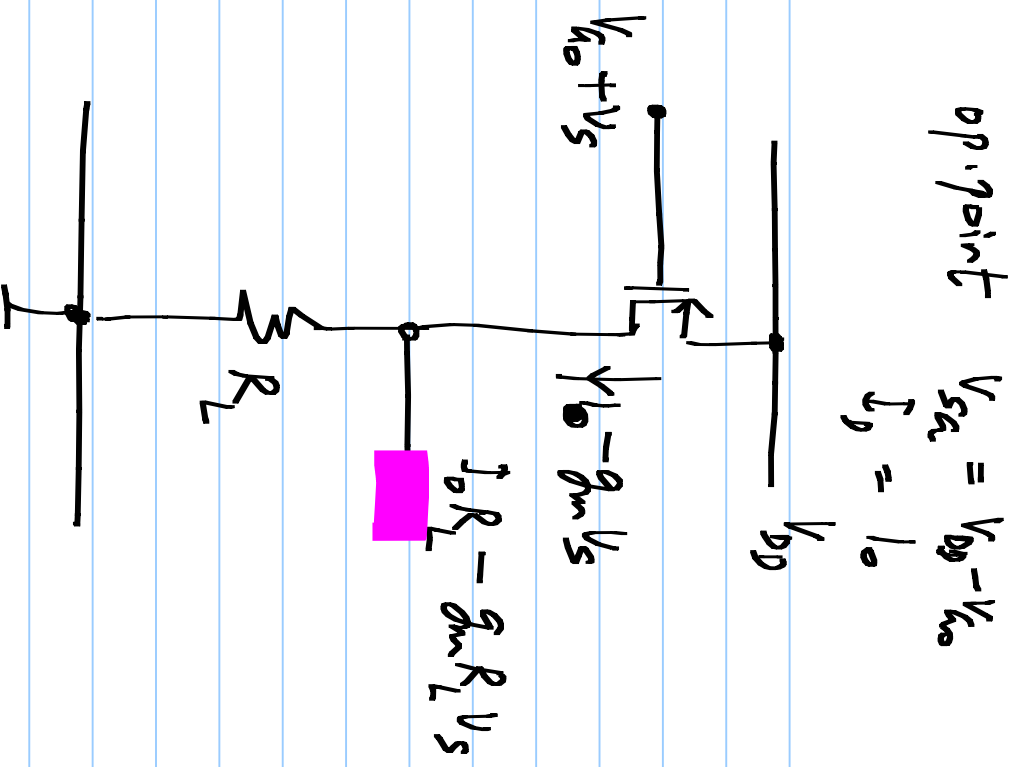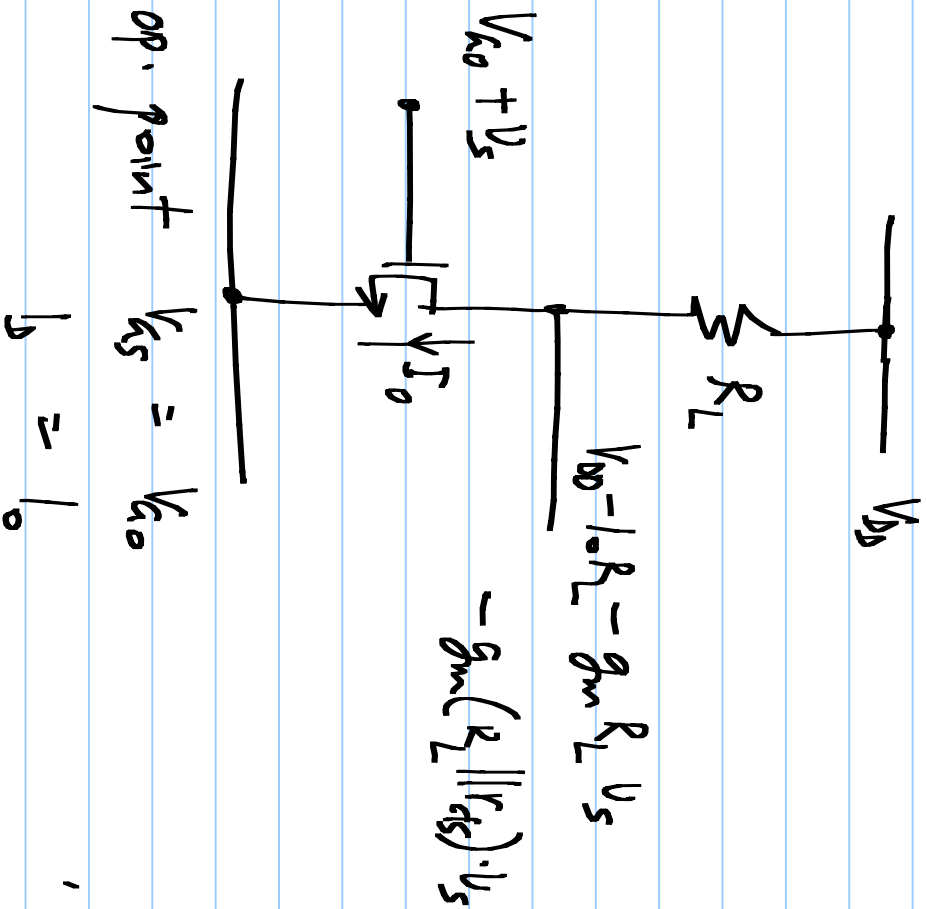

$$|gain| = g_m R_L = \frac{2I_0}{V_{GS} - V_T} \cdot R_L = 2 \cdot \frac{I_0 R_L}{(V_{GS} - V_T)}$$

min.  $V_{DS,R}$   
(possible)

$$V_{DD} = \frac{V_{DS,R} + I_0 R_L}{\sqrt{2I_0 \cdot \mu_n C_{ox} \frac{W}{L}}}$$

$$= 2 \cdot \frac{V_{DD} - (V_{GS} - V_T)}{(V_{GS} - V_T)}$$

$$= 2 \left[ \frac{V_{DD}}{V_{GS} - V_T} - 1 \right] \checkmark$$

Minimize this for maximum

$$V_{GS} - V_T = \sqrt{\frac{2I_0}{k_w}} = \sqrt{\frac{2I_0}{\mu_n C_{ox} \frac{W}{L}}}$$

$$V_{GS} - V_T \rightarrow 6 \cdot V_T = \underline{15 \text{ mV}}$$

$$|g_{\text{min}}| = 2 \left[ \frac{V_{DD}}{n_{\text{min}}(V_{GS} - V_T)} \right]^{-1}$$

$$2 \left[ \frac{1.5 \text{ V}}{0.15 \text{ V}} \right]^{-1} = \underline{18}$$



