
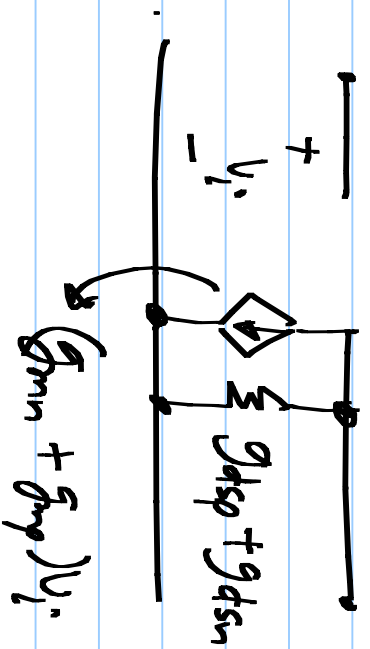
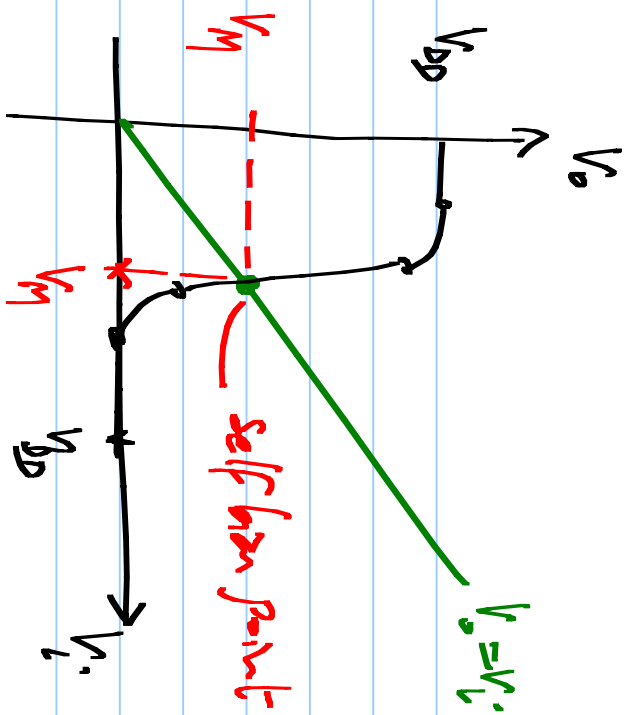


Lecture 32

CMOS inverter

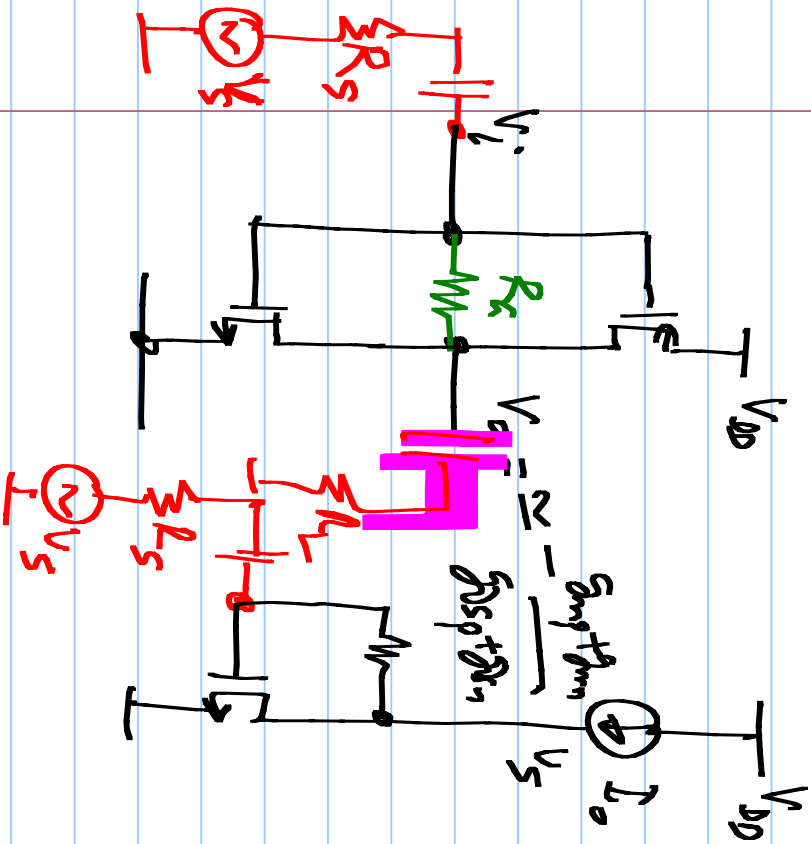


Self bias voltage:

$$V_{DD} \left[\frac{\sqrt{k_p}}{\sqrt{k_p} + \sqrt{k_n}} \right]$$




$$V_M = \frac{(V_{DD} - V_{TN})\sqrt{k_p} + V_{TN}\sqrt{k_n}}{\sqrt{k_p} + \sqrt{k_n}}$$

$$I_R = (V_{DD} - V_M - V_{TN})^2 \cdot \frac{k_p k_n}{2(\sqrt{k_p} + \sqrt{k_n})^2}$$

$k_p < k_n$





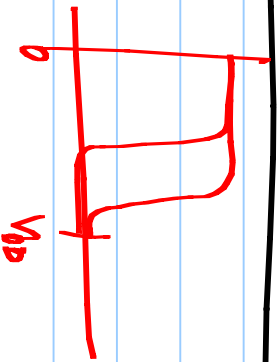


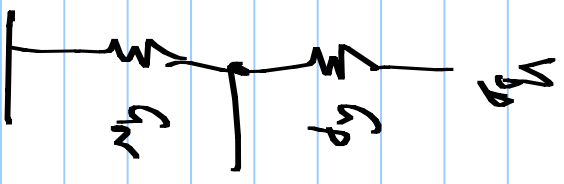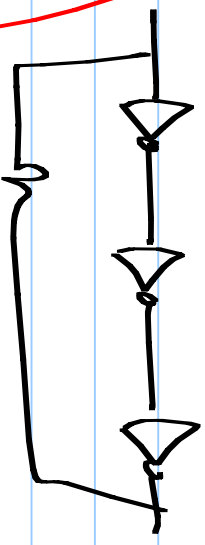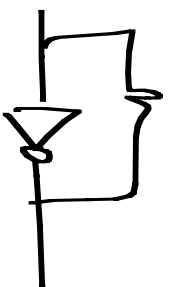
$$V_{DD} \left[\frac{\sqrt{k_p}}{\sqrt{k_p} + \sqrt{k_n}} \right]$$





Opamp:



$$V_o = A_v (V_1 - V_2)$$

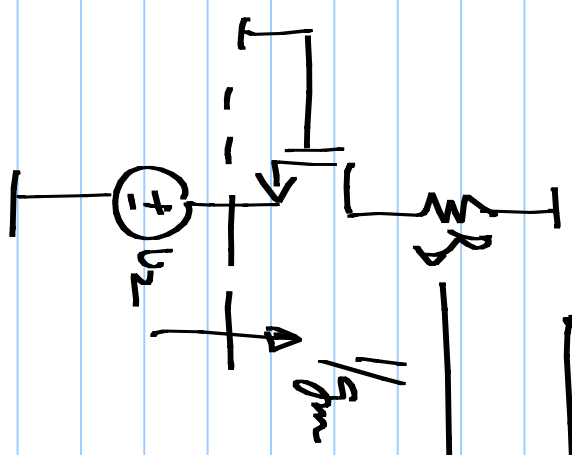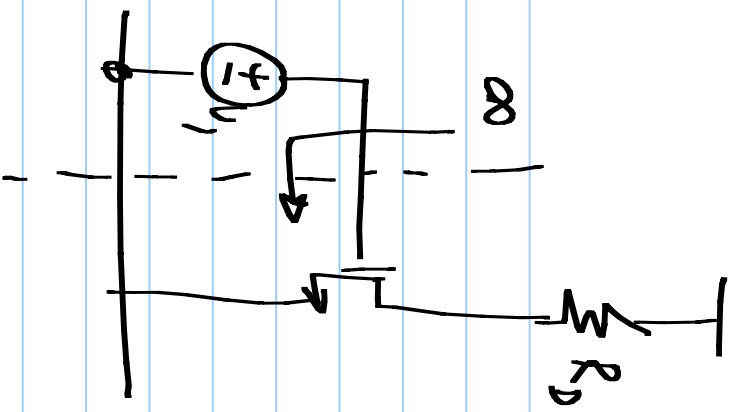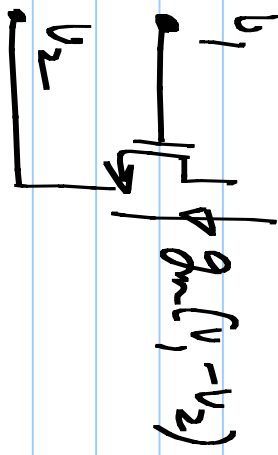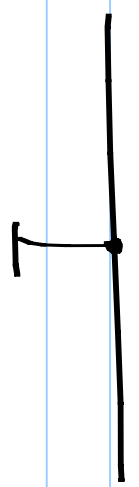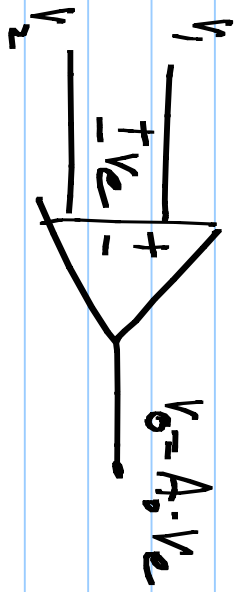


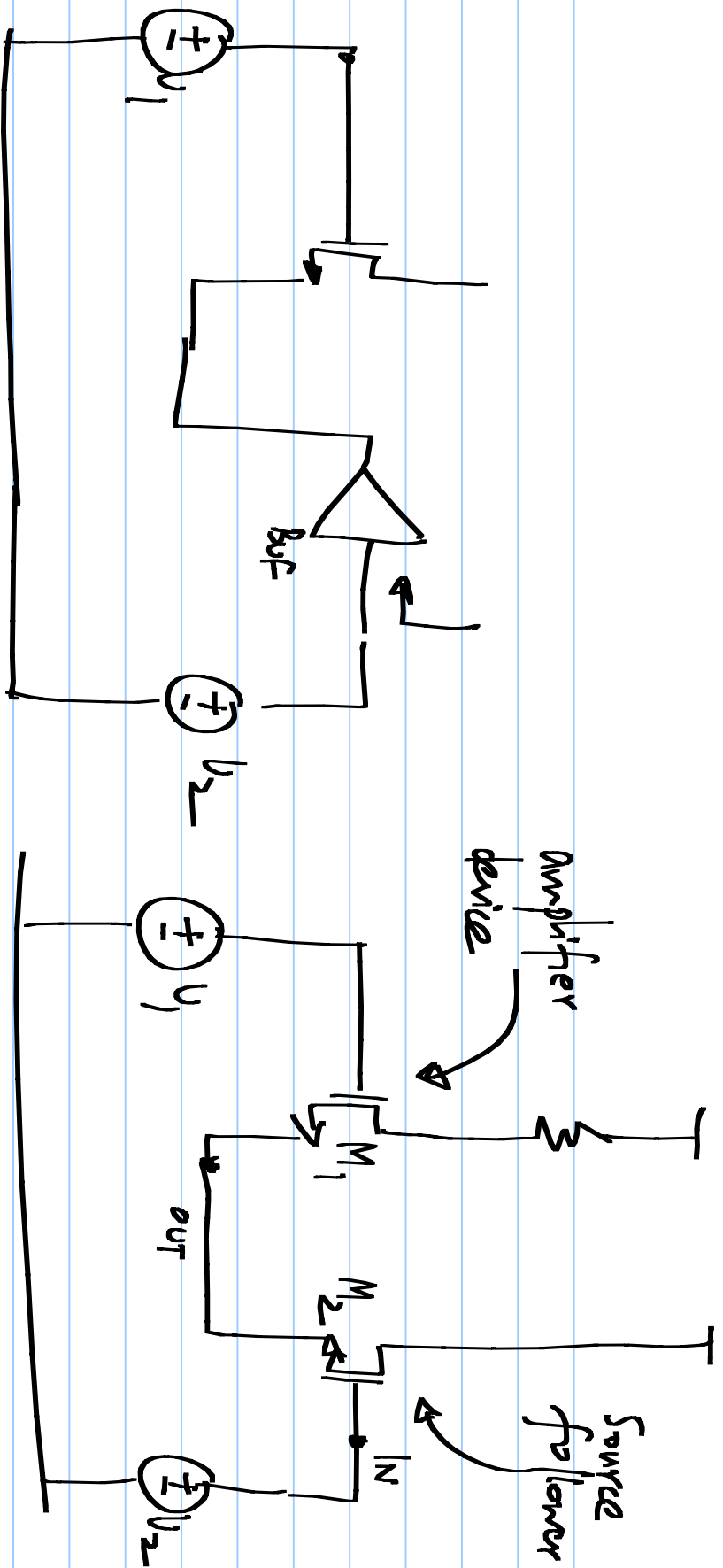

$M_{1,2}$: identical

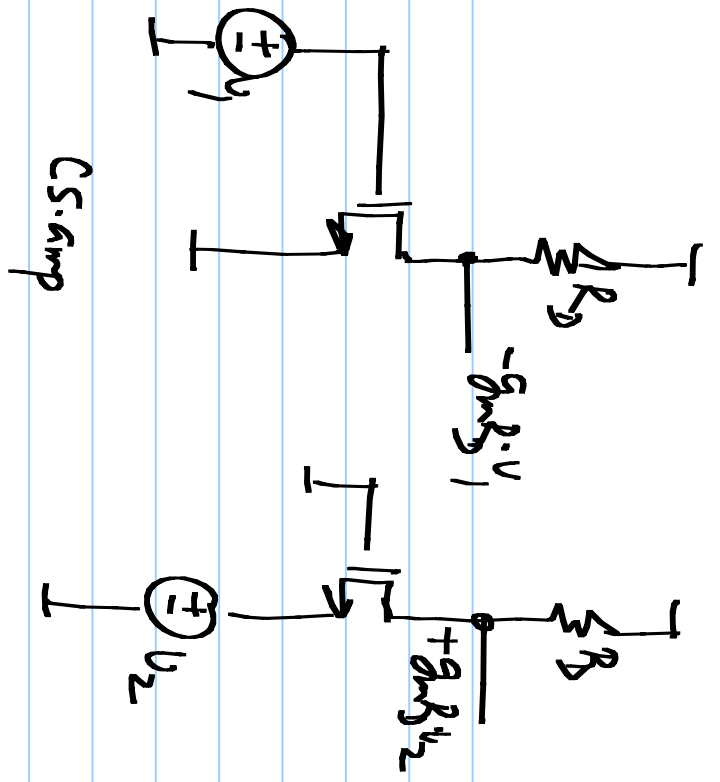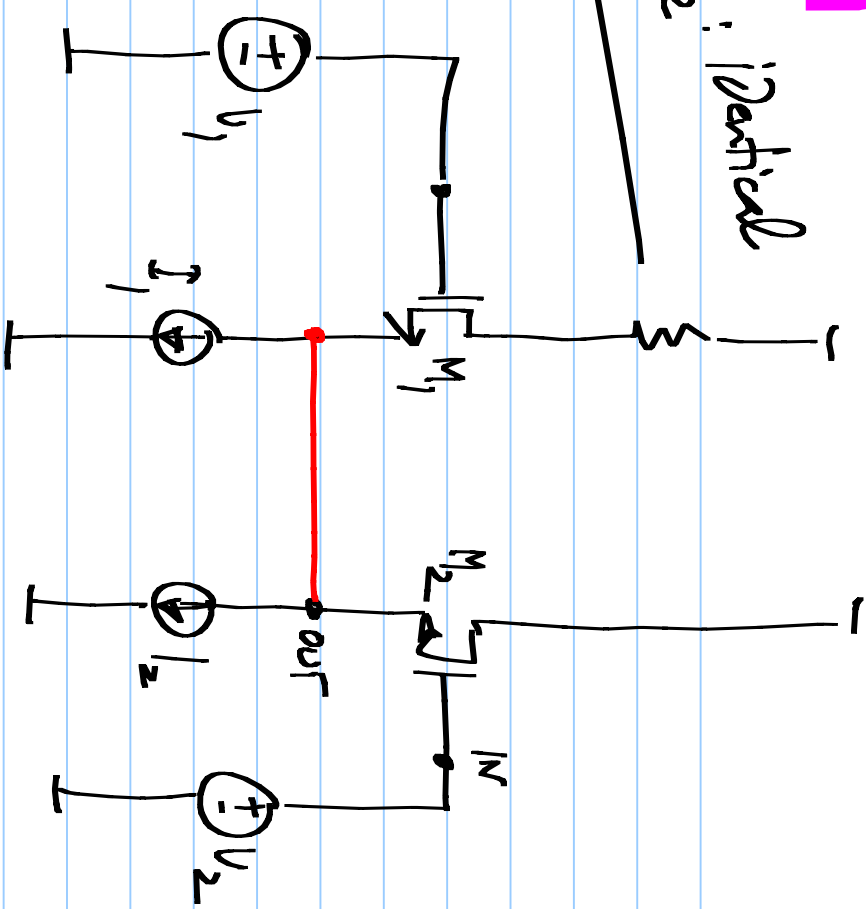

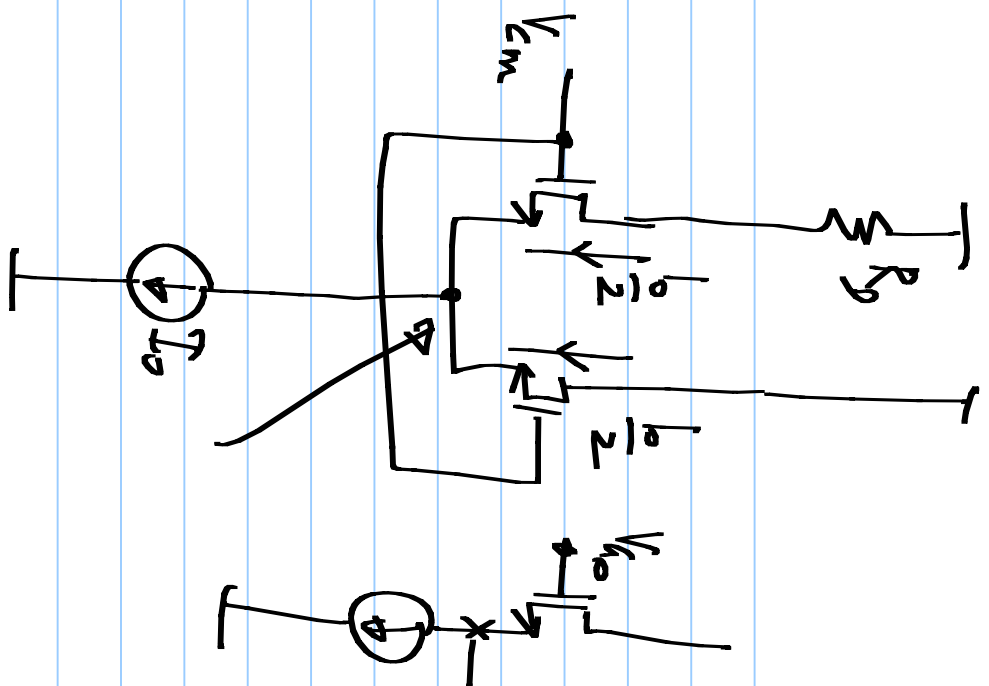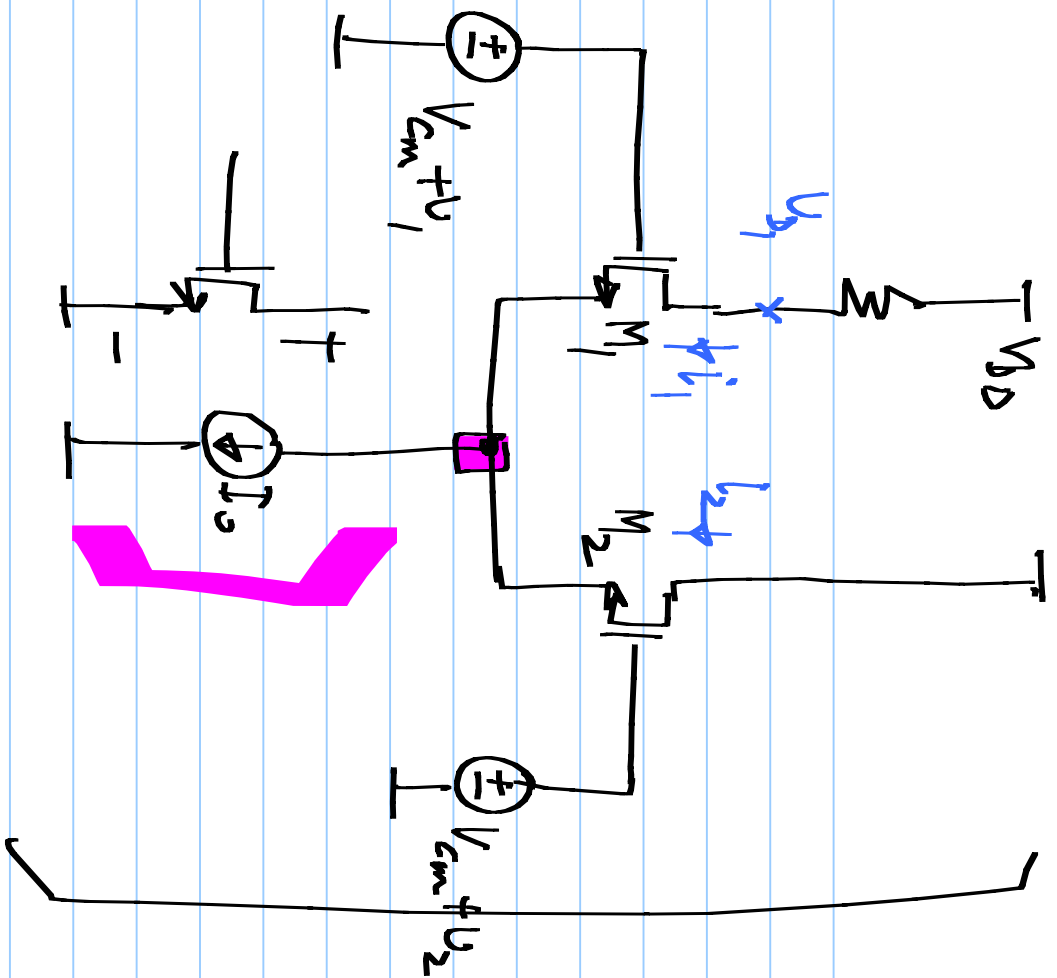


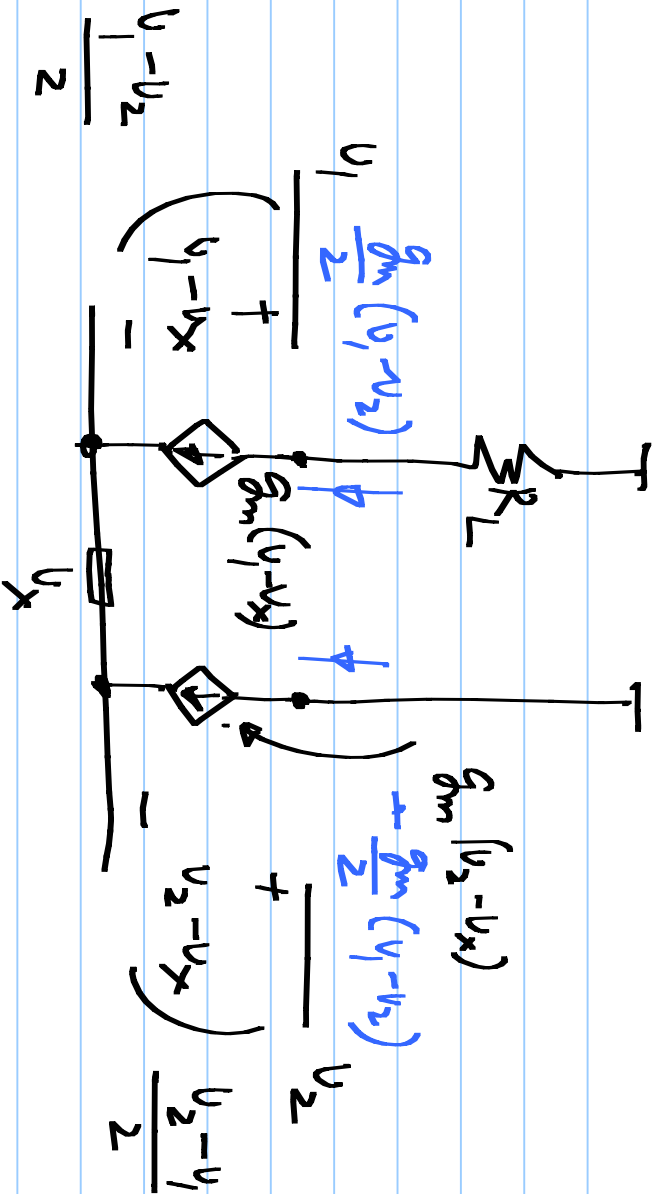

$$g_m (V_1 - V_x) + g_m (V_2 - V_x)$$


$$= 0$$

$$V_x = \frac{V_1 + V_2}{2}$$

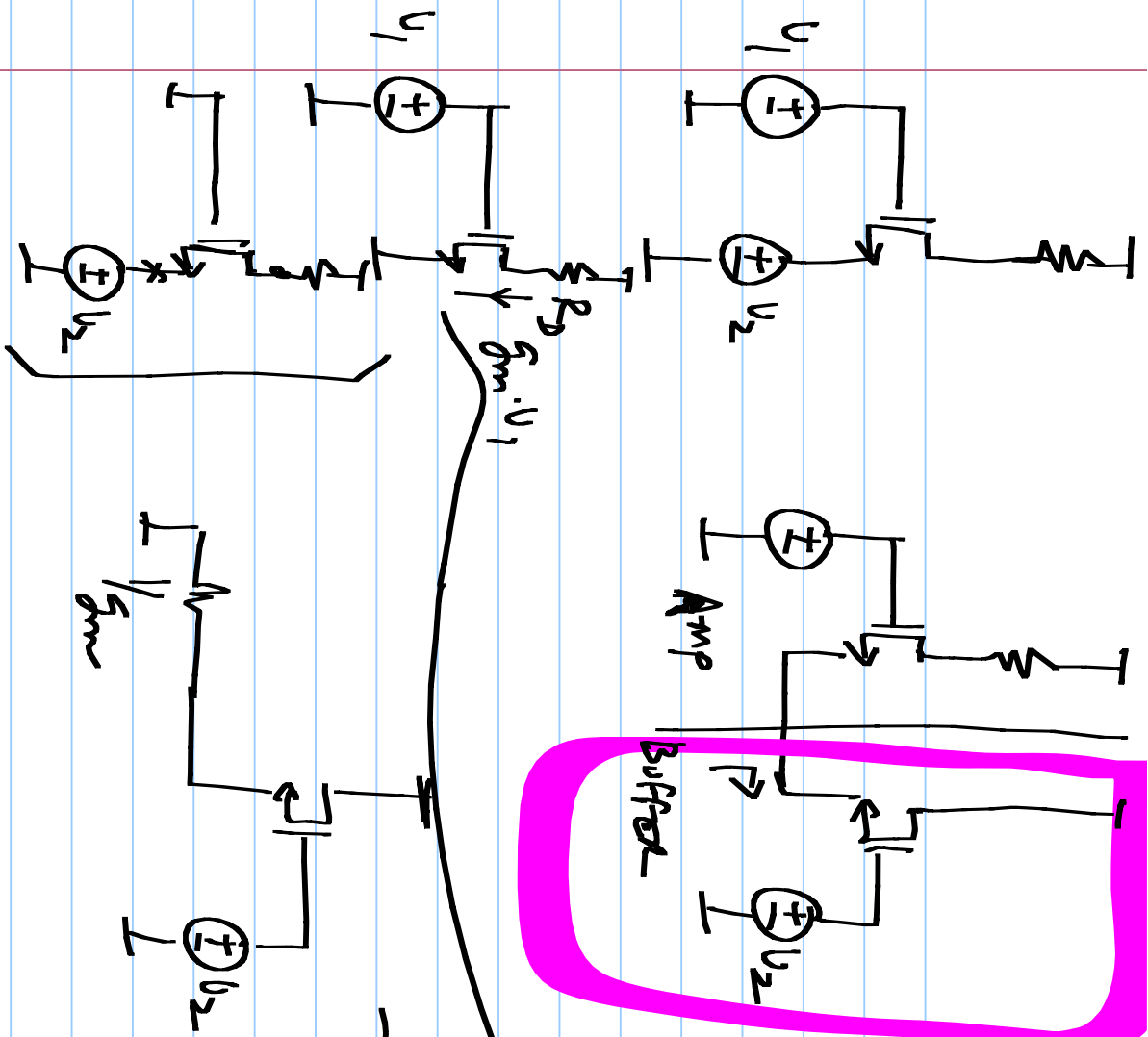

$$\frac{g_m R_L}{1 + g_m R_L} = \frac{1}{r}$$

Source degeneration

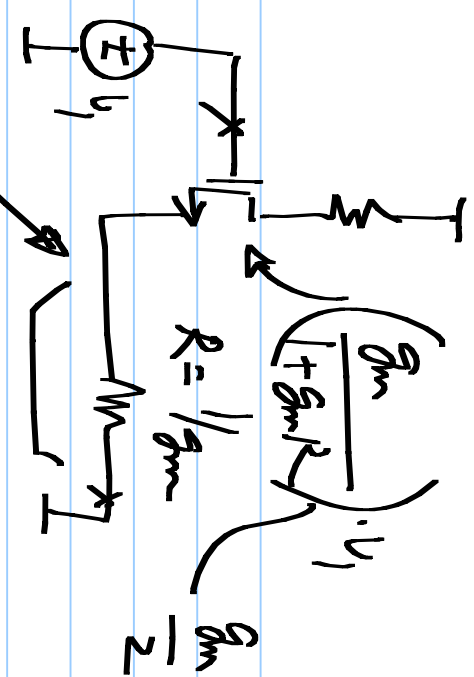

$$\left(\frac{g_m}{1 + g_m R} \right) \cdot v_1$$

$$R = 1/g_m$$

$$g_m/2$$