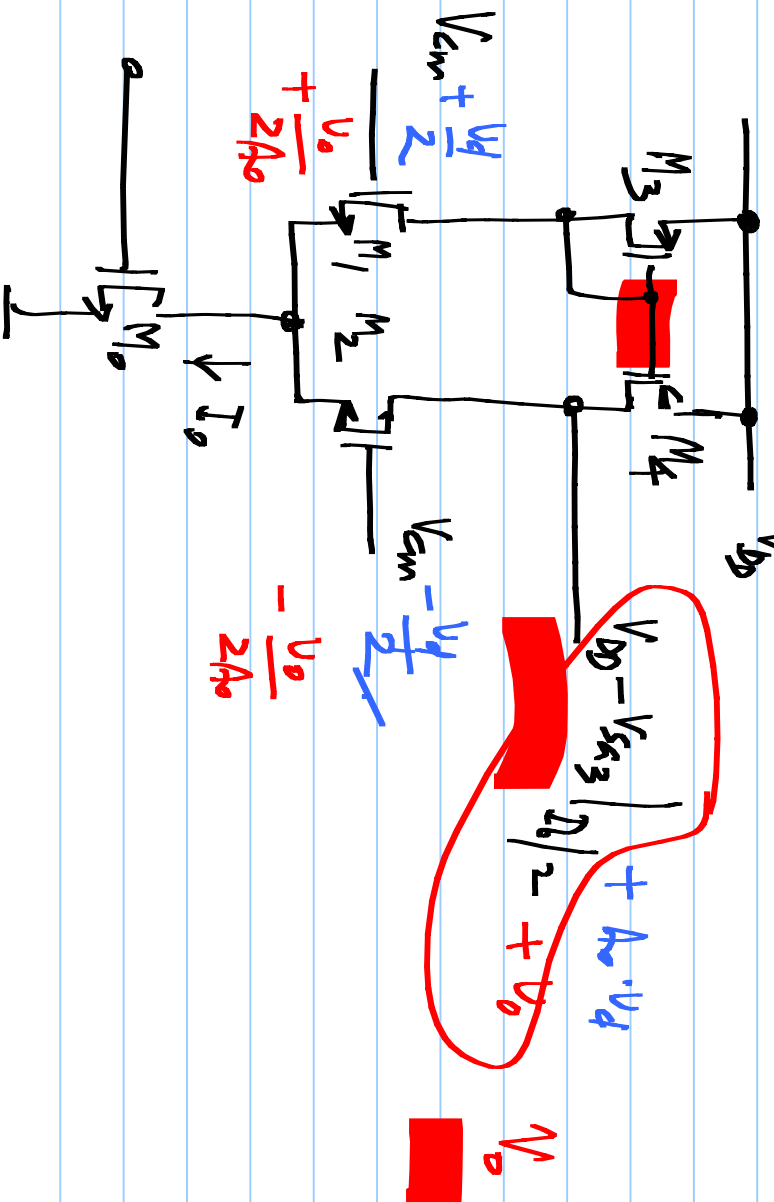


Opamp: Swing limits

$$A_o = \frac{g_{m1}}{g_{d1} + g_{d3}}$$




Upper limit on V_o

$$V_o < V_{D0} - V_{ds3} | 1/2 + V_{Tn}$$

$$V_o > V_{cm} - \frac{V_d}{2A_o} - V_{Tn}$$

$$V_o < V_{D0} - V_{ds3} | 1/2$$

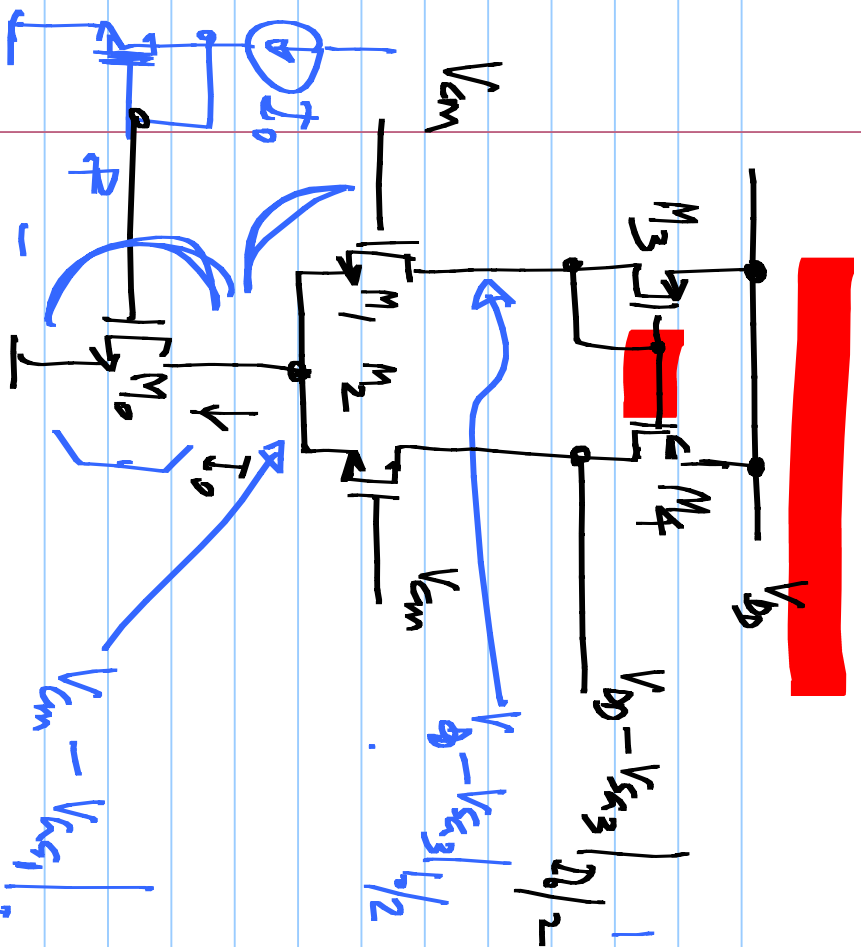


$$V_{cm} - \frac{V_{S_{K1}}}{2} > V_{DSAT0} \left| \frac{I_o}{I_o} \right|$$

$$V_{cm} > V_{Tn} + V_{DSAT1} \left| \frac{I_o}{I_o} \right| + V_{DSAT0} \left| \frac{I_o}{I_o} \right|$$


$$V_{cm} < V_{DD} - \frac{V_{Tn}}{2} - V_{DSAT3} \left| \frac{I_o}{I_o} \right| + V_{Tn}$$

PMOS input pair + NMOS current mirror


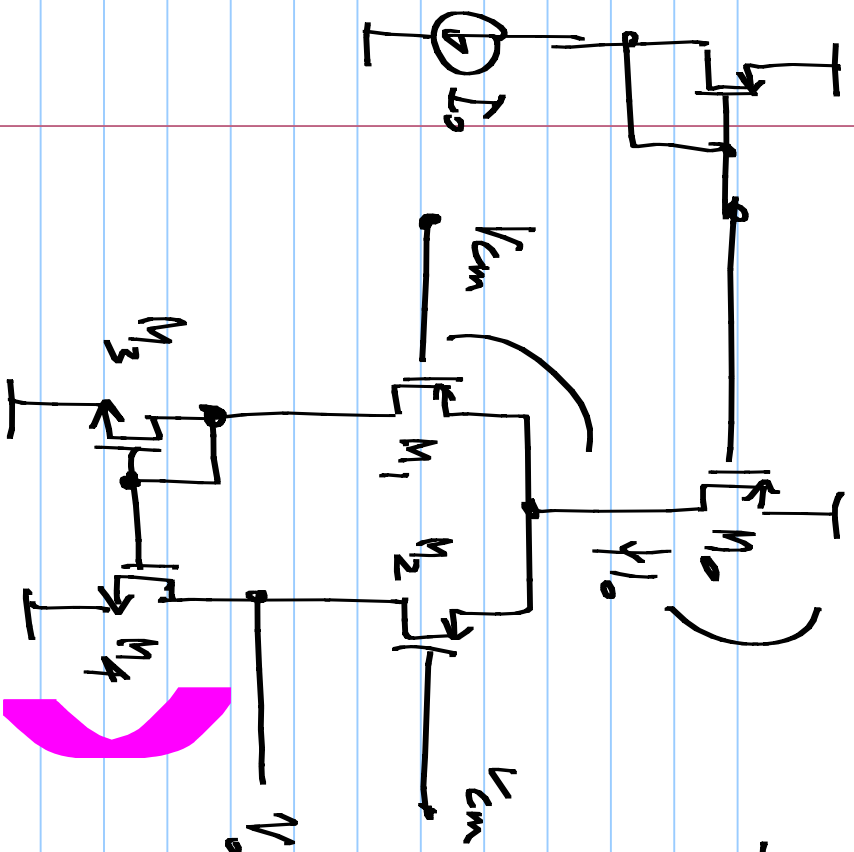


$$V_{DS1,2} / k/2 < V_o < V_{cm} + V_{TP}$$
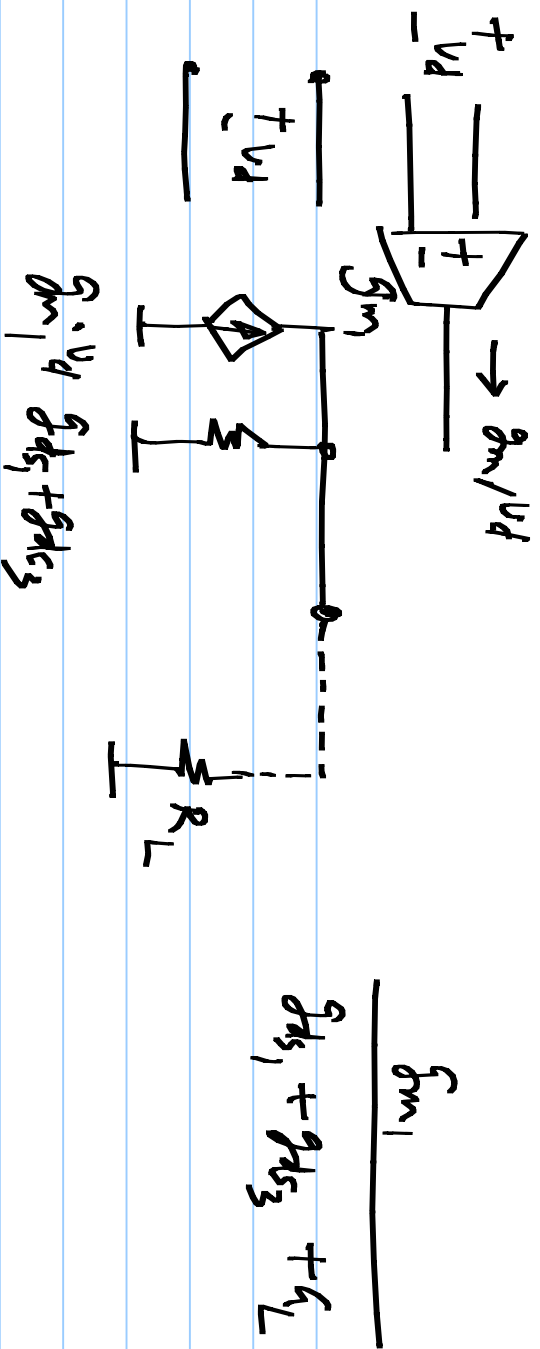
$$V_{GS3} - V_{TP} < V_{cm} < V_{DD} - \left(\frac{V_{DS4,0} + V_{DS4,1} / 2}{k/2} + V_{TP} \right)$$



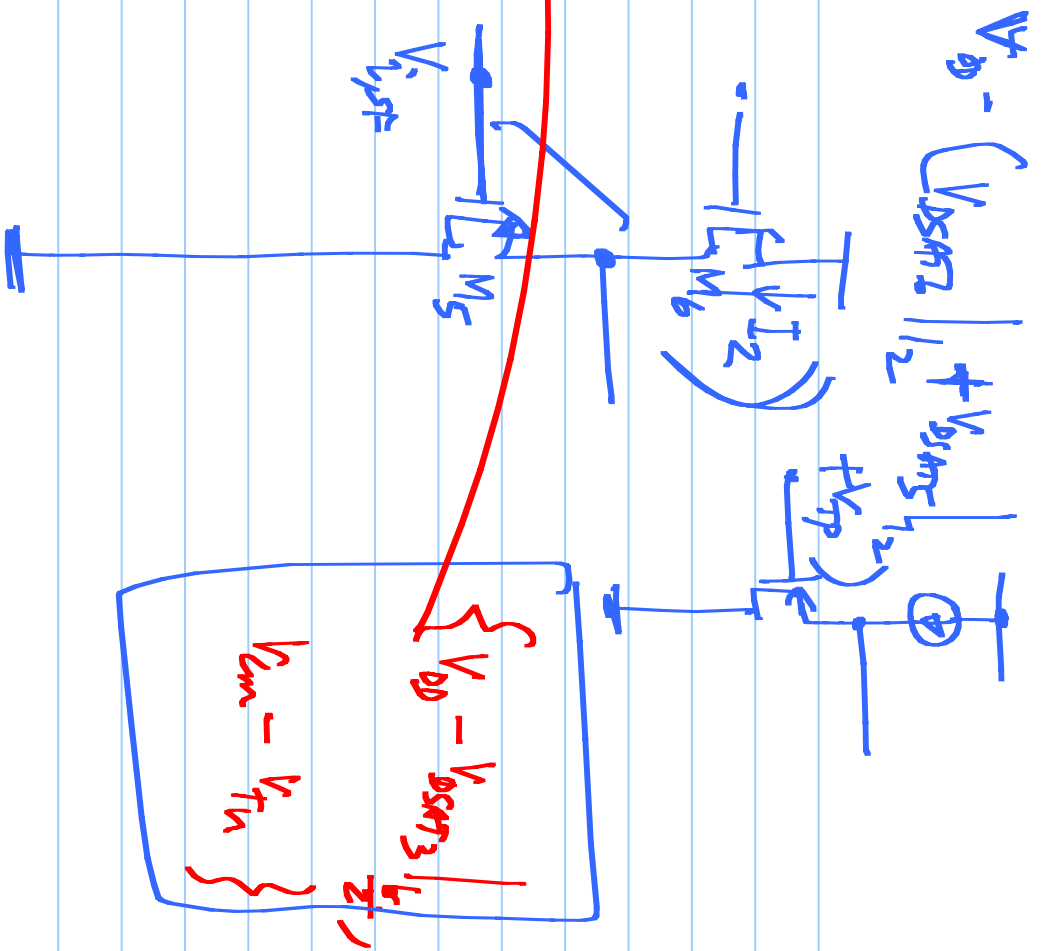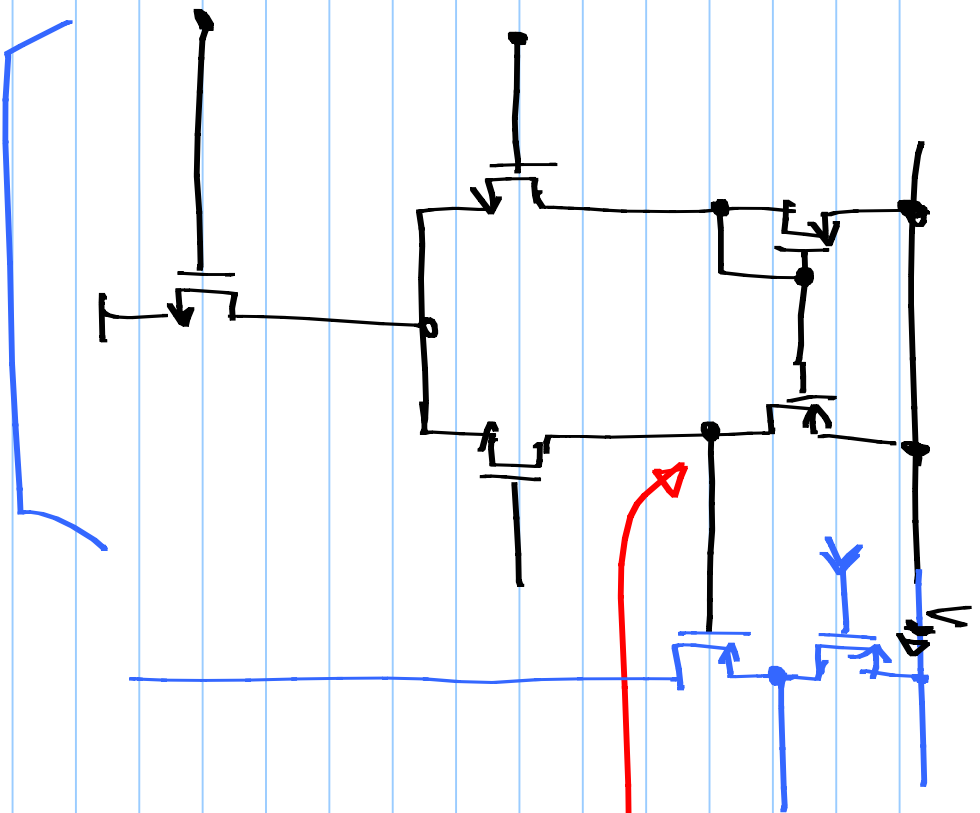Single stage opamp: VCCS: can't be used with resistive loads



$$\left\{ \begin{aligned} V_{DD} - V_{DSAT3} \\ V_{DD} - V_{TH} \end{aligned} \right\}$$

$$V_{DD} - (V_{DSAT2} + V_{DSAT1}) - A$$

$$\left(\frac{I_{D1}}{I_{D2}} \right)$$

$$\left(\frac{I_{D1}}{I_{D2}} \right)$$

opamp (diff. pair + cur. mirror)

PMOS SF

NMOS SF

